

PRAYAS

JEE 2025

ATDB.uno

Lecture -

Physics



Current Electricity

(Home Work Discussion)



70-72 Ques

By- Saleem Ahmed Sir



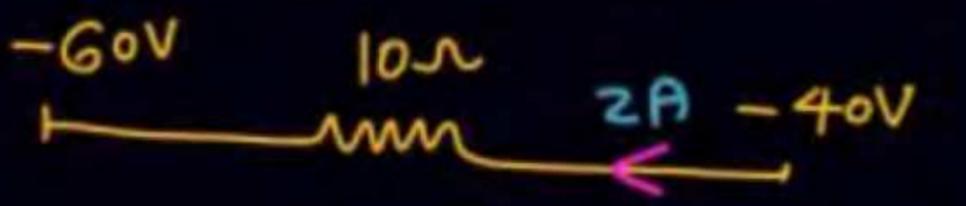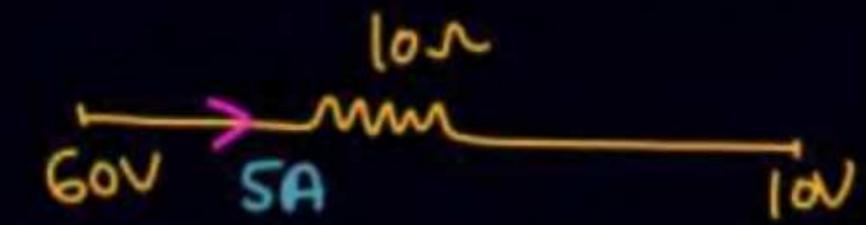


(play with circuit
mario type)

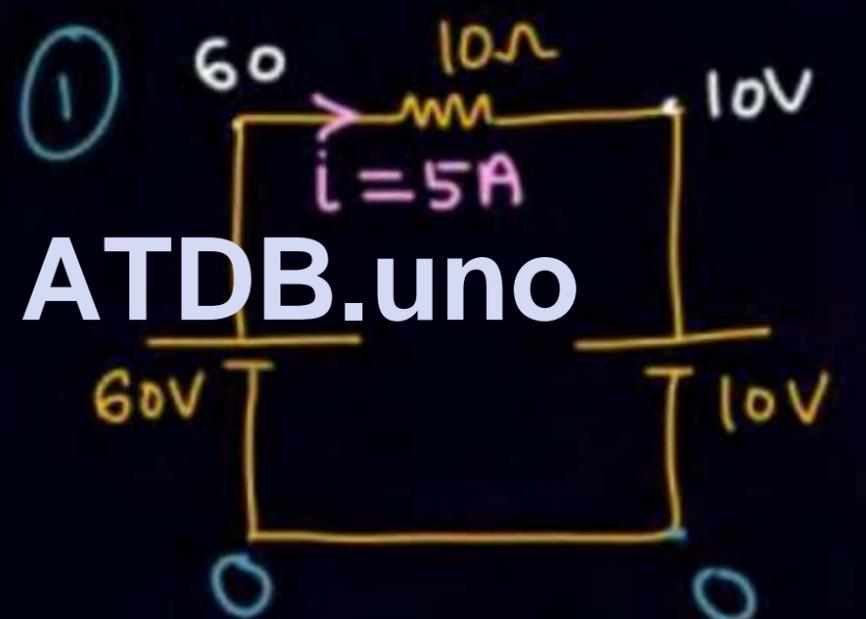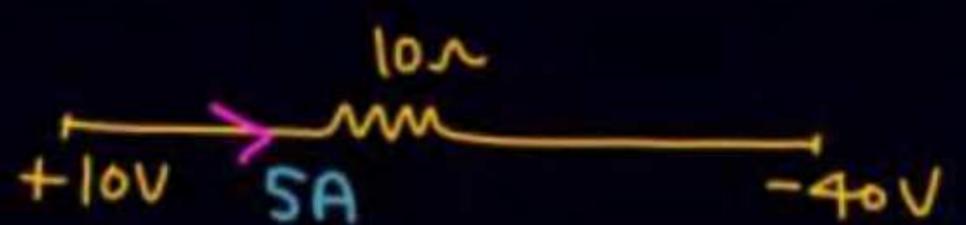

ATDB.uno




(2)

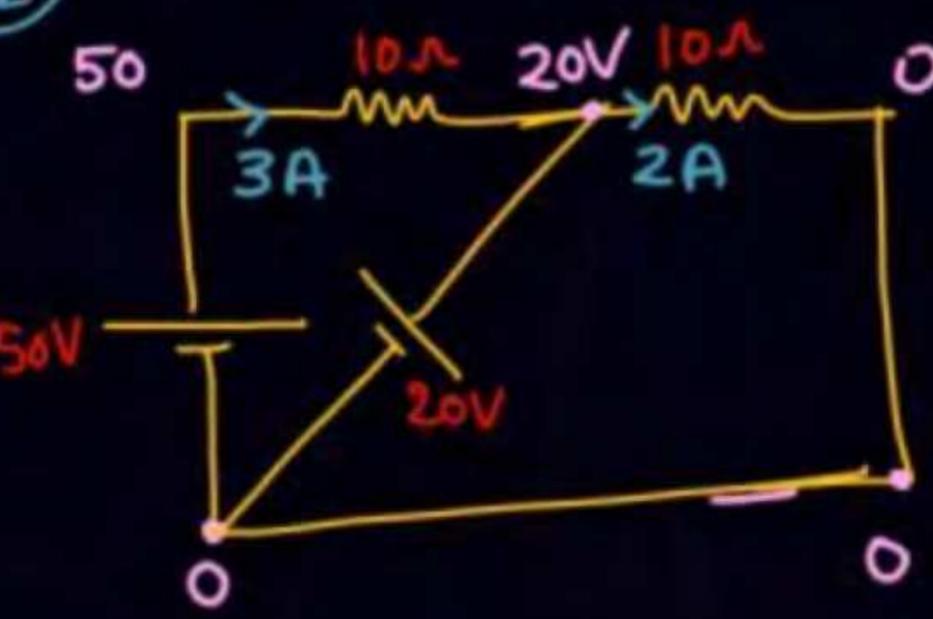


$$-30 - (-50) = 20$$

3

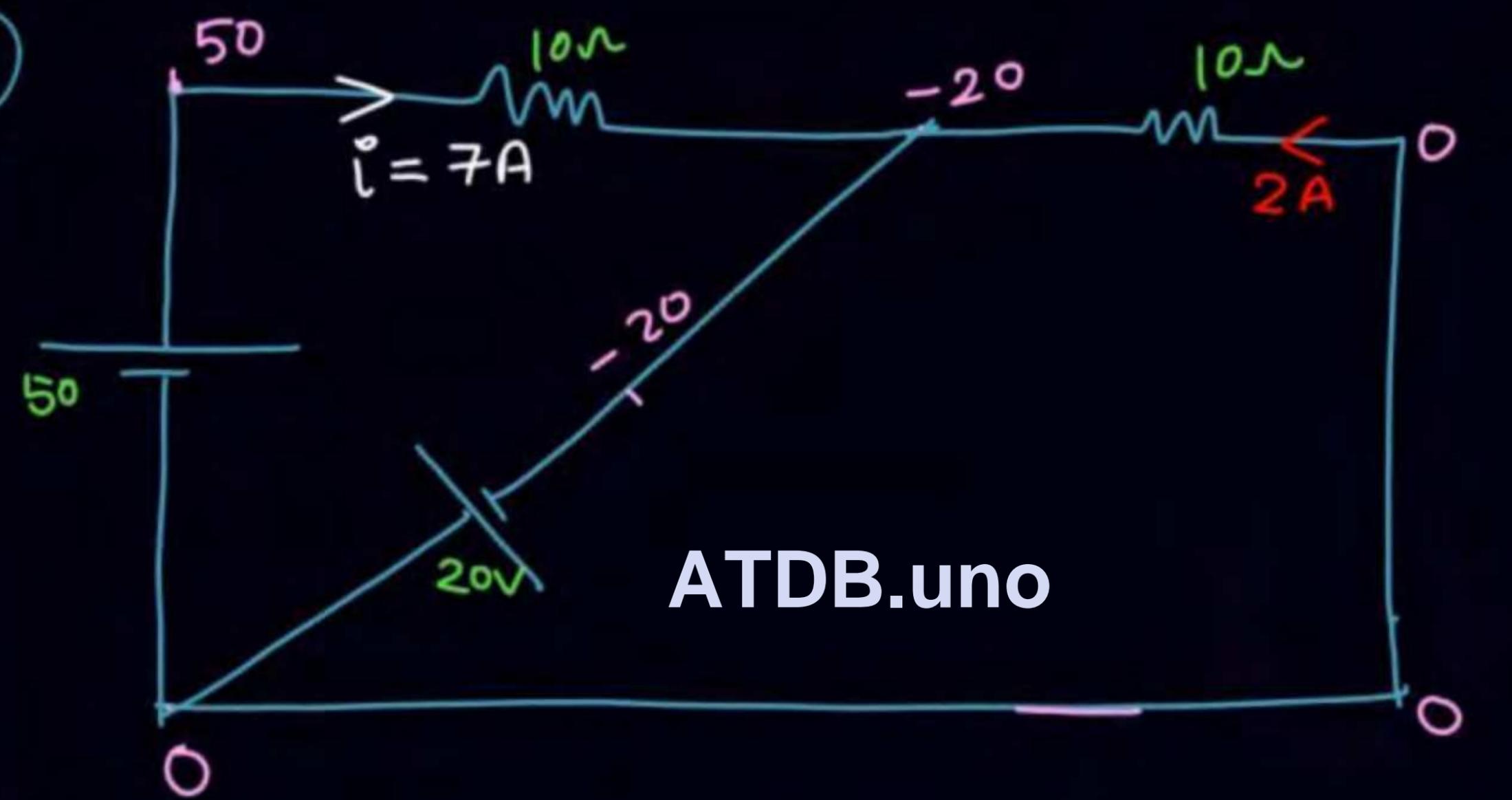


ATDB.uno

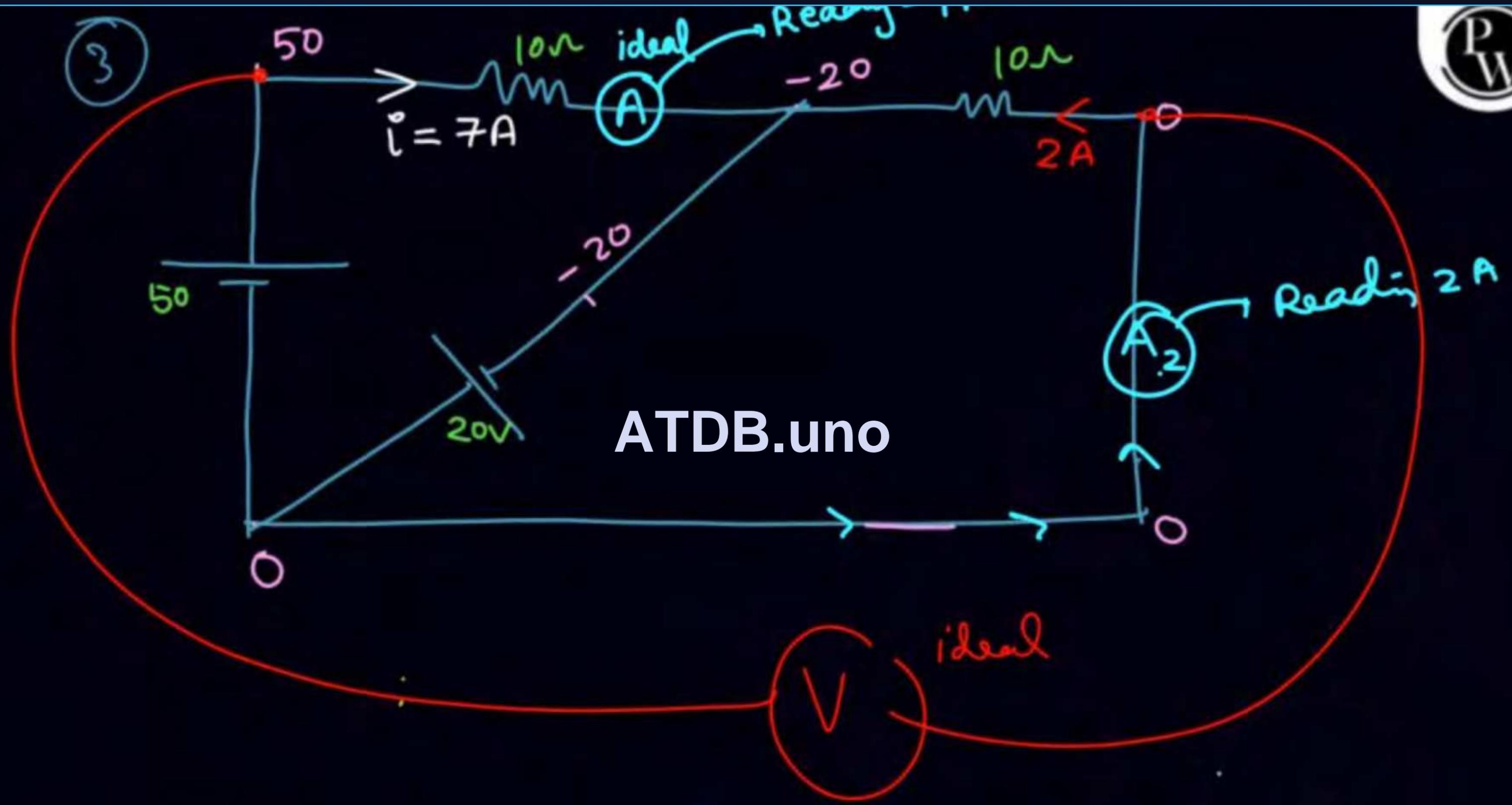

ATDB.uno

$R = 10\Omega$ (each)

④

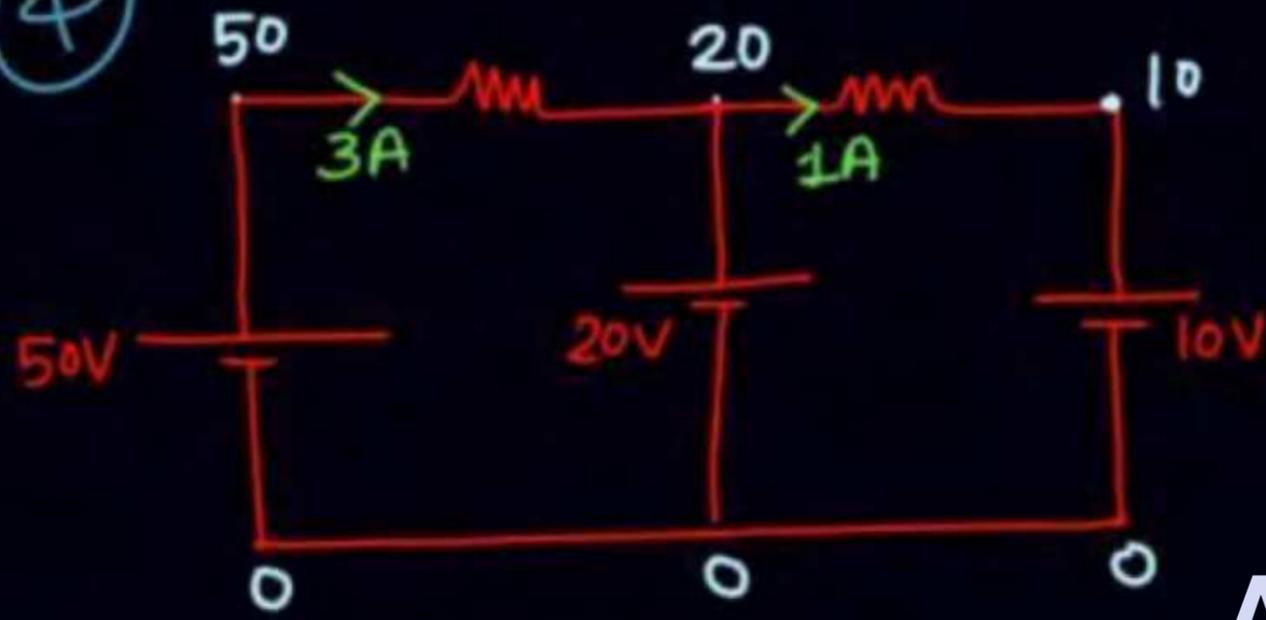

⑤




ATDB.uno



रटना कुछ
भी नहीं है
just play

$R = 10\Omega$ (each) Reading = 10V

4

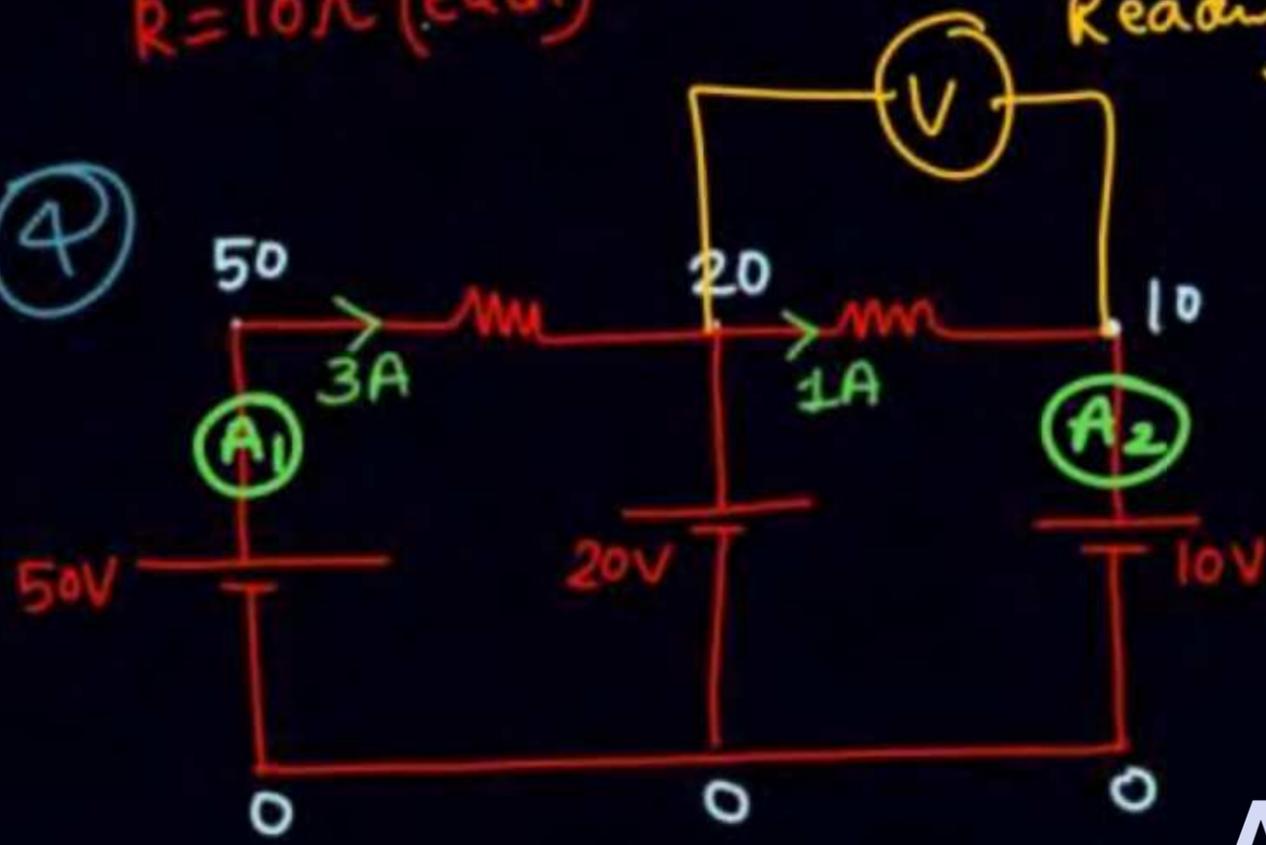


5



रटना कुछ भी नहीं है
just play


ATDB.uno

(A₁) Read → 3A
A₂ " → 1A

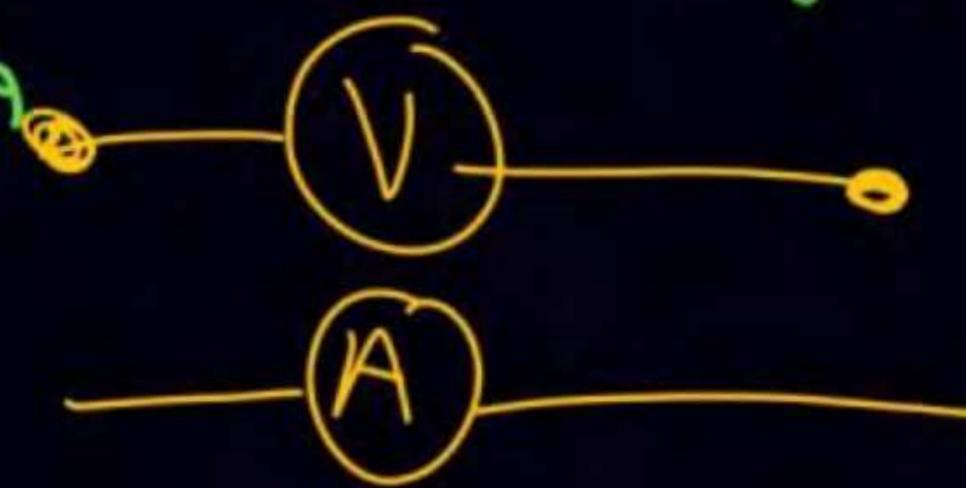



Q
6

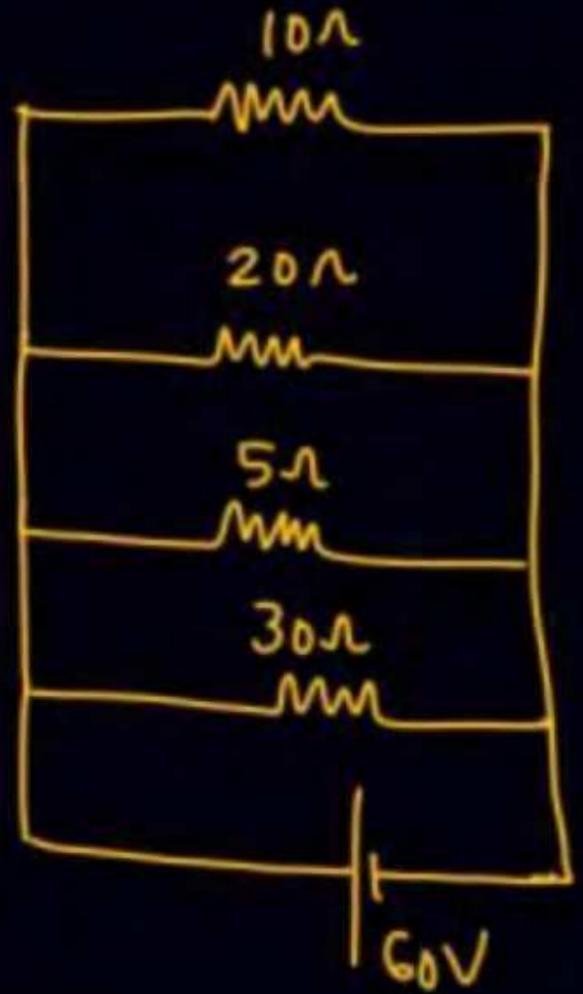


7



Battery ke side se dekhin E

8

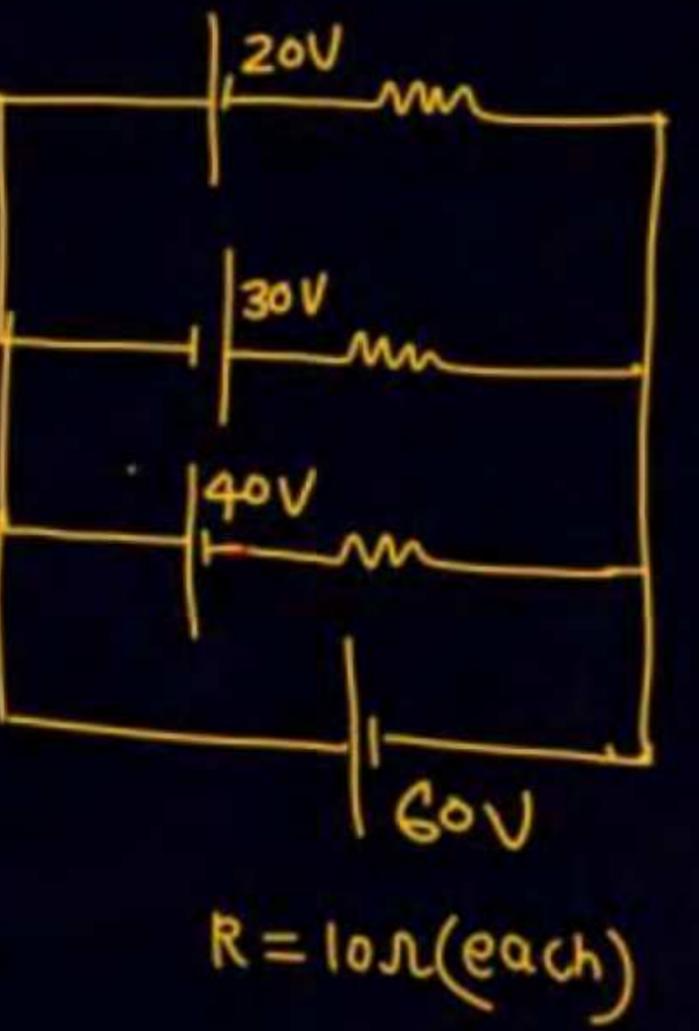


ATDB.uno



Solⁿ

6

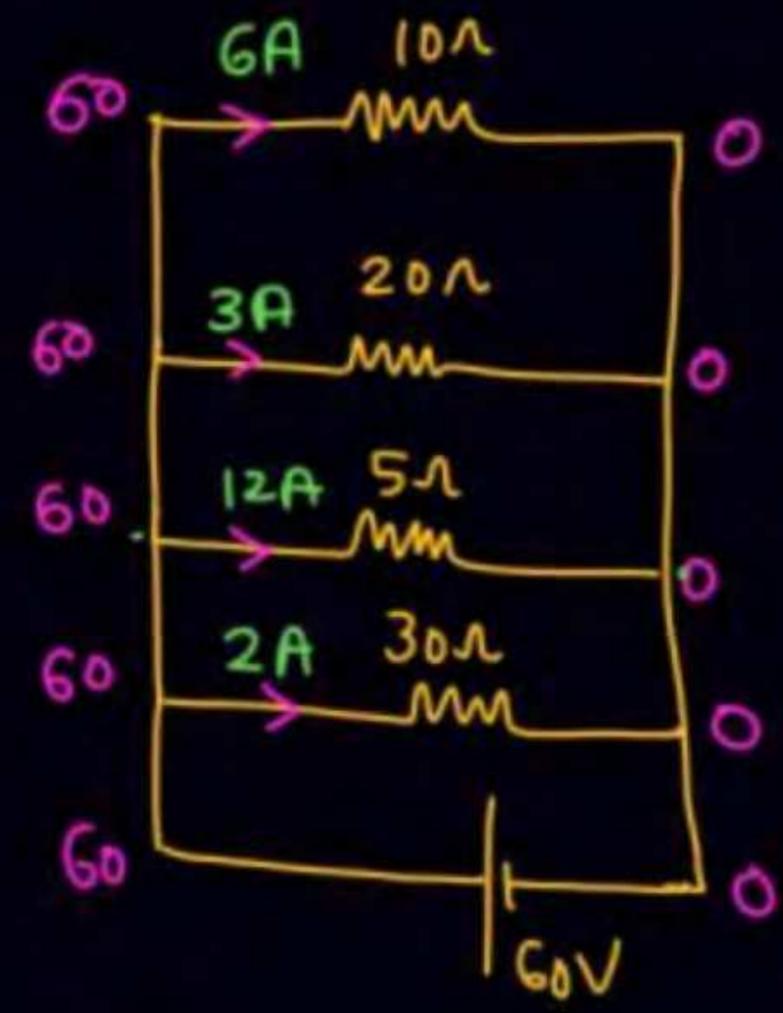


7



8

(Battery क 55 ट में देखिए)

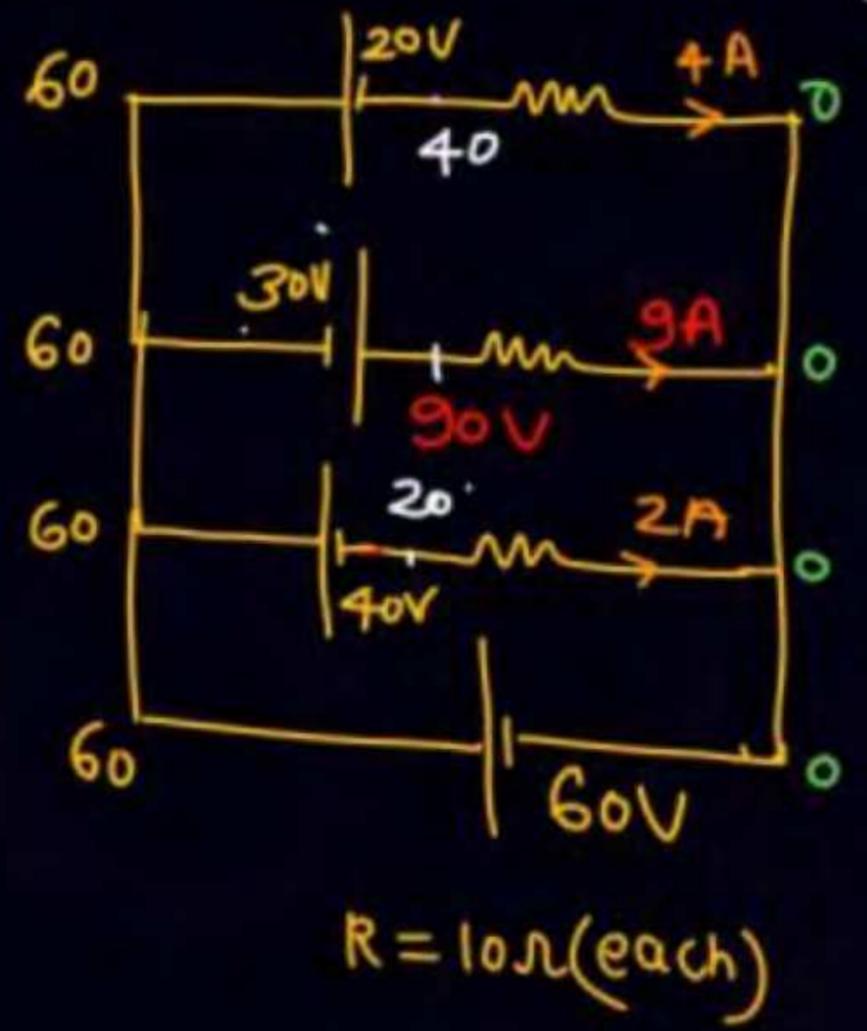




9




ATDB.uno

(R = 10Ω each)


10

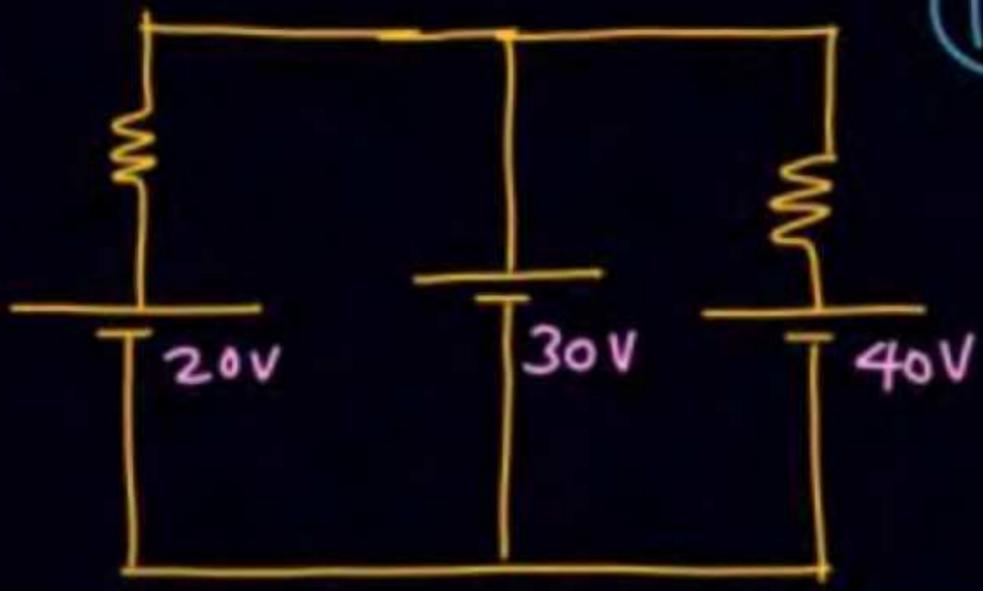




11

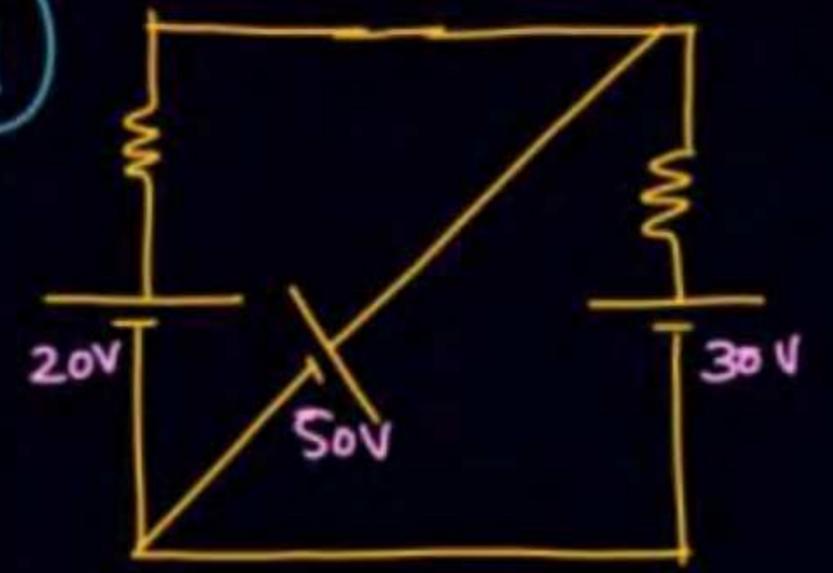

12

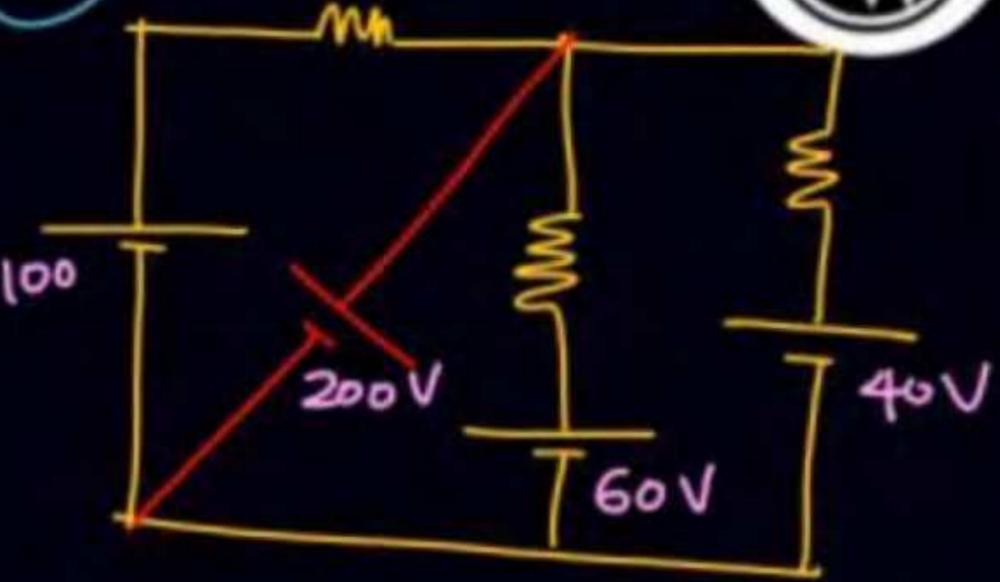


ATDB.uno

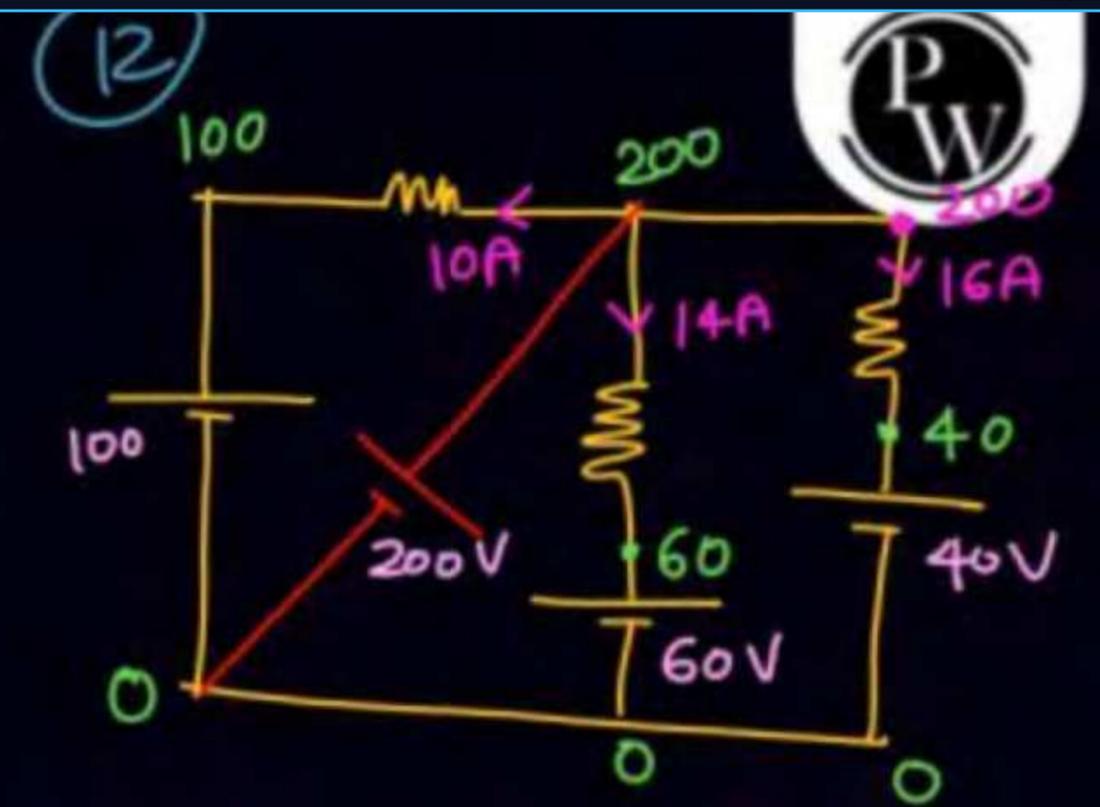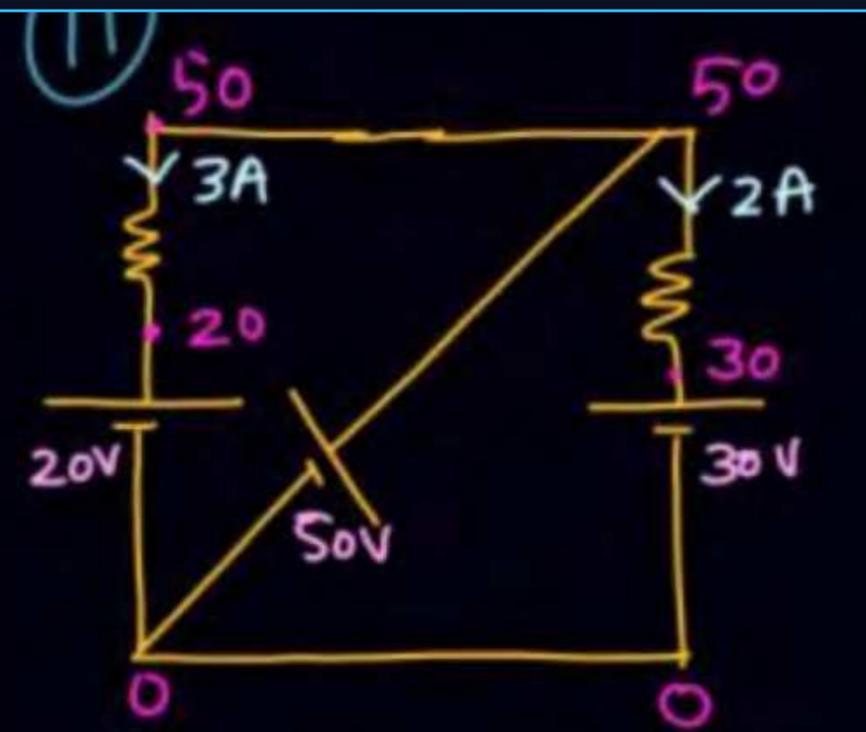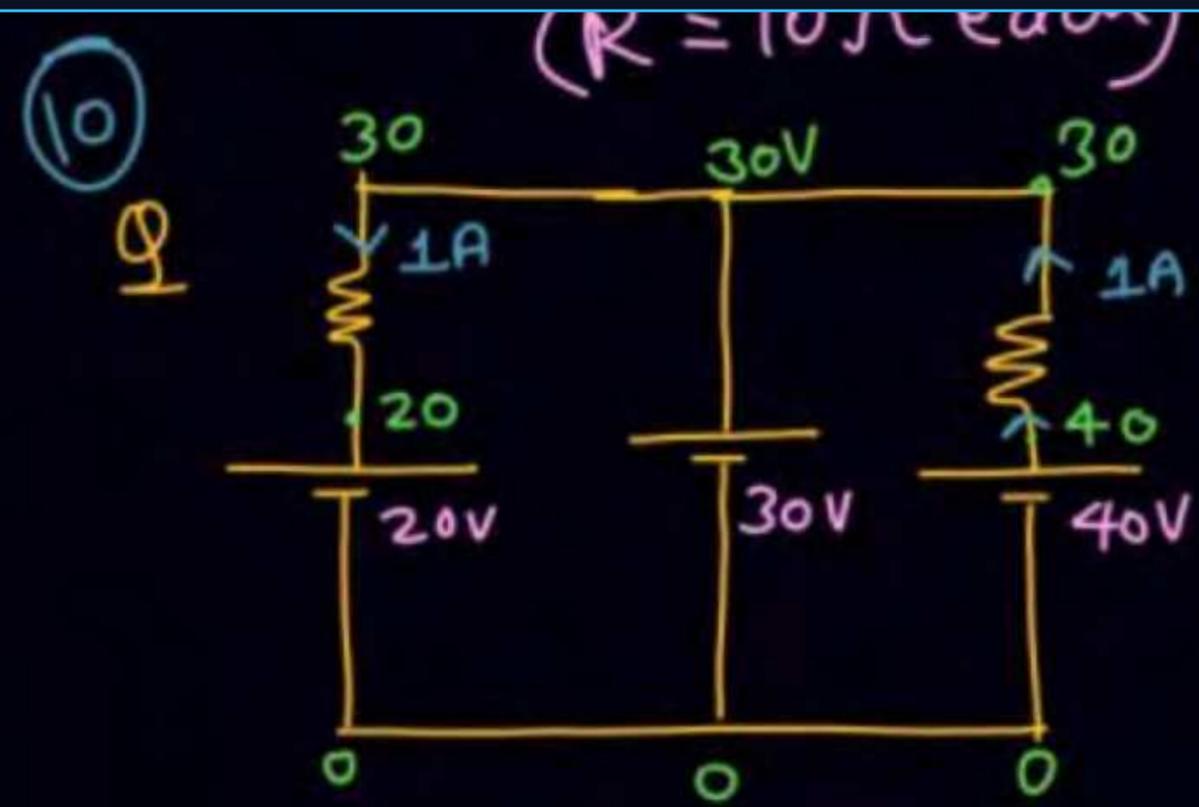

$(R = 10\Omega \text{ each})$
ATDB.uno

$(R = 10\Omega \text{ each})$

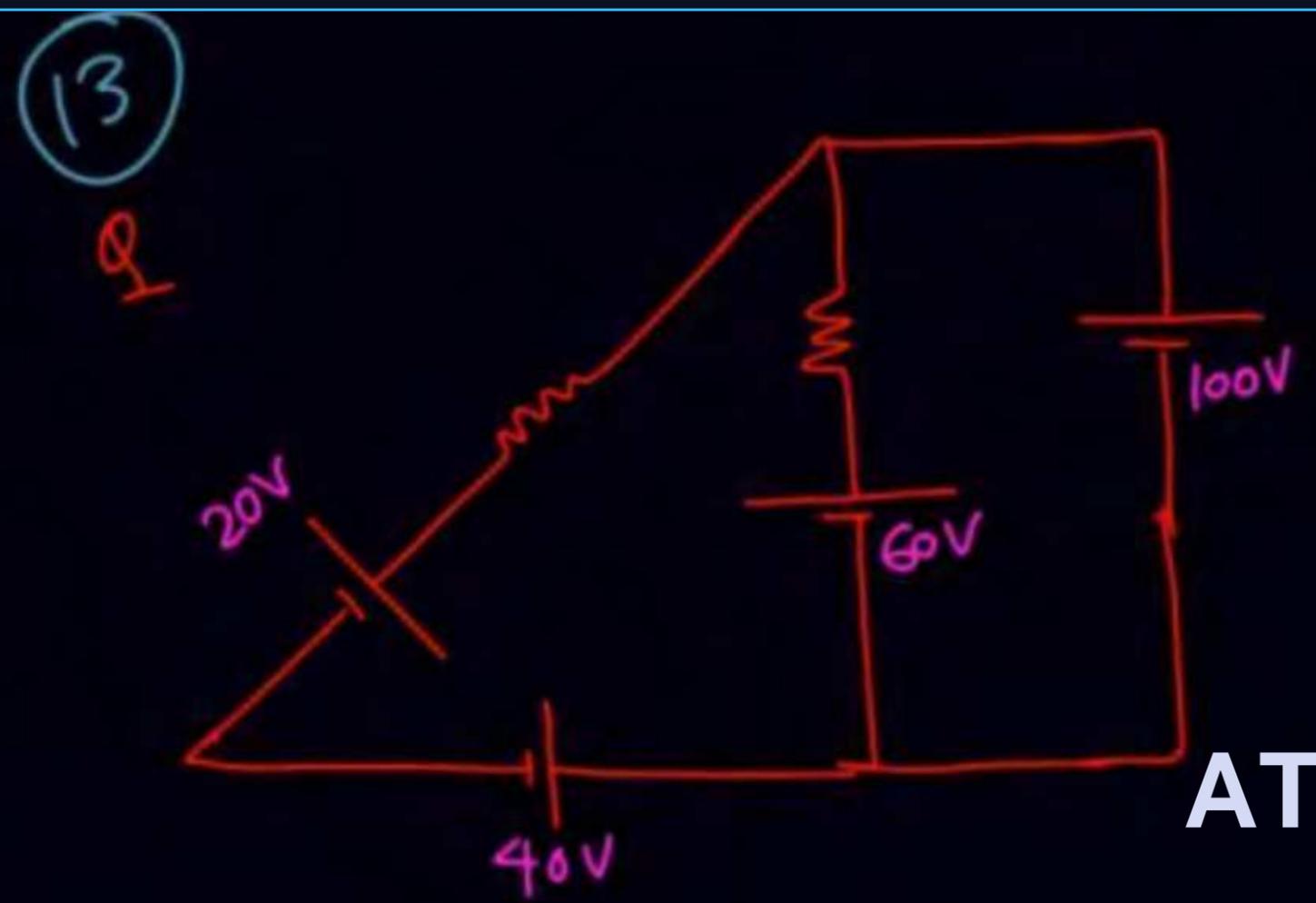


$R = 10\ \Omega$ (each)

ATDB.uno



$R = 10\ \Omega$ (each)



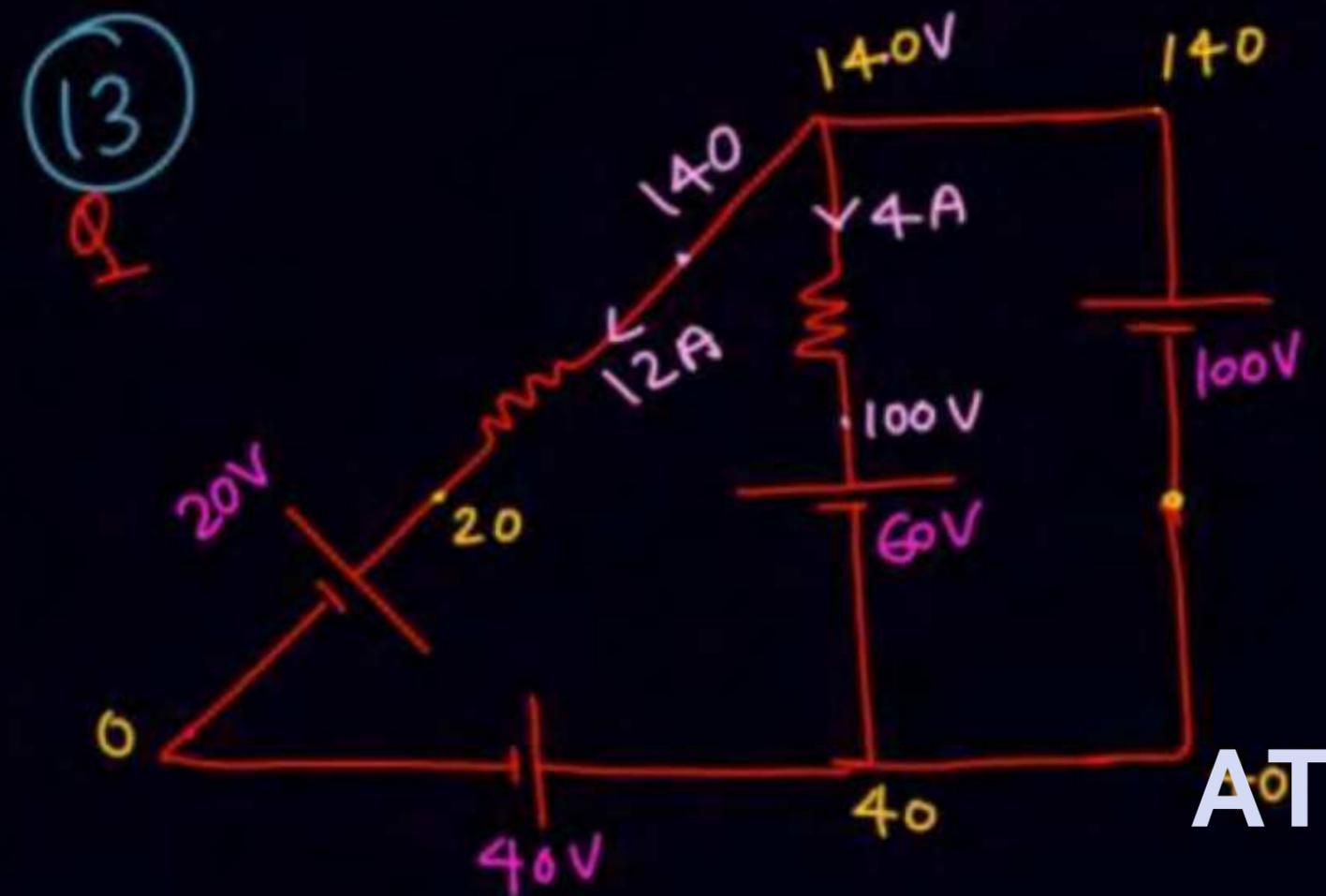

$R = 10\ \Omega$ (each)

ATDB.uno




$R = 10\ \Omega$ (each)






15

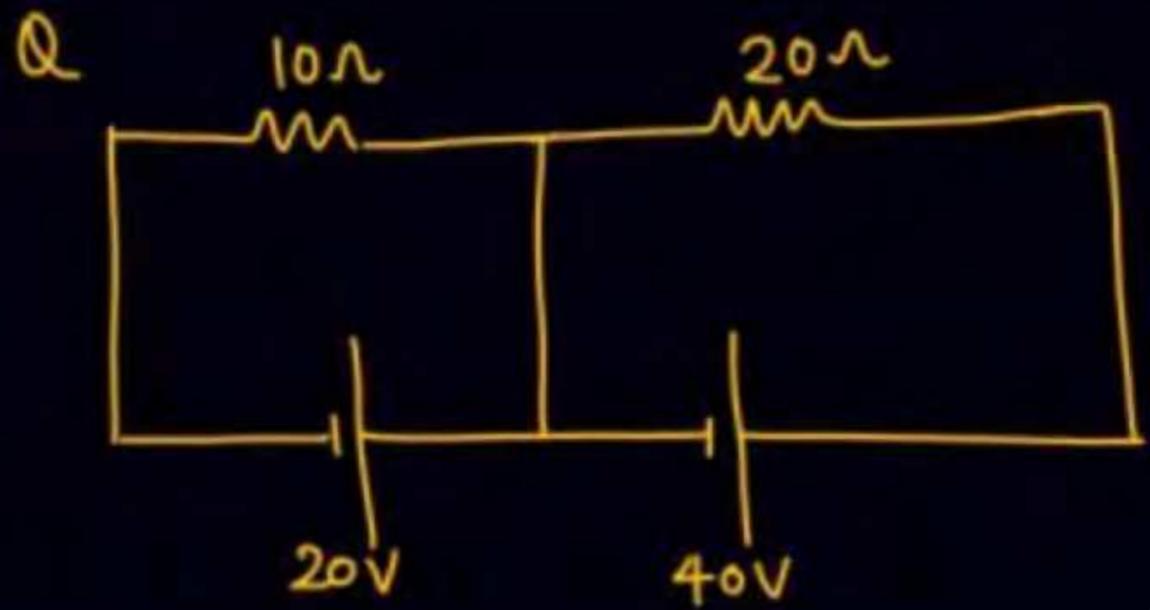

16


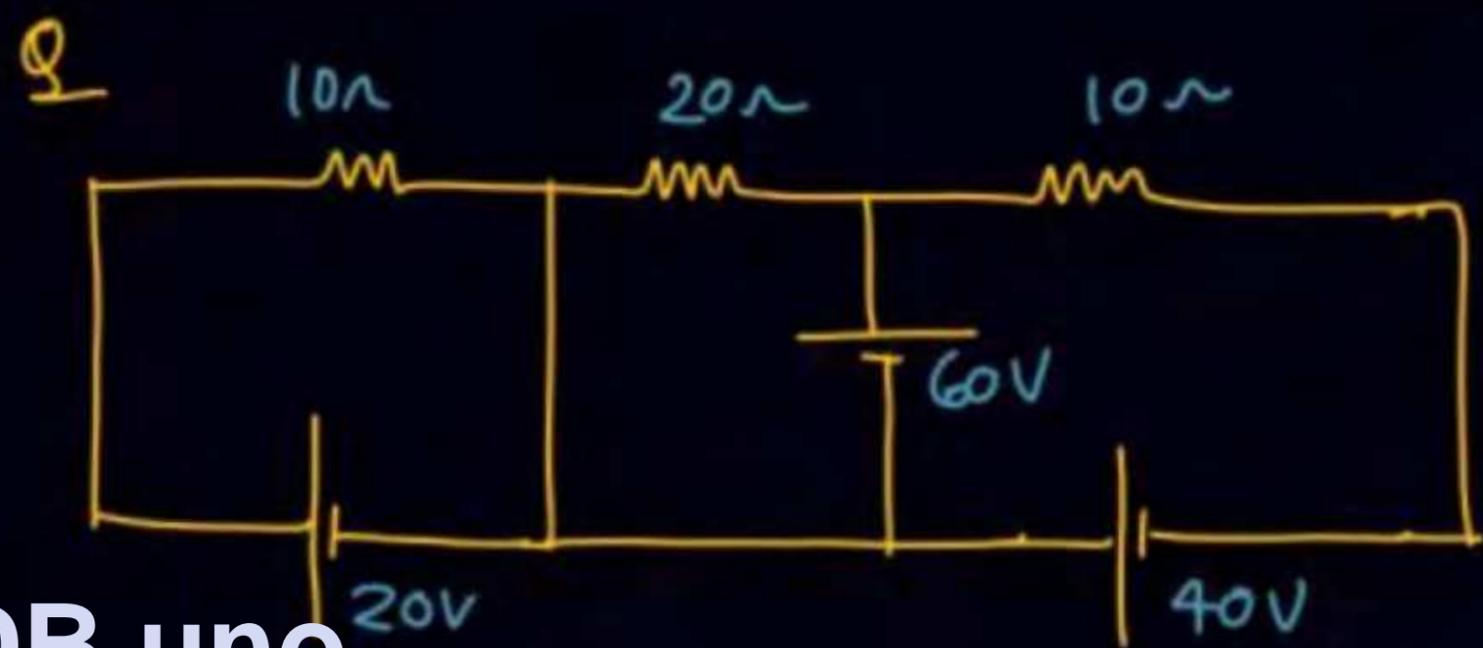


ATDB.uno





15

16

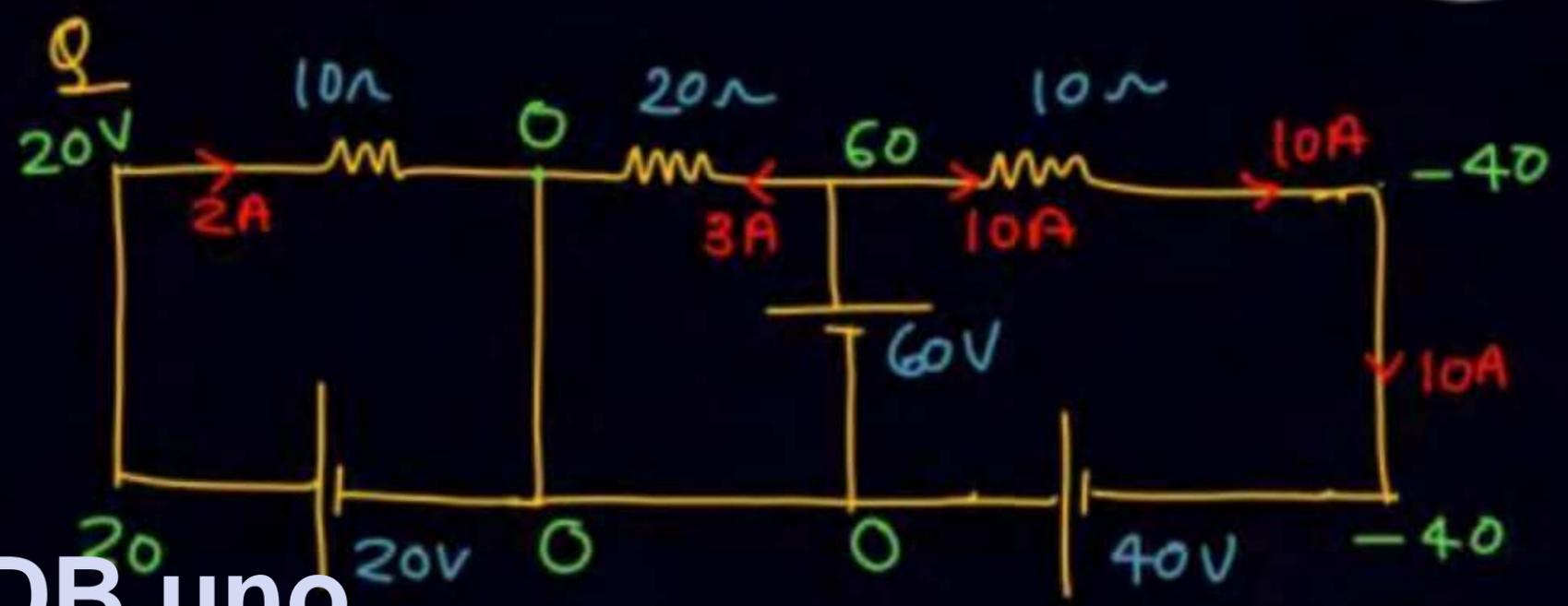
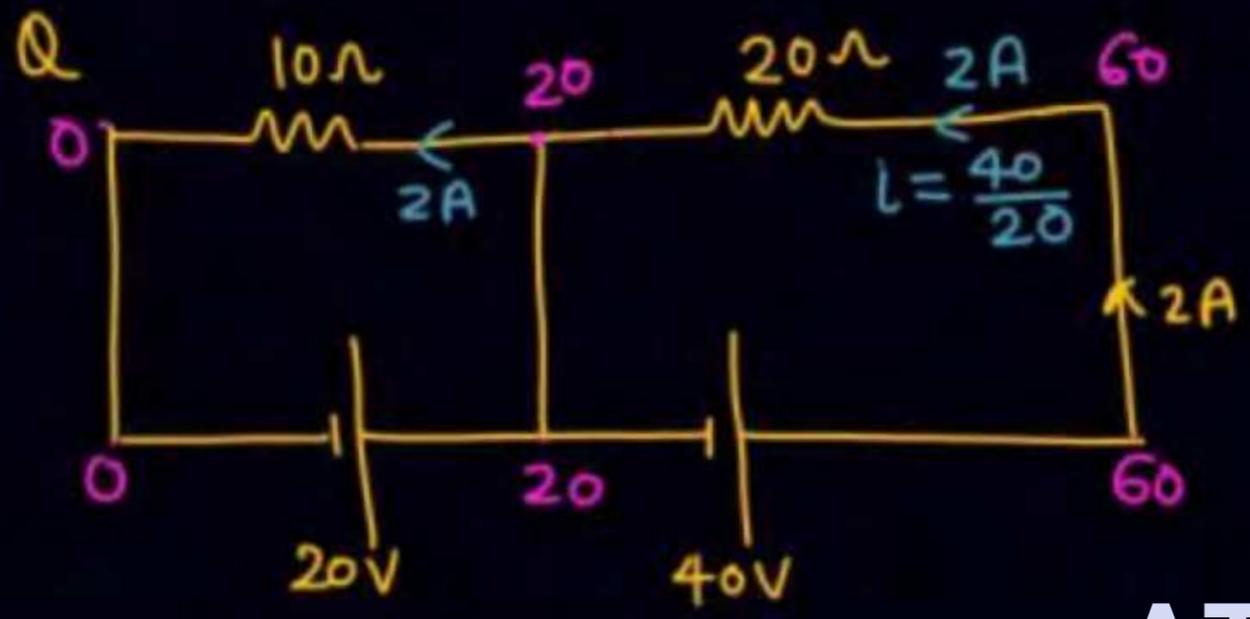


ATDB.uno

~~10~~

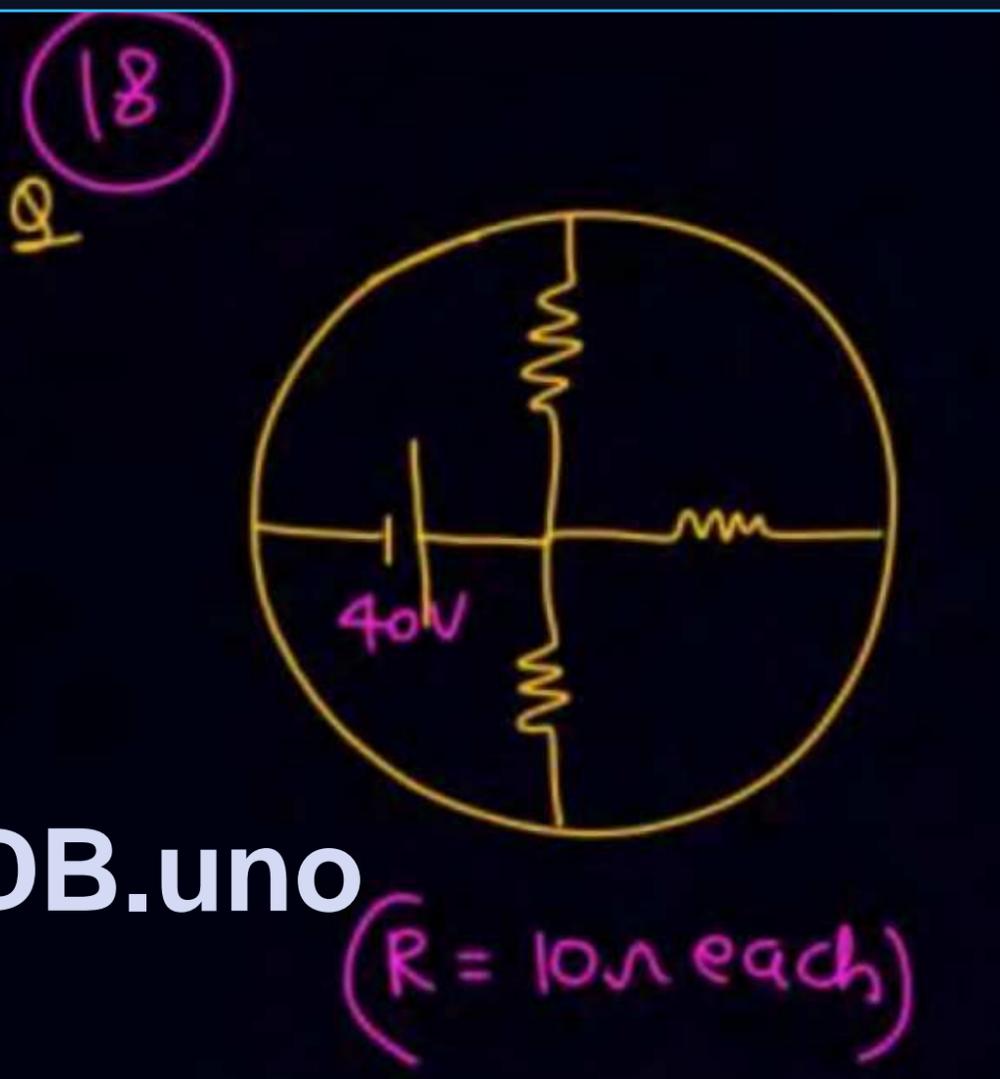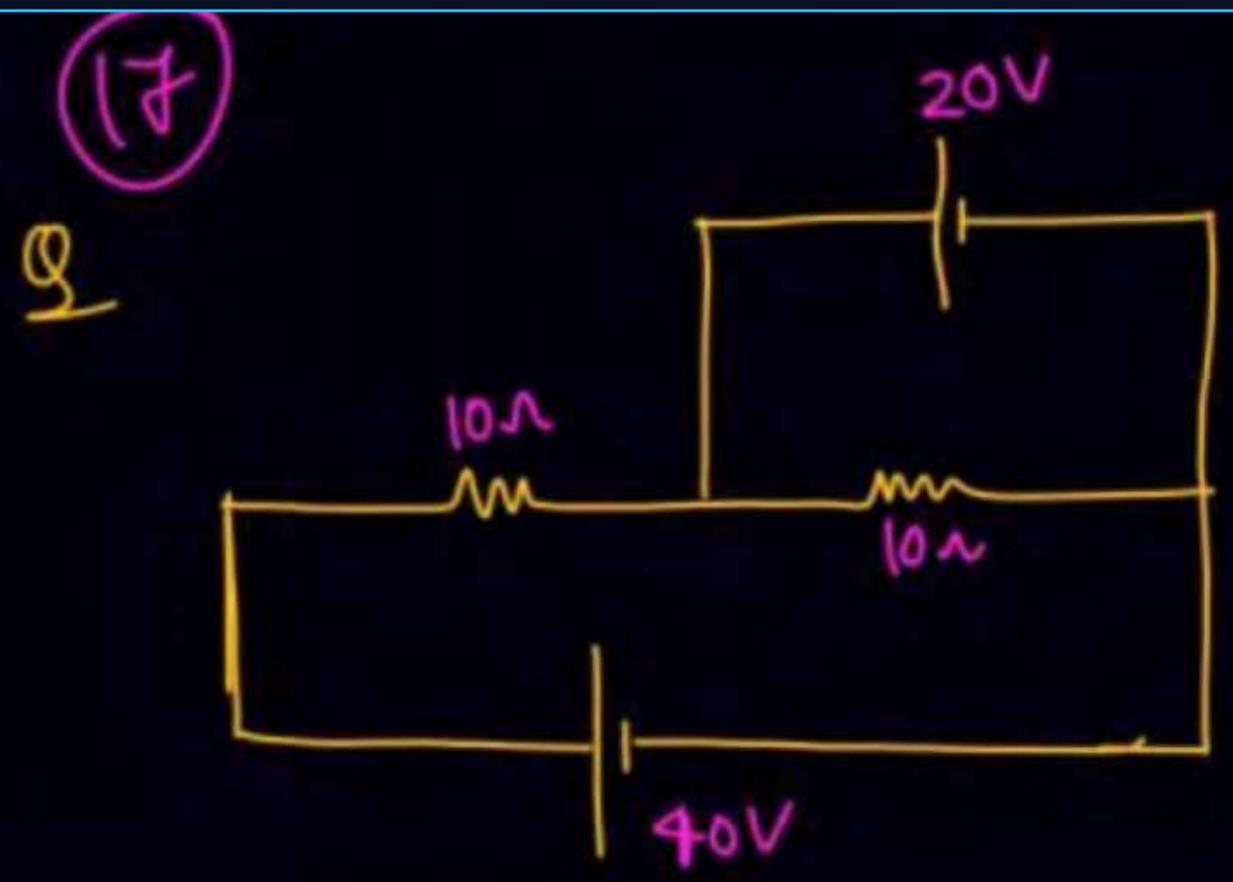


ATDB.uno

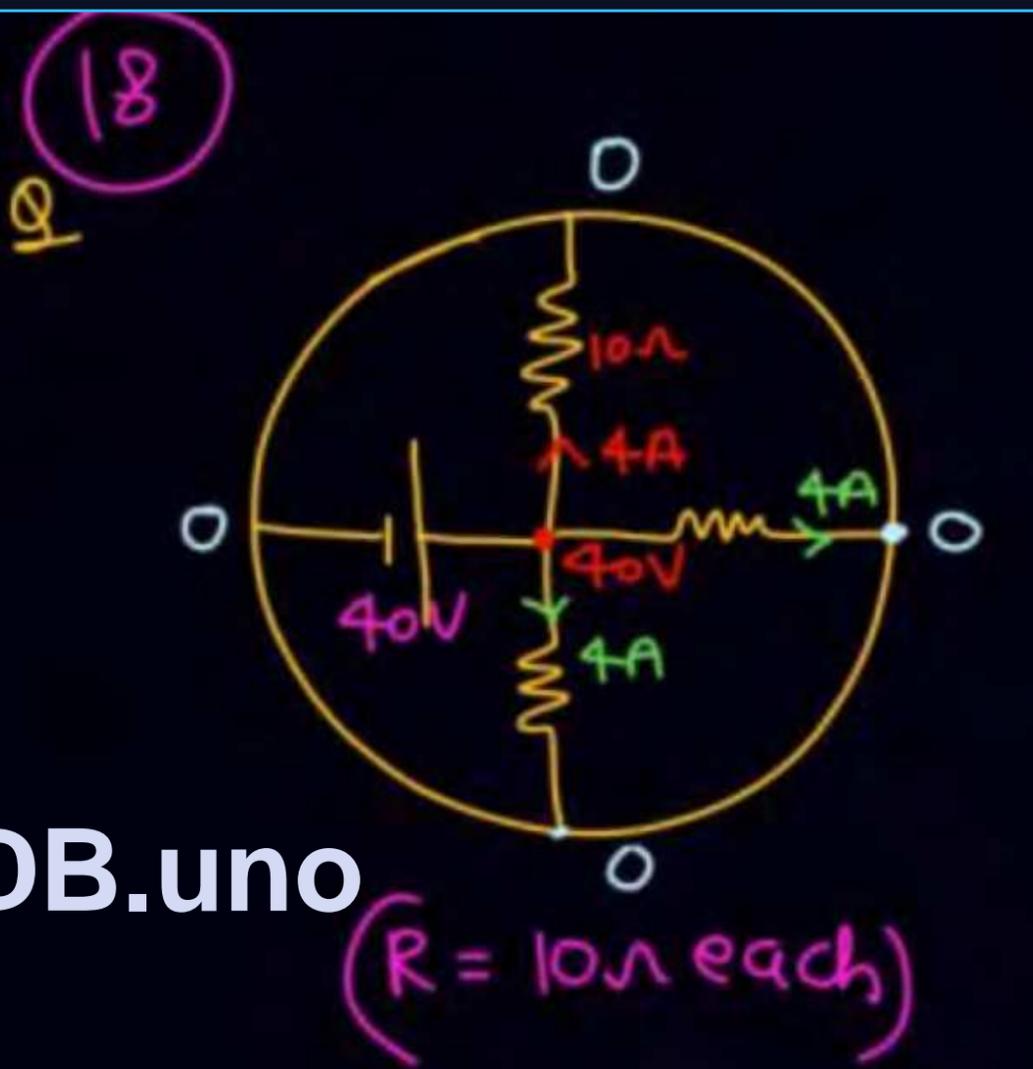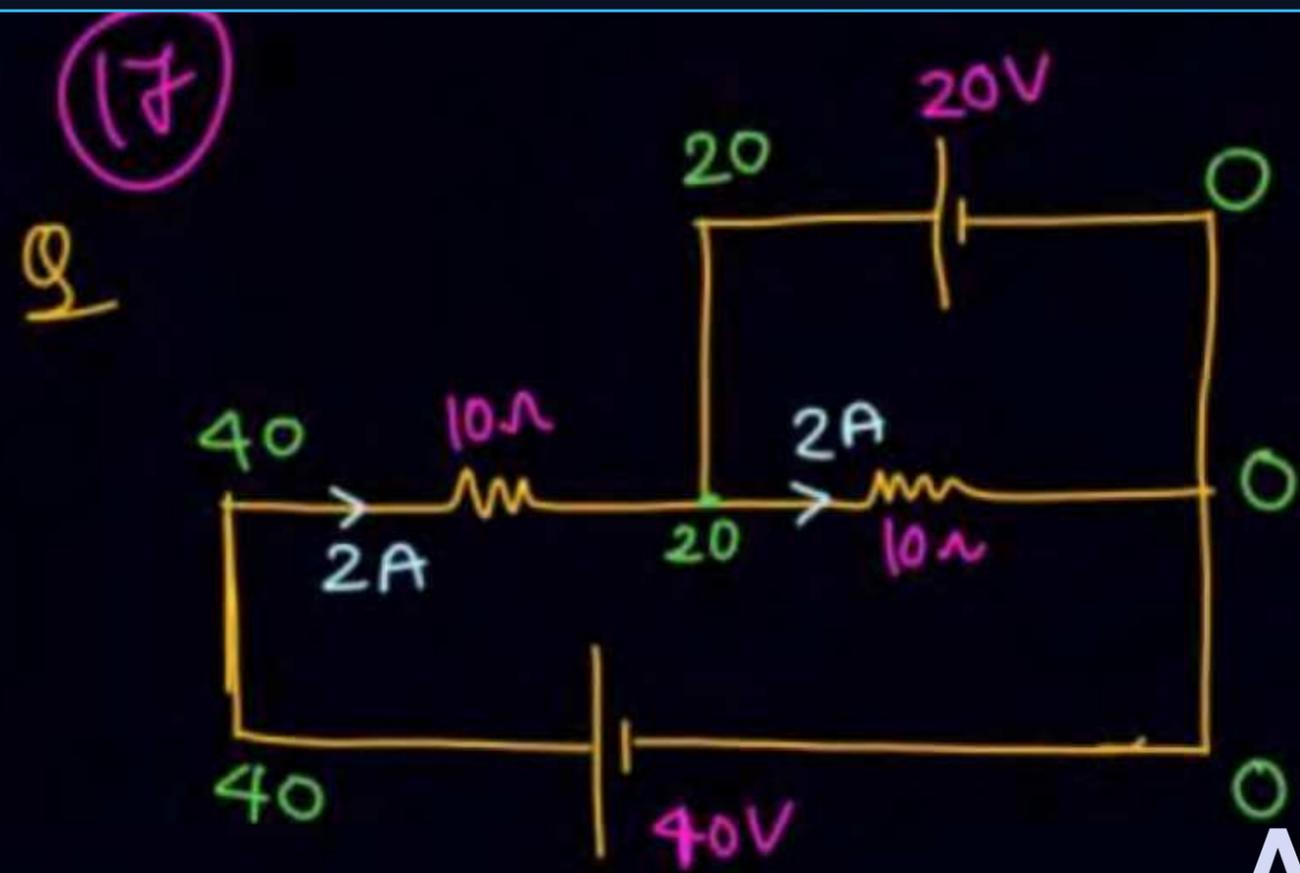

ATDB.uno



Q (19)

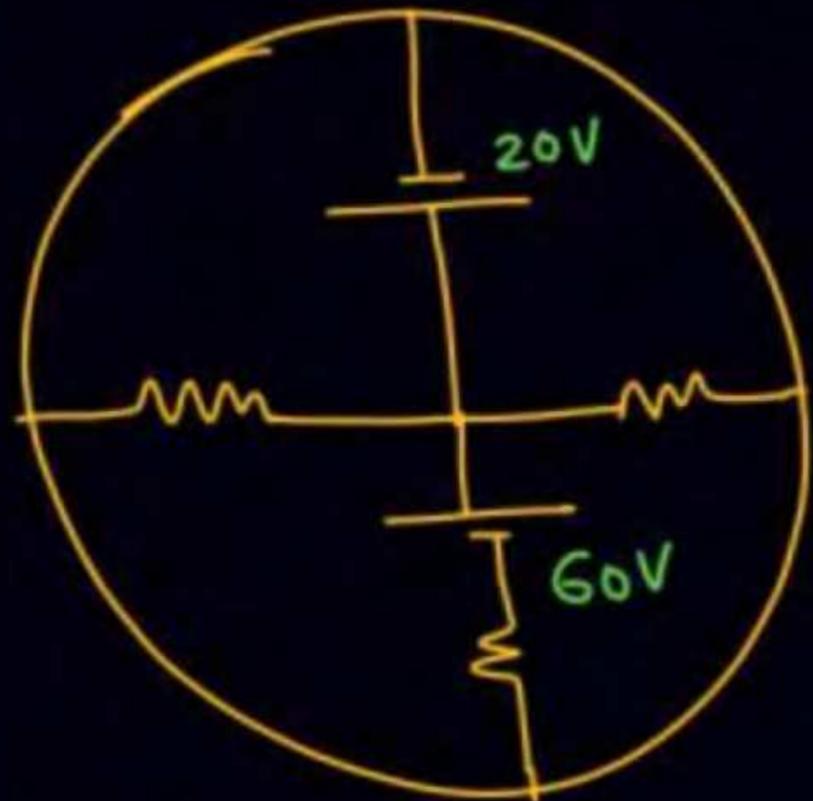


$$R = 10\Omega \text{ (each)}$$

Q (20)




$$R = 10\Omega \text{ (each)}$$

ATDB.uno

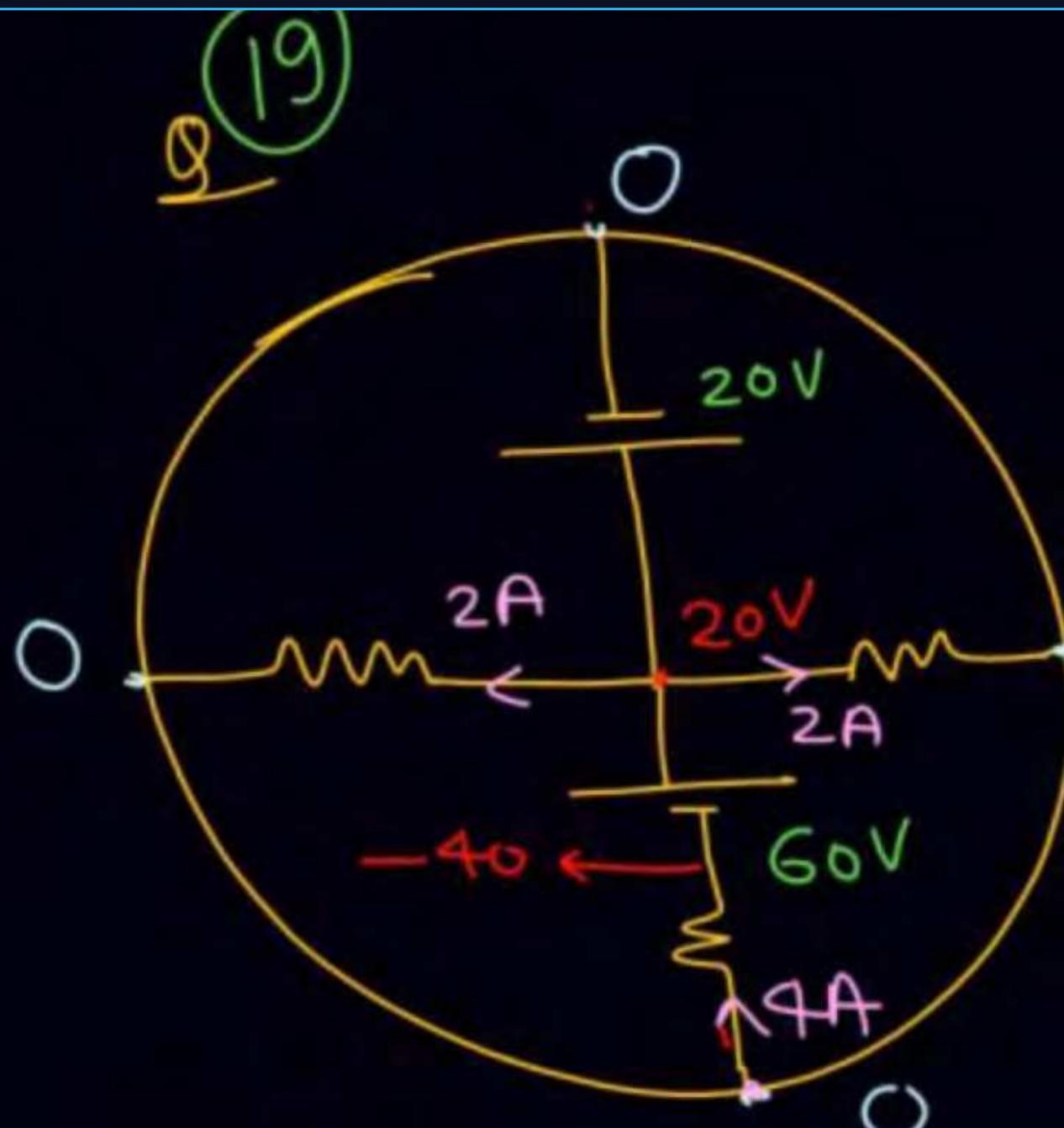

$R = 10\Omega$ (each)

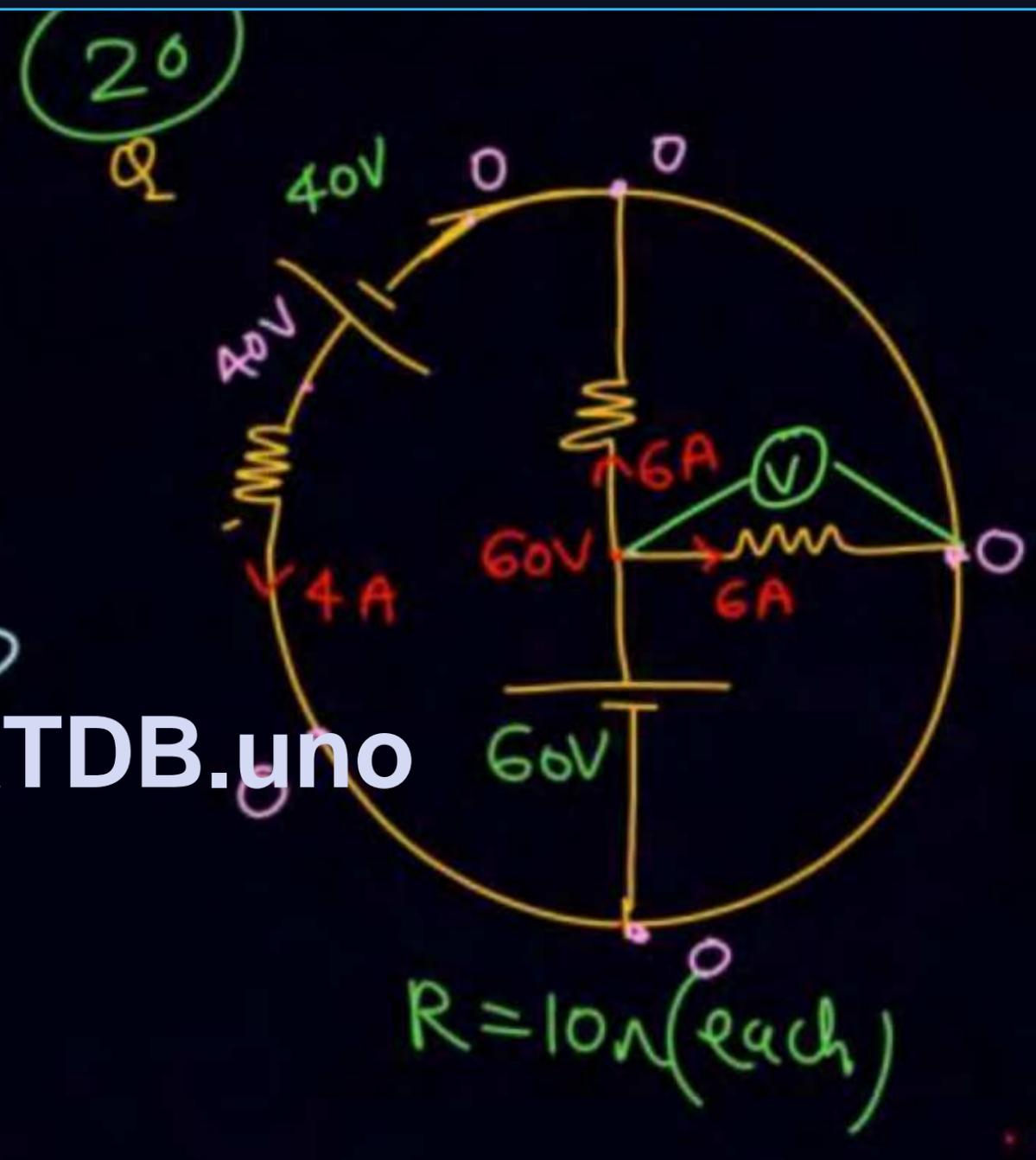


$R = 10\Omega$ (each)


ATDB.uno




21
Q

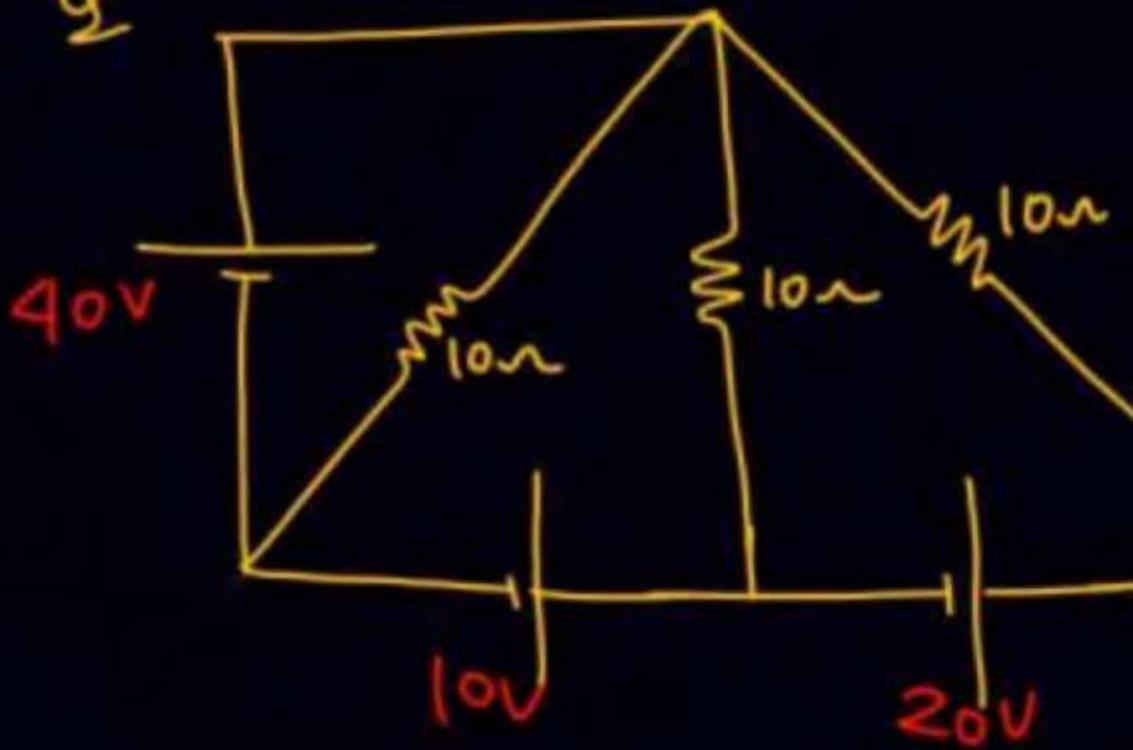


ATDB.uno

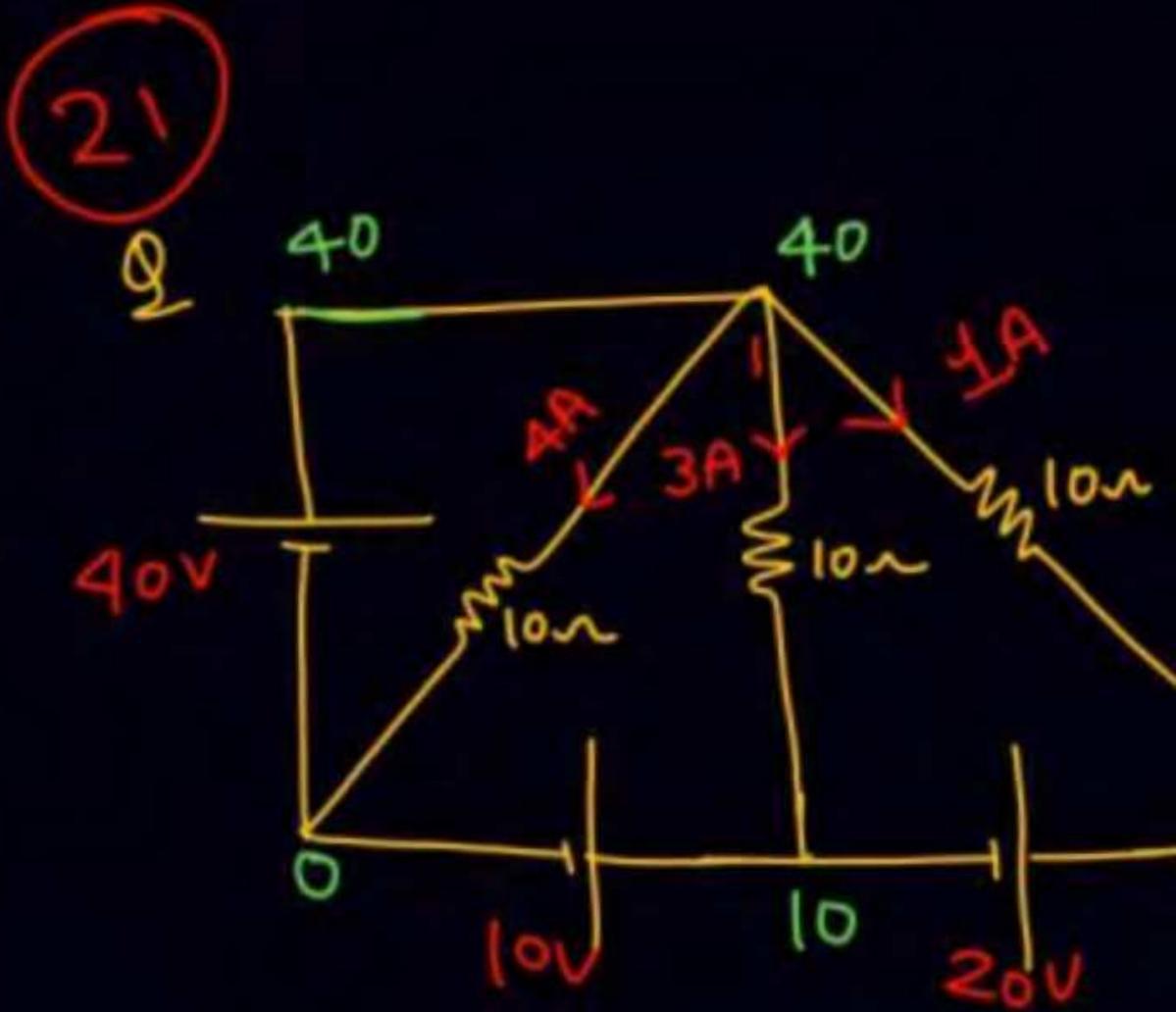


ATDB.uno

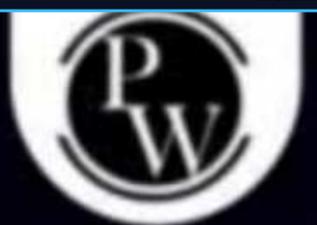

junction Law

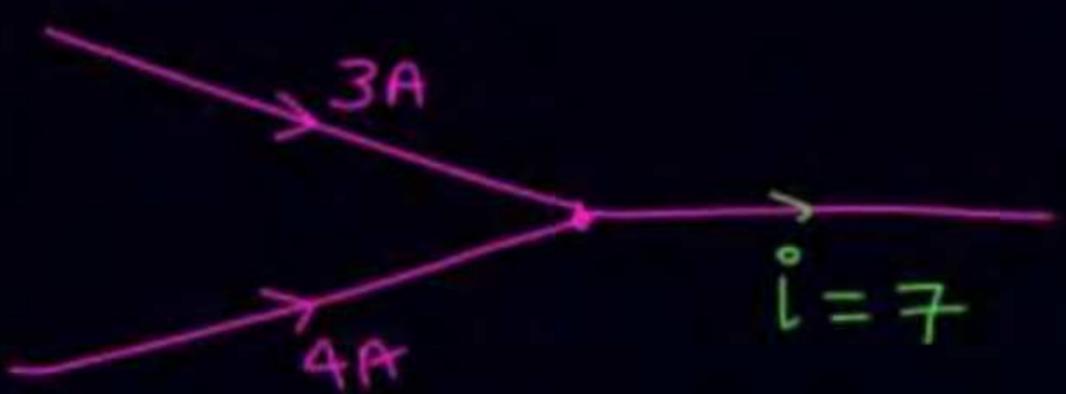


ATDB.uno

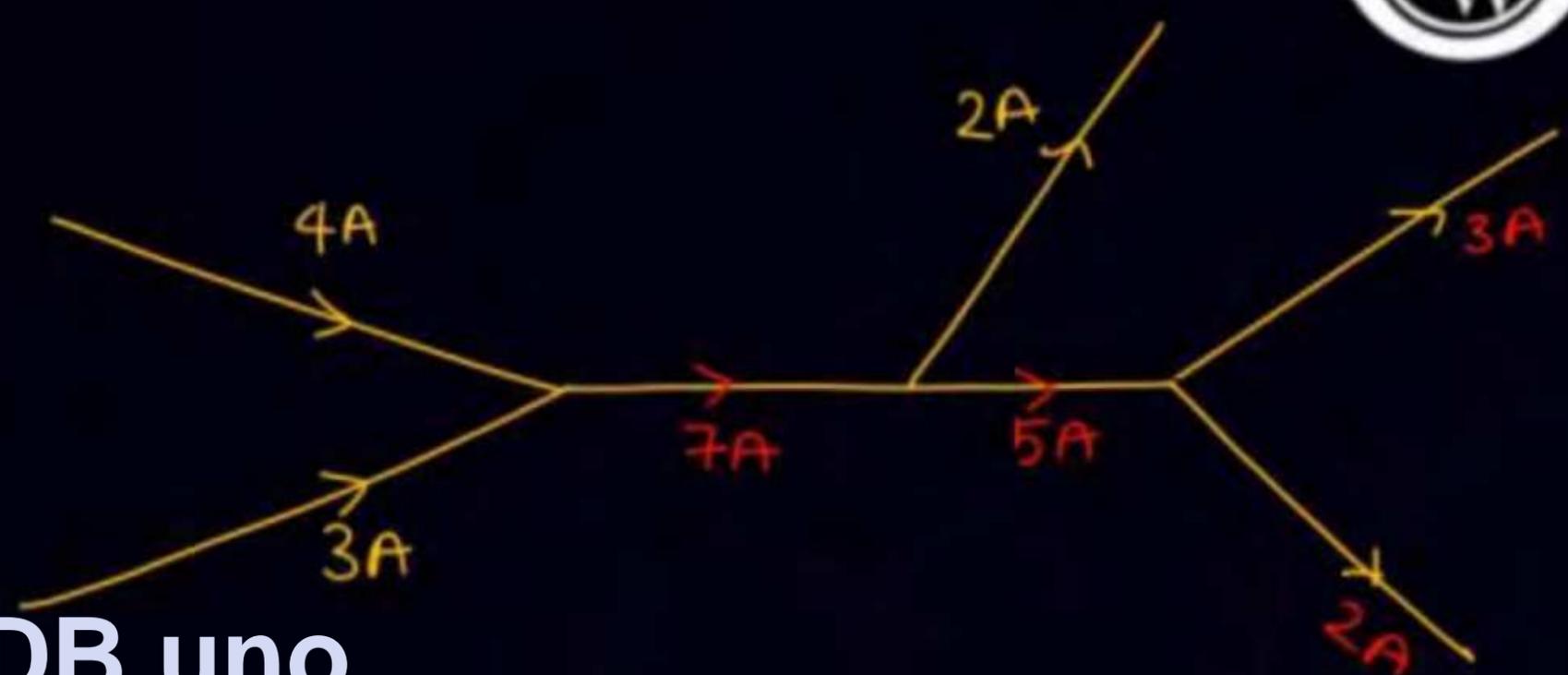

Junction Law


एल्का सा modification

जाने वाली साट current का sum = 0

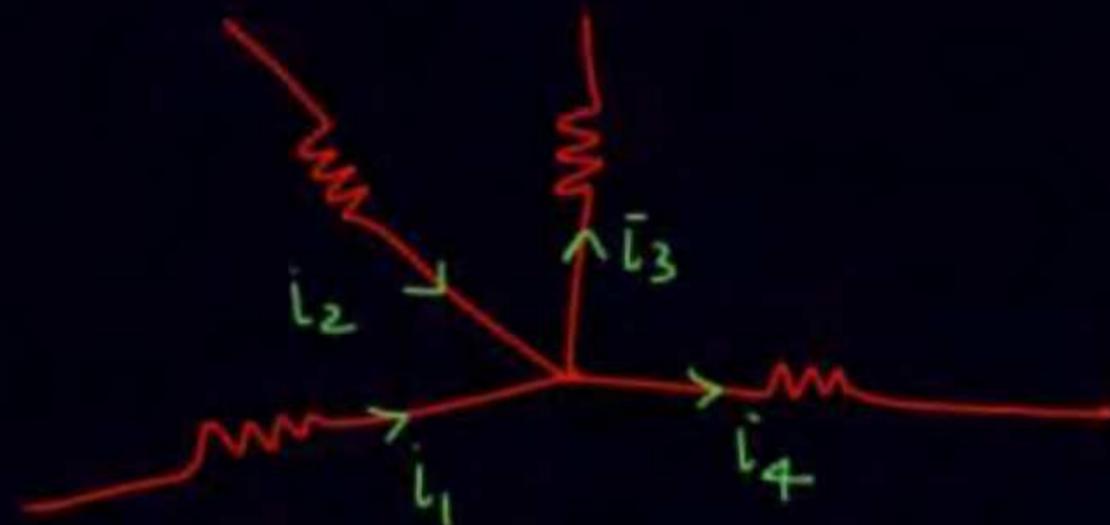

$$i_1 + i_2 = i_3 + i_4$$

ATDB.uno

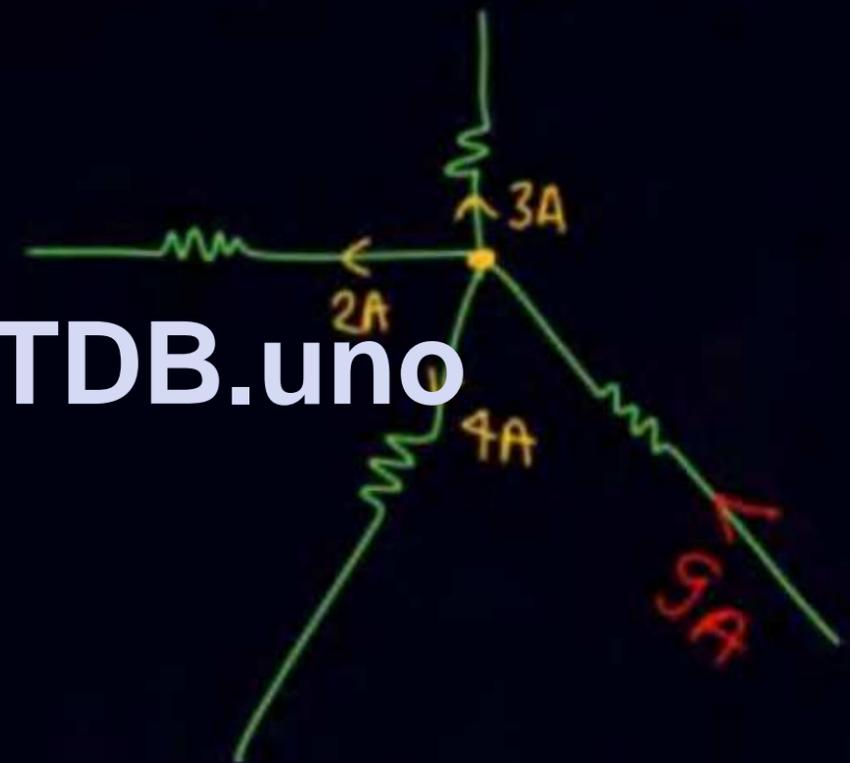

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$2 + 3 + 4 + i_4 = 0$$

$$i_4 = -9$$




काम का Jxn Law



ATDB.uno


$$i_1 + i_2 + i_3 + i_4 = 0$$

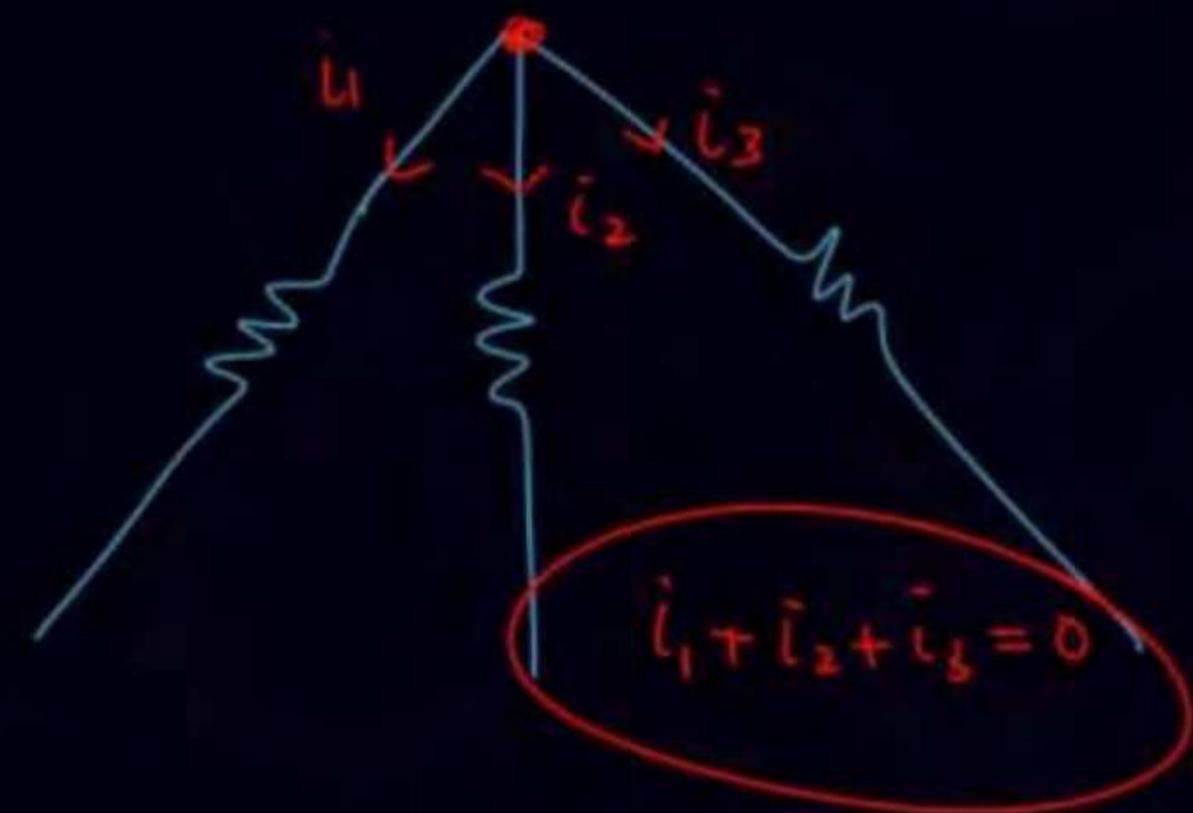



फंसने वाले सवाल

Q22

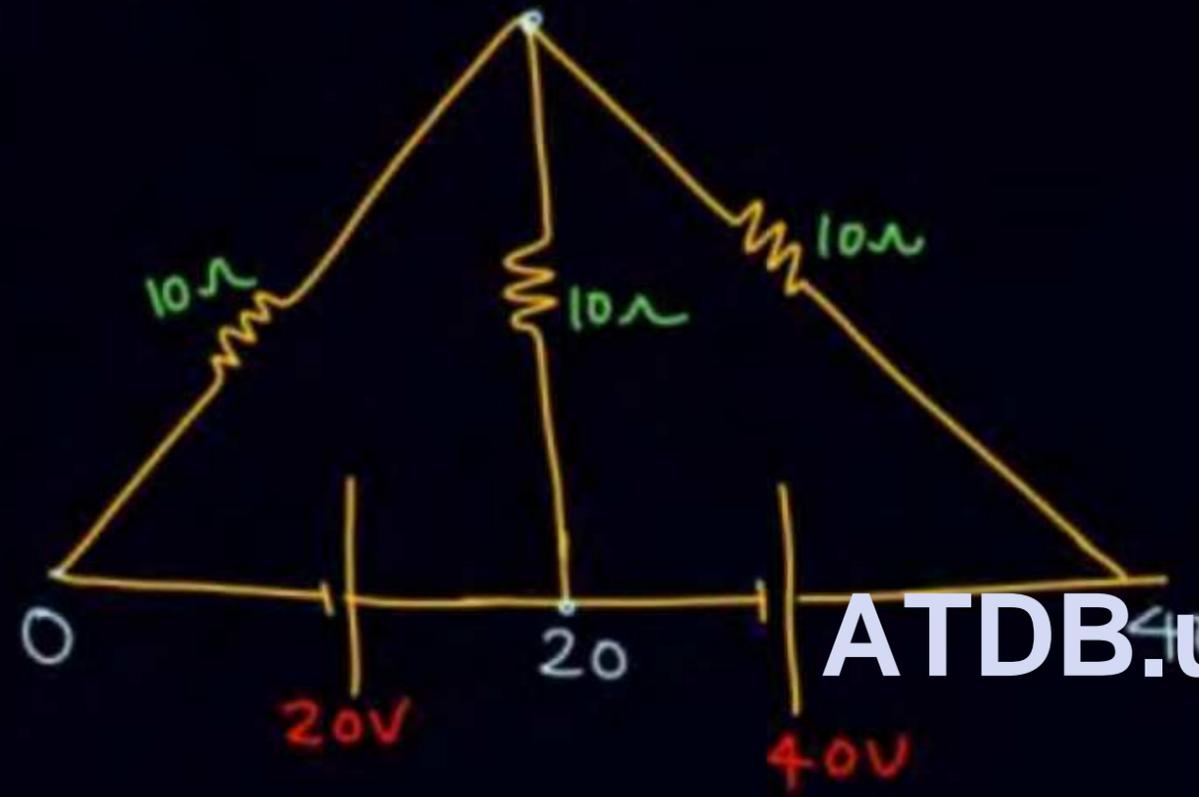


ATDB.uno



फंक्शने वाले सवाल

x (वडा मान लिए)

22

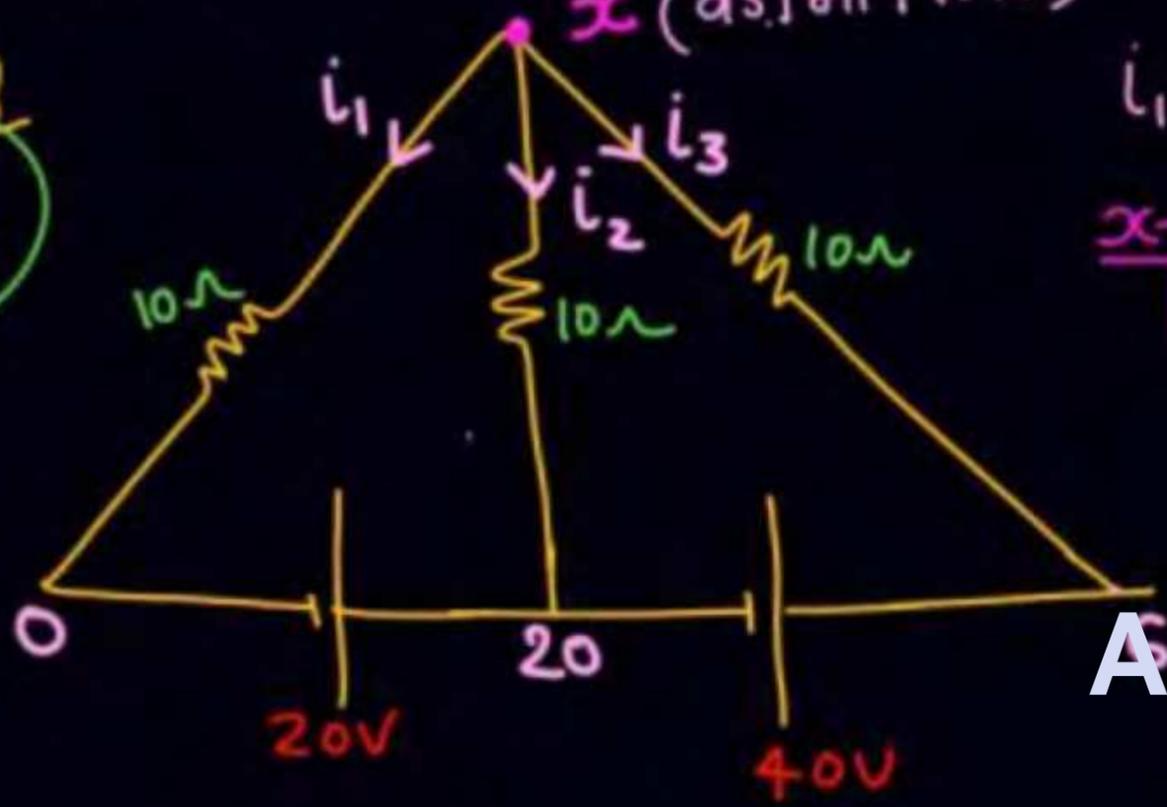

$$i_1 + i_2 + i_3 = 0$$

$$\frac{x-0}{10} + \frac{x-20}{10} + \frac{x-60}{10} = 0$$


$$x = \frac{80}{3}$$

ATDB.uno




$$i = \frac{V_A - V_B}{R}$$

$$i_0 = \frac{60 - \frac{80}{3}}{10}$$

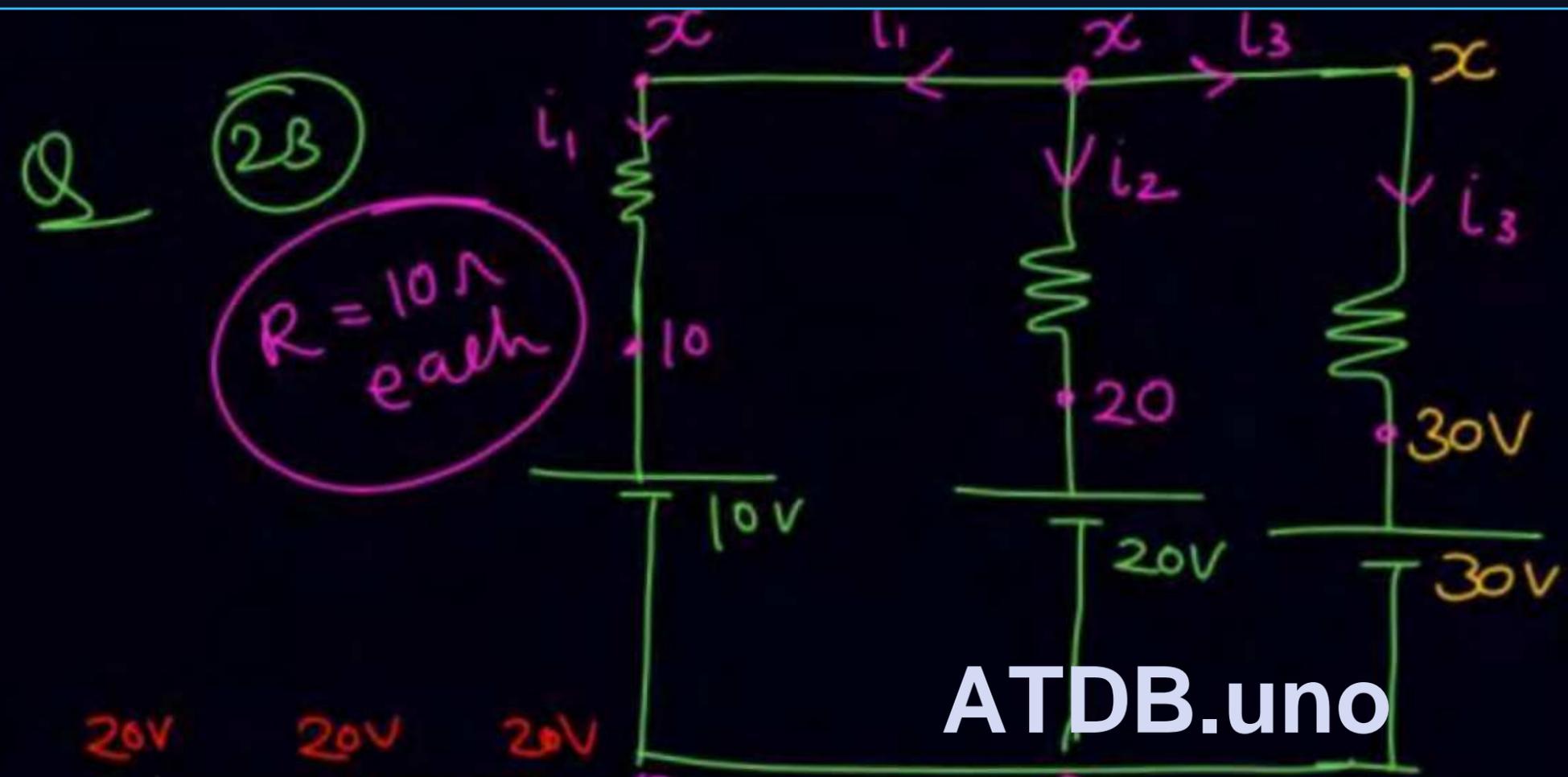


ATDB.uno

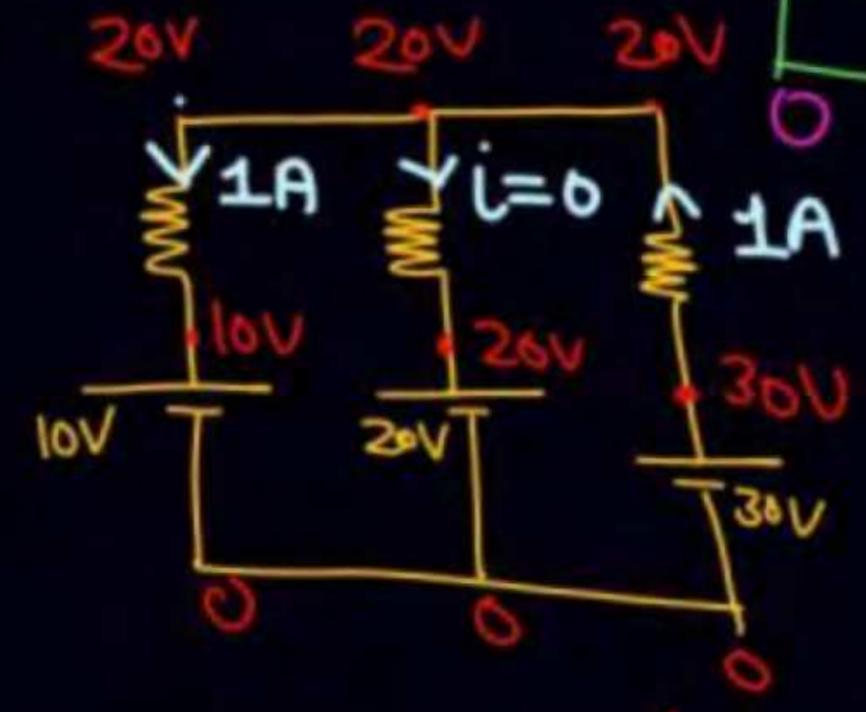


$$i_1 + i_2 + i_3 = 0$$

$$\frac{x-10}{10} + \frac{x-20}{10} + \frac{x-30}{10} = 0$$

$$x = 20$$

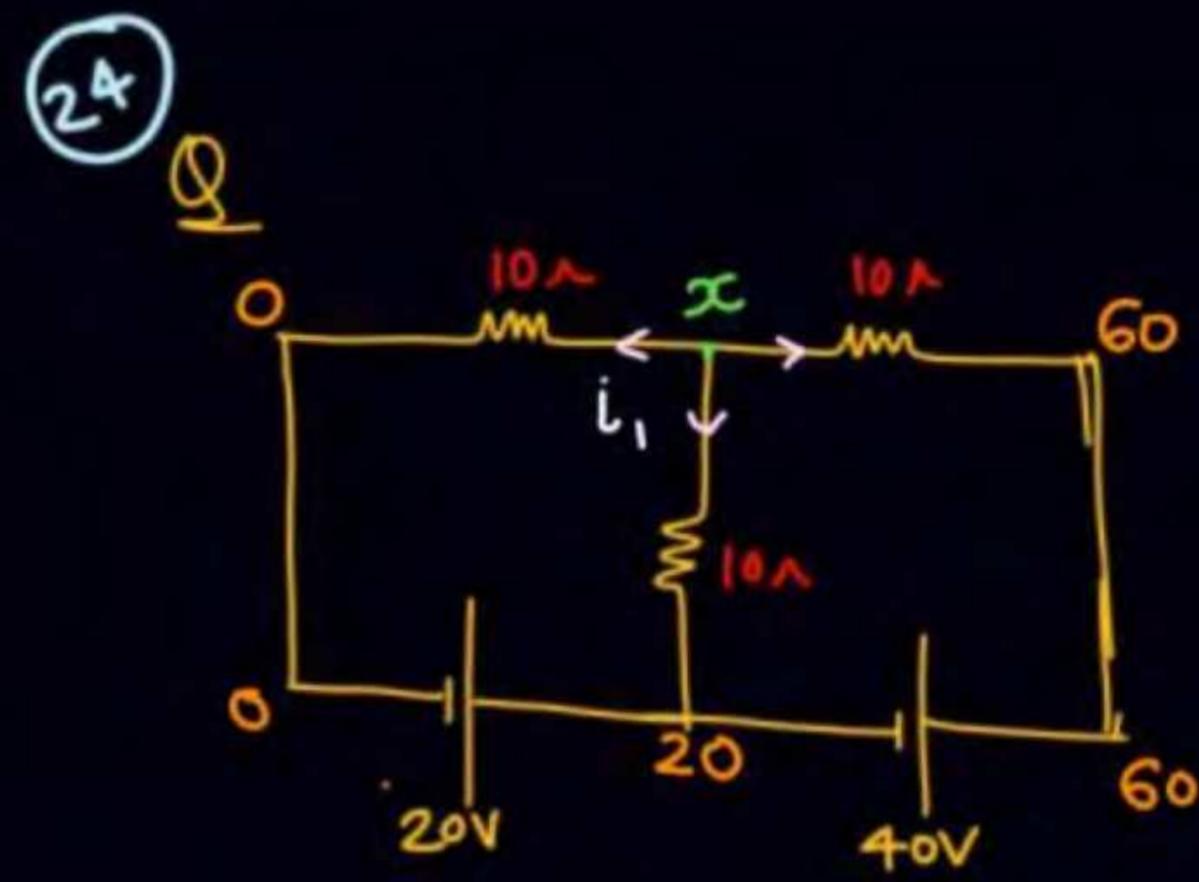

25 (tough)

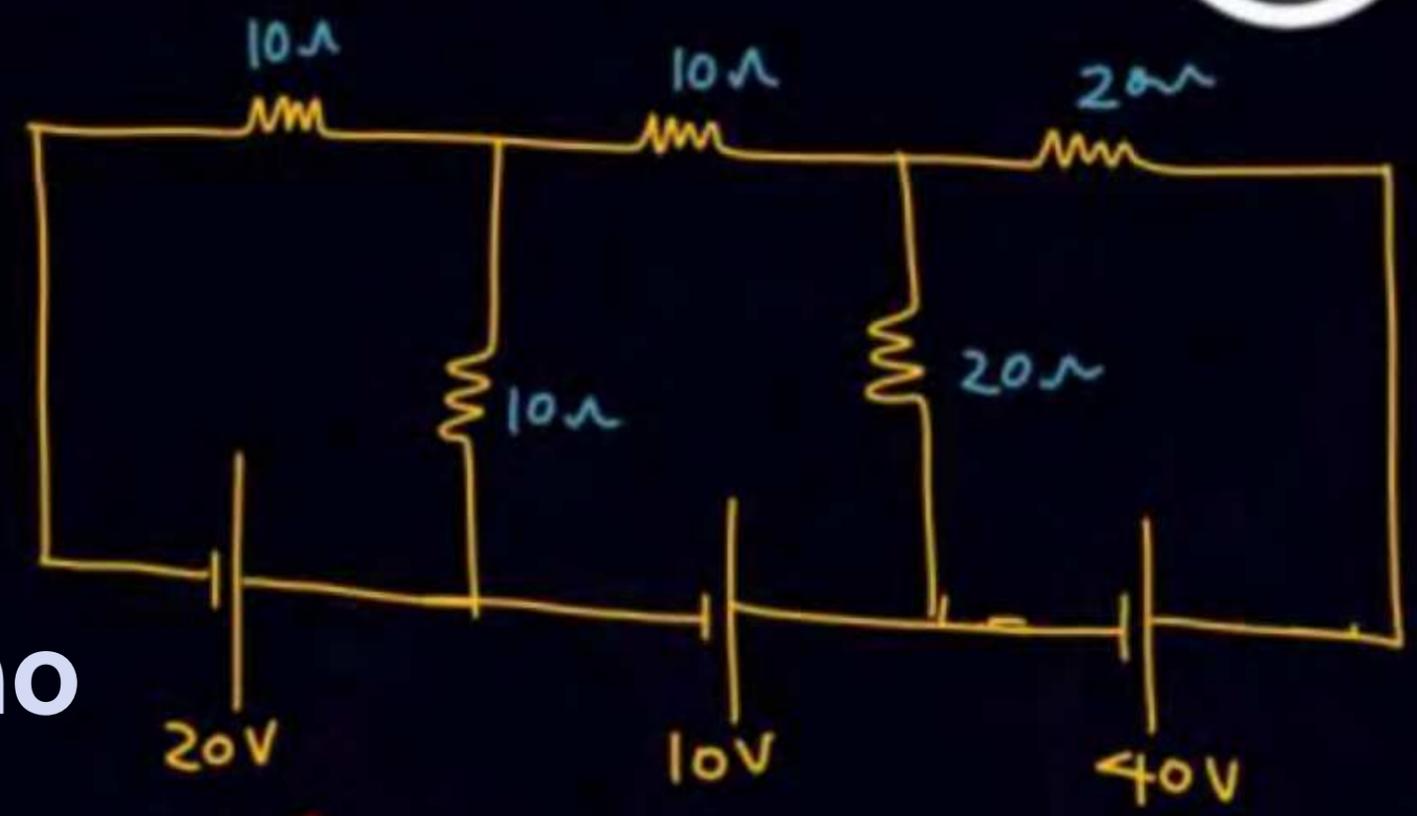

ATDB.uno

$$i_1 + i_2 + i_3 = 0$$

$$\frac{x-0}{10} + \frac{x-20}{10} + \frac{x-60}{10} = 0$$

$x = 80/3$

$$i_1 = \frac{\frac{80}{3} - 0}{10}$$

(next page)



25 (tough)


$$\frac{x-0}{10} + \frac{x-20}{10} + \frac{x-y}{10} = 0$$

$$\boxed{3x - y = 20} \quad \text{--- (1)}$$


$$\frac{y-x}{10} + \frac{y-30}{20} + \frac{y-70}{20} = 0$$

$$2y - 2x + y - 30 + y - 70 = 0$$
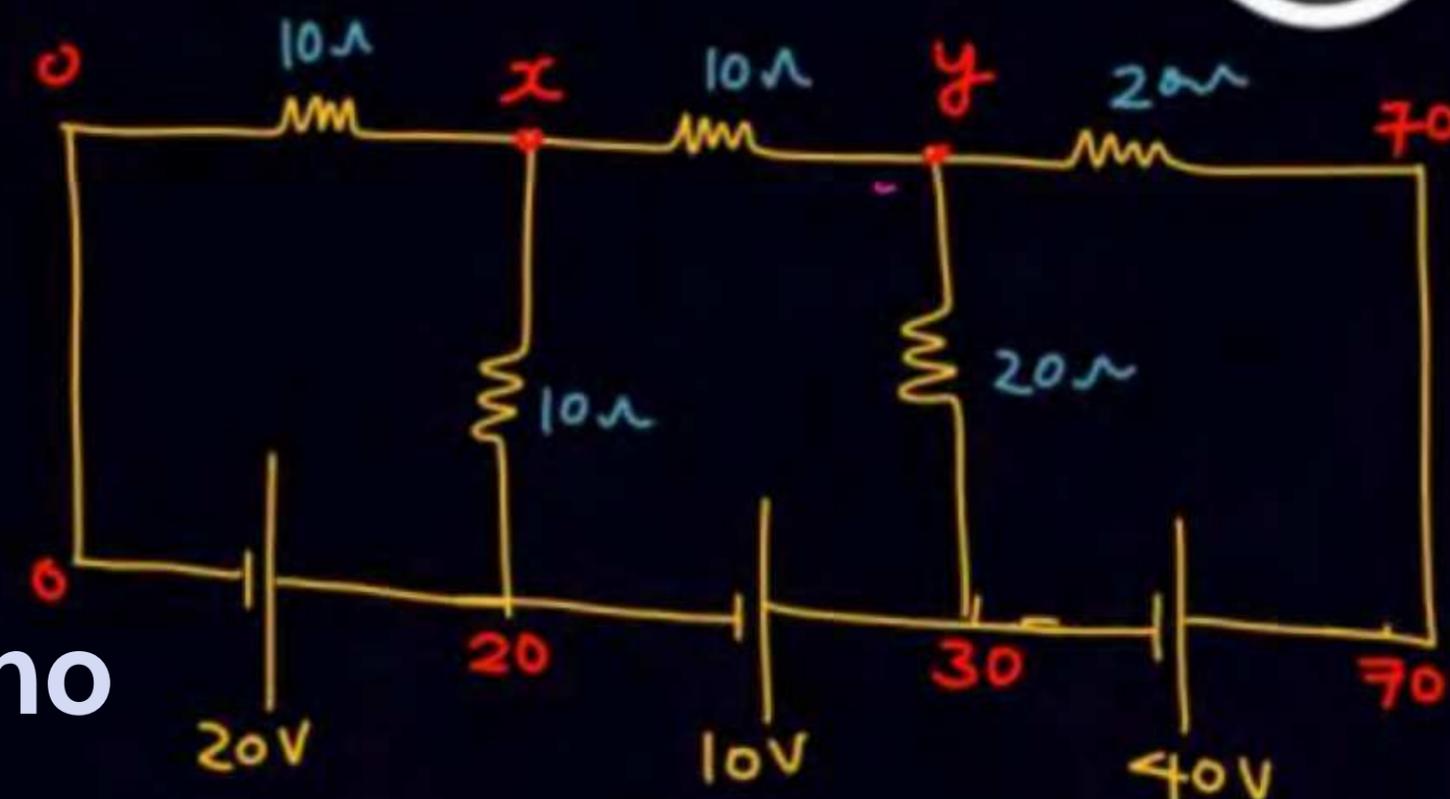
$$\boxed{4y - 2x = 100} \quad \text{--- (2)}$$



ATDB.uno

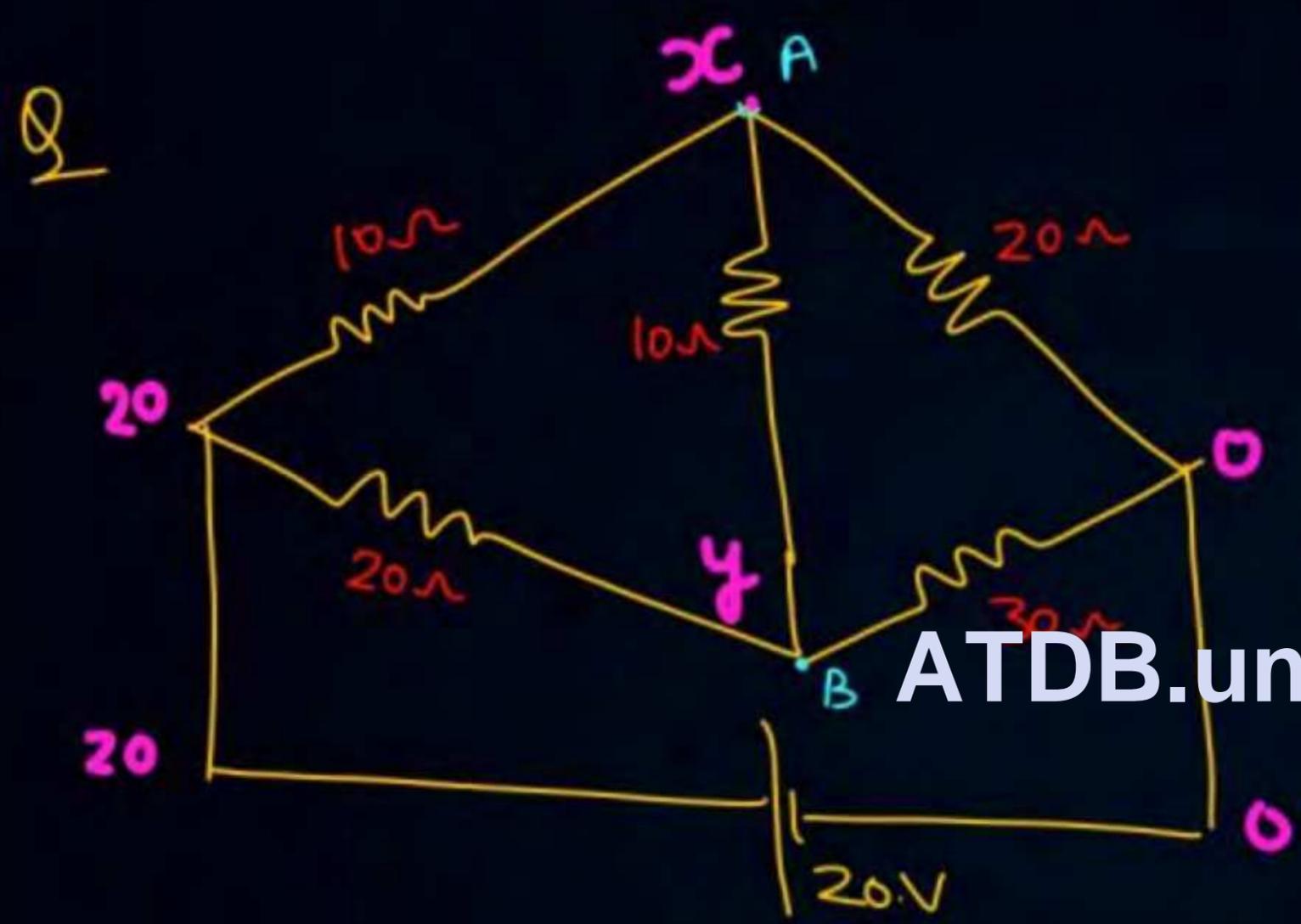

find $V_A - V_B = ?$

$$\frac{x-20}{10} + \frac{x-y}{10} + \frac{x-0}{20} = 0 \quad \left\{ \text{KCL} \right.$$

$$\frac{y-20}{20} + \frac{y-x}{10} + \frac{y-0}{30} = 0 \quad \left\{ \text{KCL} \right.$$

ATDB.uno

H/w (26)

Q




ATDB.uno

$R = 10 \Omega$ (each)



(27)

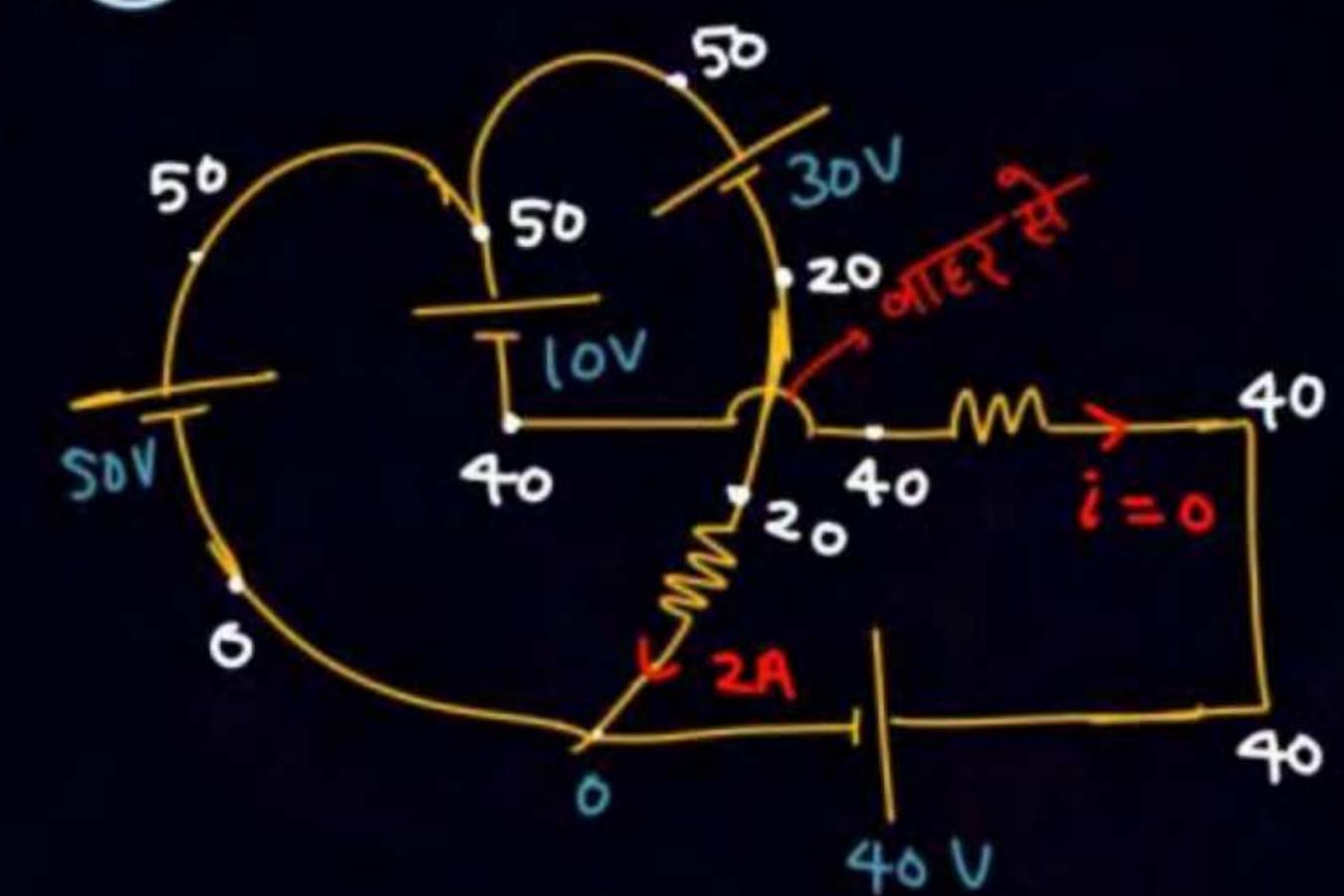



28




$$\frac{x-20}{10} + \frac{x-50}{10} + \frac{x+30}{10} = 0$$

$R = 10\Omega$ (each)

$$x = 40/3$$

29

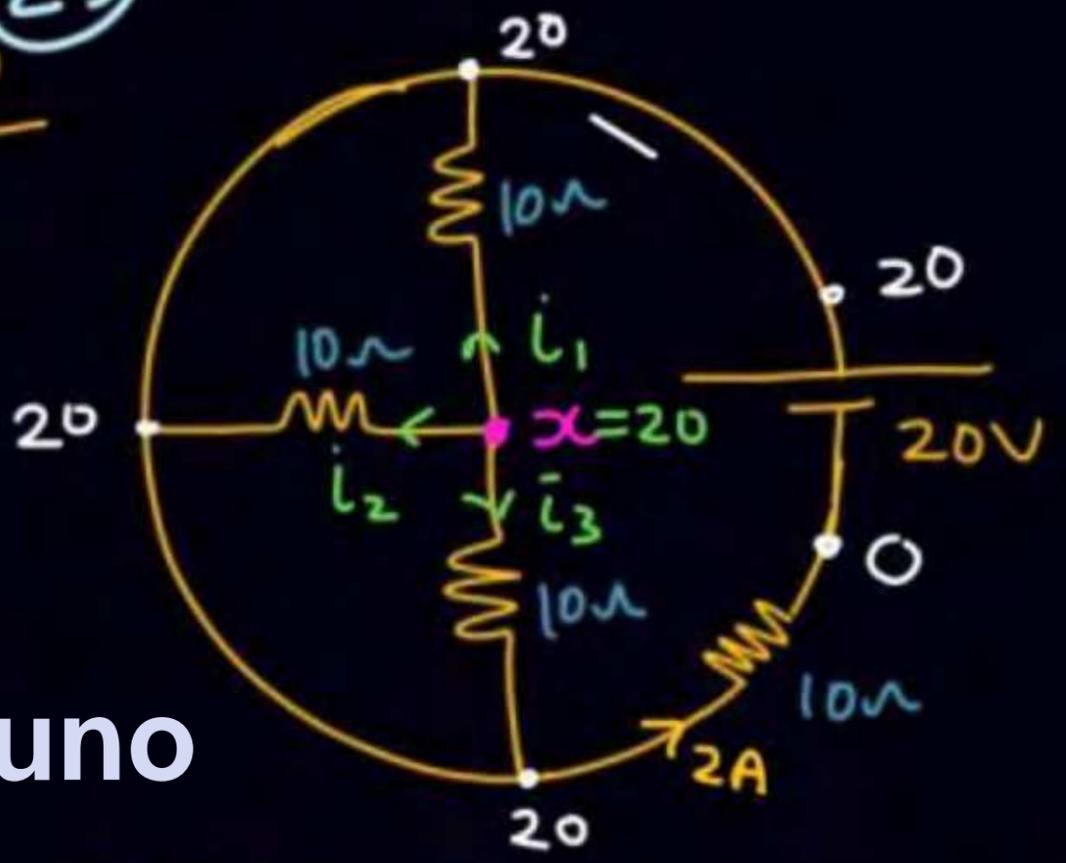

$$\frac{x-20}{10} + \frac{x-20}{10} + \frac{x-20}{10} \Rightarrow x = 20$$

$$i_1 = i_2 = i_3 = 0$$

ATDB.uno



30



ATDB.uno

$$\frac{x-0}{10} + \frac{x-10}{10} + \frac{x-0}{10} + \frac{x-y}{10} = 0 \Rightarrow$$

$$\frac{y-x}{10} + \frac{y-20}{10} + \frac{y-0}{10} = 0$$


$$\begin{cases} 4x - y = 10 \\ 3y - x = 20 \end{cases}$$

10. In the circuit shown, the current in the 1Ω resistor is :-

[JEE-Main 2015]

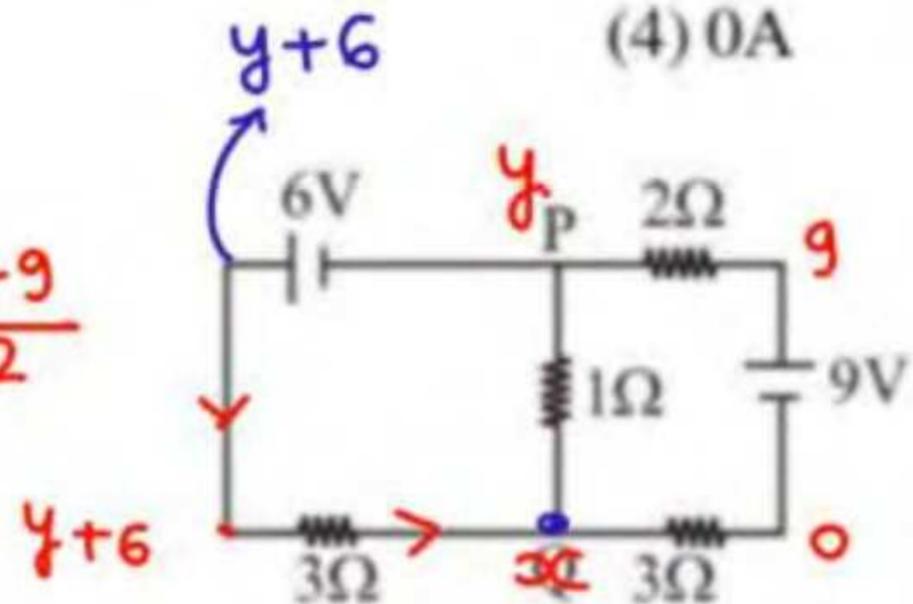- (1) 0.13 A, from Q to P
 (2) 0.13 A, from P to Q
 (3) 1.3 A, from P to Q
 (4) 0A

$$0 = \frac{y+6-x}{3} + \frac{y-x}{1} + \frac{y-9}{2}$$



$$\frac{x-(y+6)}{3} + \frac{x-y}{1} + \frac{x-9}{3} = 0$$

$$Aw = \frac{x-y}{1}$$

ATDB.uno

दर्शाये गये परिपथ में 1Ω प्रतिरोधक से प्रवाहित धारा होगी :-

[JEE-Main 2015]


- (1) 0.13 A, Q से P को
 (2) 0.13 A, P से Q को
 (3) 1.3 A, P से Q को
 (4) 0 A



Ans. (1)

32

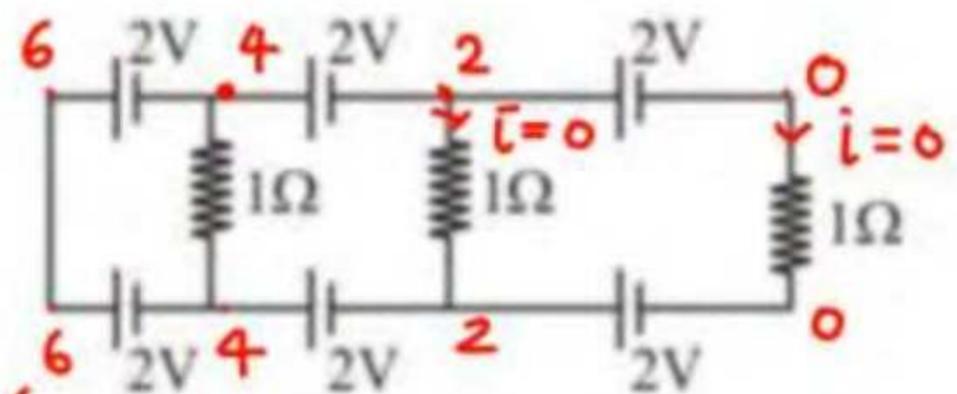ऊपर दिये गये परिपथ में प्रत्येक प्रतिरोध में धारा का मान होगा :-



(1) 0.5 A

 (2) 0 A

(3) 1 A

(4) 0.25 A

Ans. (2)


ATDB.uno

33

across AB in volts is

दो बैटरियाँ जिनके विद्युत वाहक बल तथा आंतरिक प्रतिरोध भिन्न-भिन्न हैं, को चित्र में दर्शाये अनुसार जोड़ा गया है। बिंदुओं A व B के बीच विभवान्तर ज्ञात कीजिए।

[IIT-JEE 2011]

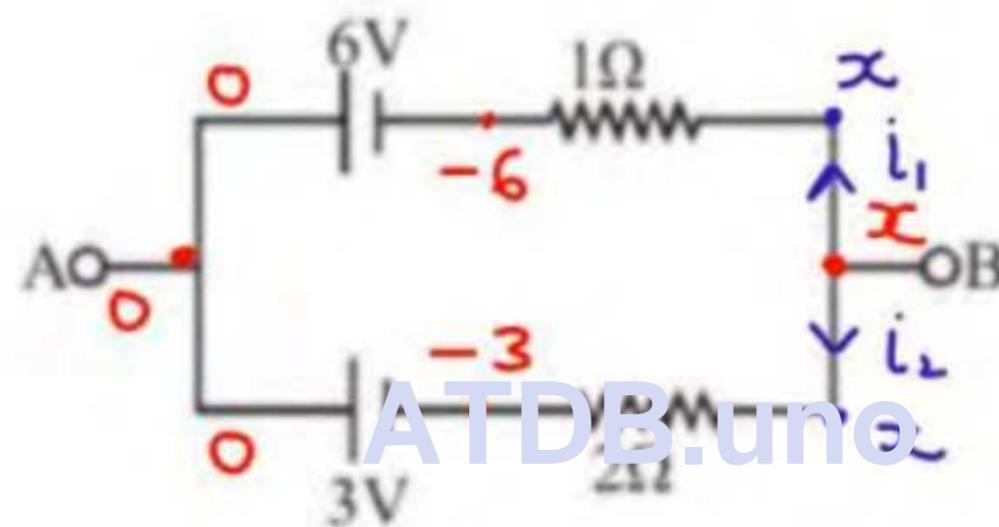

$$i_1 + i_2 = 0$$

$$\frac{x+6}{1} + \frac{x+3}{2} = 0$$

$$2x + 12 + x + 3 = 0$$

$$3x = -15$$

$$x = -5$$

Ans. 5

34

the figure. The current in resistance R_2 would be zero if :-

[JEE Advanced 2014]


(A) $V_1 = V_2$ and $R_1 = R_2 = R_3$

(C) $V_1 = 2V_2$ and $2R_1 = 2R_2 = R_3$

(B) $V_1 = V_2$ and $R_1 = 2R_2 = R_3$

(D) $2V_1 = V_2$ and $2R_1 = R_2 = R_3$

R_2 कितना भी हो
जर्क नहीं पड़ता

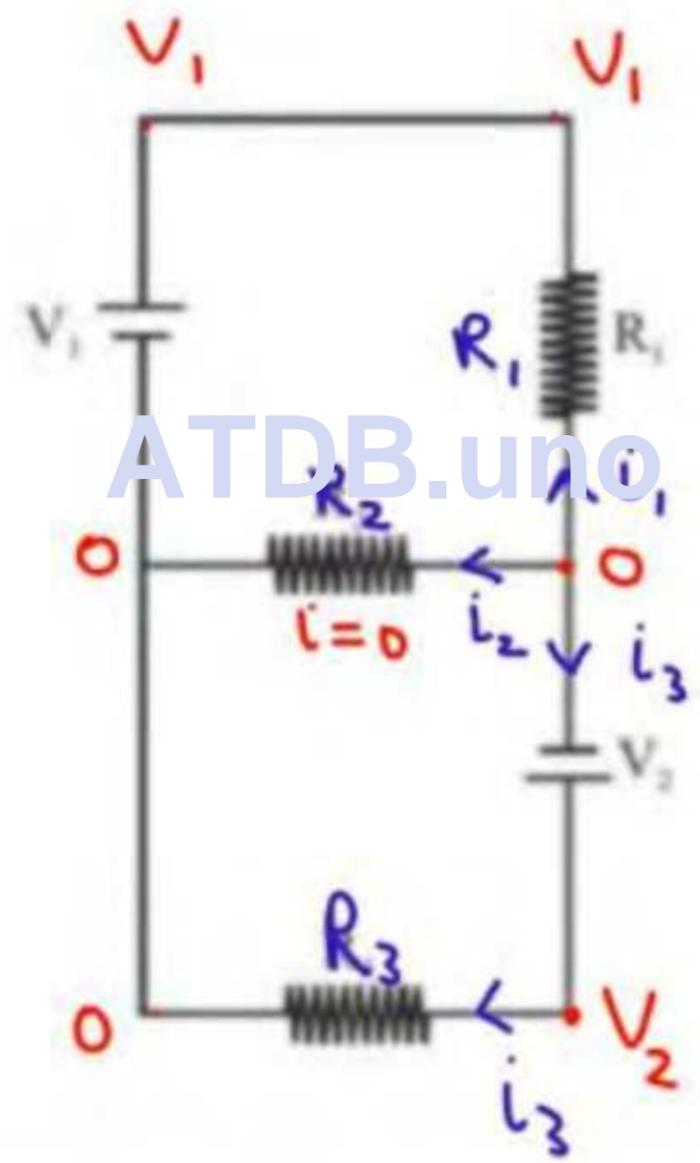

$$i_1 + i_2 + i_3 = 0$$

$$\frac{0 - V_1}{R_1} + 0 + \frac{V_2 - 0}{R_3} = 0$$


$$\boxed{\frac{V_1}{R_1} = \frac{V_2}{R_3}}$$

$$\frac{V_1}{R_1} = \frac{2V_1}{R_3}$$

$$\boxed{R_3 = 2R_1}$$

35

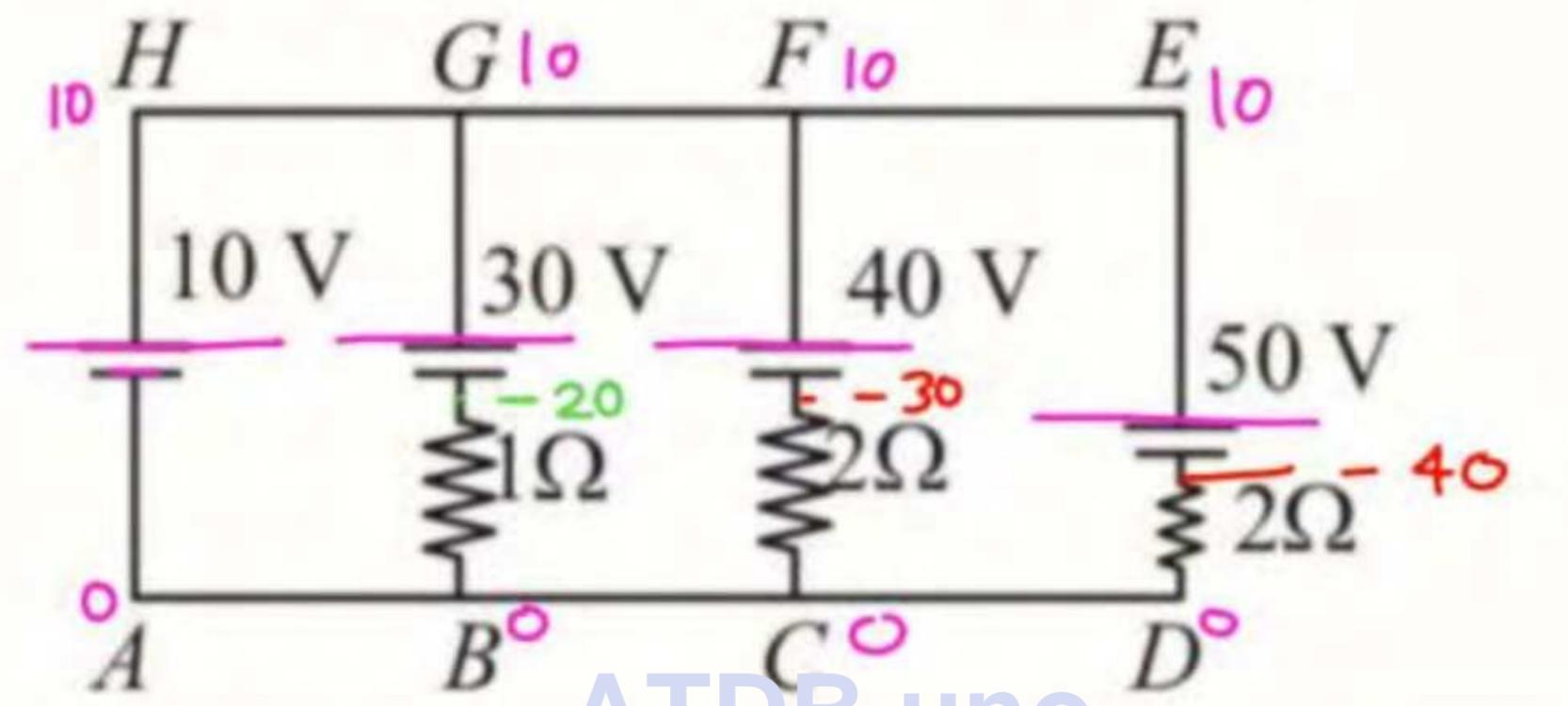Example 35. Find the current in each wire.





ATDB.uno

37

For what value of R in the circuit as shown, current through 4Ω will be zero?

- (a) 1Ω
- (b) 2Ω
- (c) 3Ω
- (d) 4Ω

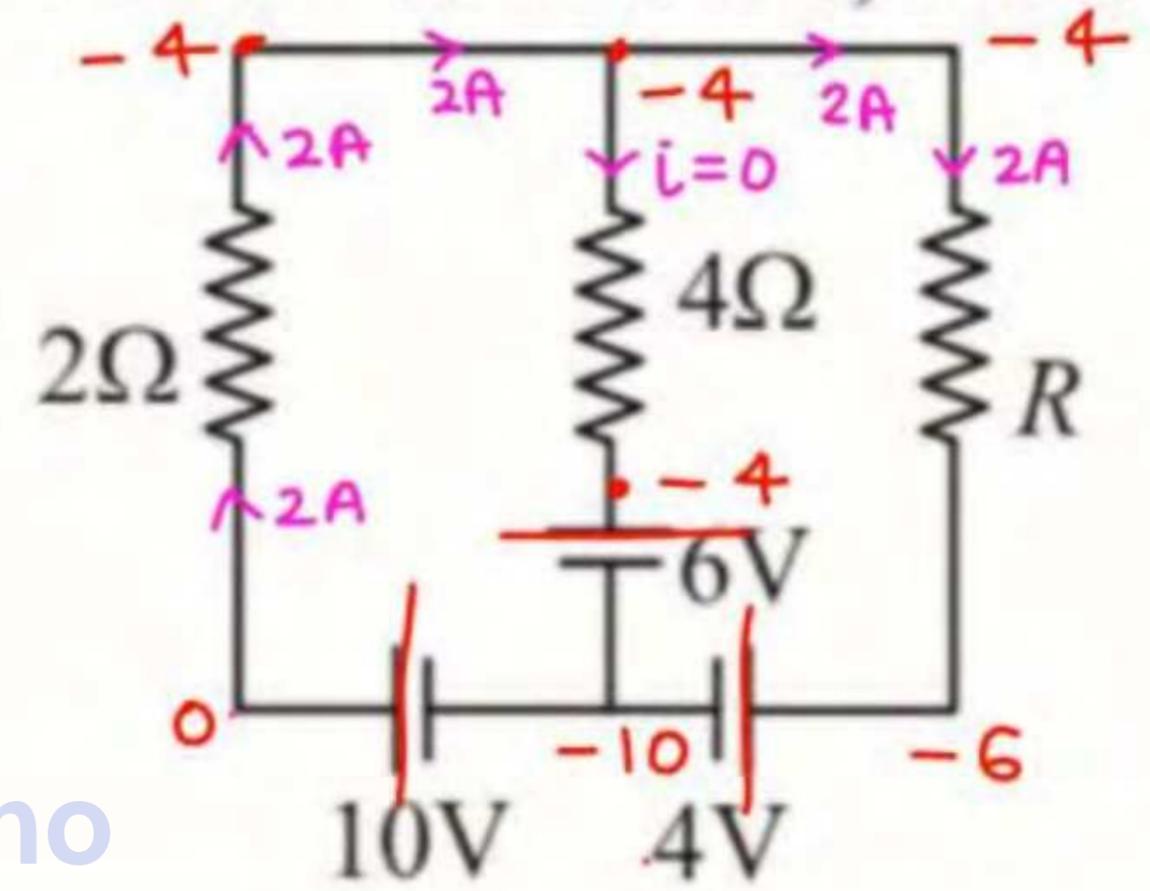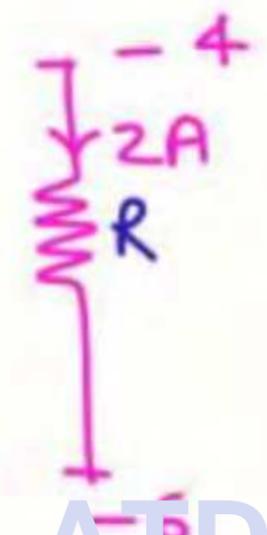

$$V = iR$$

$$2 = 2 \times R$$

ATDB.uno

38

Find the currents I , I_1 and I_2 (all in amperes) for the circuit shown.

(a) 2, 1 and 1

(b) $\frac{1}{2}$, $\frac{1}{2}$ and 0

(c) $\frac{3}{2}$, $\frac{1}{2}$ and 1


(d) $\frac{1}{2}$, 0 and $\frac{1}{2}$

$$\frac{x-4.5}{3} + \frac{x-0}{6} + \frac{x-3}{10} = 0 \quad x$$

$$10x - 45 + 5x + 3x - 9 = 0$$

$$18x = 54$$

$$x = 3$$

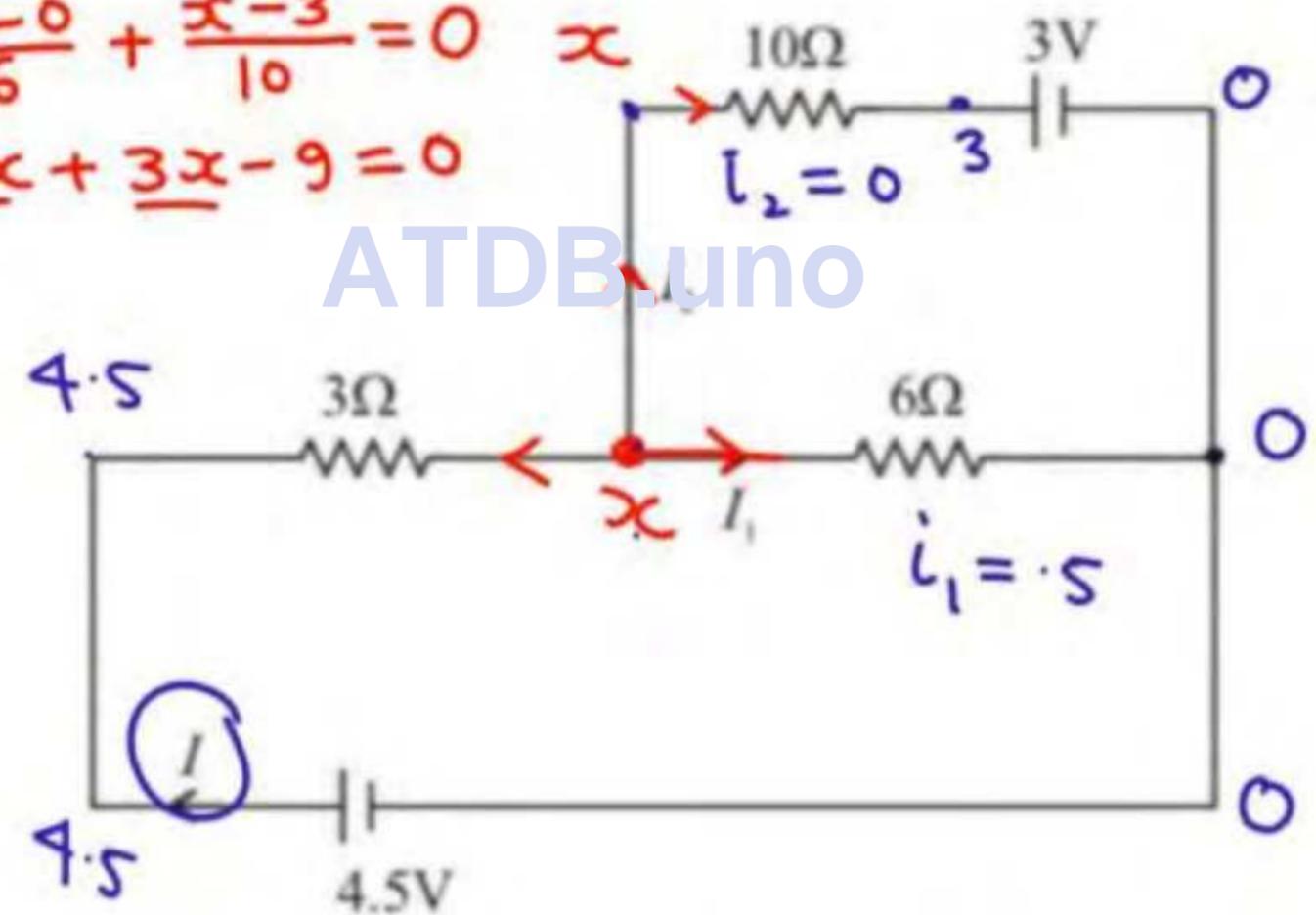


(JEE Lakshya Physics M-1)



39. Current in $3\ \Omega$ resistance is


$$i_3 = \frac{\frac{30}{7} - 0}{6}$$

(a) 1 A

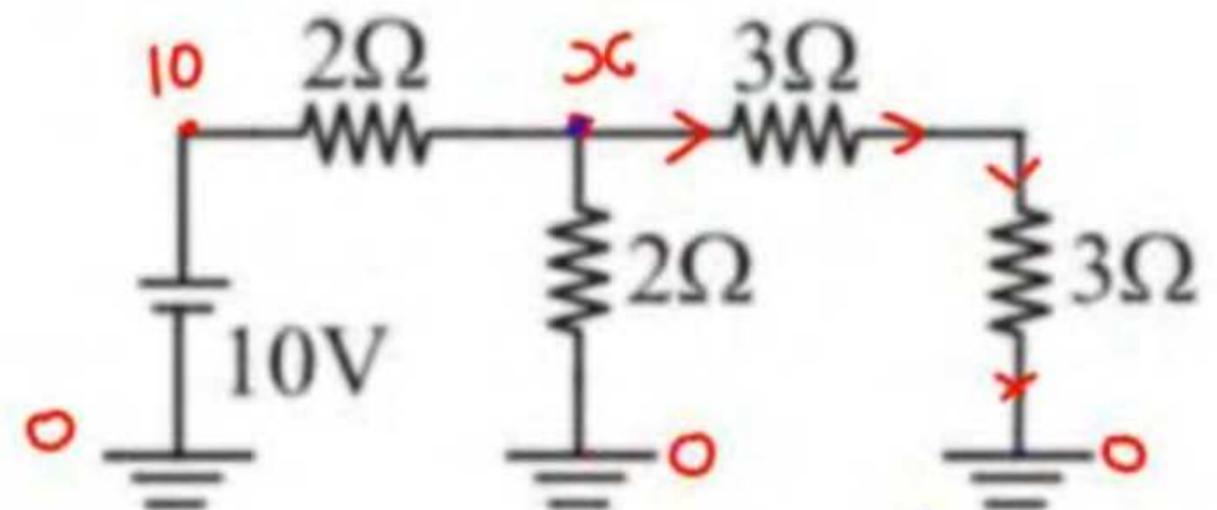

(b) $\frac{1}{7}$ A

(c) $\frac{5}{7}$ A

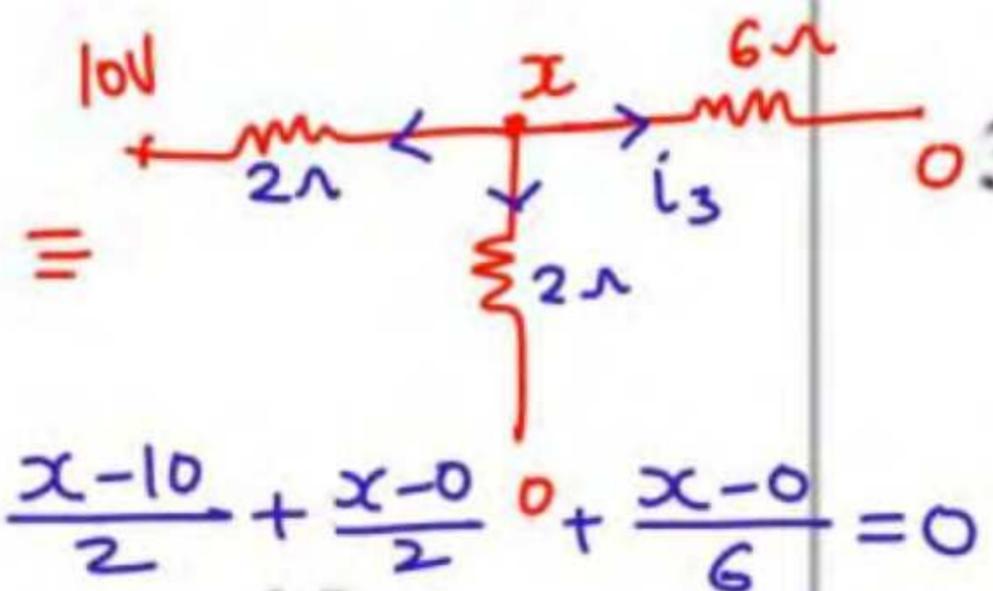

$$\frac{x-10}{2} + \frac{x-0}{2} + \frac{x-0}{6} = 0$$


(d) $\frac{15}{7}$ A

$$3x - 36 + 3x + x = 0$$

$$x = \frac{36}{7}$$

Find out the current in the wire BD shown in the figure.

~~4A~~

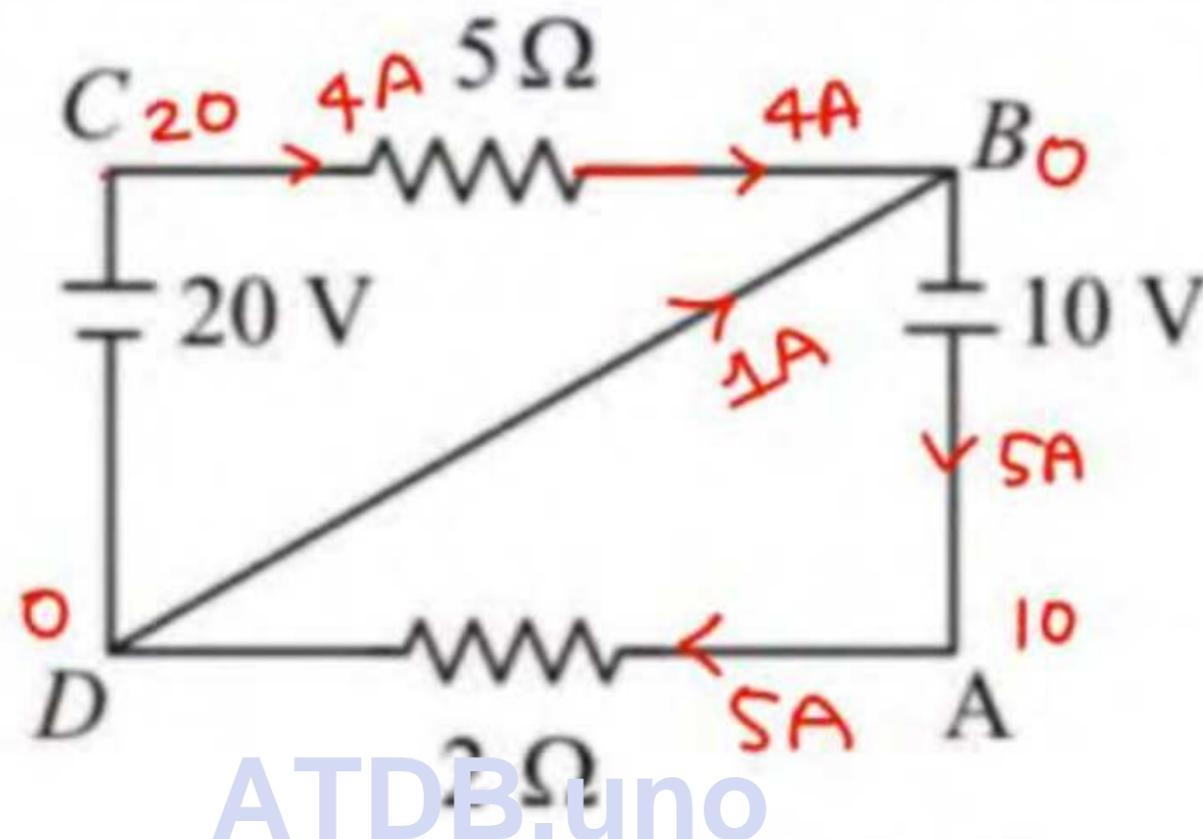

(a) 1A


(b) 2A

(c) 3A

(d) 4A

(JEE Lakshya Physics M-1)

41 In the shown circuit

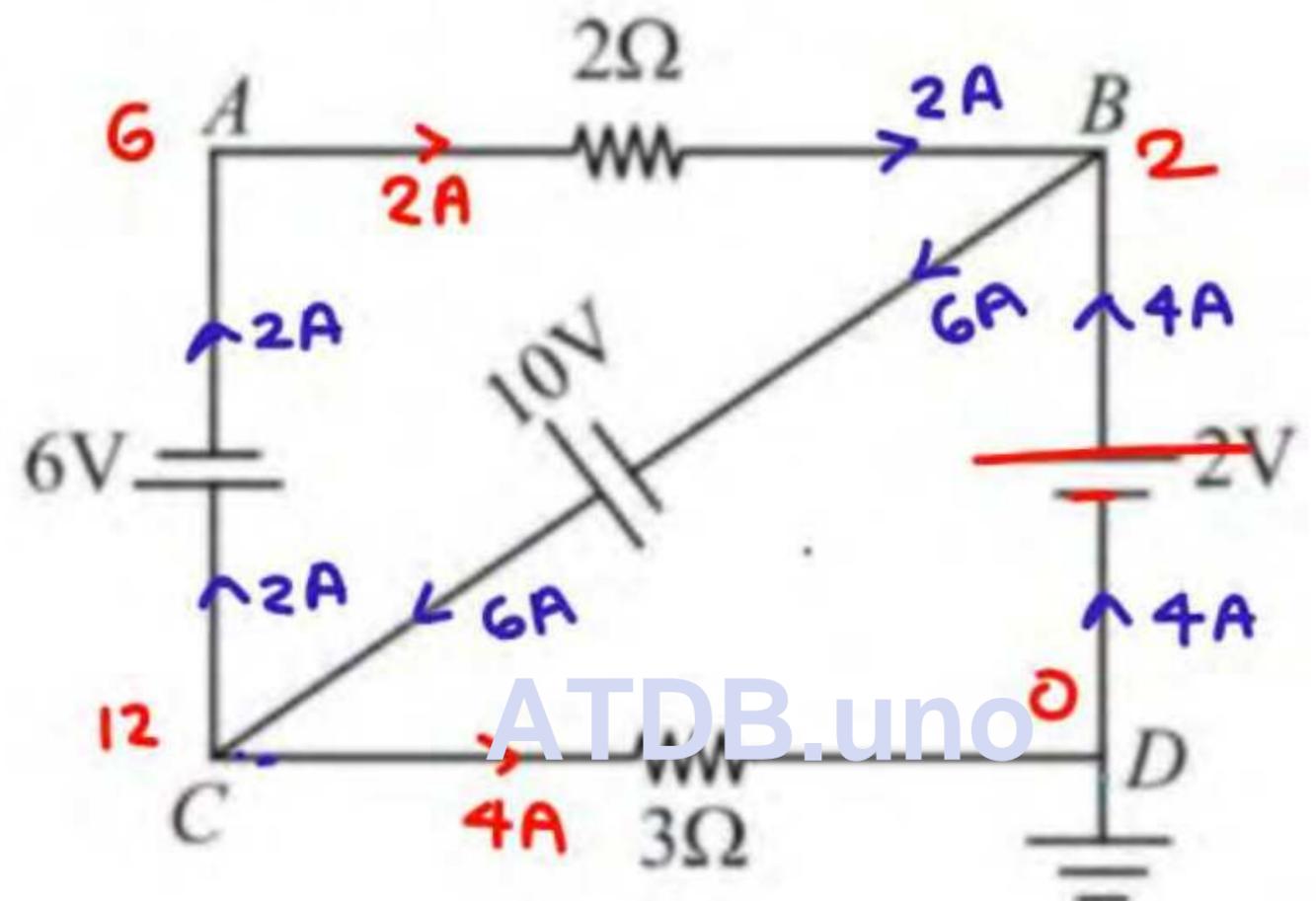


- (a) current passing through $2\ \Omega$ resistance is $2\ \text{A}$
- (b) current passing through $3\ \Omega$ resistance is $4\ \text{A}$
- (c) current in the wire between D to earth is zero
- (d) potential of point A is $10\ \text{V}$

(JEE Lakshya Physics M-1)

36. Find the potential difference $V_a - V_b$ in the circuits shown in figure (32-E12).

42


0-x Ans

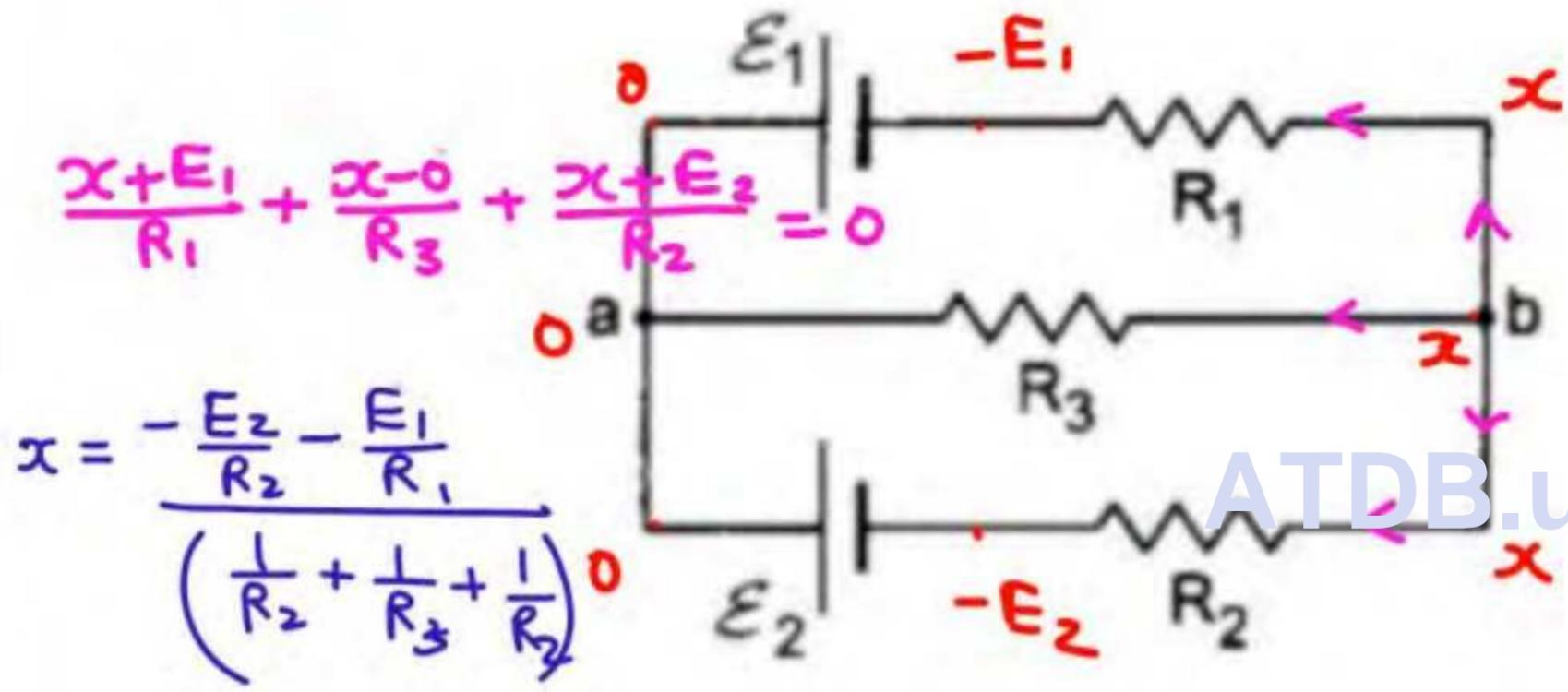

$$\frac{x+E_1}{R_1} + \frac{x-0}{R_3} + \frac{x+E_2}{R_2} = 0$$

$$x = \frac{-\frac{E_2}{R_2} - \frac{E_1}{R_1}}{\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_1}\right)}$$

(a)

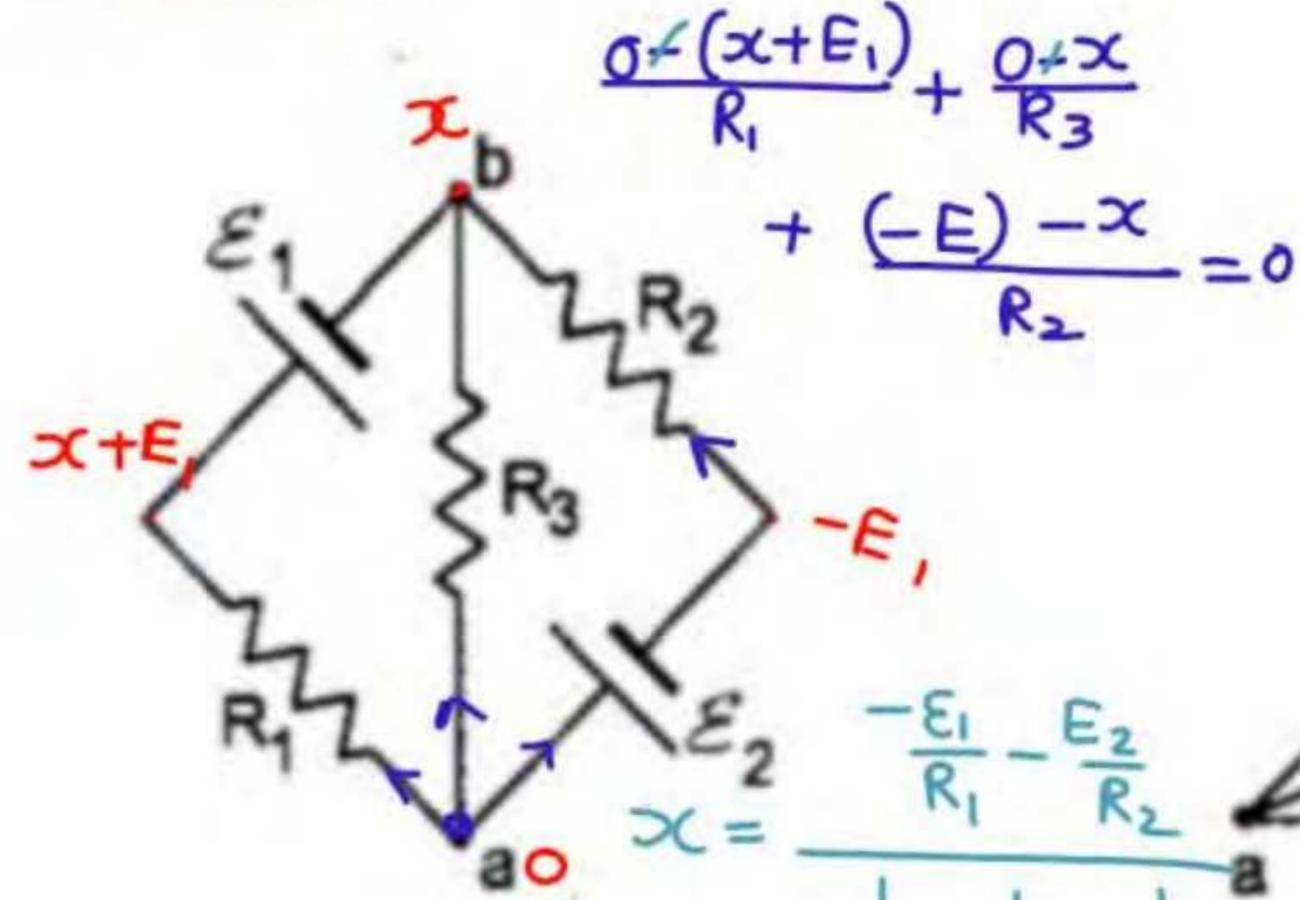

$$\frac{0-(x+E_1)}{R_1} + \frac{0-x}{R_3} + \frac{(-E_2)-x}{R_2} = 0$$

$$x = \frac{-\frac{E_1}{R_1} - \frac{E_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

(b)

Ans 0-x

HCV 38

38. Find the current through the 10Ω resistor shown in figure (32-E14).

$$\frac{x-4.5}{3} + \frac{x-3}{10} + \frac{x-0}{6} = 0$$

$$10x - 45 + 3x - 9 + 5x = 0$$

$$18x = 54$$

$$x = 3$$

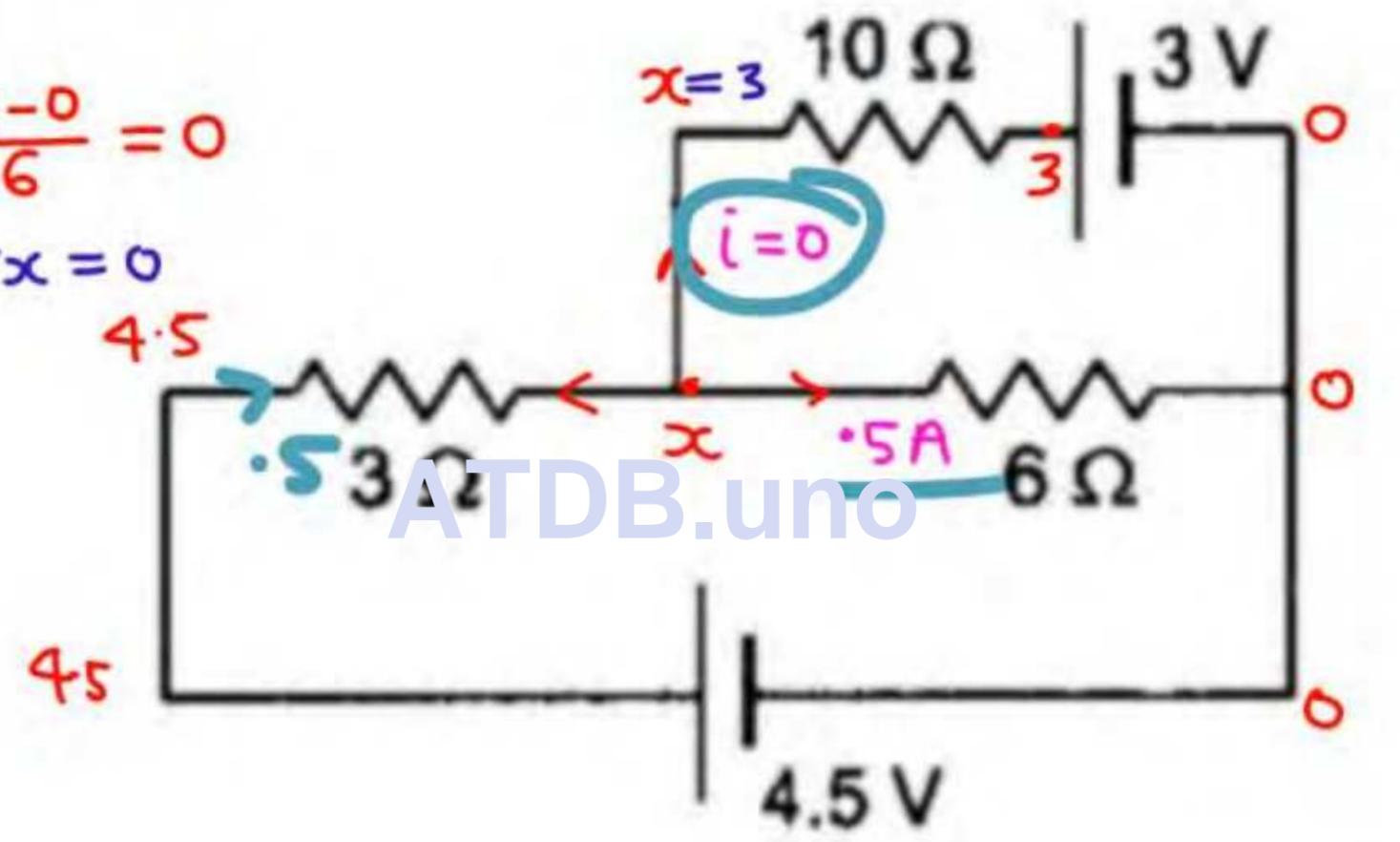


Figure 32-E14

44
HCV

In the circuit shown in figure (32-E13), $\mathcal{E}_1 = 3\text{ V}$, $\mathcal{E}_2 = 2\text{ V}$, $\mathcal{E}_3 = 1\text{ V}$ and $r_1 = r_2 = r_3 = 1\ \Omega$. Find the potential difference between the points A and B and the current through each branch.

$$0 = \frac{x-3}{1} + \frac{x-2}{1} + \frac{x-1}{1}$$

$$x = 2$$


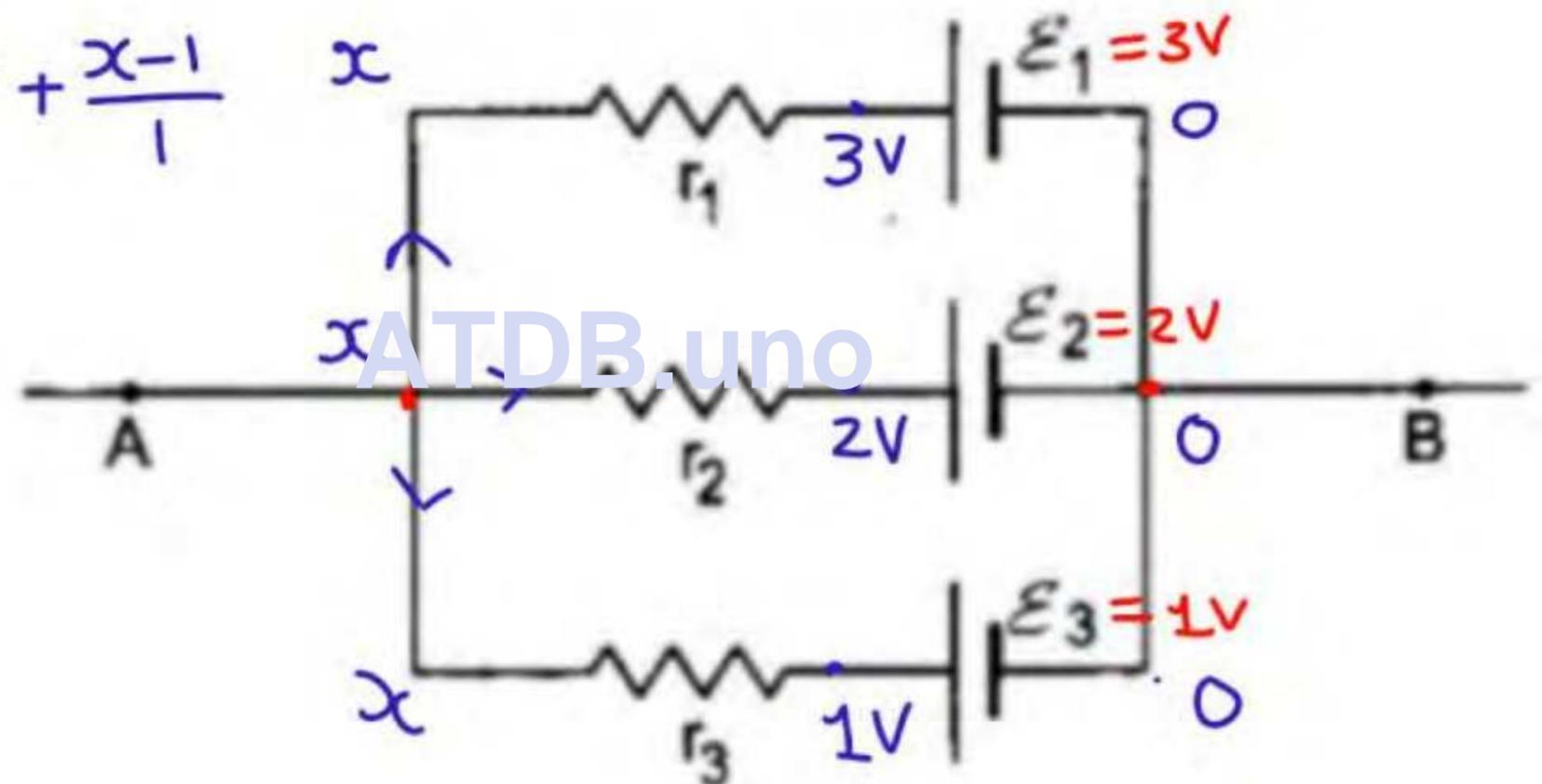


Figure 32-E13

10. In the circuit shown in figure

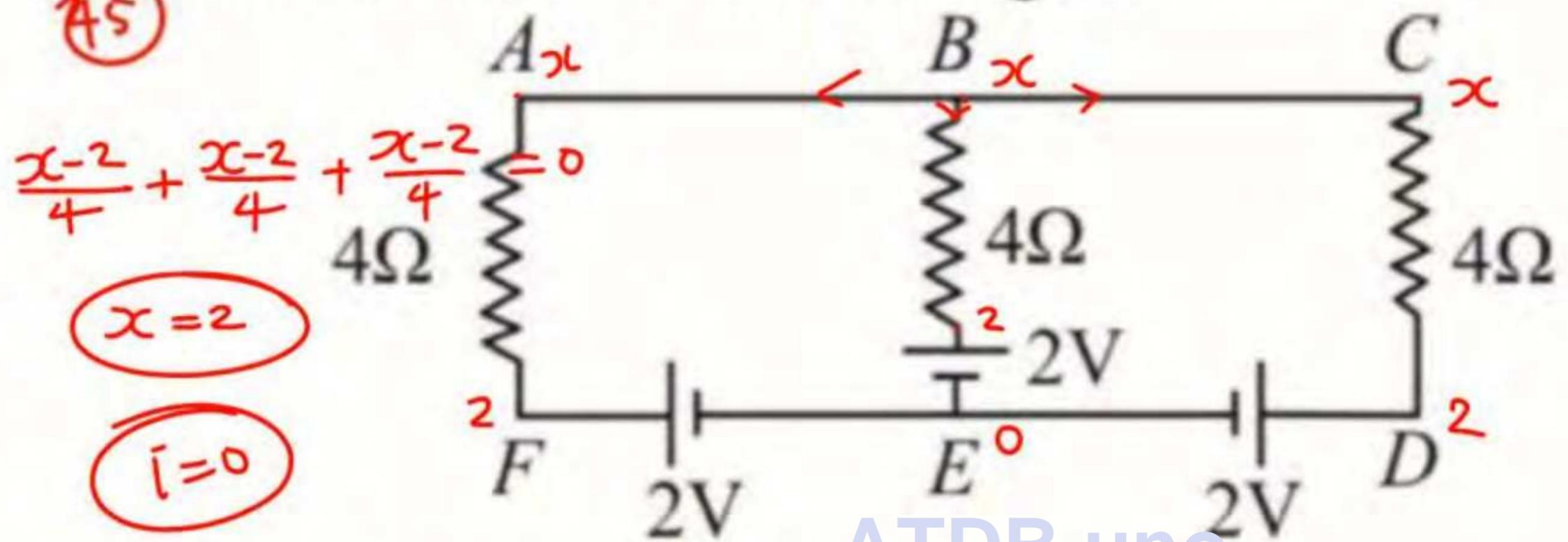


- (a) Current in wire AF is $1A$ ~~X~~
- (b) Current in wire CD is $1A$ ~~X~~
- (c) Current in wire BE is $2A$ ~~X~~
- (d) None of these



ATDB.uno

$1 \mu\text{F}$ capacitor
 $10q_2$) (in μC).

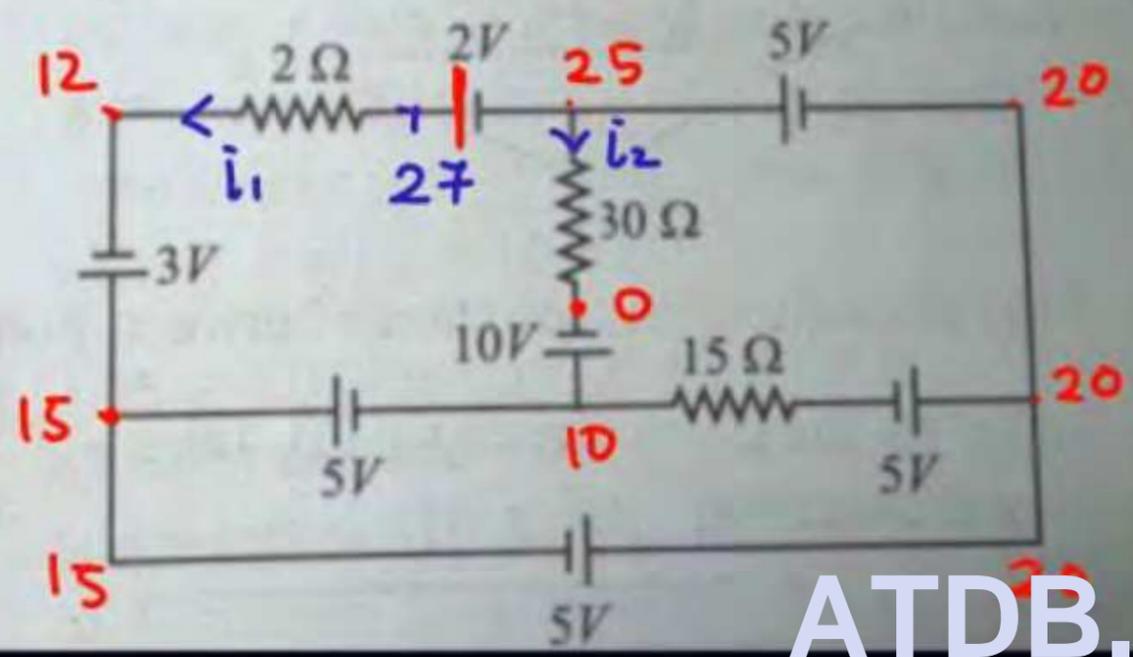47. In the circuit shown, current through the resistance 2Ω is i_1 and current through the resistance 30Ω is i_2 . Find the ratio i_1 / i_2 .





$$i_1 = \frac{15}{2}$$

$$i_2 = \frac{25}{30}$$

$$\frac{i_1}{i_2} = \frac{\frac{15 \times 30}{2 \times 25}}{\frac{25}{30}} = \frac{90}{10} = 9$$

ATDB.uno **ANS 9**



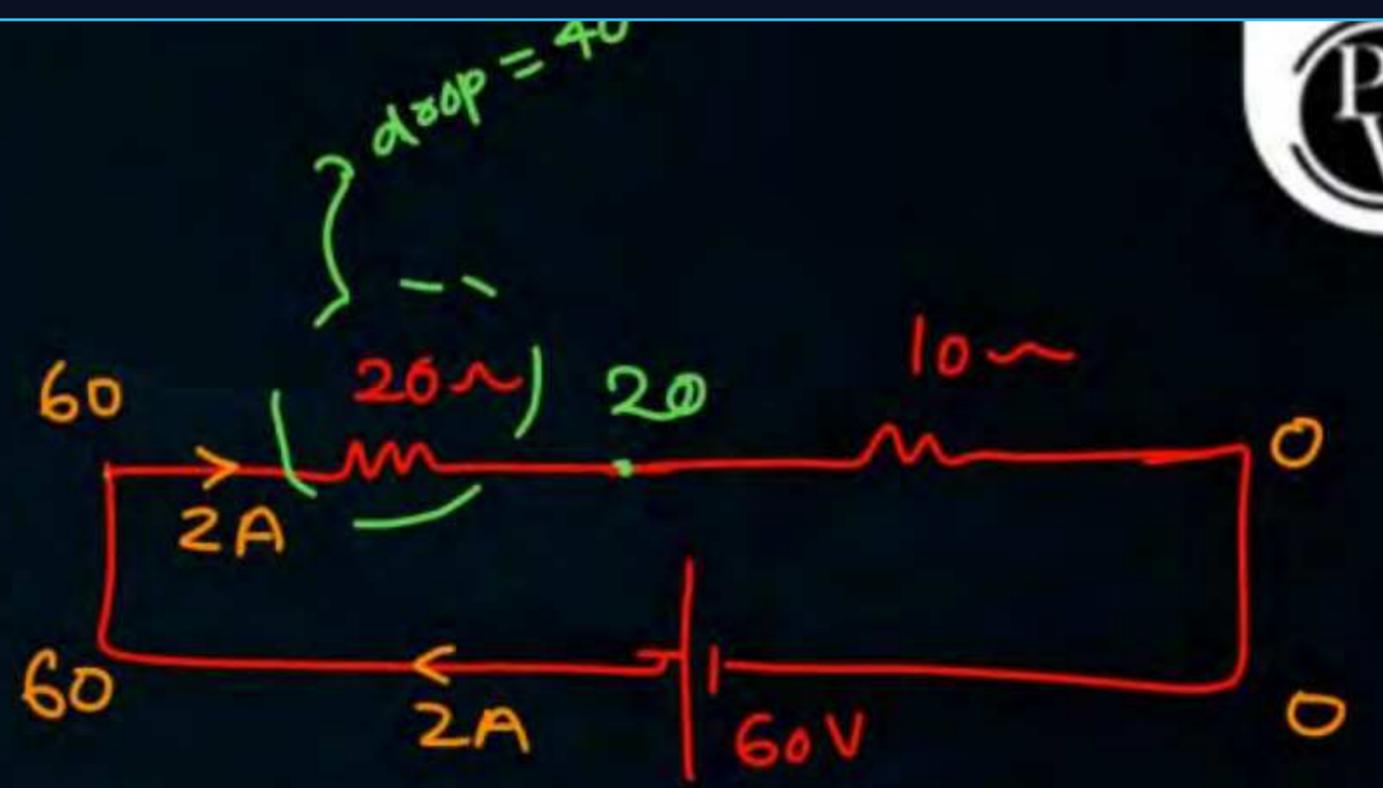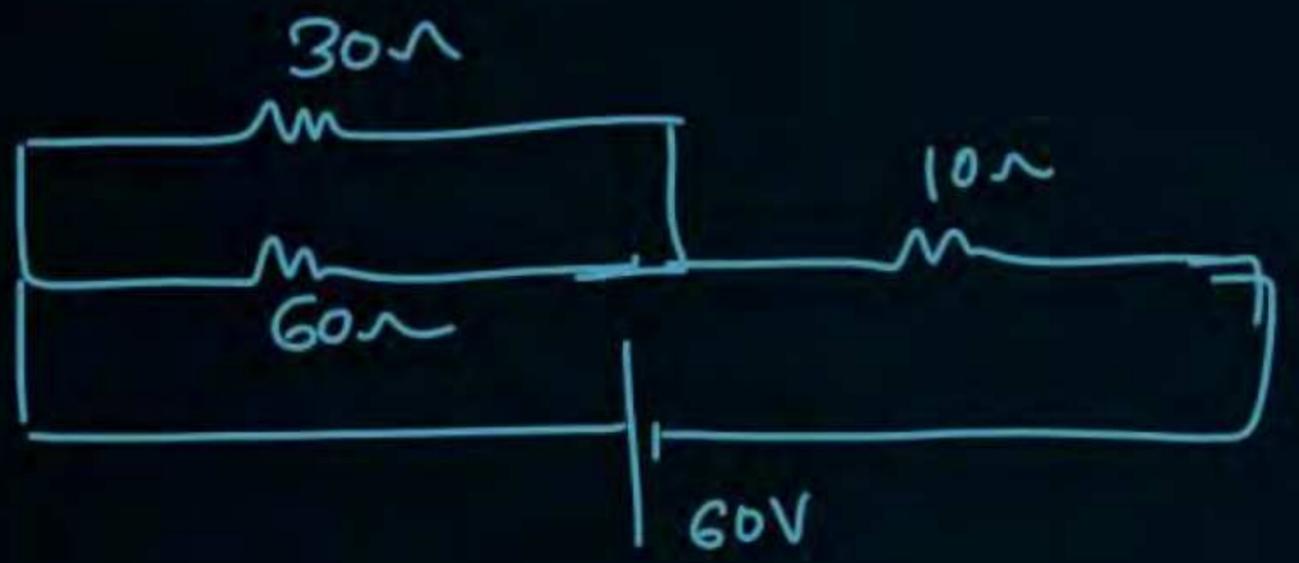

ATDB.uno



50



$$i_1 = \frac{60}{30+60} \times 2 = \frac{120}{90} = \frac{4}{3}$$

Find ratio of current through 30Ω before switch close to after switch close




$$\text{Ans } \frac{(i_1)_i}{(i_1)_f} = \frac{4/3}{2} = \frac{4}{6}$$




54

4

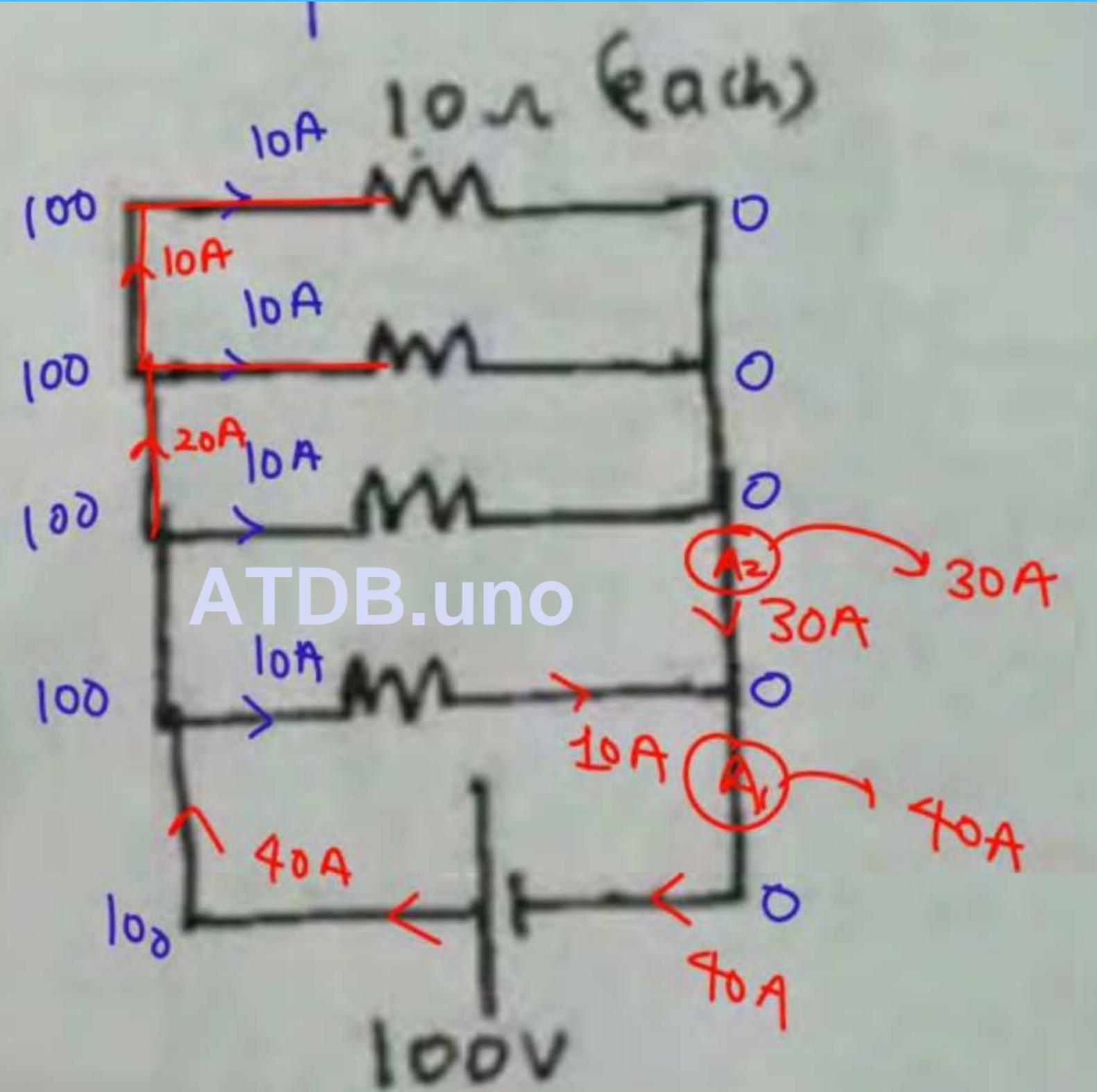

ATDB.uno

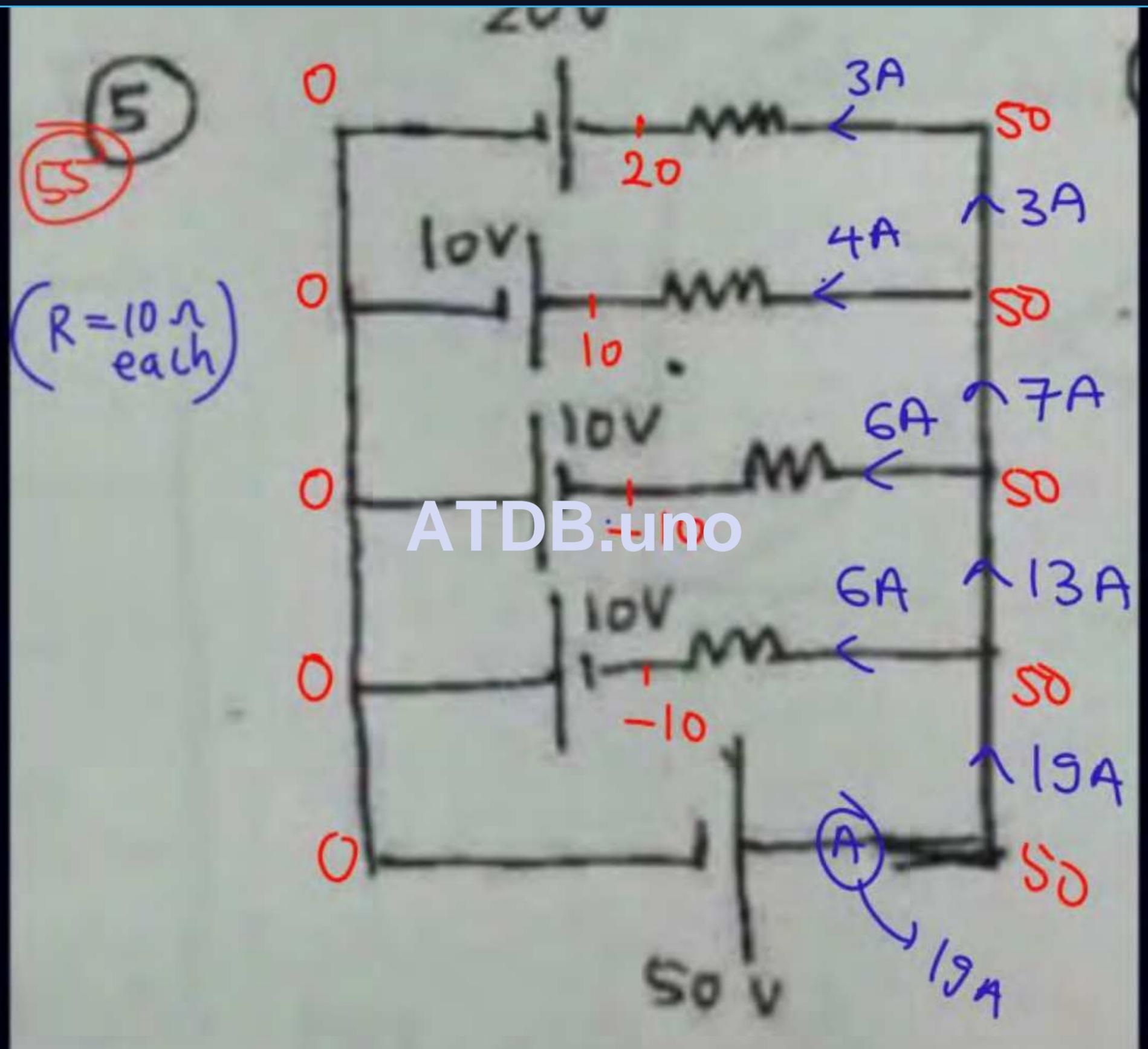


ATDB.uno




(56)


$R = 20\Omega$
each

H
* * * *

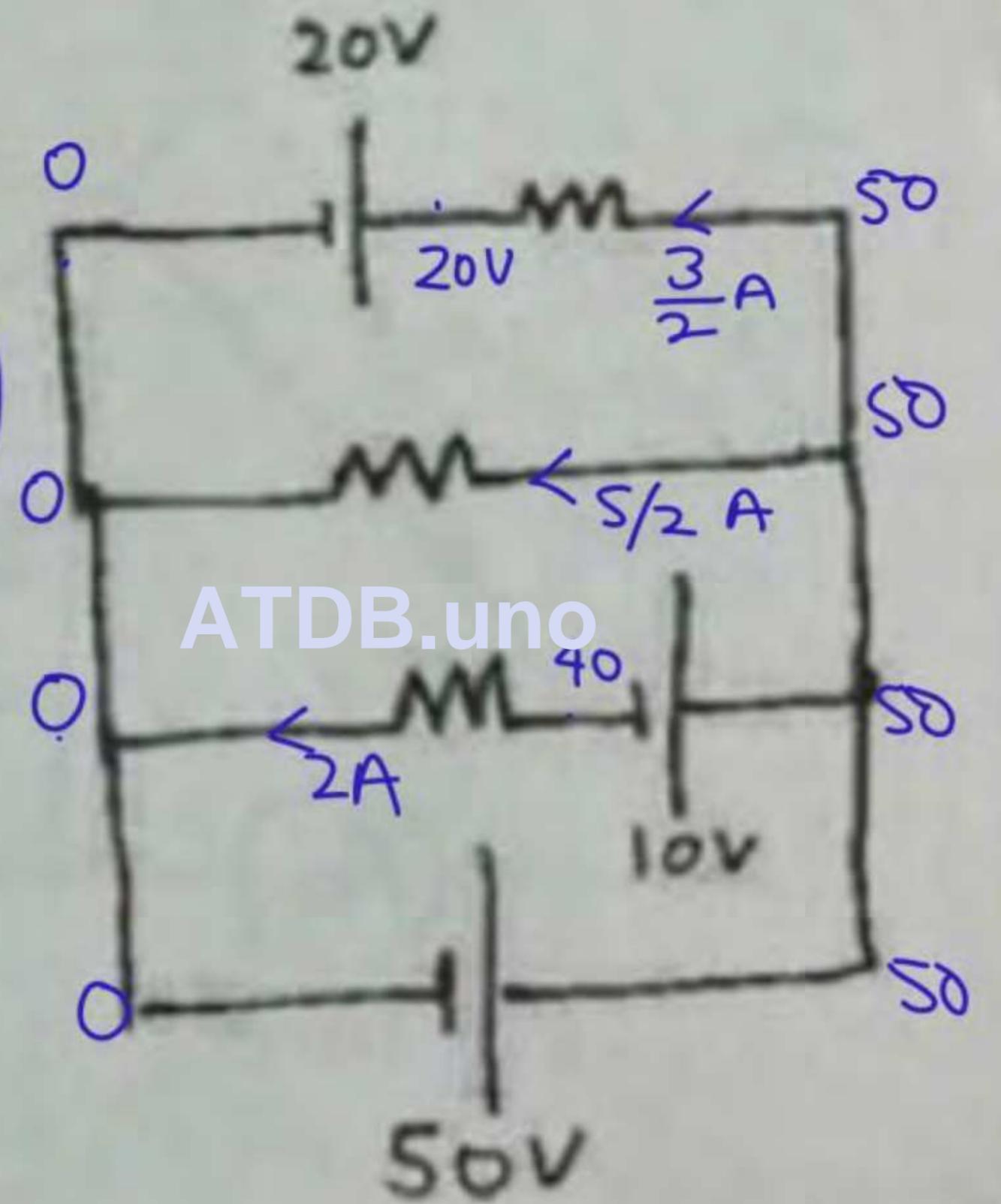

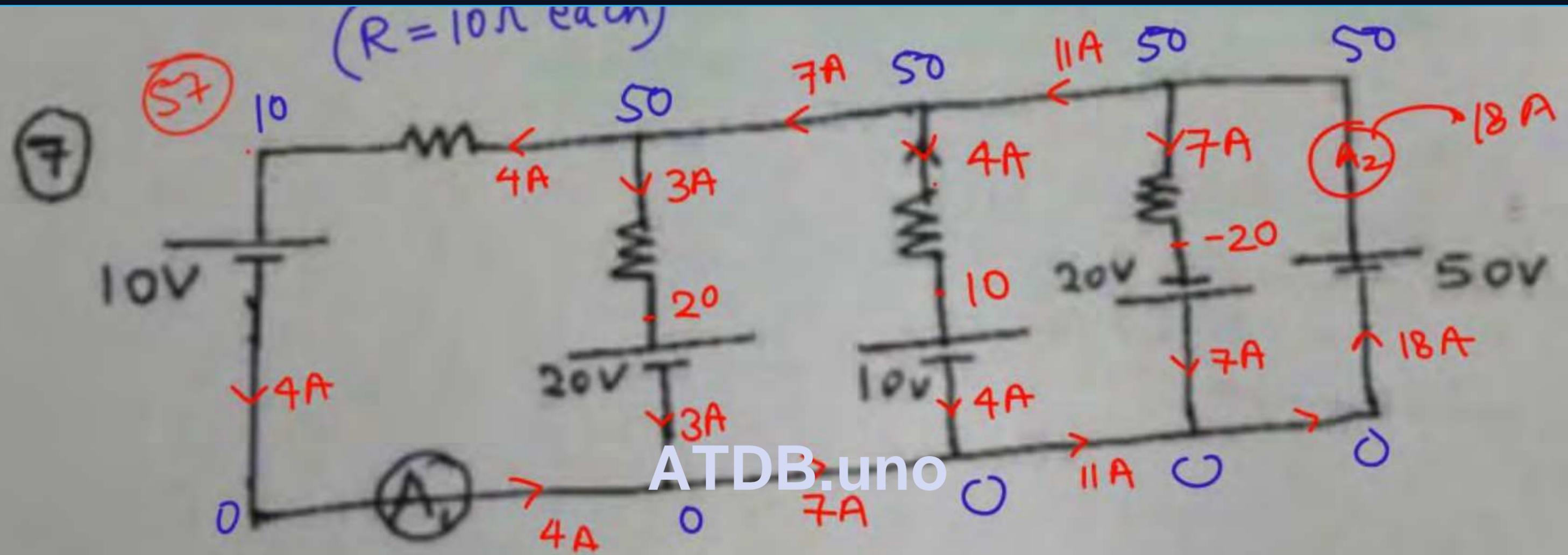


Reading of $A_1 = 4A$

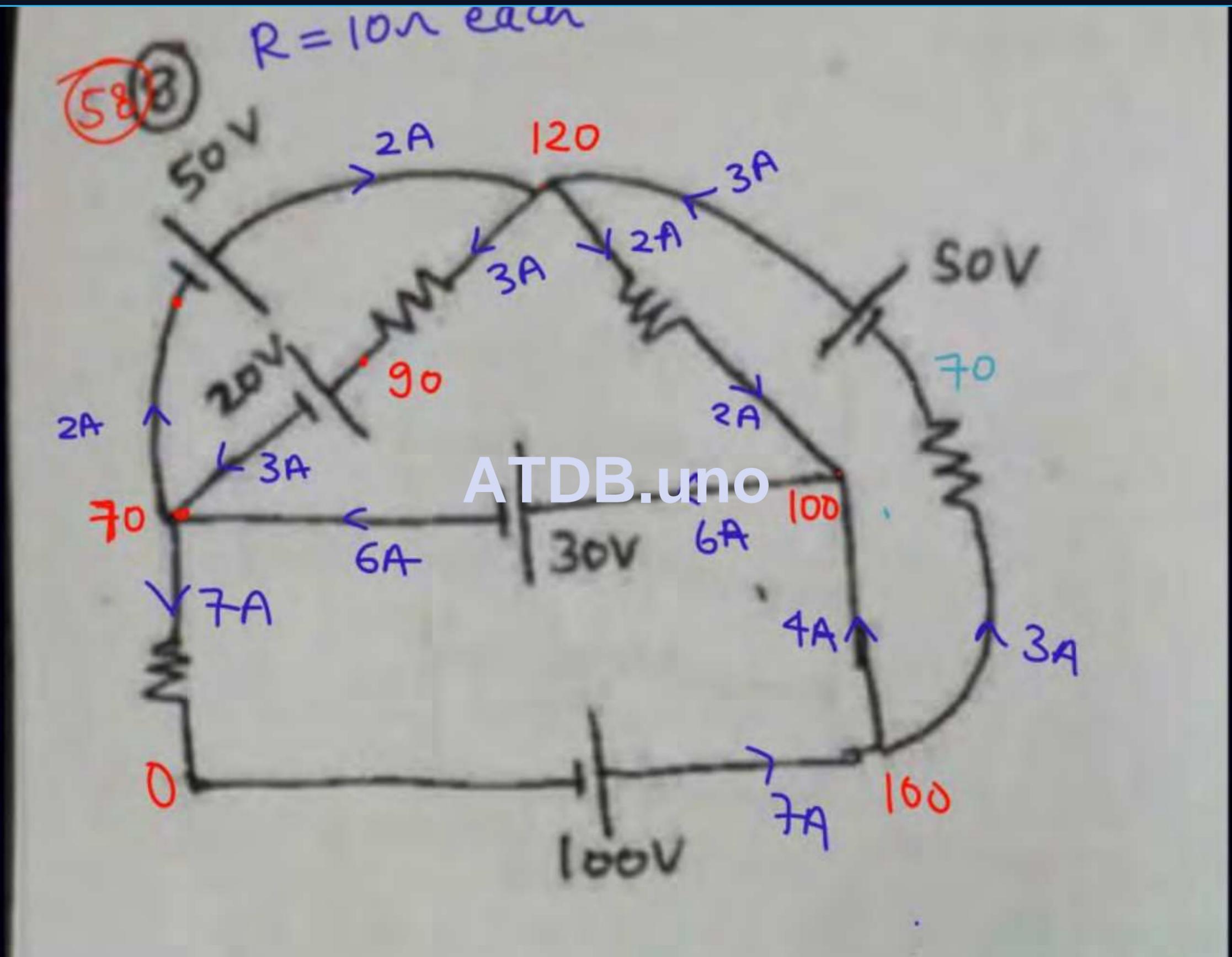




80
59

$R = 10\Omega$ (each)

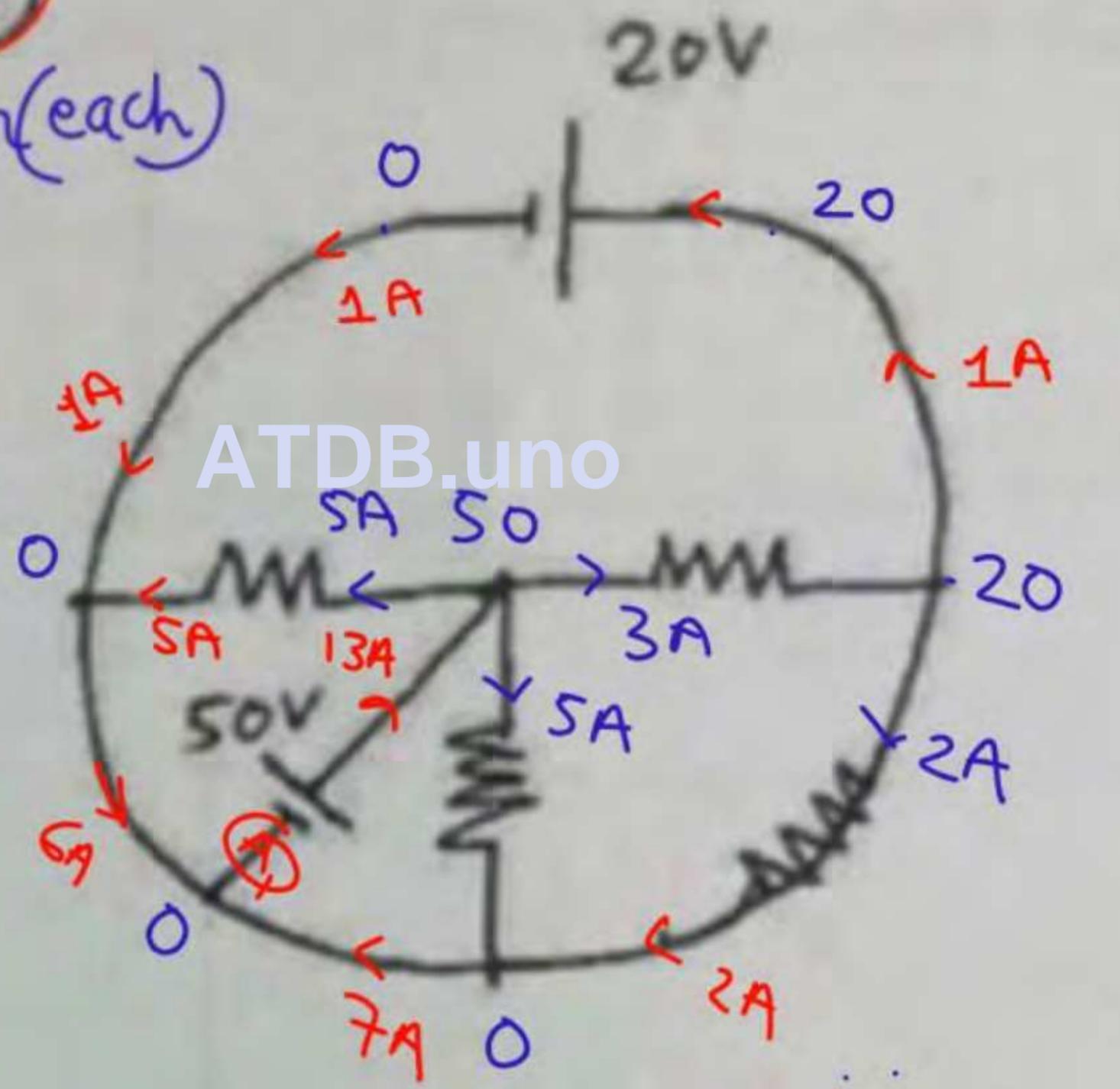


ATDB.uno

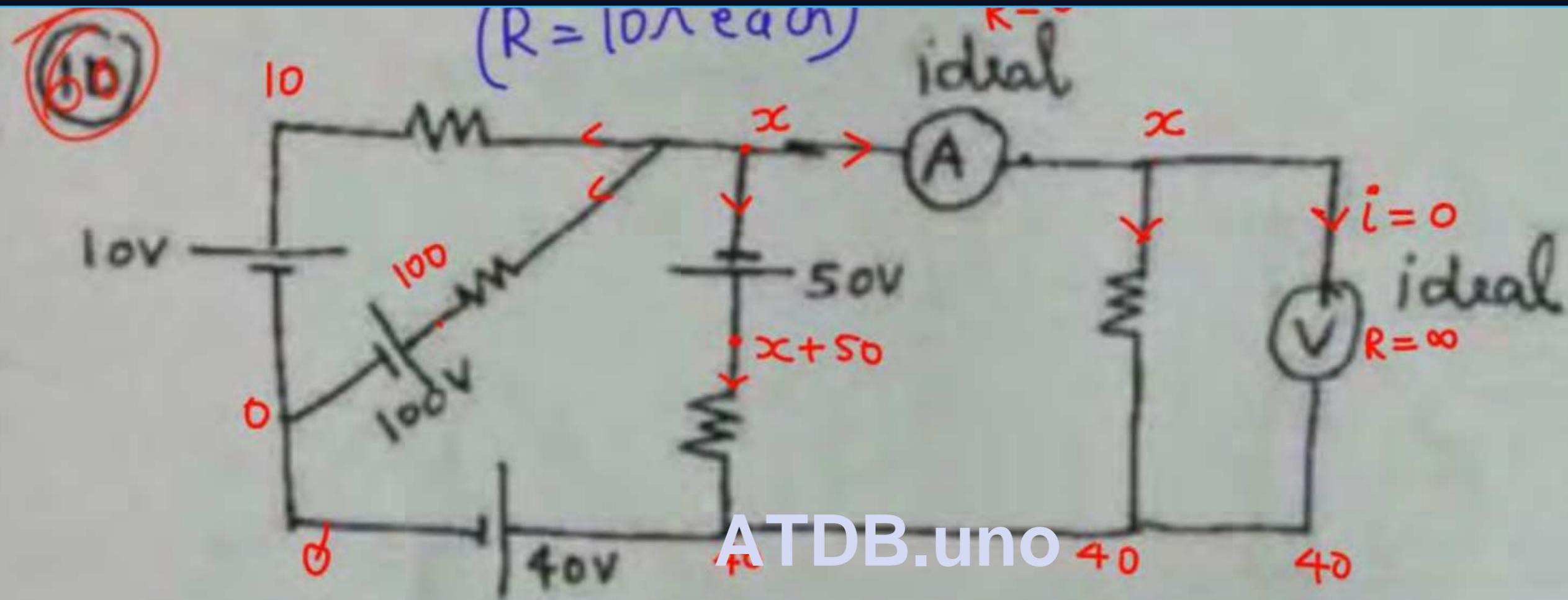


$$\frac{x-10}{10} + \frac{x-100}{10} + \frac{x+50-40}{10} + \frac{x-40}{10} = 0$$

$$4x = 140$$

✓ (check)

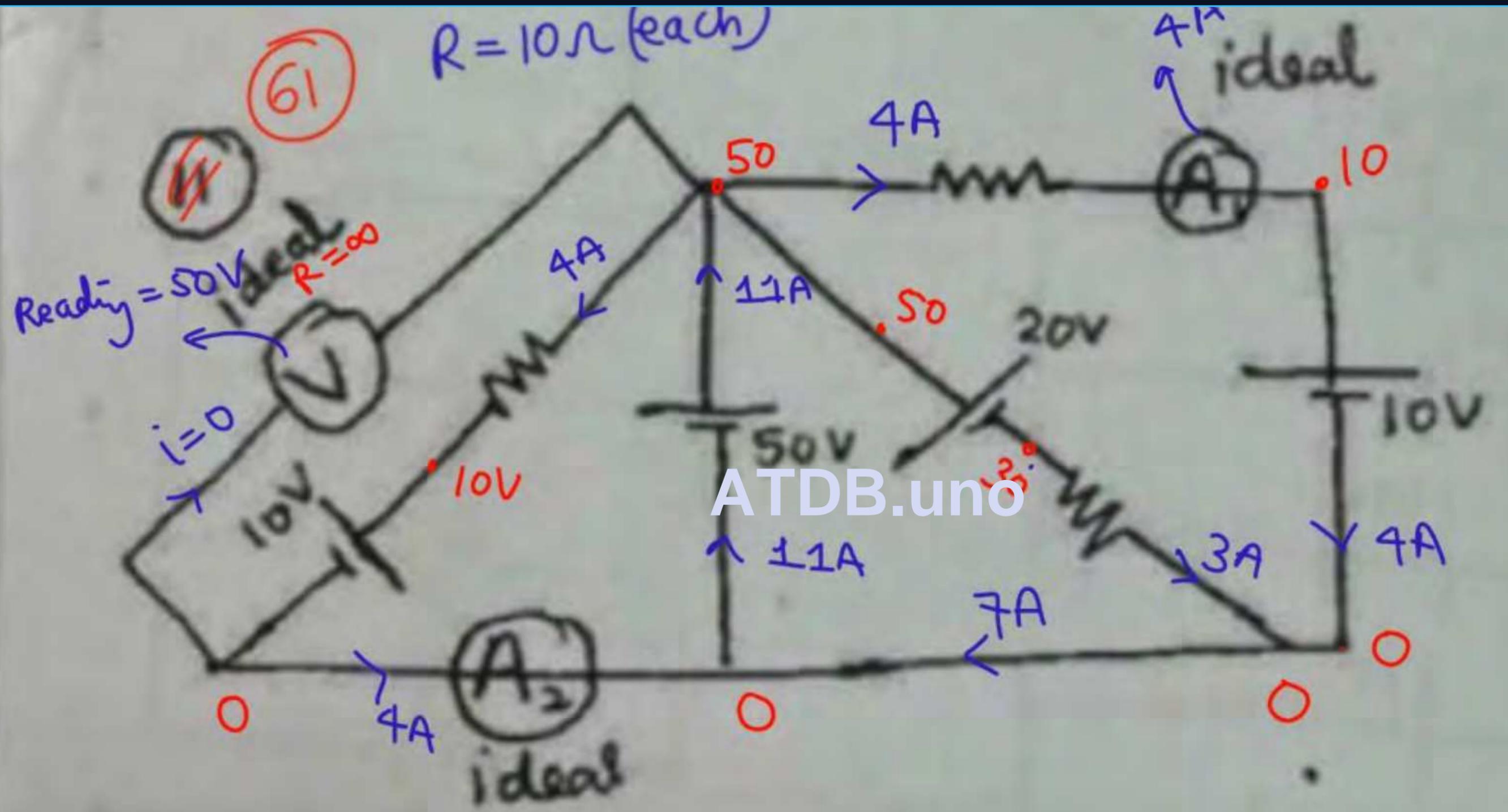


ATDB.uno

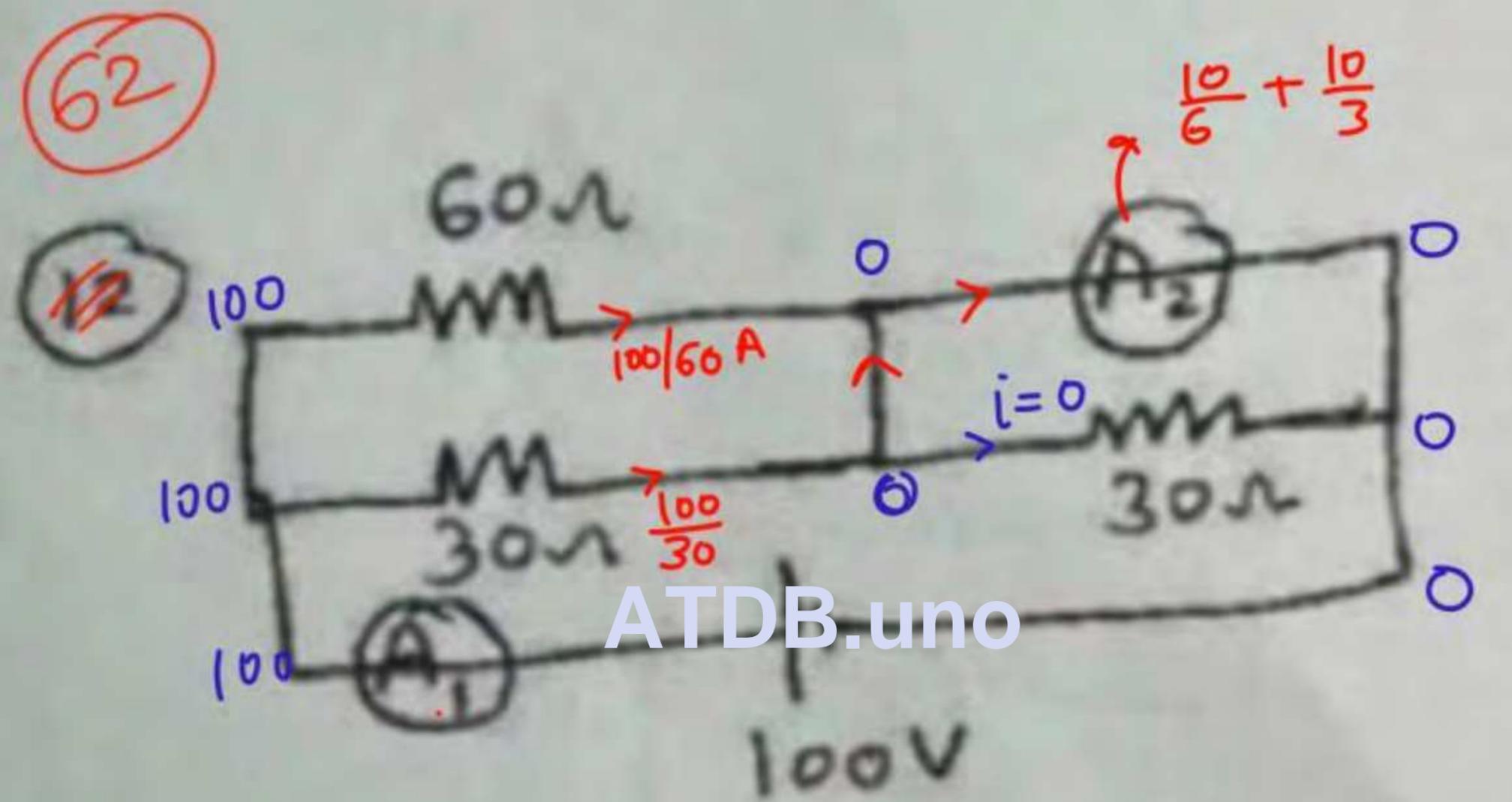


ATDB.uno

13 If volt meter/Ammeter are not ideal

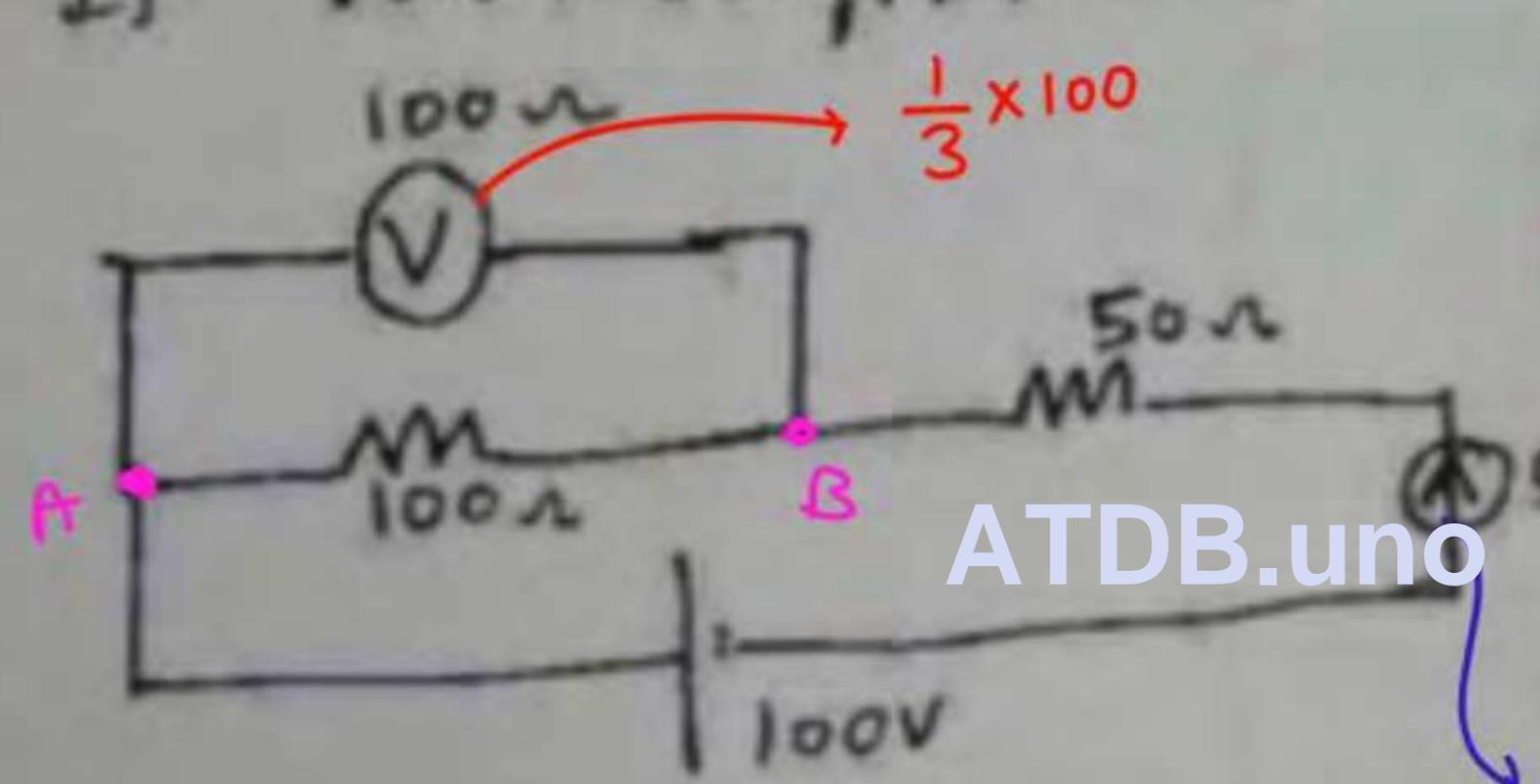


$\frac{1}{3} \times 100$

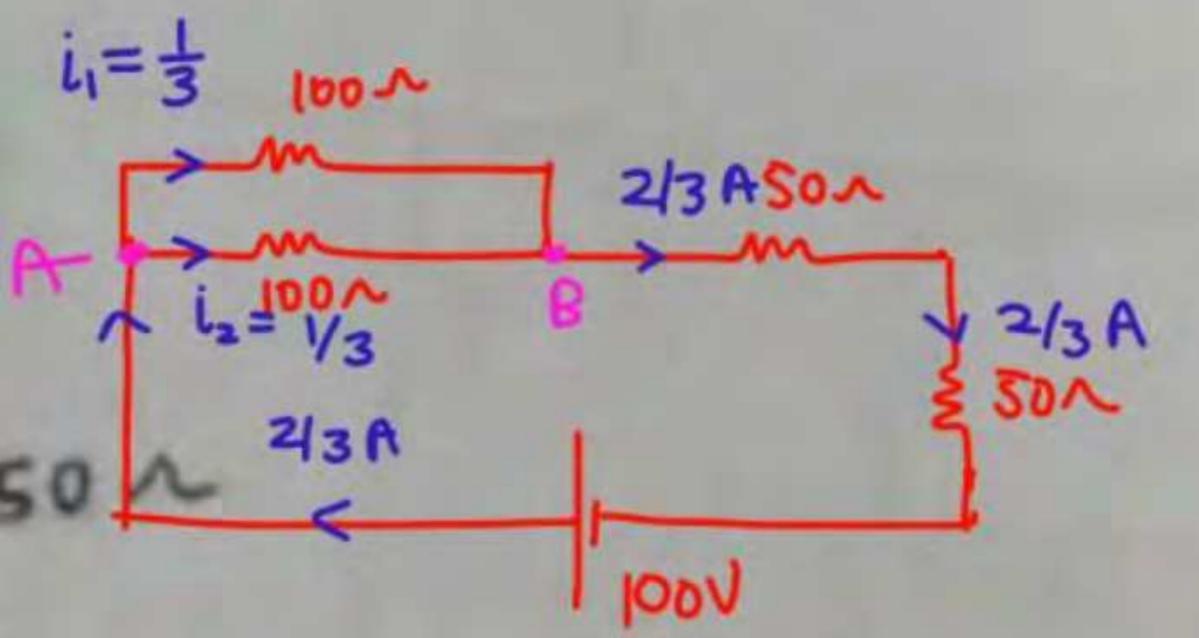

$i = \frac{100}{150} = \frac{2}{3}$






$\frac{2}{3} A$

ATDB.uno

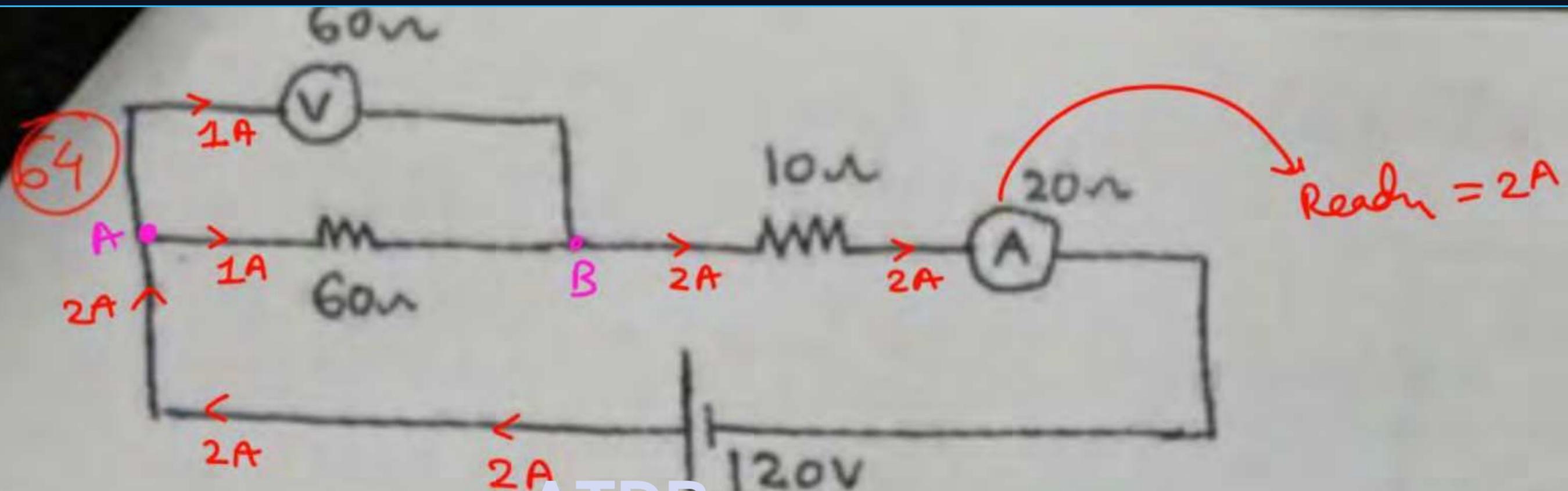


ATDB.uno

$$V_{AB} = 1 \times 60 = 60$$

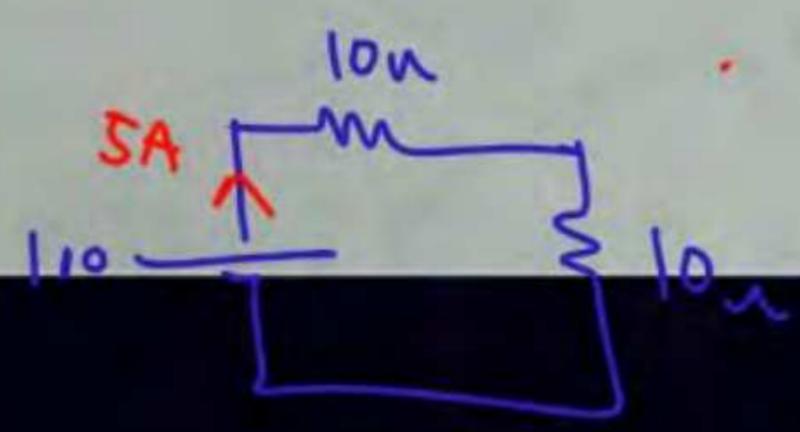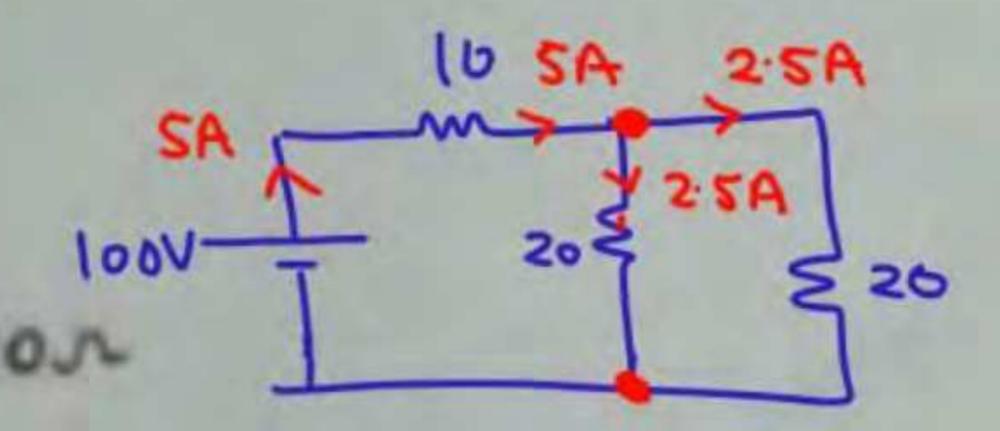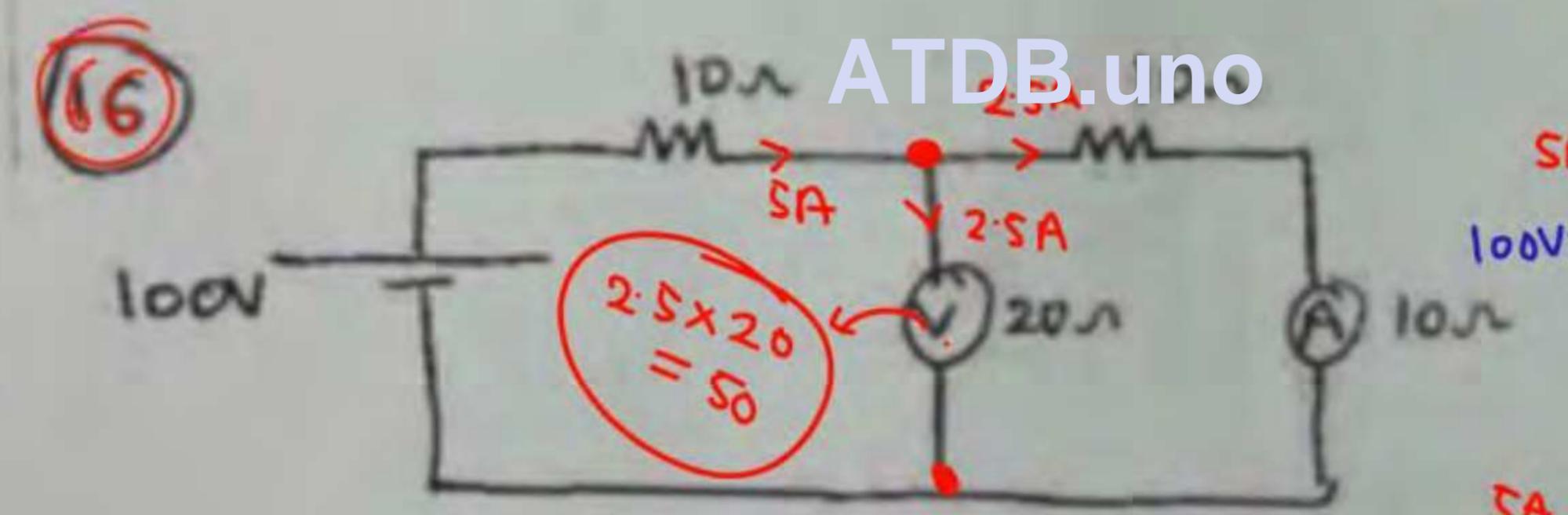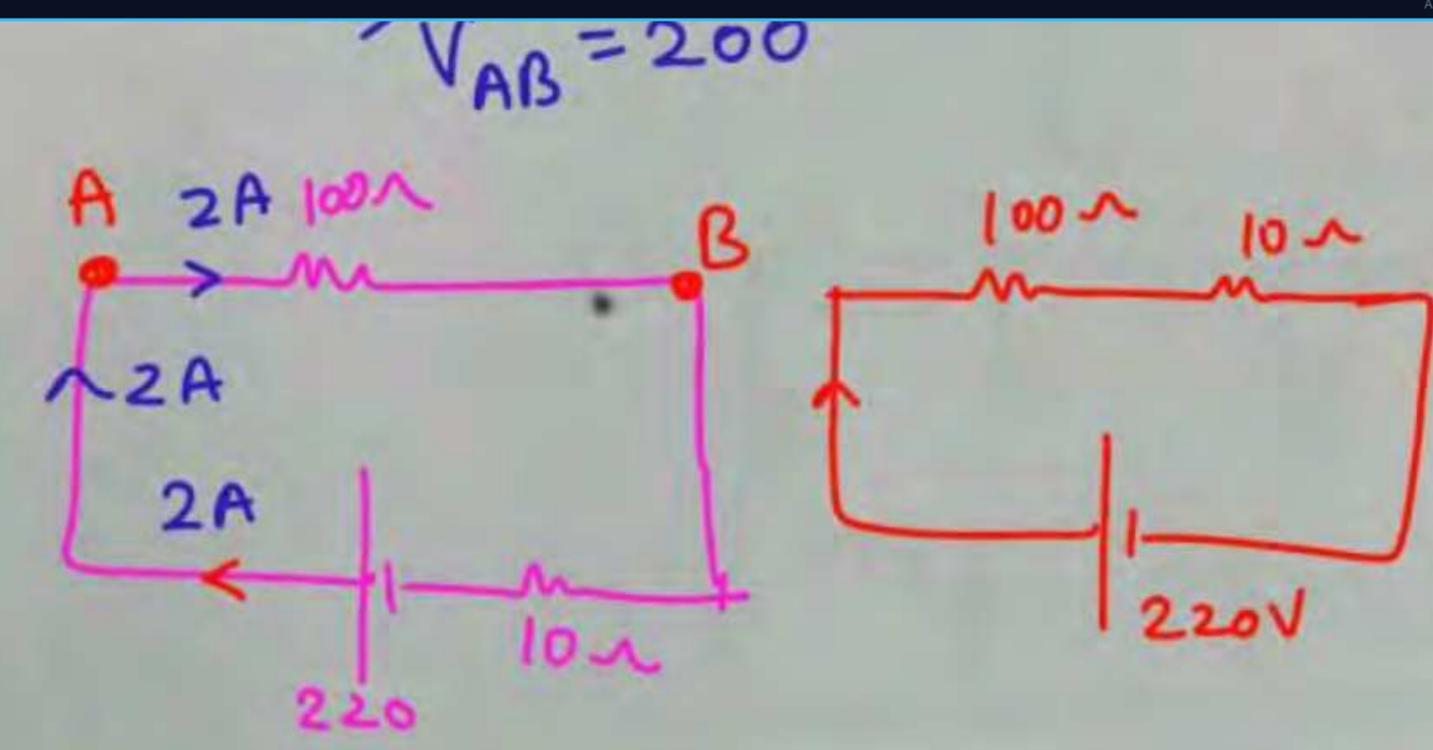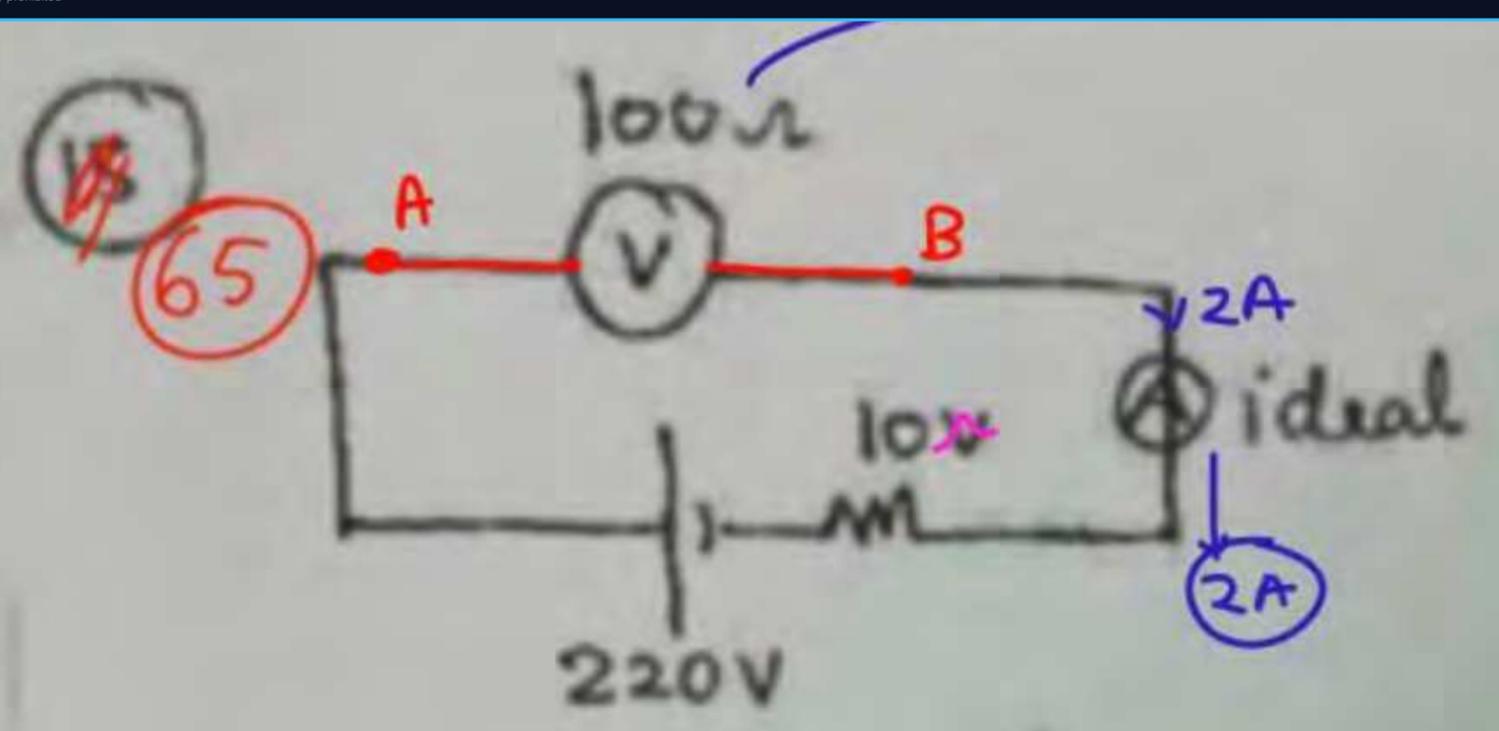




67

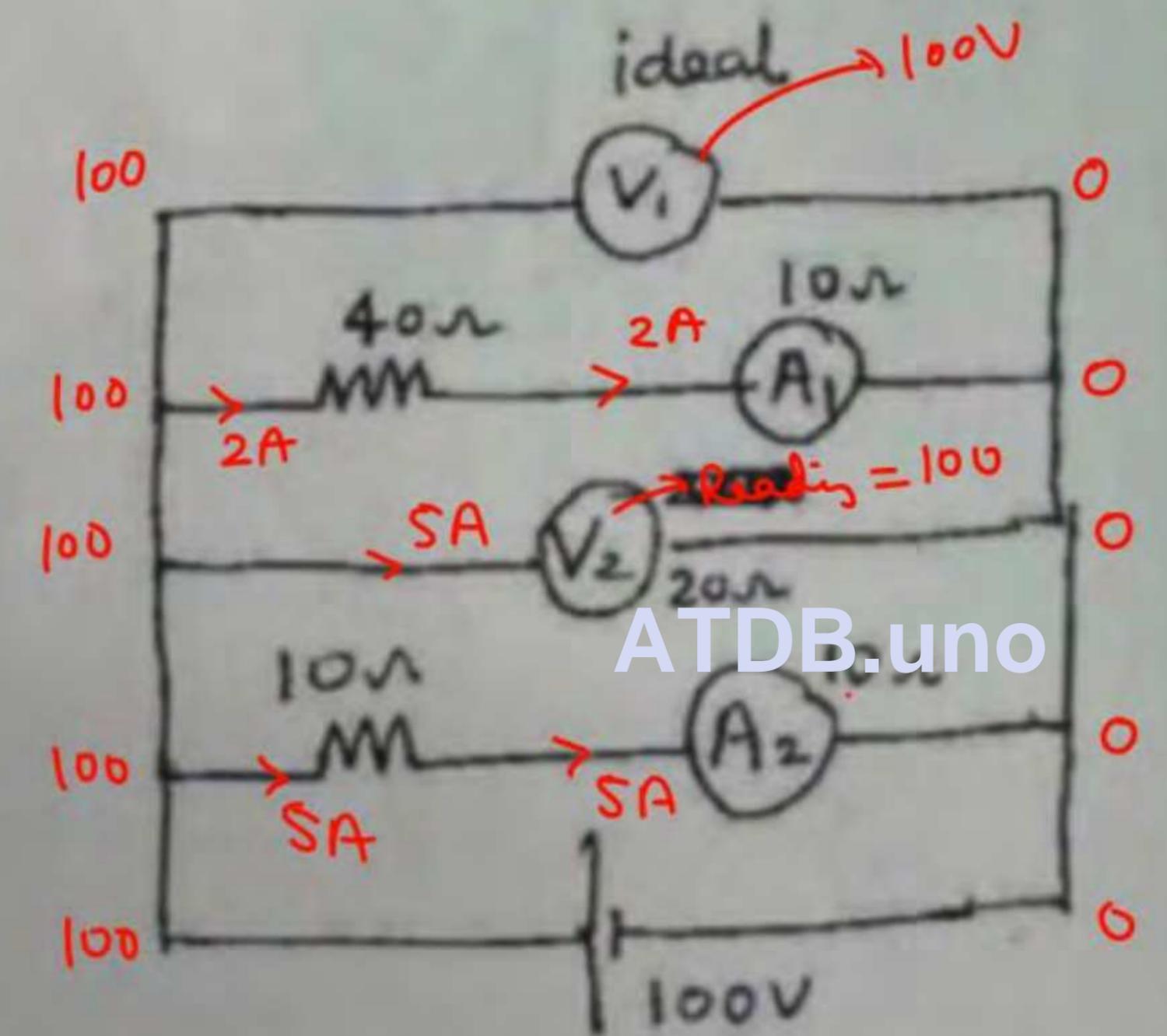

ATDB.uno

18

फॉर्मने वाले वृत्त

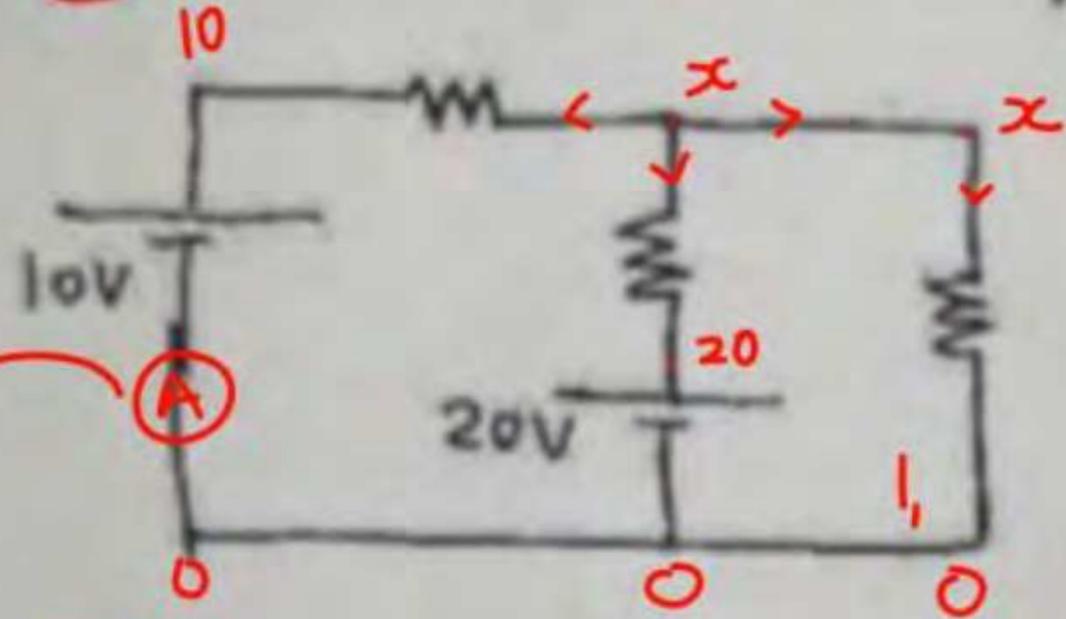

$R = 10\Omega$ (each)


$$\frac{x-10}{10} + \frac{x-20}{10} + \frac{x-0}{10} = 0$$

$x = 10$

ATDB.uno


69

19

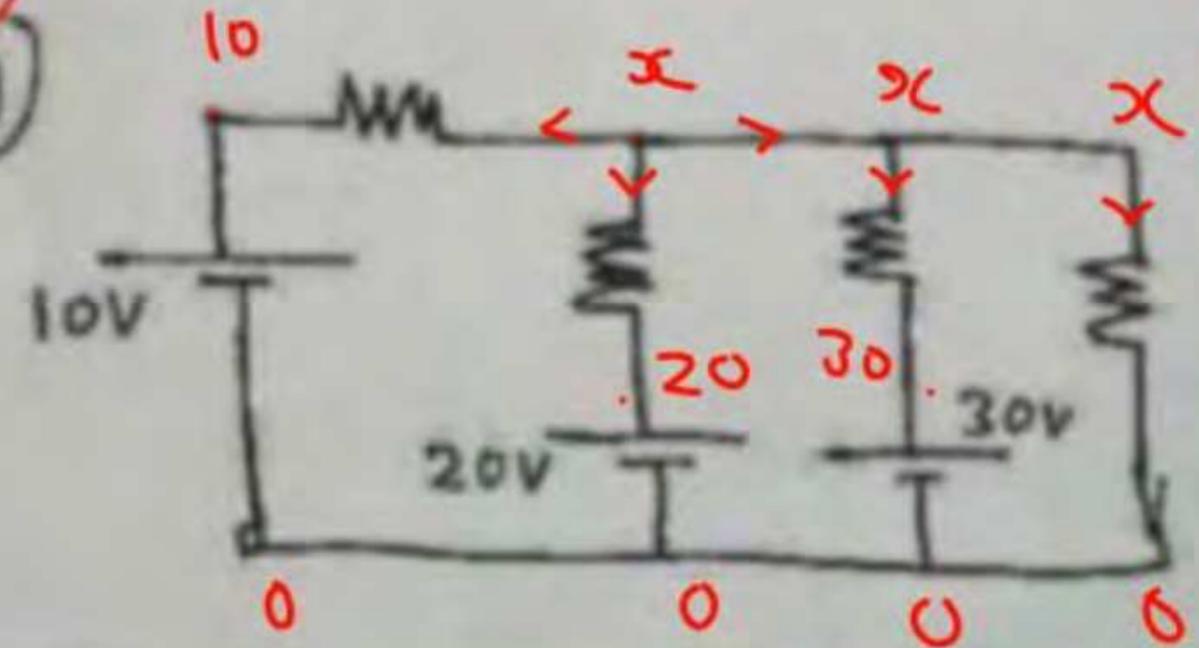

$$\frac{x-10}{10} + \frac{x-20}{10} + \frac{x-30}{10} + \frac{x-0}{10} = 0$$


$R = 10\Omega$ (each)

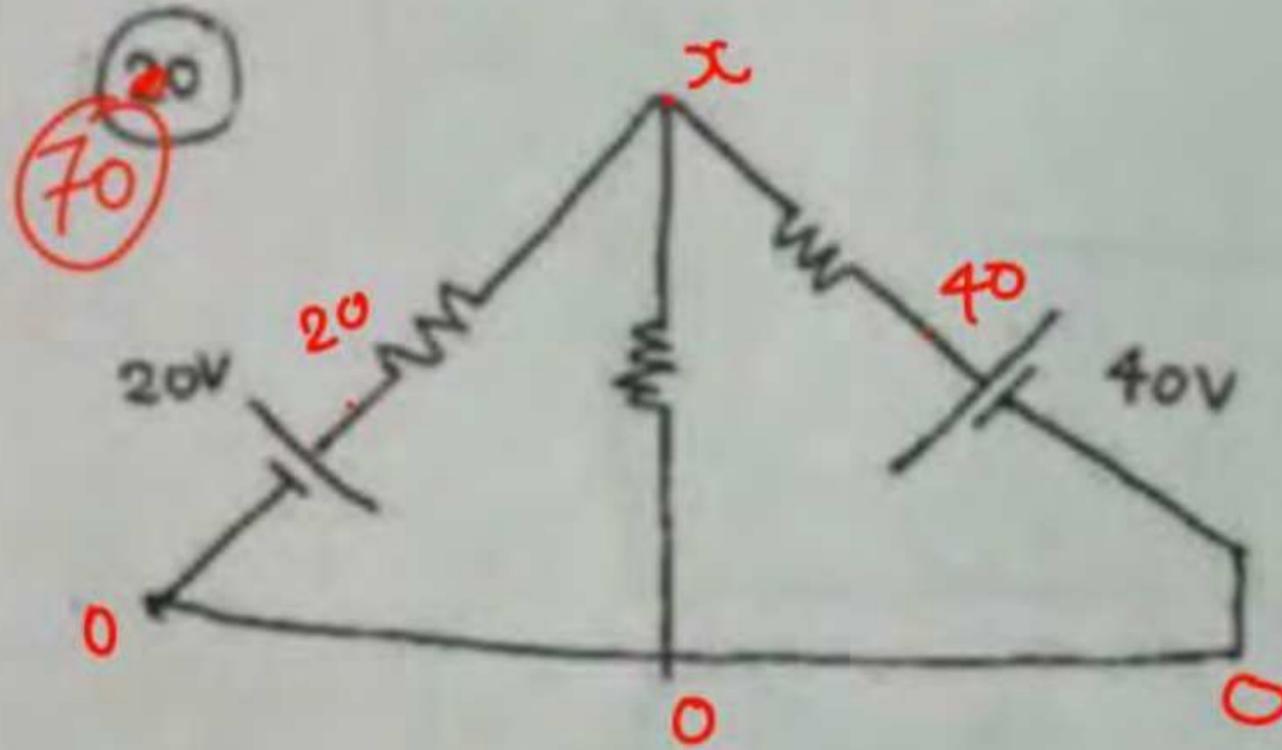

$(R = 10\Omega \text{ each})$


$$\frac{x-20}{10} + \frac{x-0}{10} + \frac{x-40}{10} = 0$$

ATDB.uno

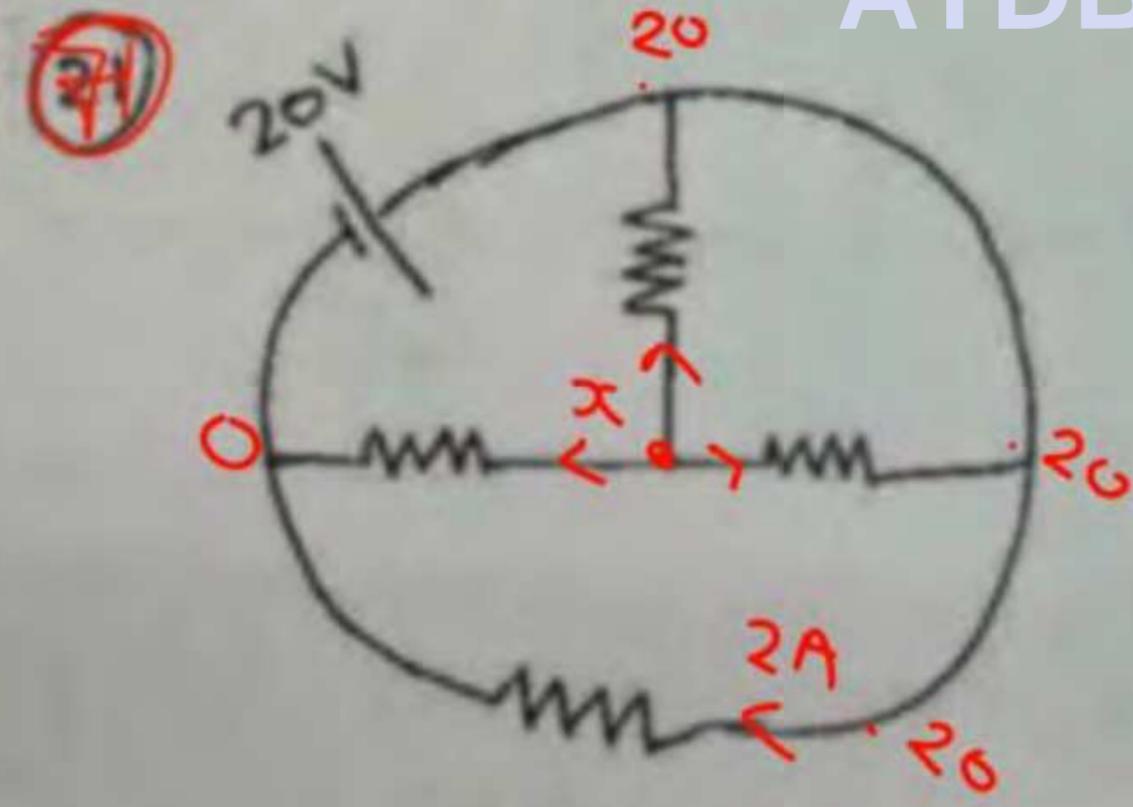

$R = 10\Omega \text{ (each)}$
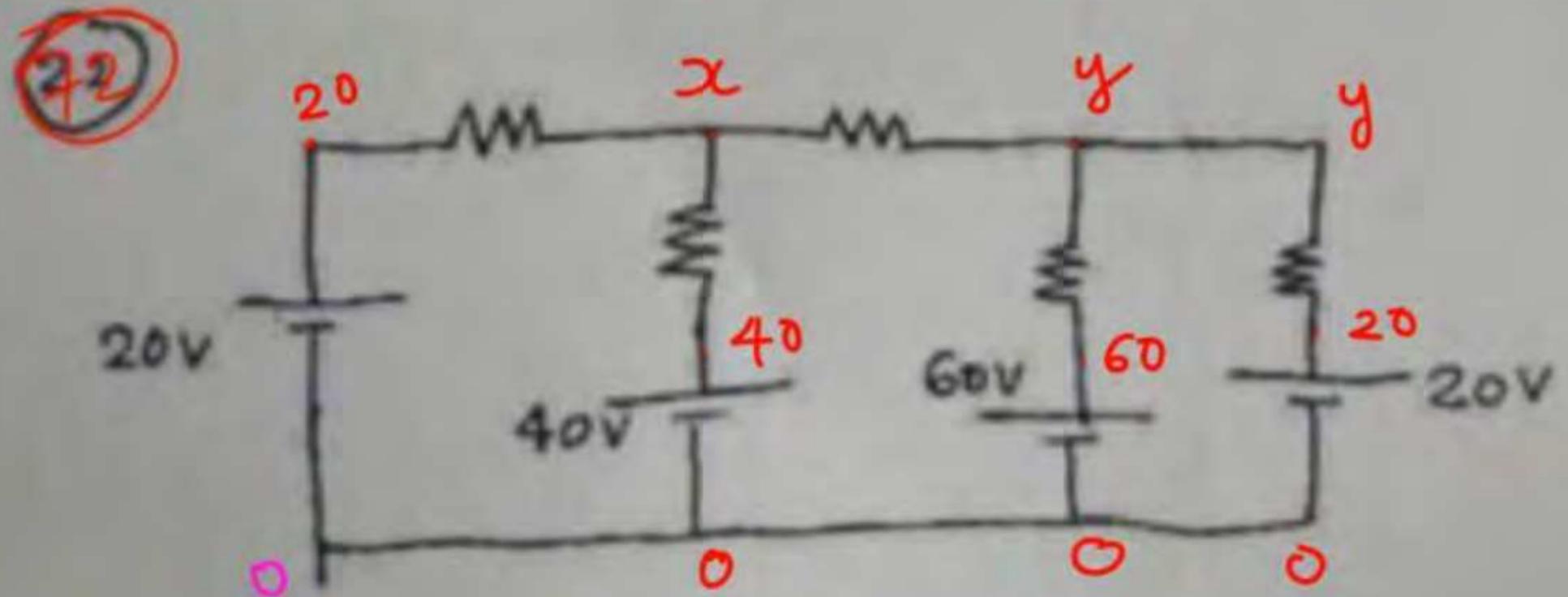
$$\frac{x-20}{10} + \frac{x-0}{10} + \frac{x-20}{10} = 0$$



$$R = 10 \Omega \text{ (each)}$$

ATDB.uno

$$\frac{x-20}{10} + \frac{x-40}{10} + \frac{x-y}{10} = 0$$

$$\frac{y-x}{10} + \frac{y-60}{10} + \frac{y-20}{10} = 0$$



THANK YOU

ATDB.uno

