

Prayas JEE (2025)


Physics

Capacitor

DPP: 4

- Q1** A parallel plate capacitor having air as dielectric medium is charged by a potential difference of V volt. After disconnecting the battery, the distance between the plates of the capacitor is increased using an insulated handle. As a result, potential difference between the plates
- (A) Increases
 - (B) Does not change
 - (C) Becomes zero
 - (D) Decreases

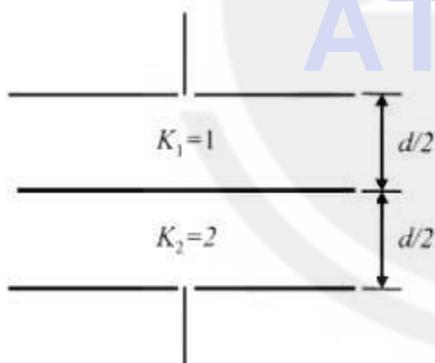- Q2** Two parallel plates of area A are separated by two different dielectric as shown in figure. The net capacitance is



- (A) $\frac{\epsilon_0 A}{2d}$
- (B) $\frac{\epsilon_0 A}{d}$
- (C) $\frac{3\epsilon_0 A}{d}$
- (D) $\frac{4\epsilon_0 A}{3d}$

- Q3** A metal foil of negligible thickness is introduced between two plates of a capacitor

at the centre. The capacitance of capacitor will be

- (A) Same
- (B) Double
- (C) Half
- (D) K times

- Q4** Two identical air core capacitors are connected in series to a voltage source of 15 V . If one of the capacitors is filled with a medium of dielectric constant 4 , the new potential across this capacitor is
- (A) 5 V
 - (B) 8 V
 - (C) 3 V
 - (D) 12 V

- Q5** If dielectric is inserted in charged capacitor (battery removed), then quantity that remains constant is
- (A) Capacitance
 - (B) Potential
 - (C) Intensity
 - (D) Charge

- Q6** An air parallel plate capacitor has capacity C . The capacity and distance between plates are doubled when immersed in a liquid. Then dielectric constant of the liquid is
- (A) 1
 - (B) 2
 - (C) 3
 - (D) 4

- Q7** A parallel plate air capacitor has a capacitance C . When it is half filled with a dielectric constant 5 , the percentage increase in the capacitance will be
- (A) 400%
 - (B) 66.6%
 - (C) 33.3%
 - (D) 200%



[Android App](#)


[iOS App](#)

[PW Website](#)

- Q8** Two capacitors of capacitance $2\mu\text{F}$ and $4\mu\text{F}$ respectively are connected in series. The combination is connected across a potential difference of 10 V . The ratio of energies stored by capacitors will be
- (A) $1 : \sqrt{2}$
 - (B) $2 : 1$
 - (C) $1 : 4$
 - (D) $4 : 1$


(D) $8\mu\text{F}$

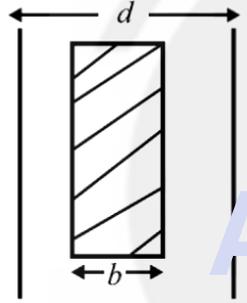- Q9** A slab of copper of thickness b is inserted in between the plates of parallel plate capacitor as shown in figure. The separation between the plates is d if $b = d/2$, then the ratio of capacities of capacitors after and before inserting the slab will be



- (A) $\sqrt{2} : 1$
- (B) $2 : 1$
- (C) $1 : 1$
- (D) $1 : \sqrt{2}$

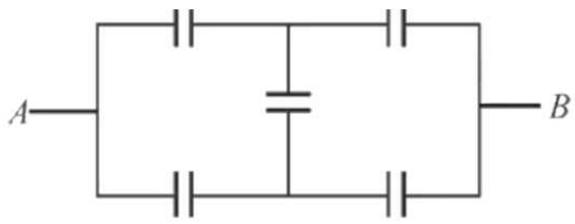- Q10** Each capacitor shown in figure is $2\mu\text{F}$. Then the equivalent capacitance between points A and B is



- (A) $2\mu\text{F}$
- (B) $4\mu\text{F}$
- (C) $6\mu\text{F}$

Answer Key

Q1 A
Q2 D
Q3 A
Q4 C
Q5 D

Q6 D
Q7 B
Q8 B
Q9 B
Q10 A



[Android App](#)

| [iOS App](#)

| [PW Website](#)

