

PRAYAS

JEE 2025

ATDB.uno

Lecture - 02

Physics

H.W Discussion (Capacitors)
(16 ques)

By- Saleem Ahmed Sir






Homework of the class soñ pdf

ATDB.uno




①

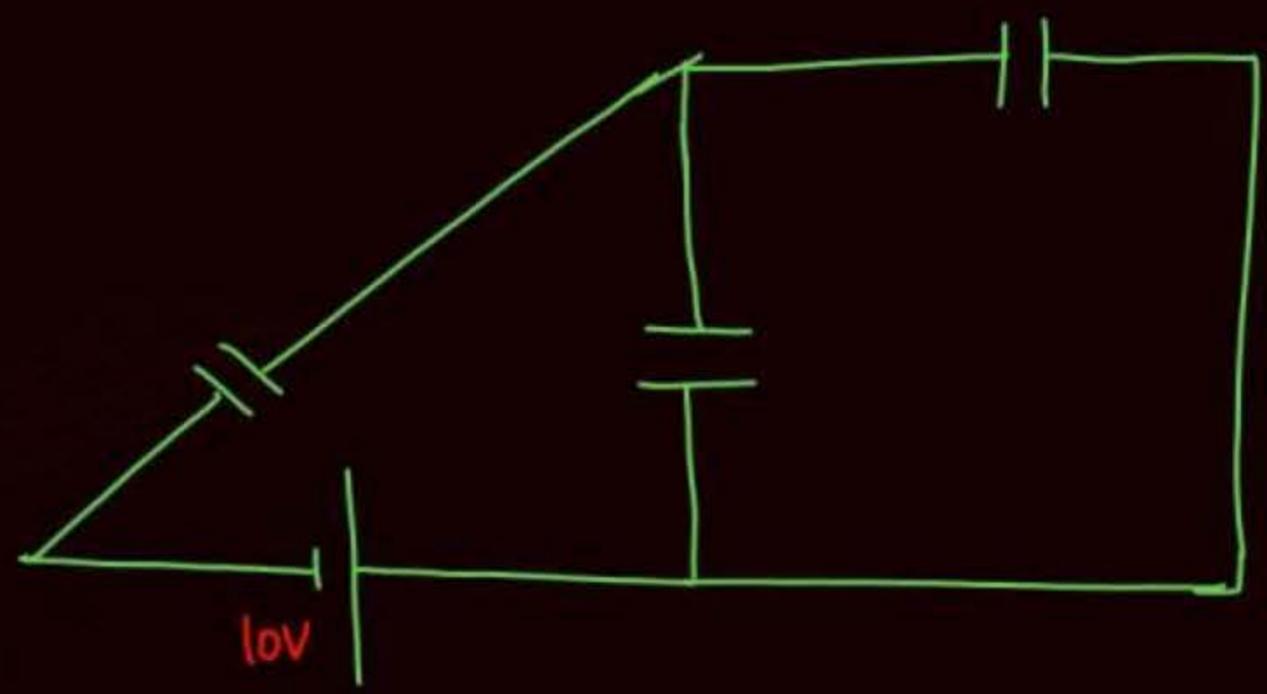


$C = 2F$ (each)

②

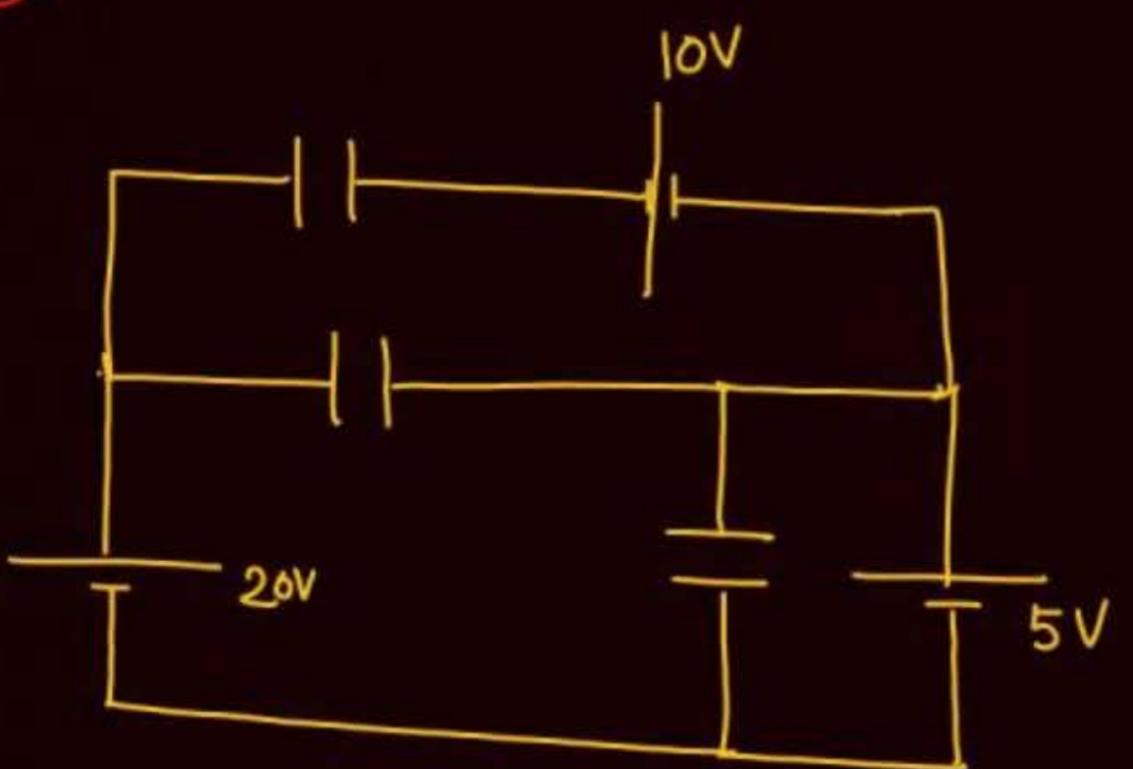

$C = 2F$ (each)


ATDB.uno

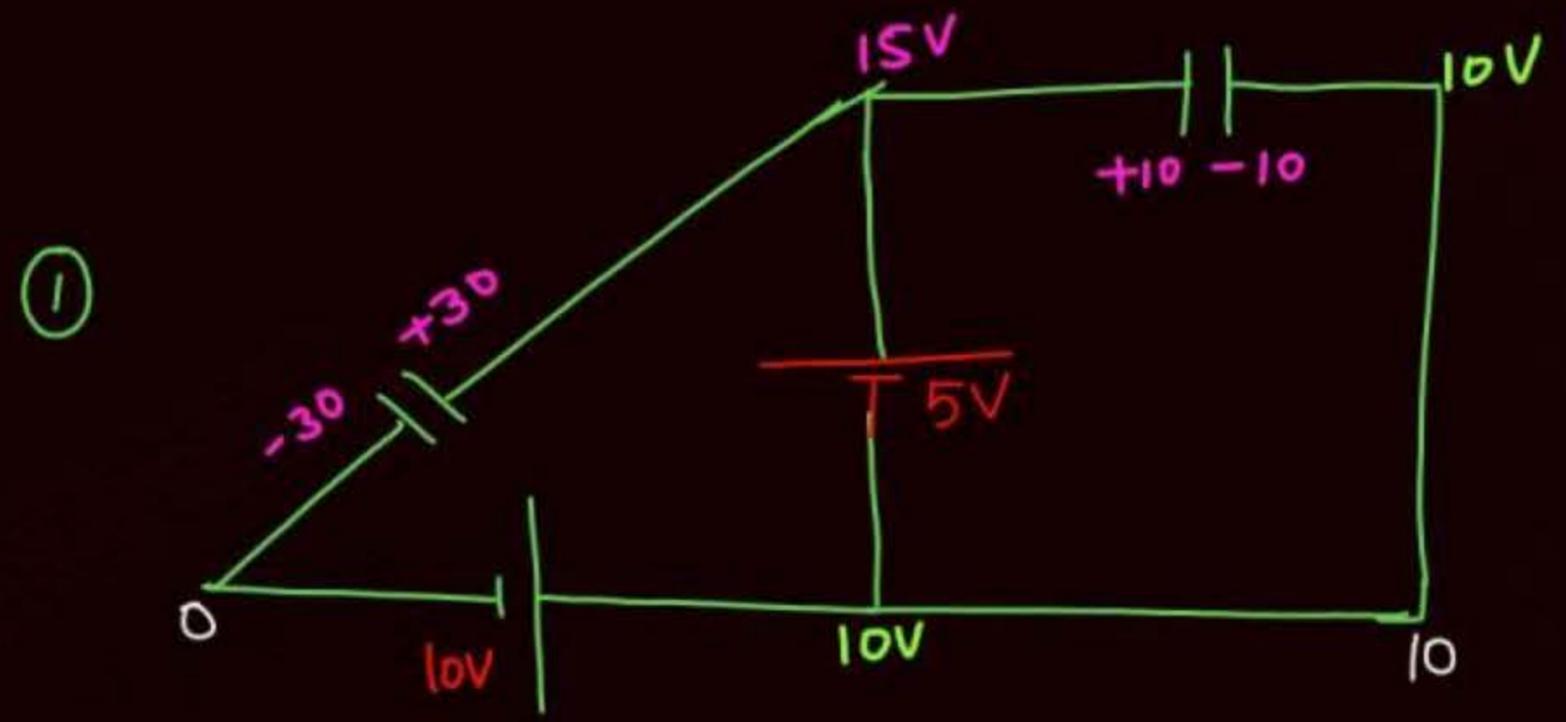

$C = 2F$ (each)

ATDB.uno


$\theta = CV$

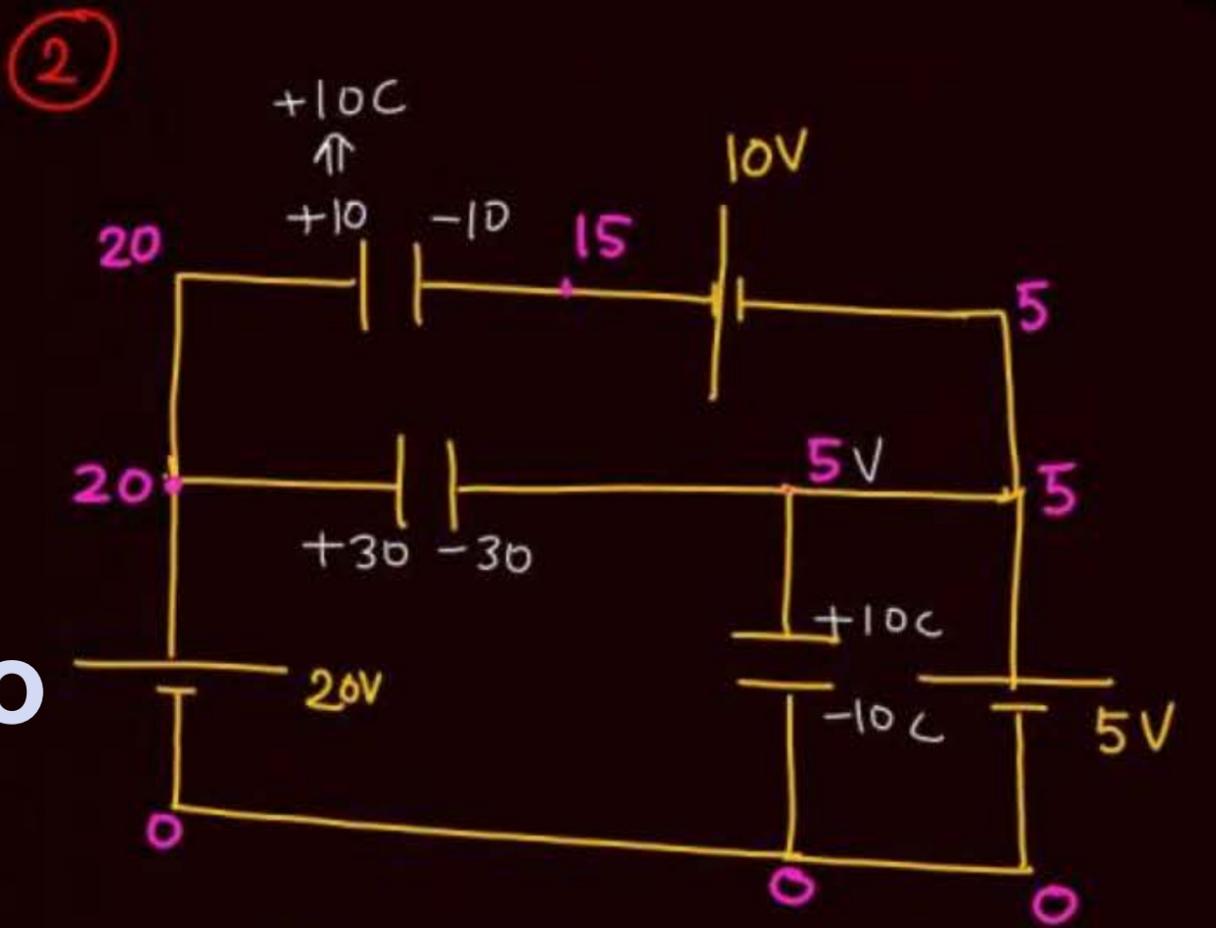

$C = 2F$ (each)



3

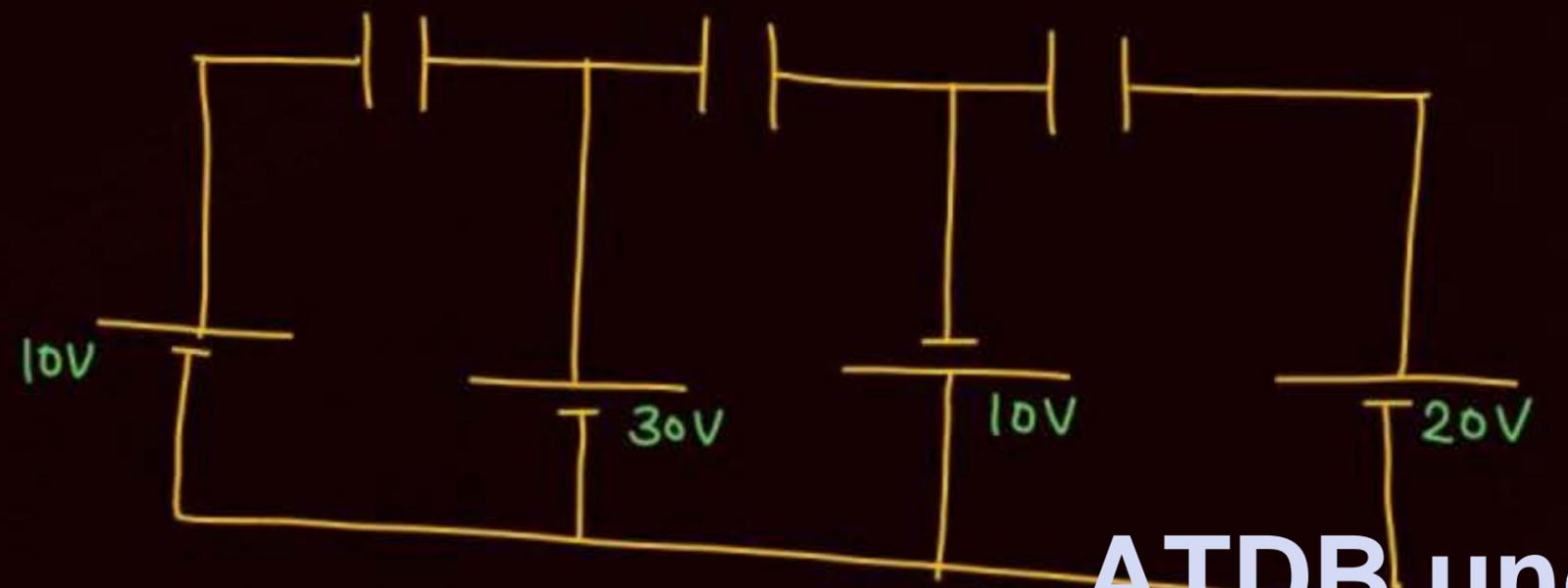


ATDB.uno

4

Q


$C = 2F$ (each)

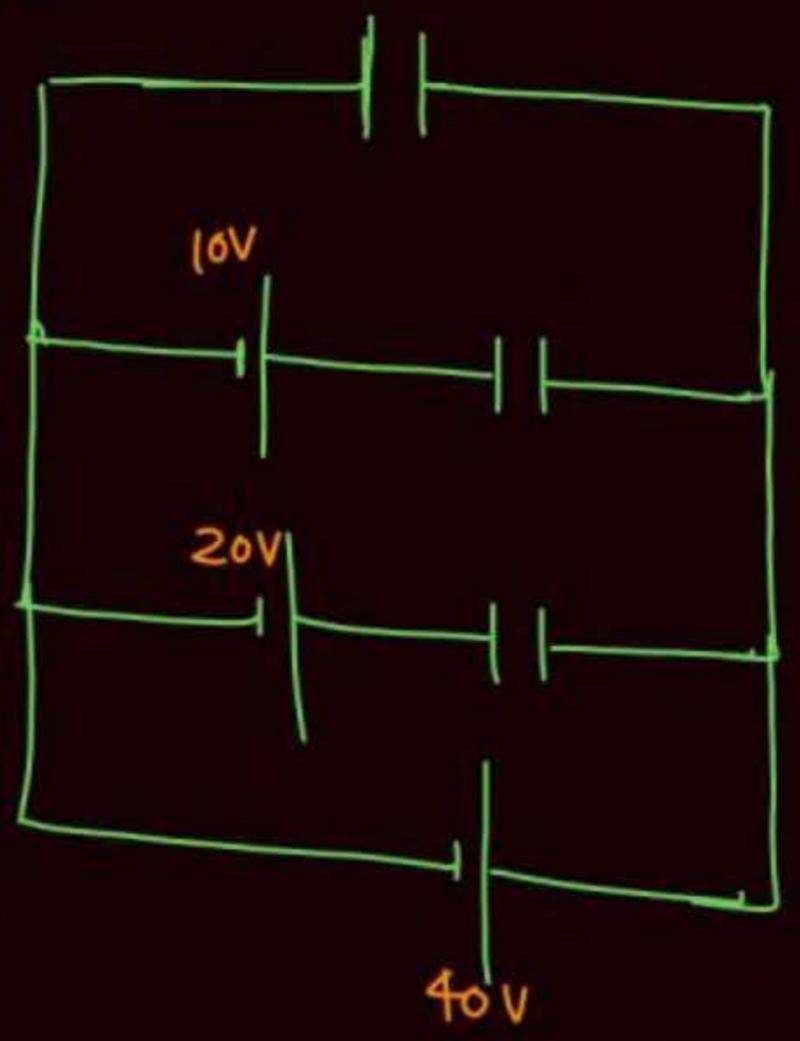



$C = 2F$
 $Q = CV$


3

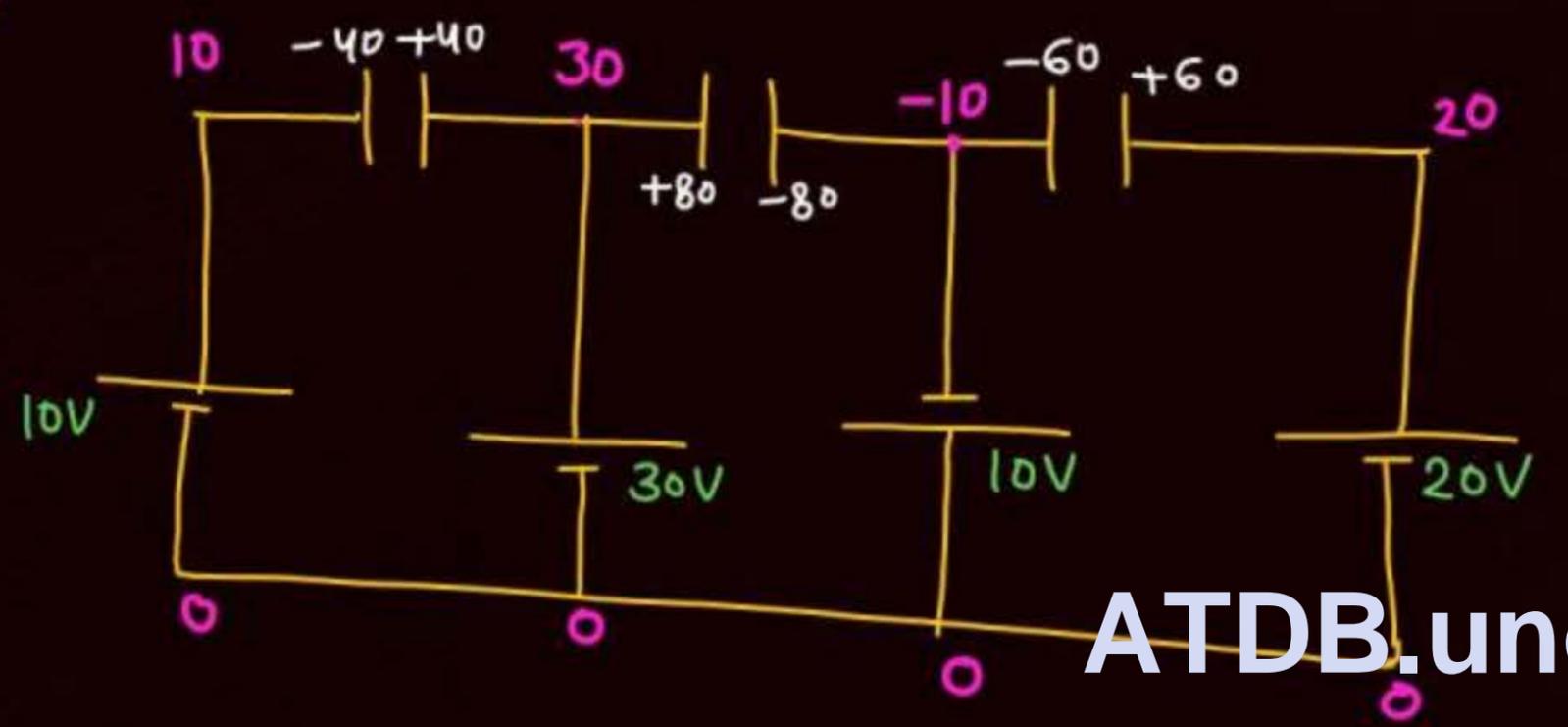


ATDB.uno

4

$C = 2F$ (each)

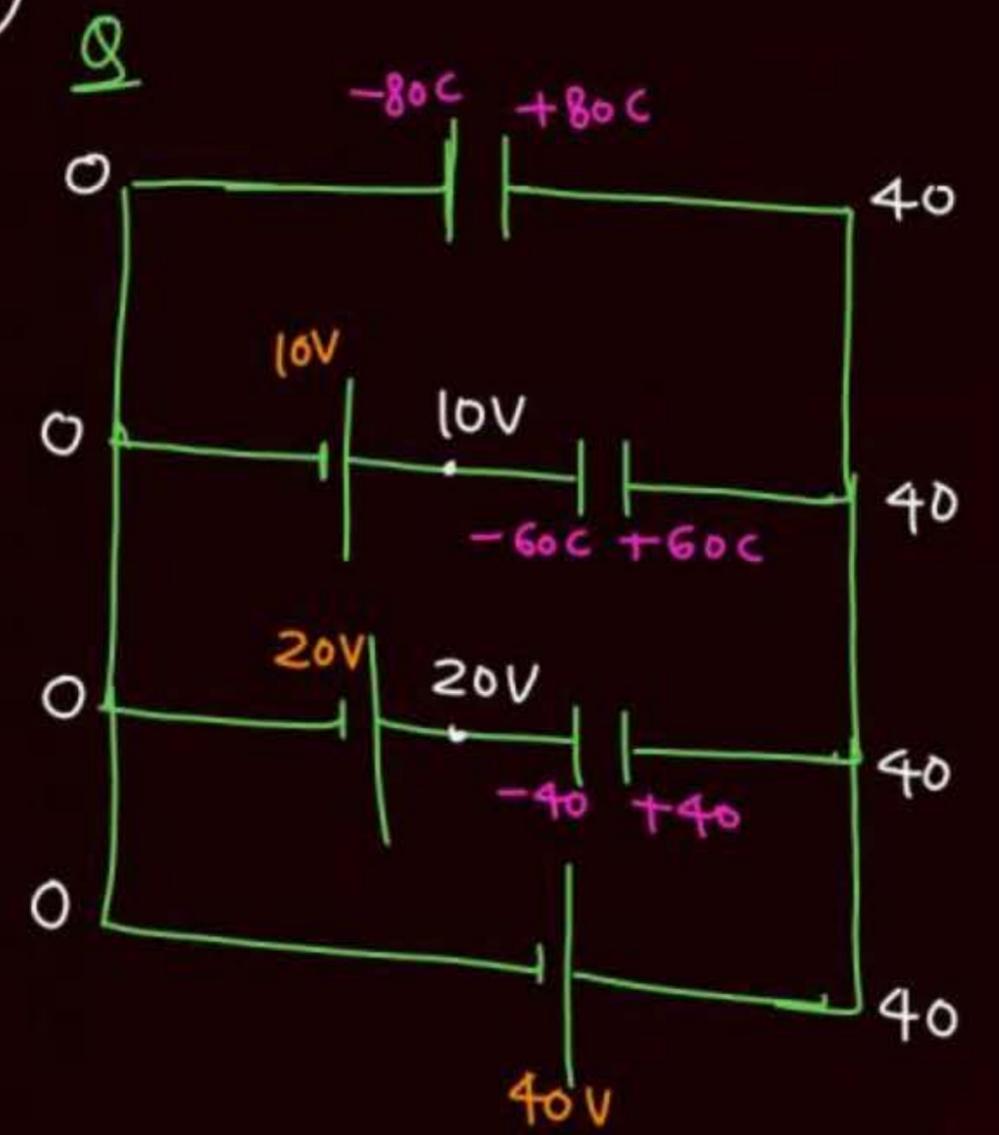

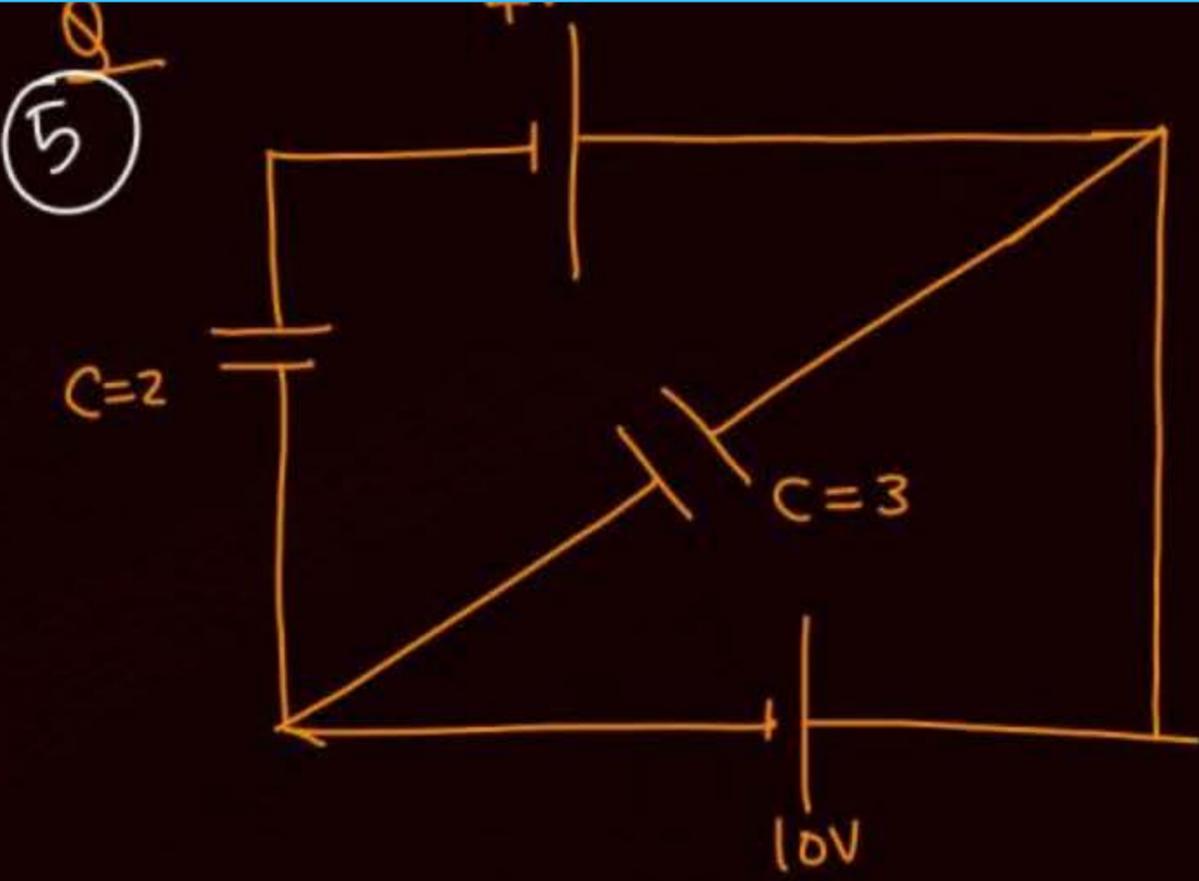

6

Q




Find charge on capacitor C_1 & C_2 and current through 2Ω and 3Ω

ATDB.uno




7

Q

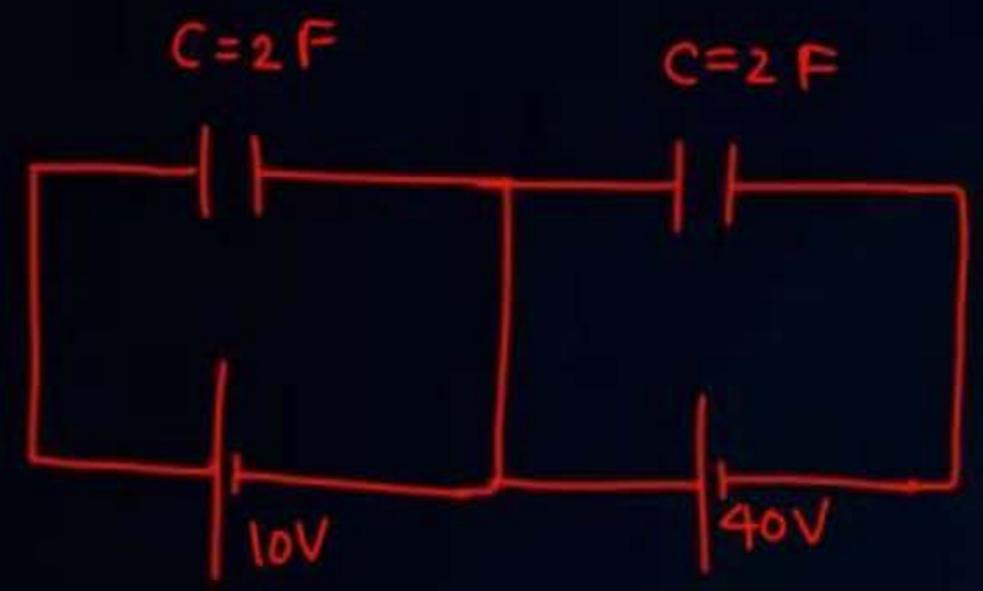

8

Q

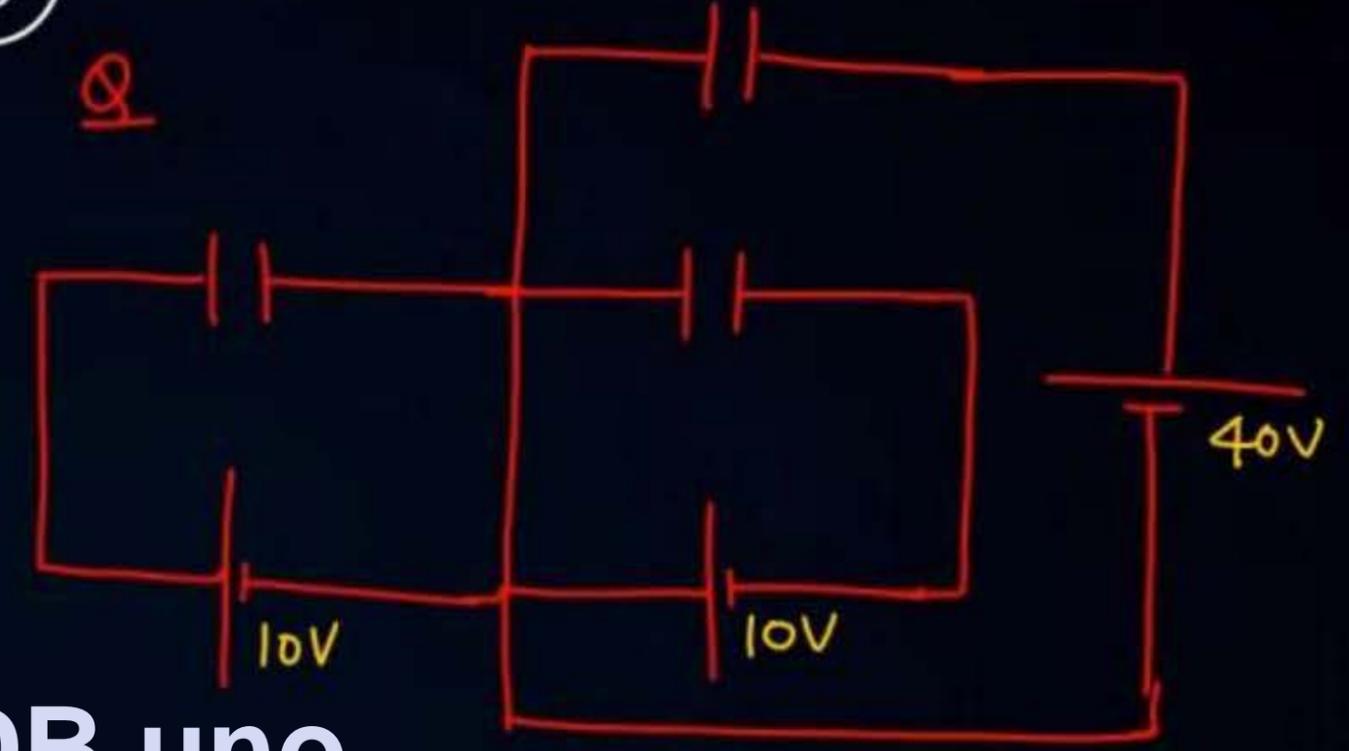


ATDB.uno

C=2F (each)




7

Q

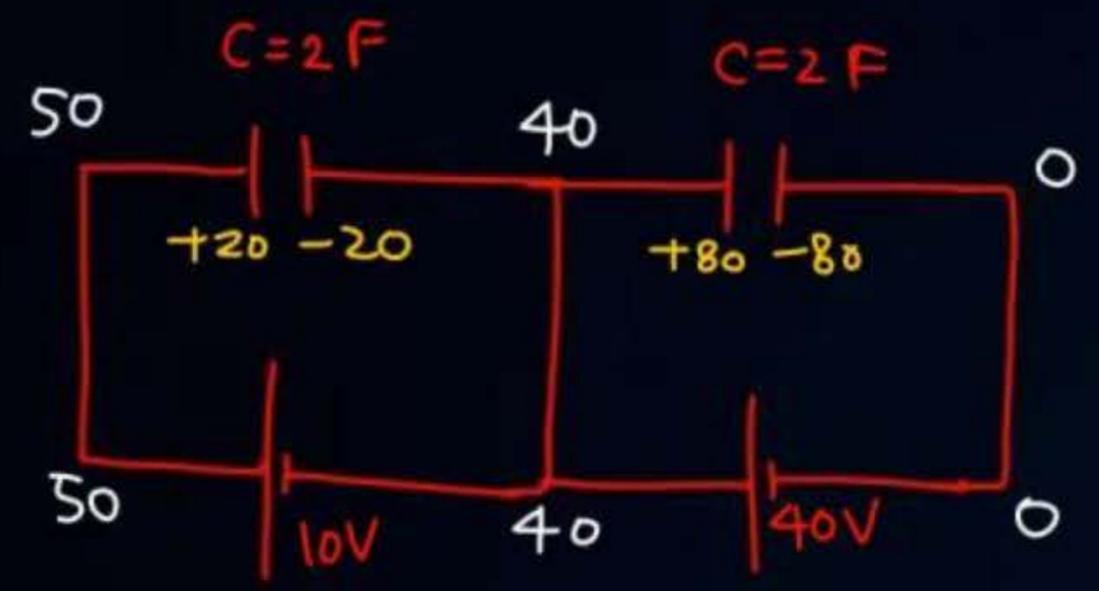

8

Q

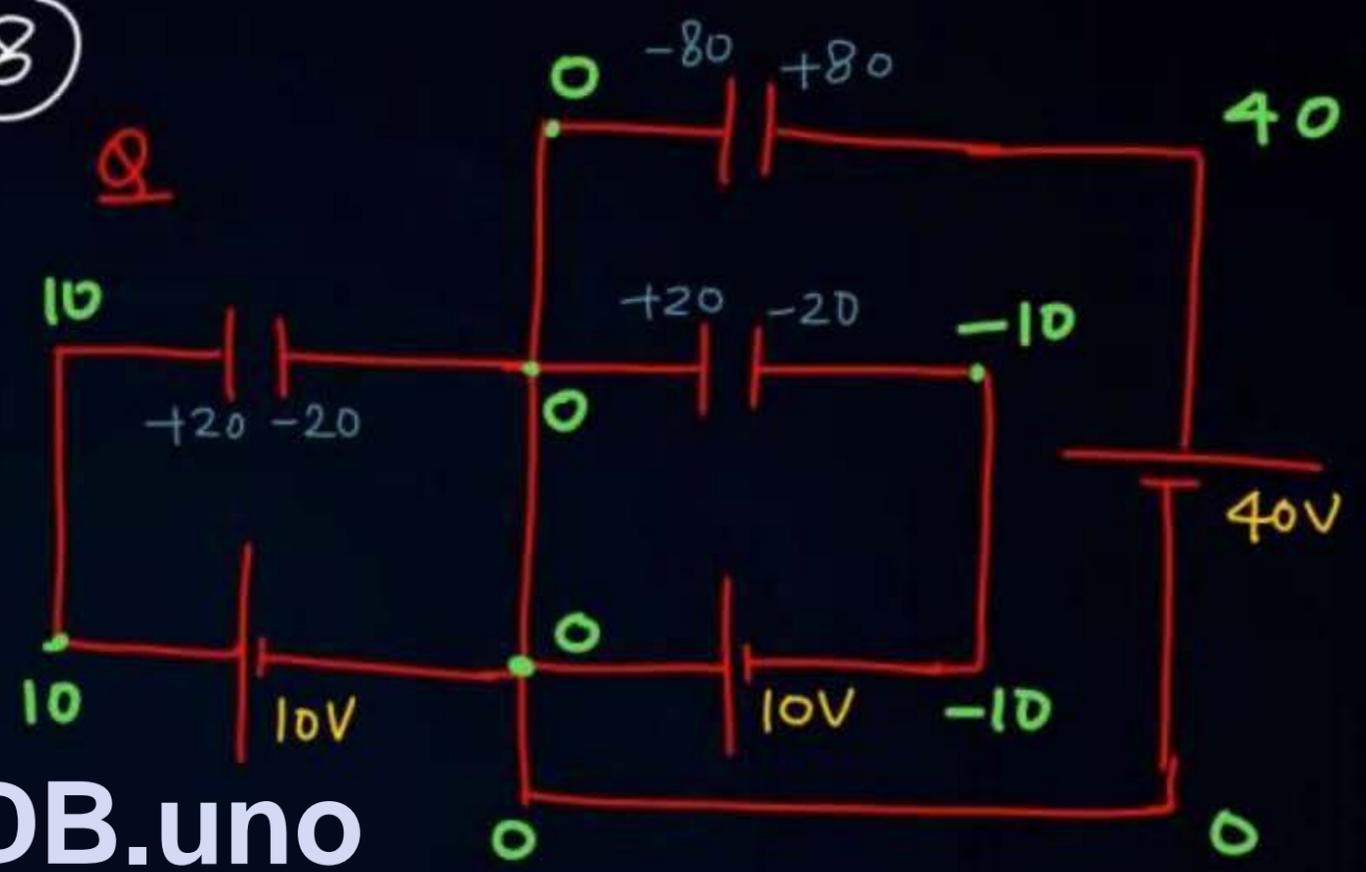


ATDB.uno

C=2F (each)




9

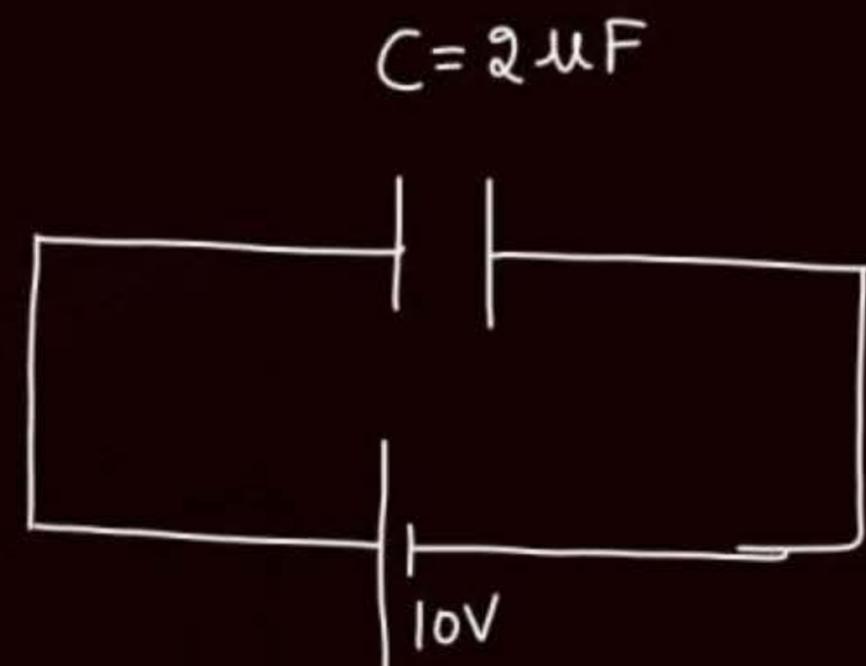


$$C = 2 \mu F = 2 \times 10^{-6} F$$

10

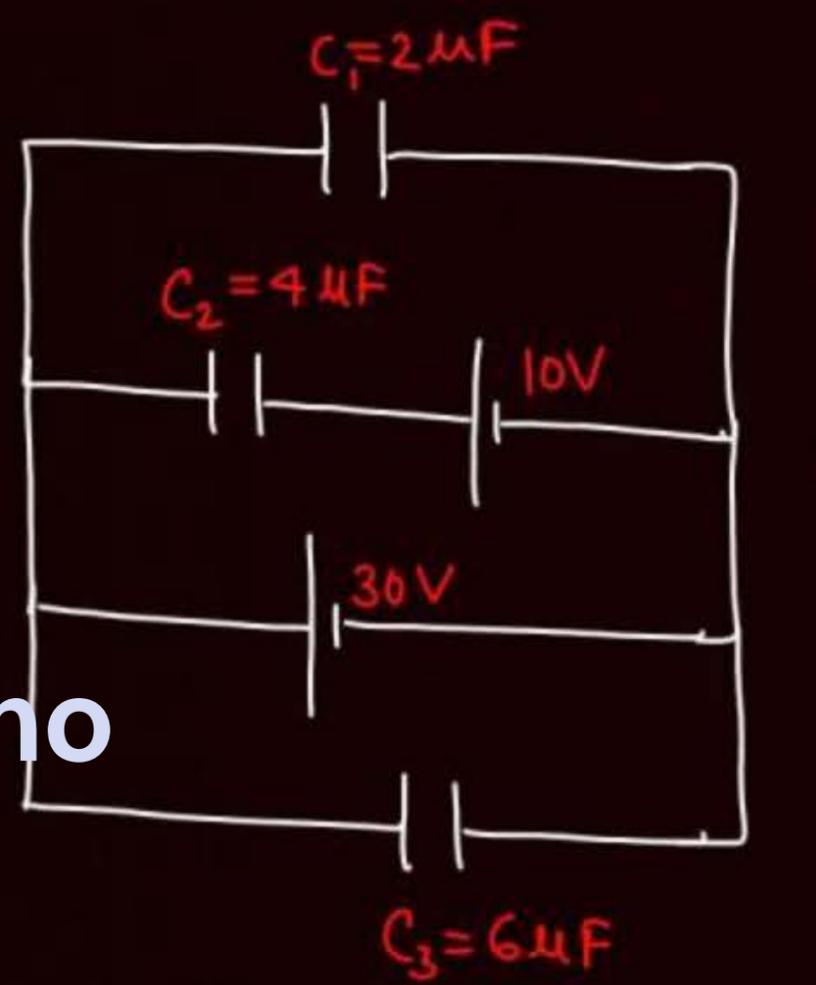

ATDB.uno

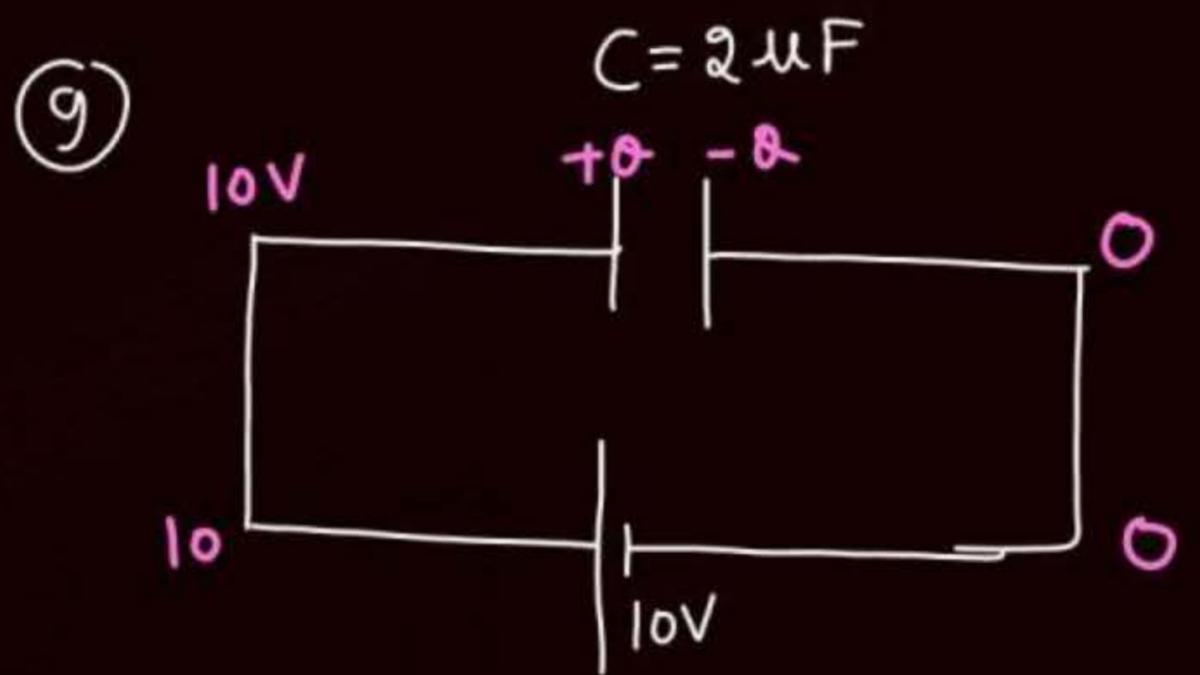


$$C = 2 \mu F = 2 \times 10^{-6} F$$

$$Q = CV = 2 \times 10^{-6} \times 10$$

$$= 20 \times 10^{-6} \text{ Coulomb}$$

$$= 20 \mu C$$

ATDB.uno

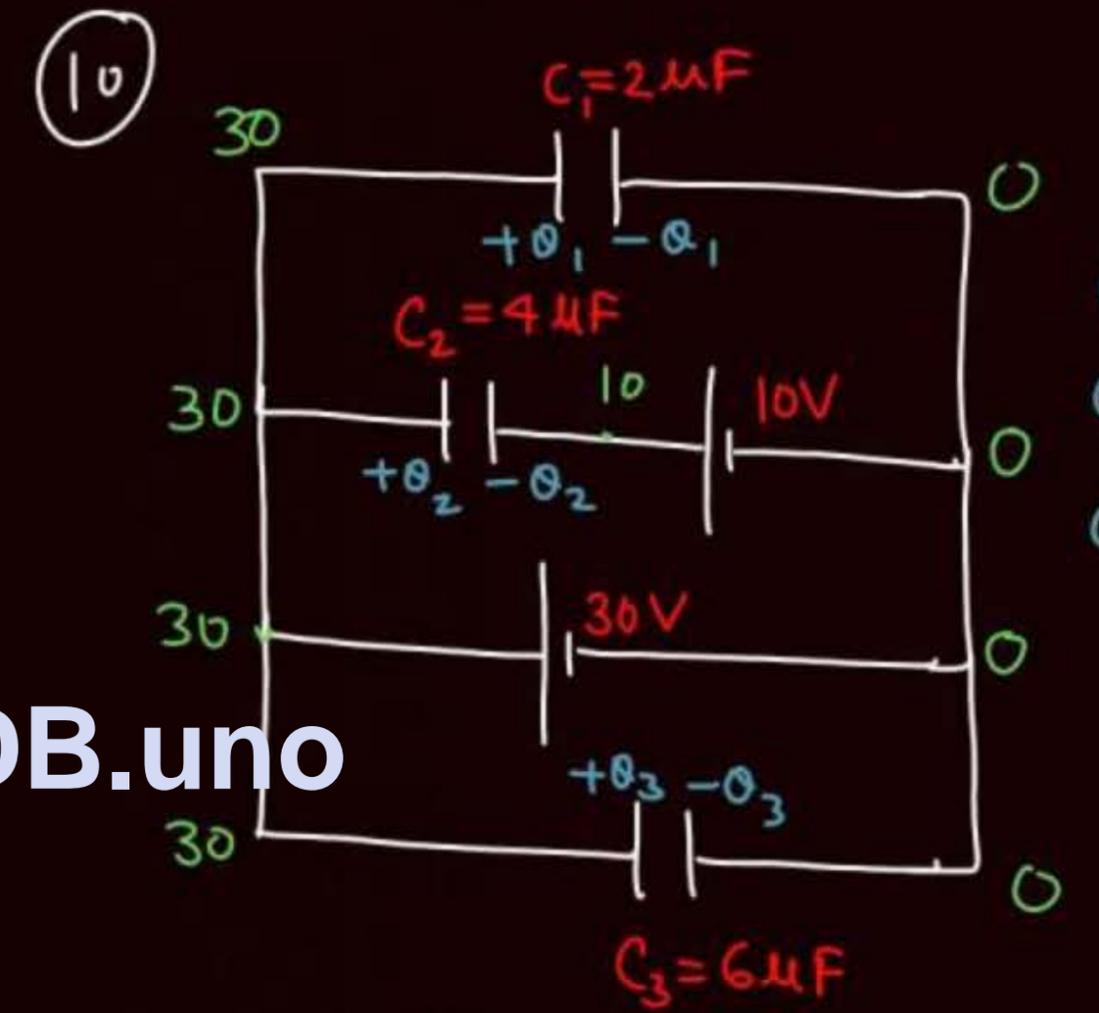


$$Q_1 = 2 \times 30 = 60 \mu C$$

$$Q_2 = 4 \times 20 = 80 \mu C$$

$$Q_3 = 6 \times 30 = 180 \mu C$$




(12)

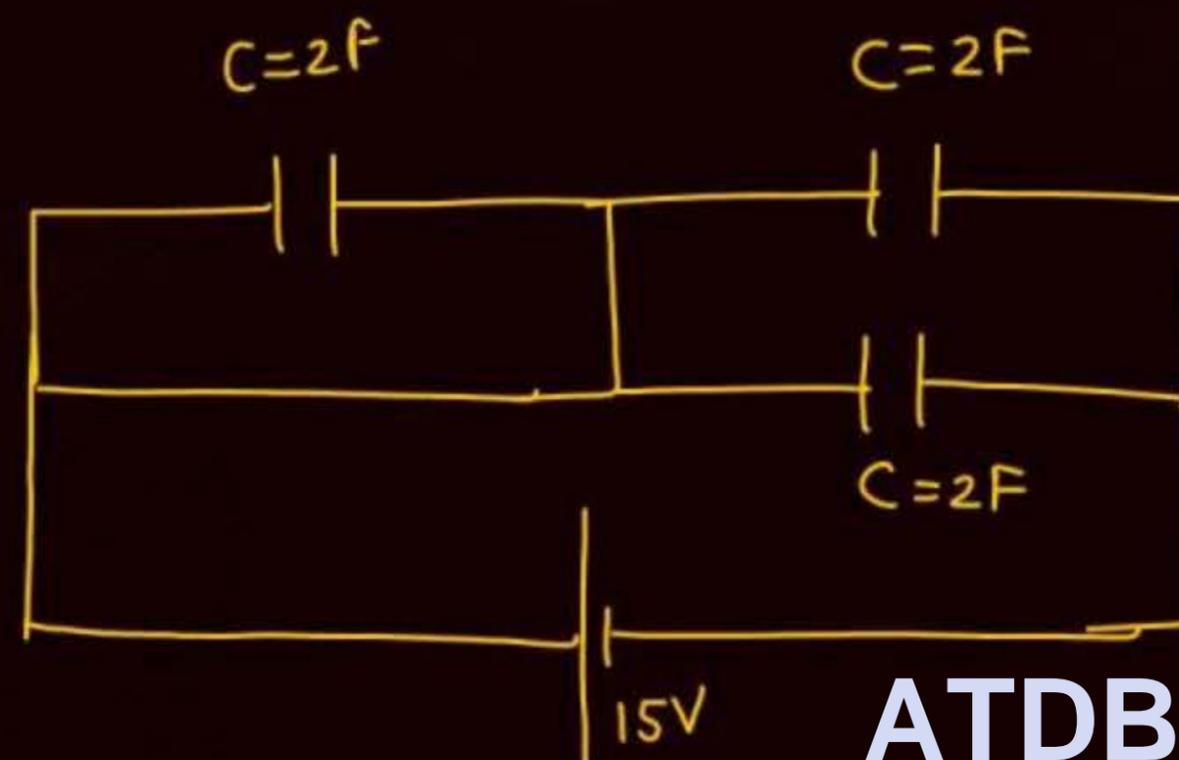


ATDB.uno

Q (13)

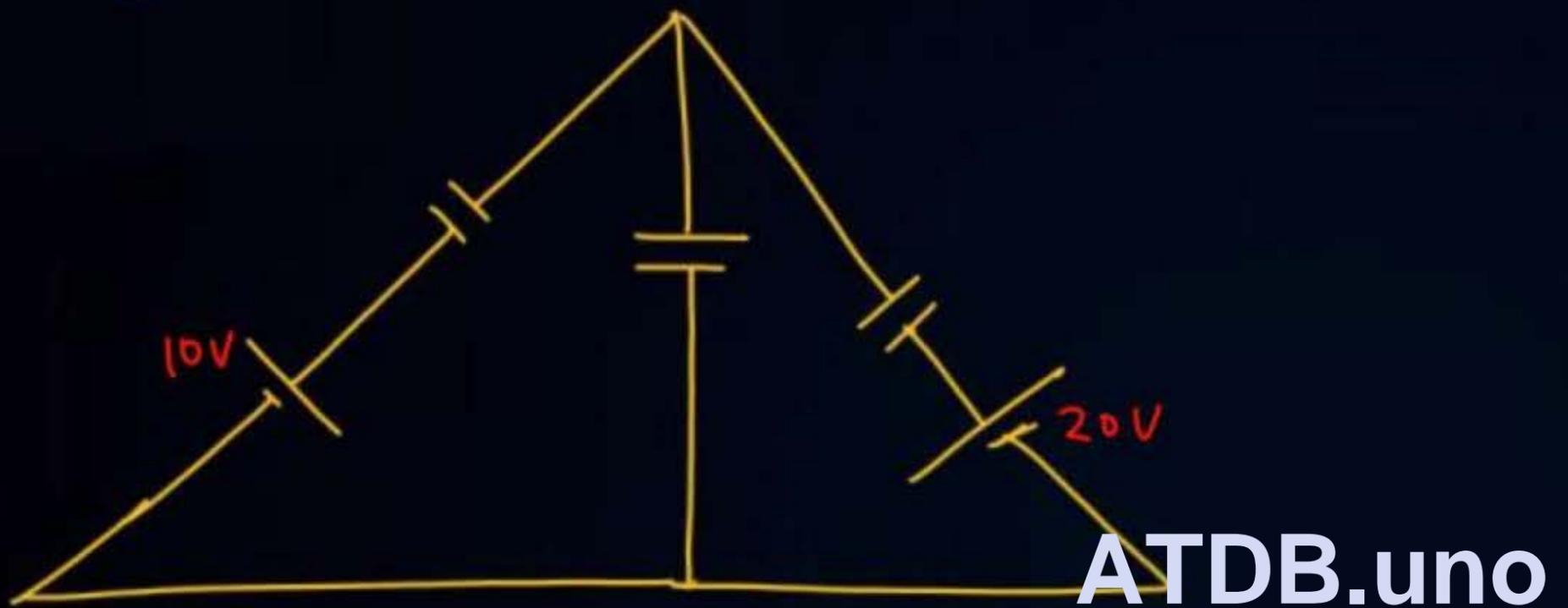


Q (13) Assume initially charge on all capacitors was zero

$C = 2F$ (each)

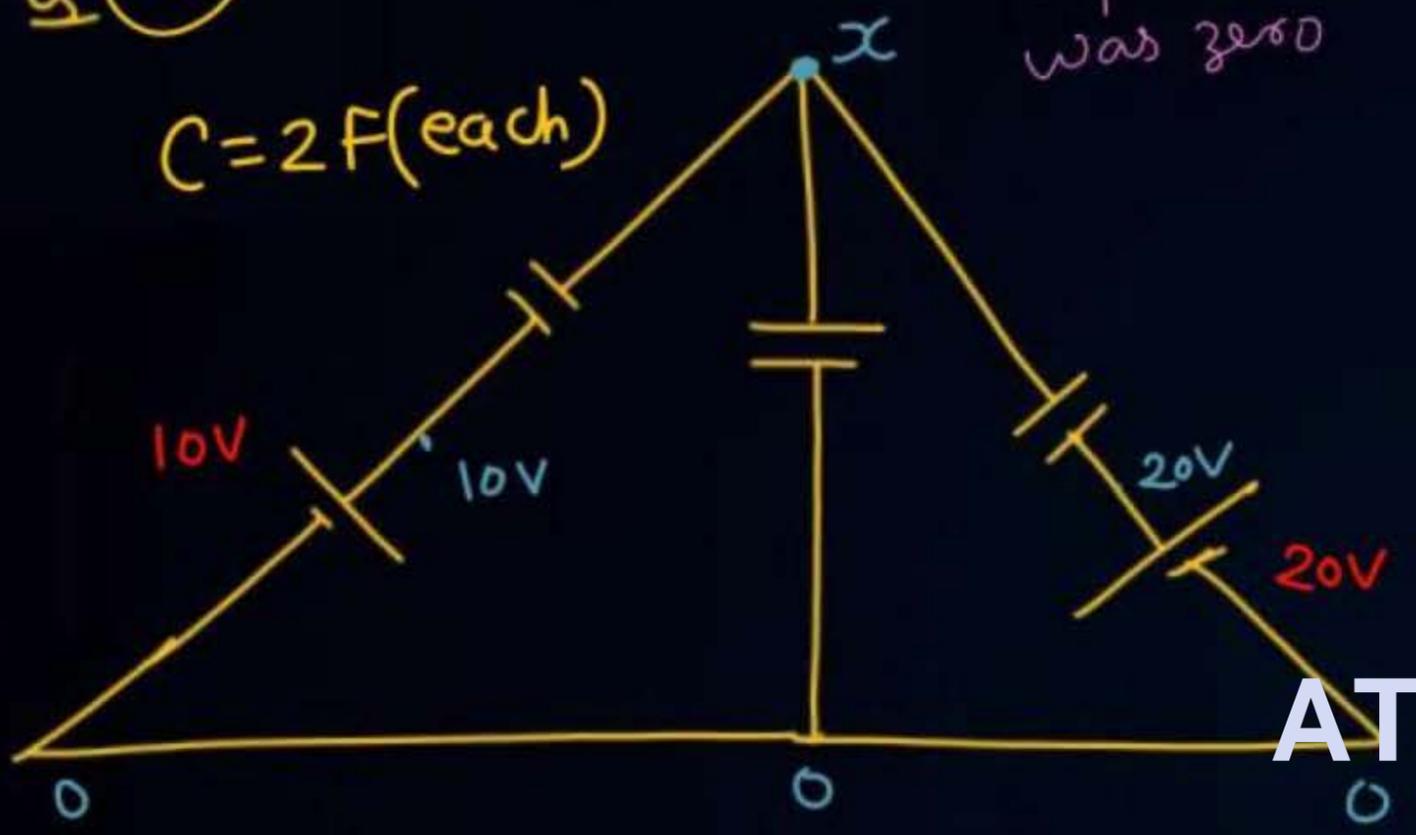

Junction Law

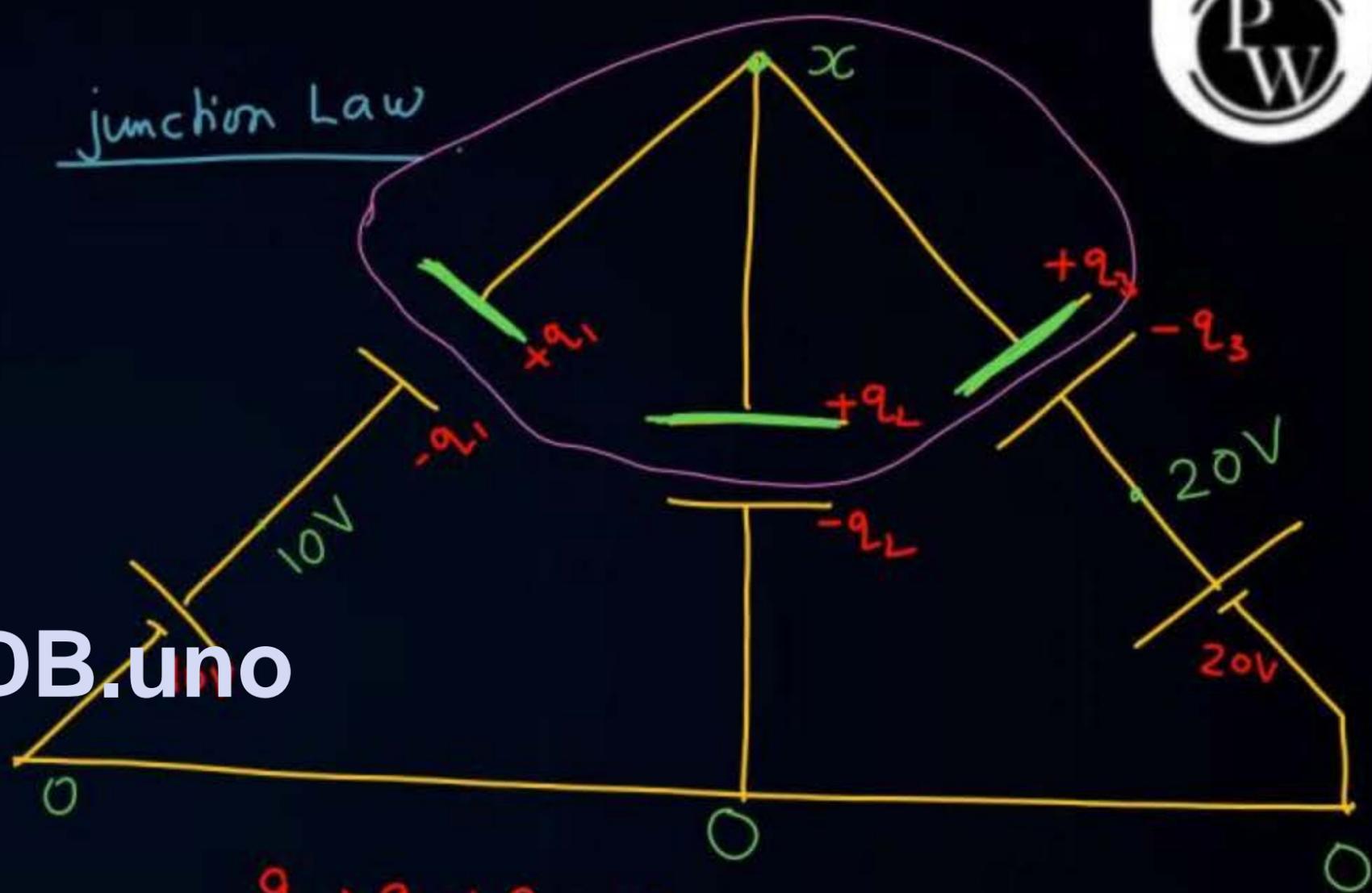

ATDB.uno

$$q_1 = 2 \times 0 = 0$$

$$q_2 = 2 \times 10 = 20$$

$$q_3 =$$



$$q_1 + q_2 + q_3 = 0$$

$$2 \times (x - 10) + 2 \times (x - 0) + 2 \times (x - 20) = 0$$

$$6x - 20 - 40 = 0$$

$$x = 10$$



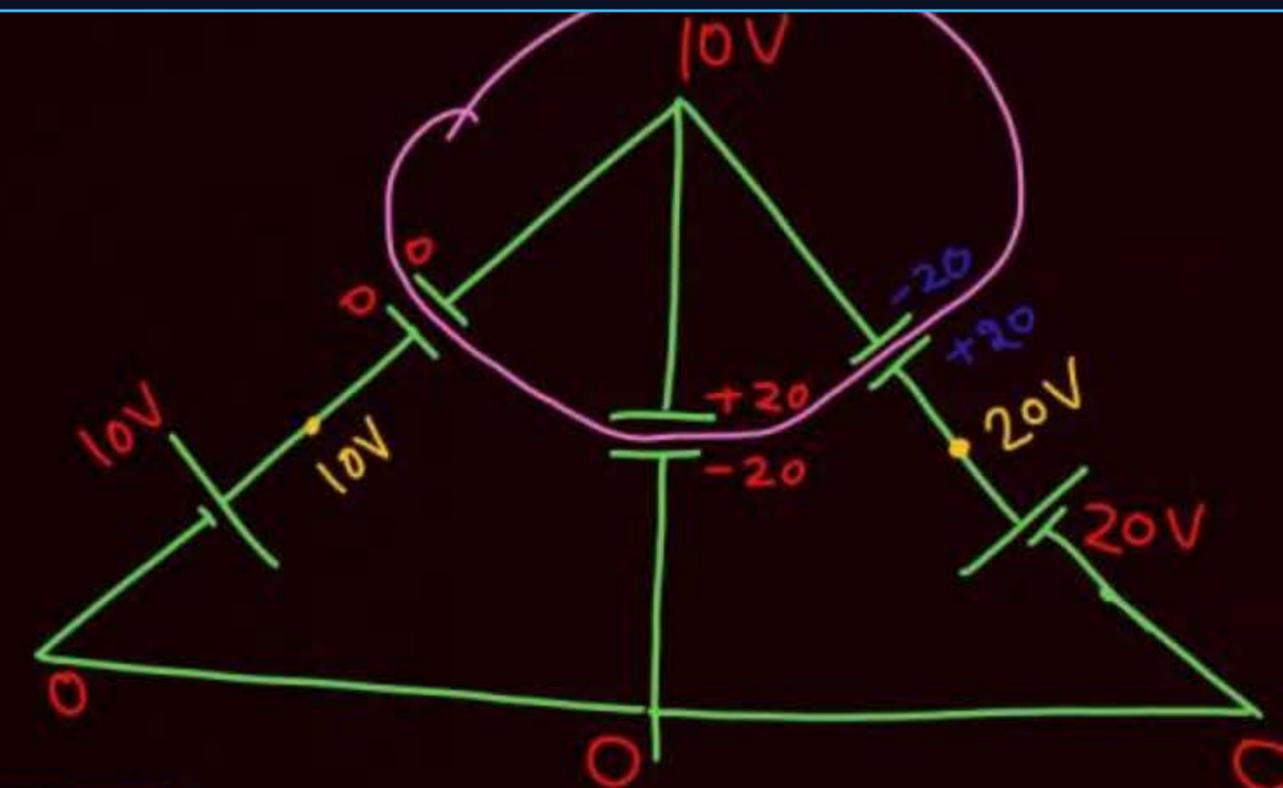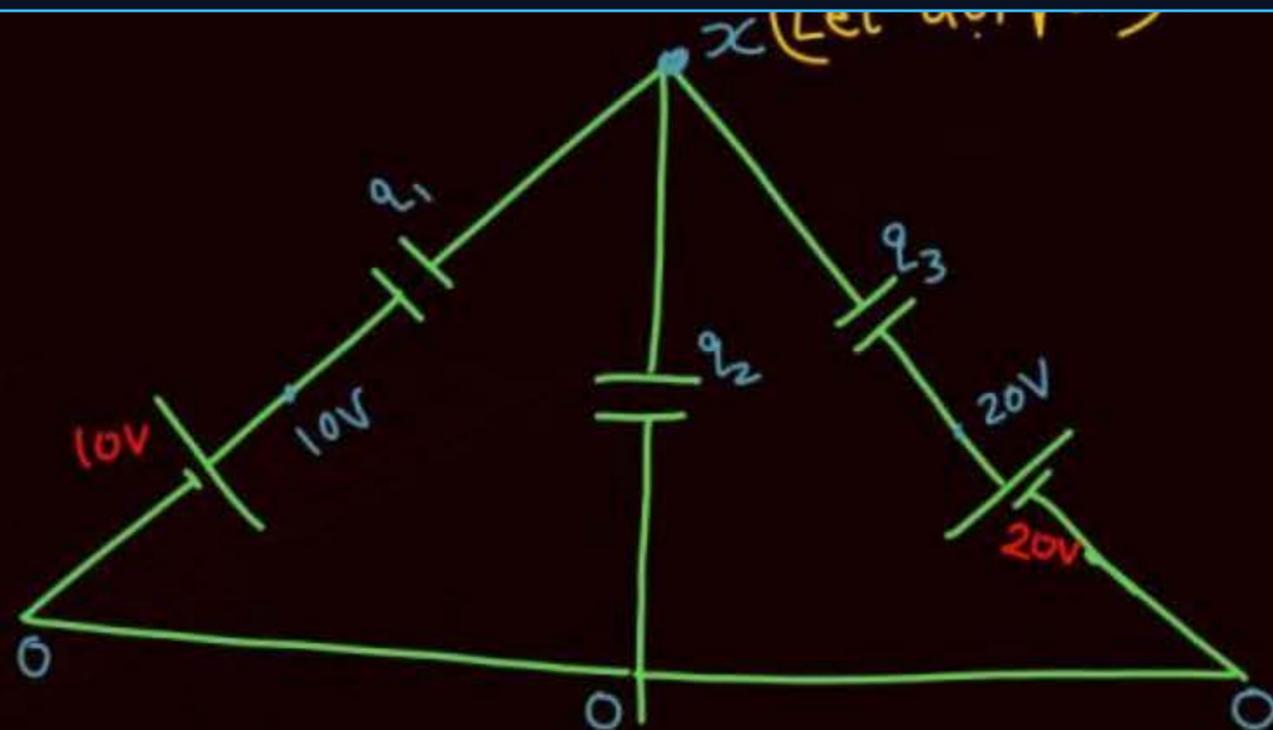

$$C = 2 \text{ F (each)}$$


$$q = CV = QC$$

$$q_1 + q_2 + q_3 = 0$$

$$(x - 10) \times 2 + (x - 0) \times 2 + (x - 20) \times 2 = 0$$

$$6x = 60$$


$$x = 10 \text{ (matlab)}$$

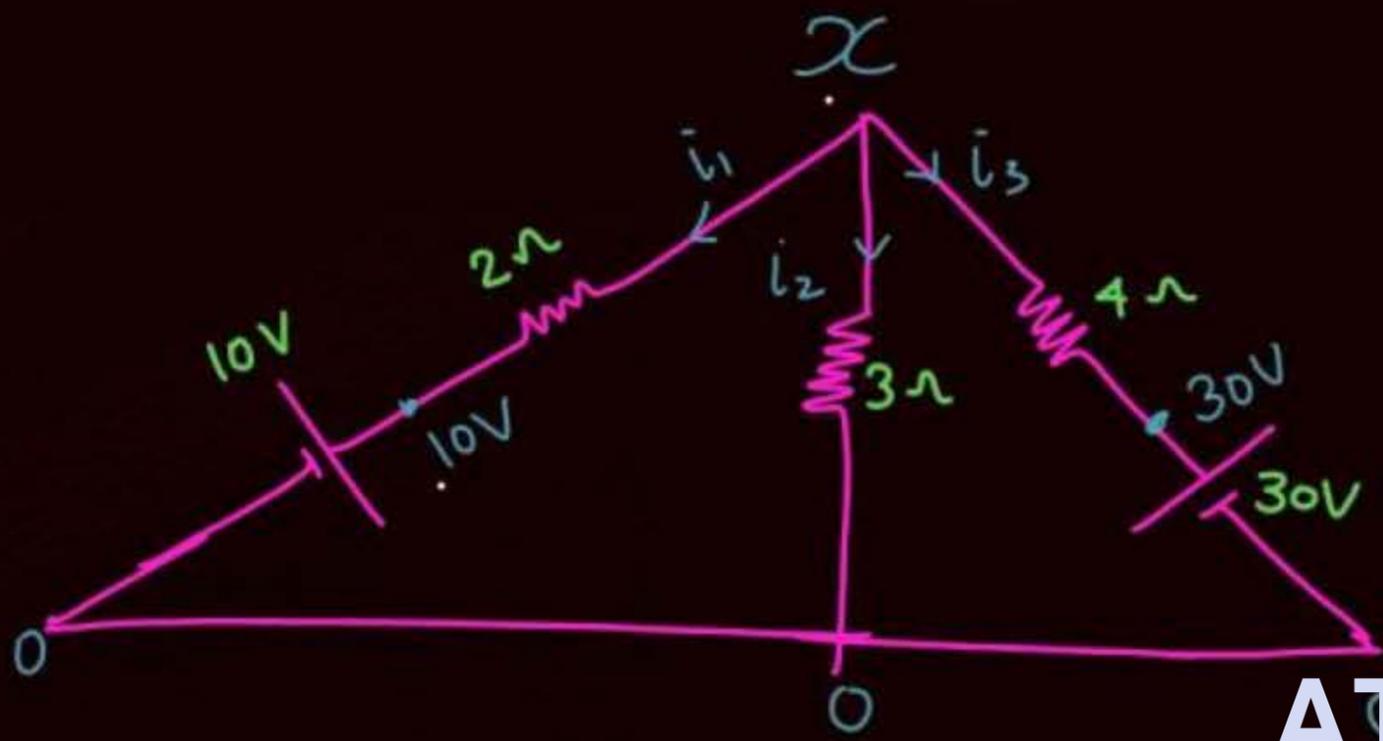

ATDB.uno

$$i_1 + i_2 + i_3 = 0$$
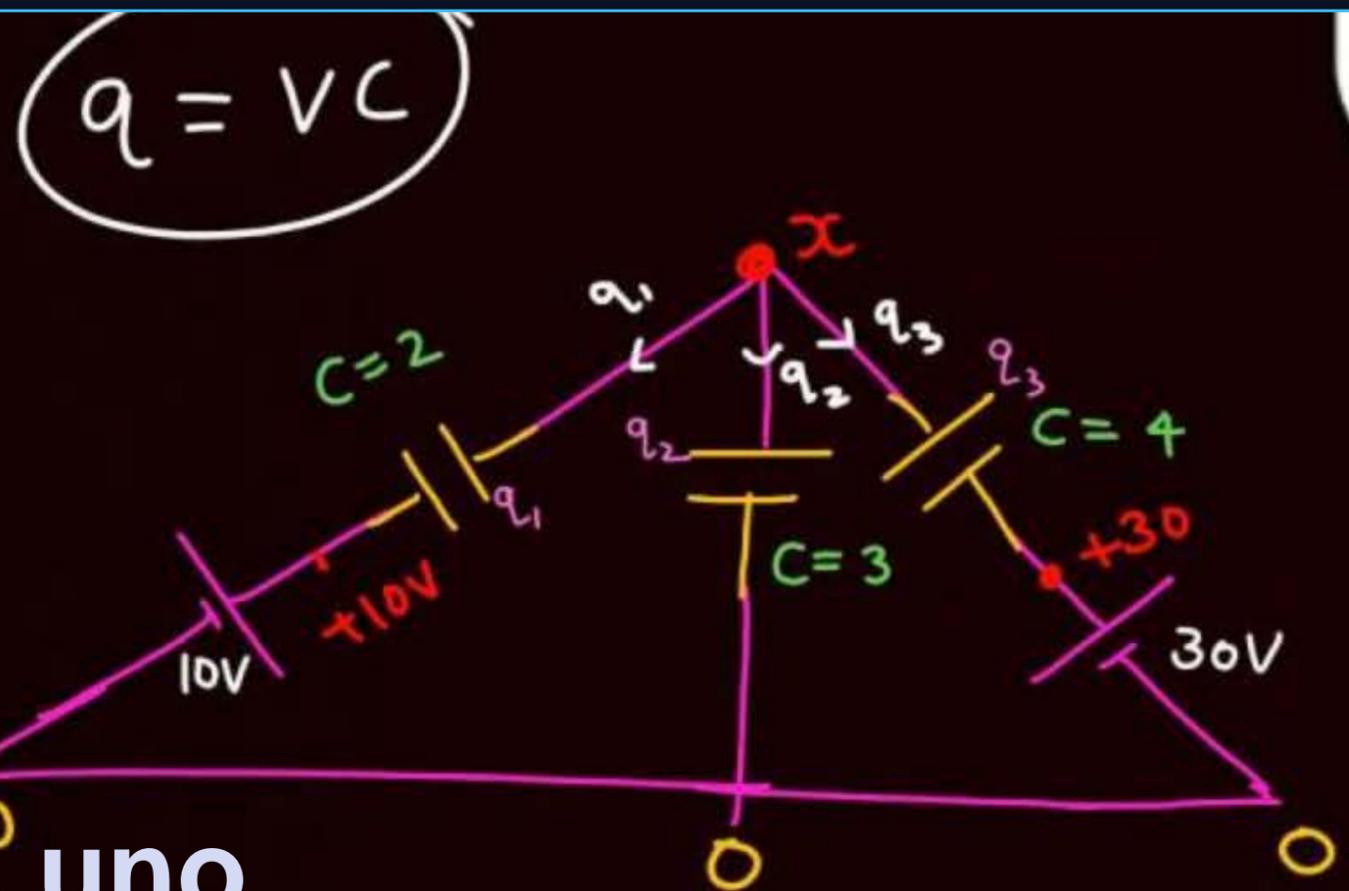
$$\frac{x-10}{2} + \frac{x-0}{3} + \frac{x-30}{4} = 0$$




$$q = VC$$

$$q_1 + q_2 + q_3 = 0$$

$$(x-10) \times 2 + (x-0) \times 3 + (x-30) \times 4 = 0$$



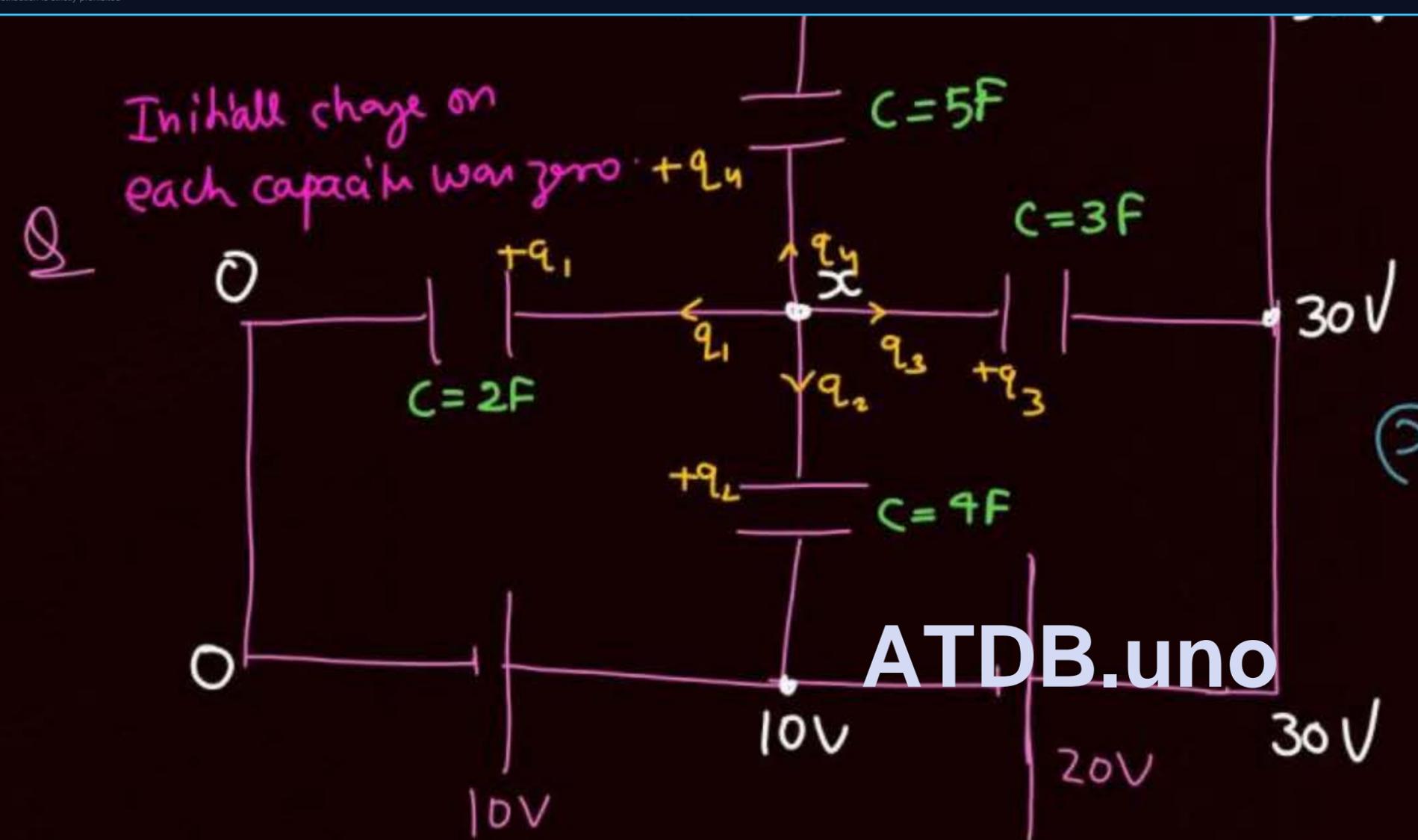Initial charge on each capacitor was zero



$$q_1 + q_2 + q_3 + q_4 = 0$$



$$(x - 0) \times 2 + (x - 10) \times 4 + (x - 30) \times 3 + (x - 30) \times 5 = 0$$

ATDB.uno



$Q = CV$

$C = 2F$

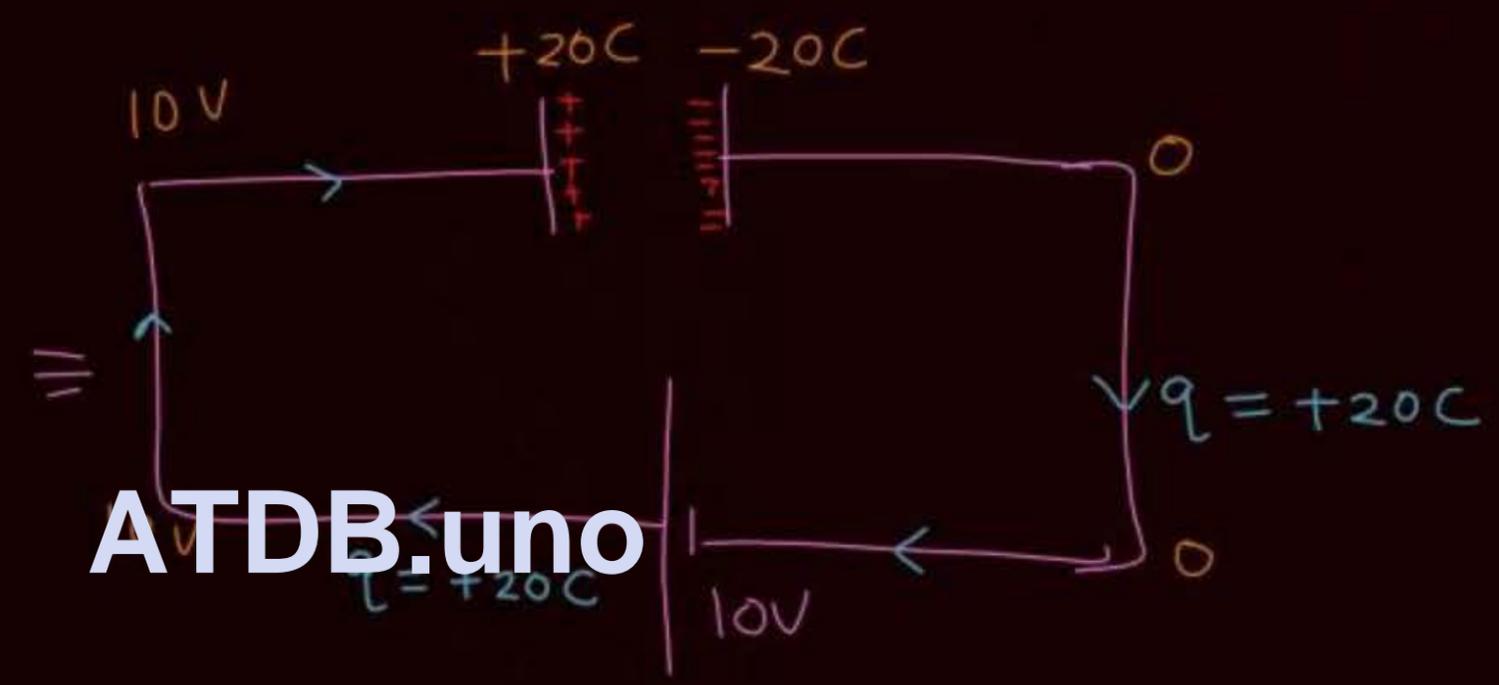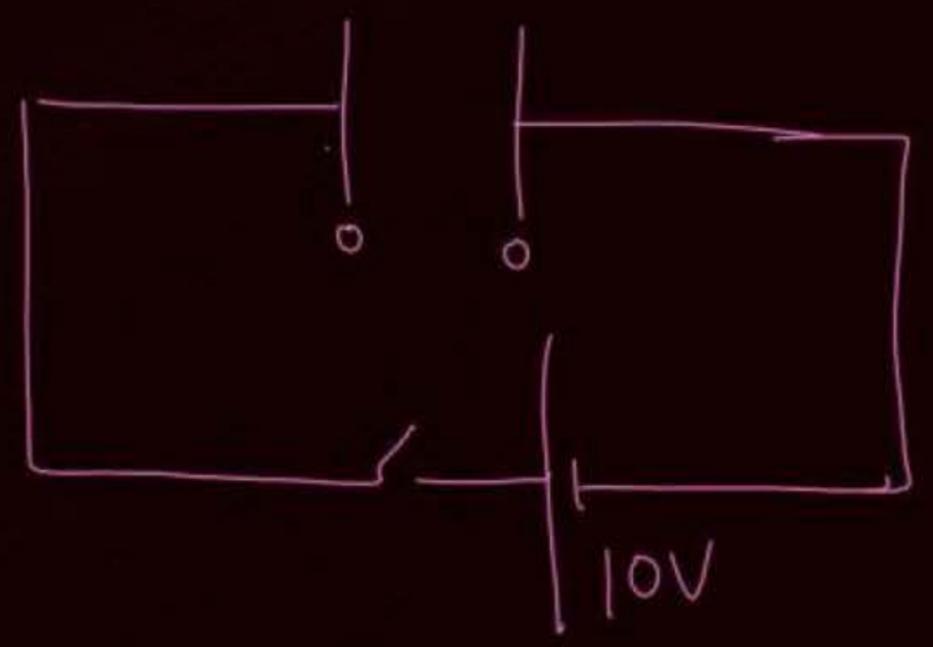


ATDB.uno



14


$C = 2F$ (each)

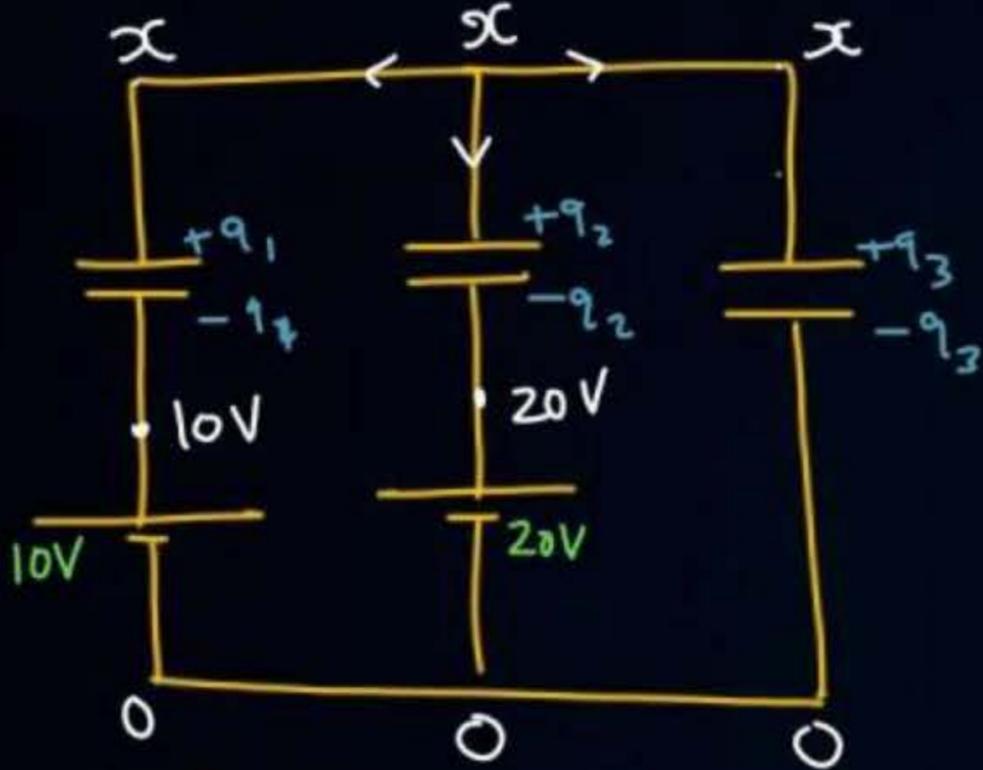

$$(x-10)^2 + (x-20)^2 + (x-0) \times 2 = 0$$

15

Q

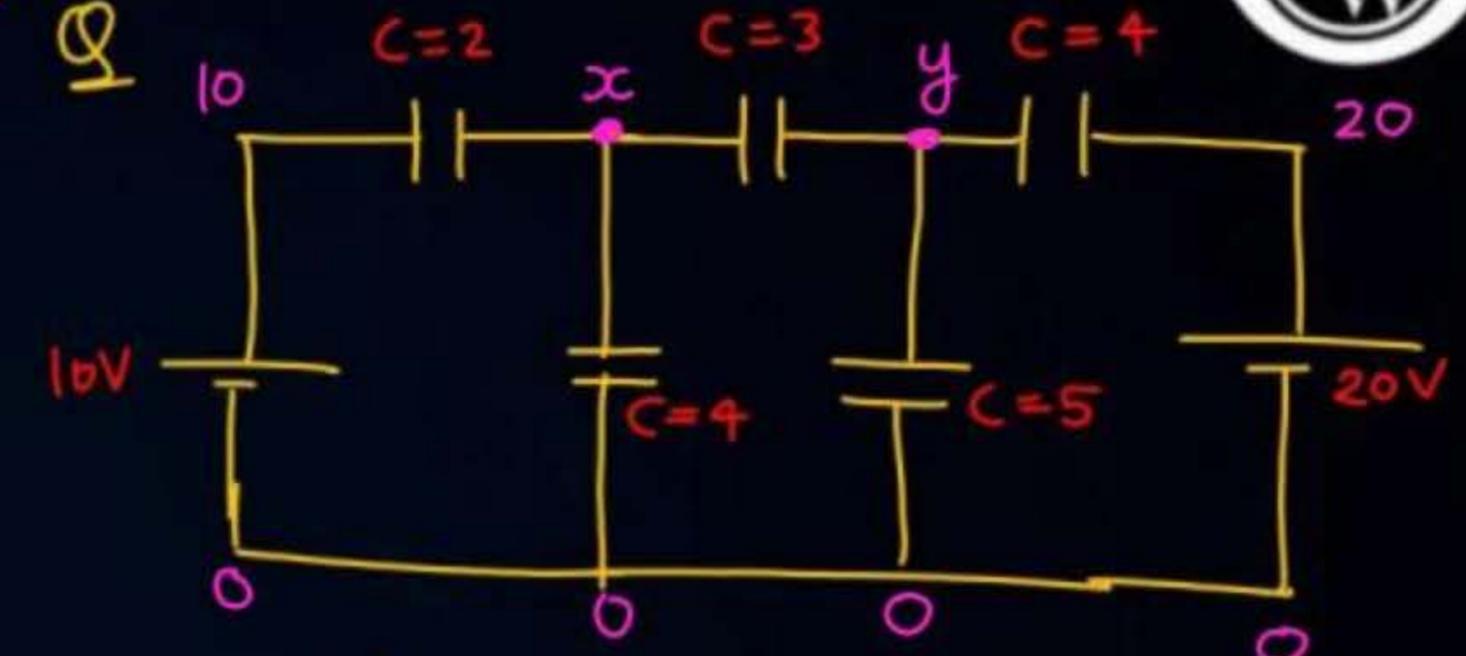

$$(x-10)^2 + (x-0)^4 + (x-y) \times 3 = 0$$


$$(y-x) \times 3 + (y-0) \times 5 + (y-20) \times 4 = 0$$

ATDB.uno




14

$C = 2F$ (each)

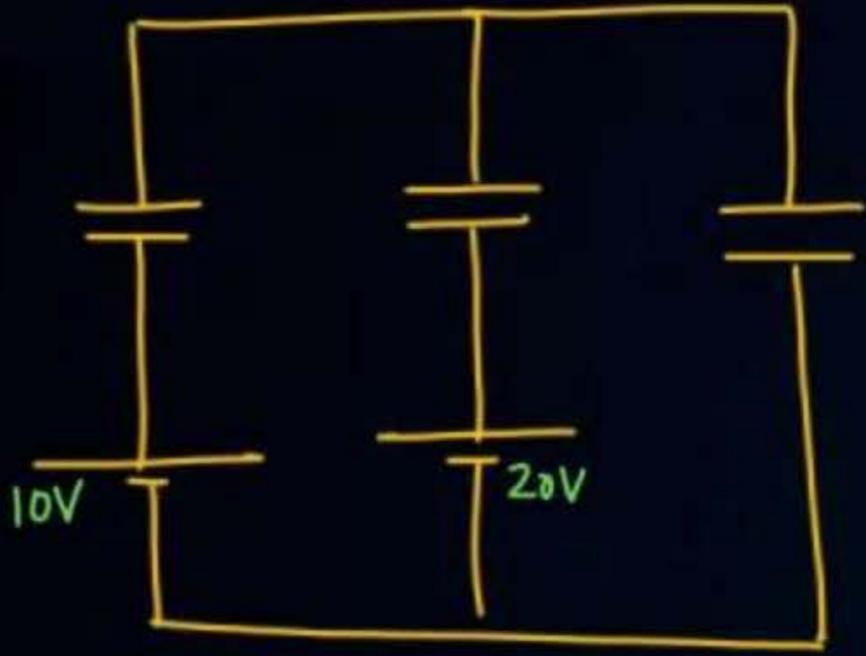


15

Q

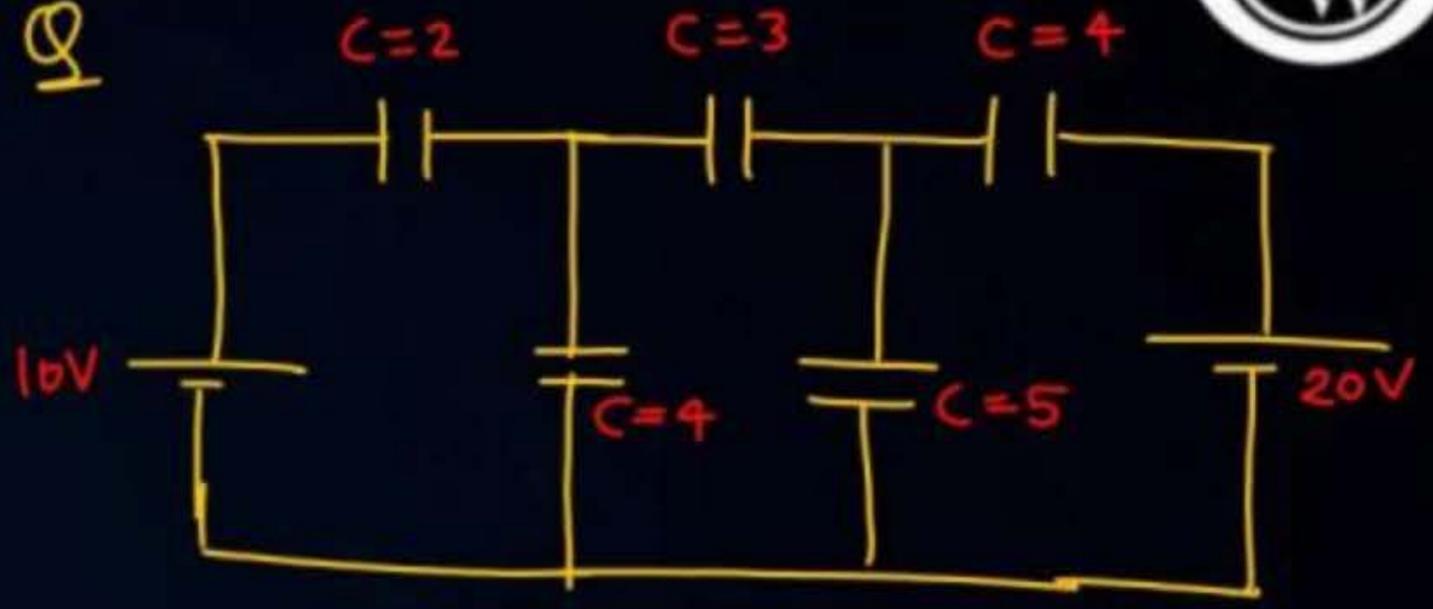


ATDB.uno

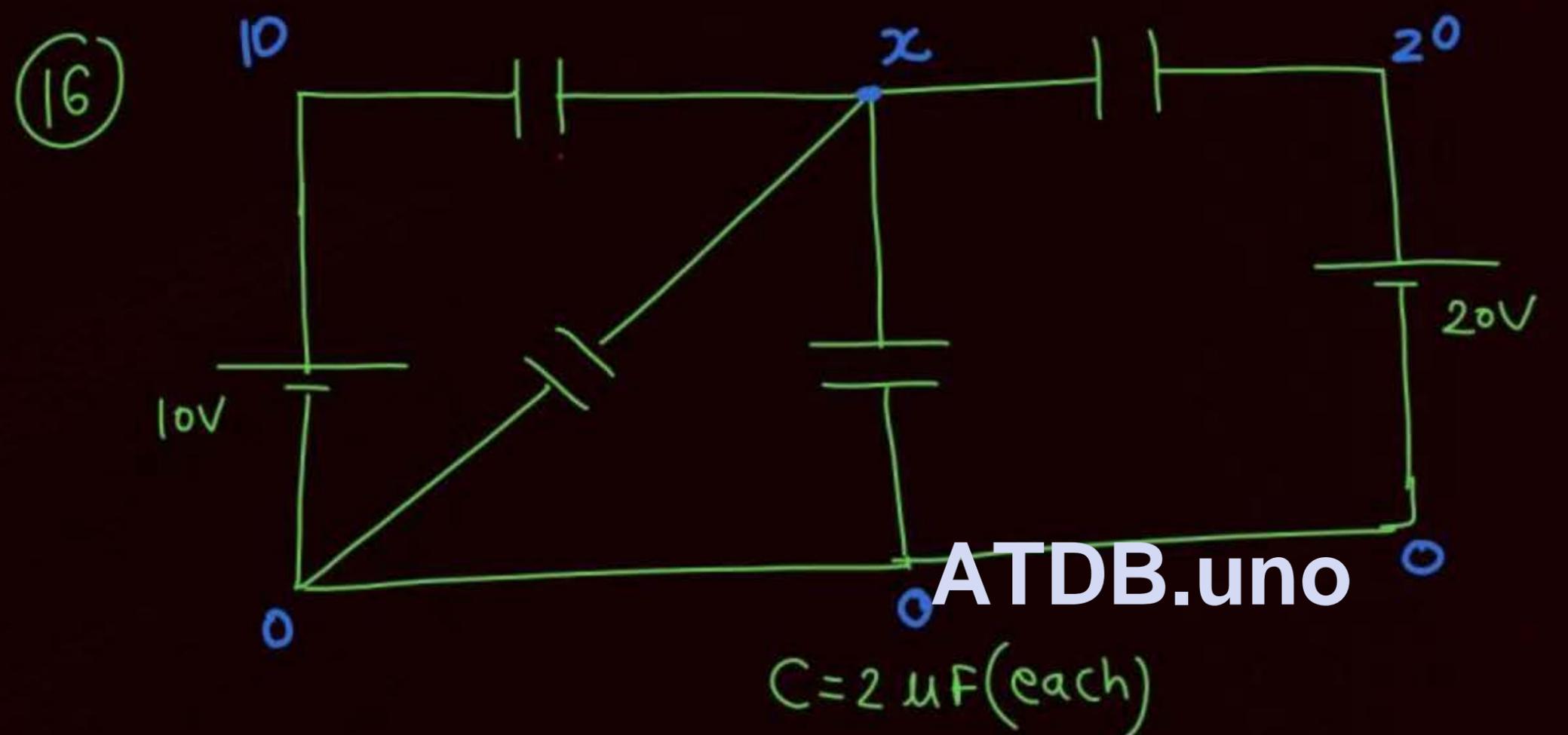

$$(x - 10)^2 + (x - 0) \times 2 + (x - 0) \times 2 + (20 - x) \times 2 = 0$$



16

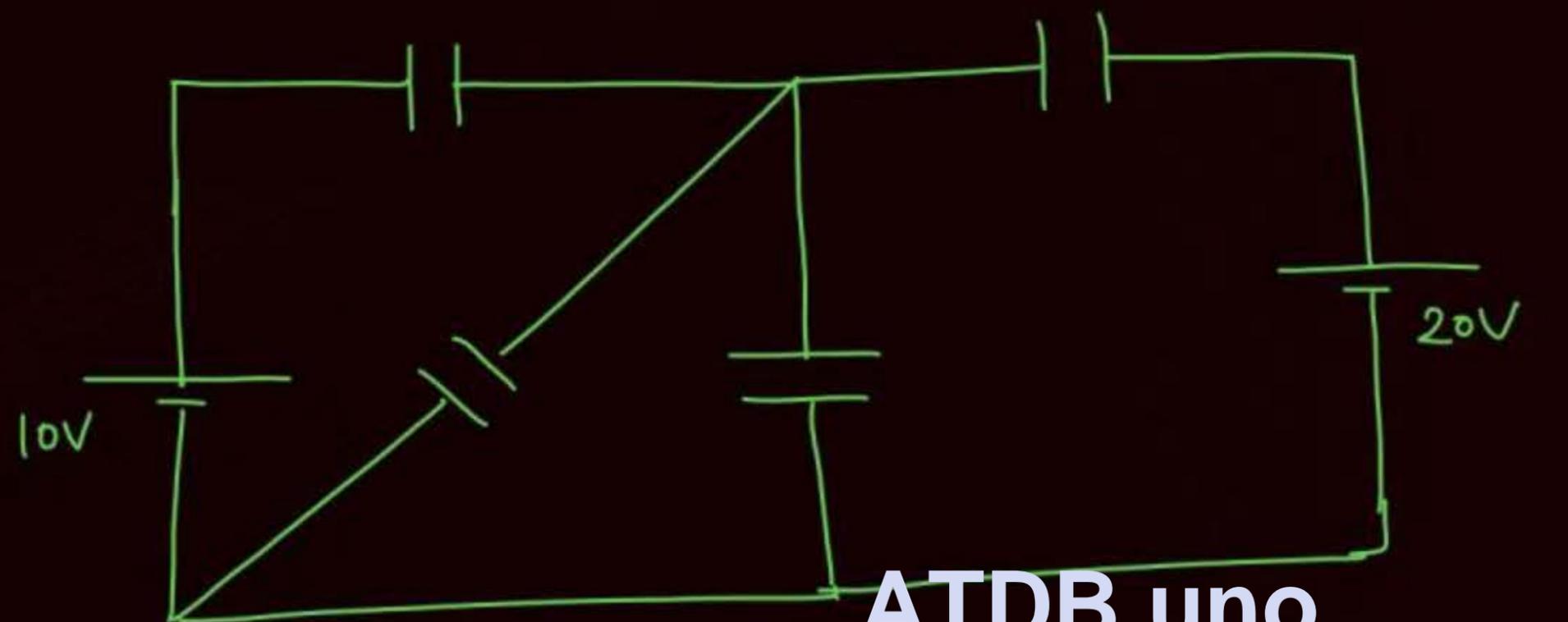

ATDB.uno

$$C = 2 \mu\text{F} (\text{each})$$



THANK YOU

ATDB.uno

