

PRAYAS

JEE 2025

ATDB.uno

Lecture - **02**

Physics

Capacitor

By- Saleem Ahmed Sir



Today's Goal




— Circuit Analysis

ATDB.uno



Cube each of length l , Resistanca R

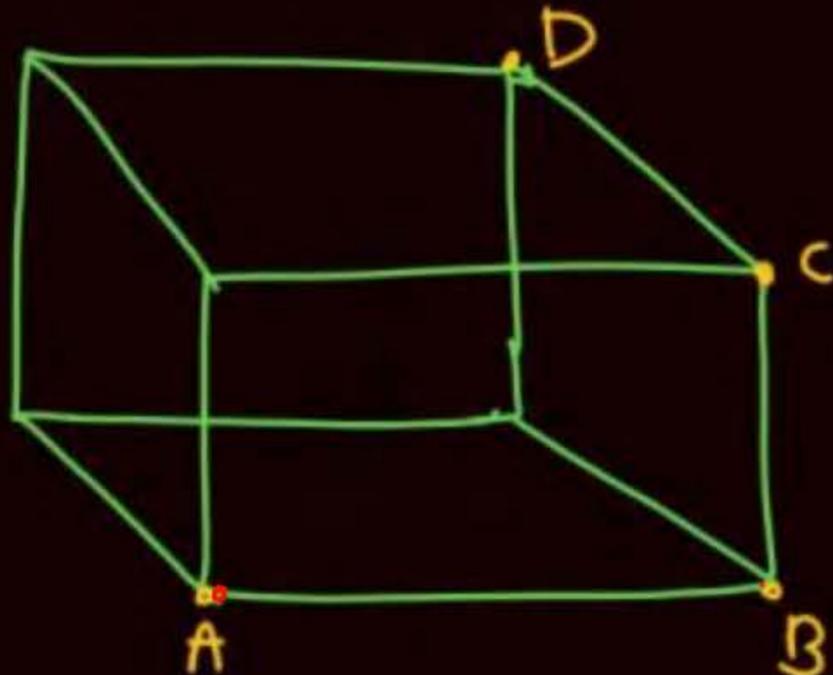

$\frac{7R}{12}$ $\frac{3R}{4}$ $\frac{5}{6}R$
 पास-पास शोडाहूट स्वसंरु

R_{AB} R_{AC} R_{AD}
ATDB.uno

$\frac{7R}{12}$ $\frac{3R}{4}$ $\frac{5R}{6}$

(Not in mains/Advans)
Colour coding




Black	→	B	→	0
Brown	→	B	→	1
Red	→	R	→	2
Orange	→	O	→	3
Yellow	→	Y	→	4
Green	→	G	→	5
Blue	→	B	→	6
Violet	→	V	→	7
Grey	→	G	→	8
White	→	W	→	9

Gold → 5%
 Silver → 10%
 no colour → 20%

Value ⇒ $I II \times 10^{III} \pm IV \%$ ↖ tolerance

Q Red green blue gold

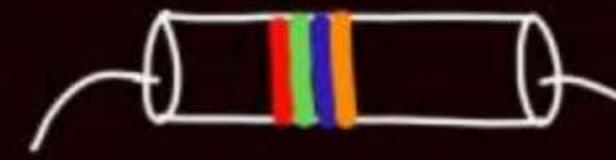

$25 \times 10^6 \pm 5\%$

ATDB.uno


Q Violet Blue Red silver
 $76 \times 10^2 \pm 10\%$

Q $5200 \Omega \pm 5\%$ ⇒ colour sequence = ?

$52 \times 10^2 \pm 5\% = 5200 \Omega \pm 5\%$
 ⇒ RR Gold




meter Bridge

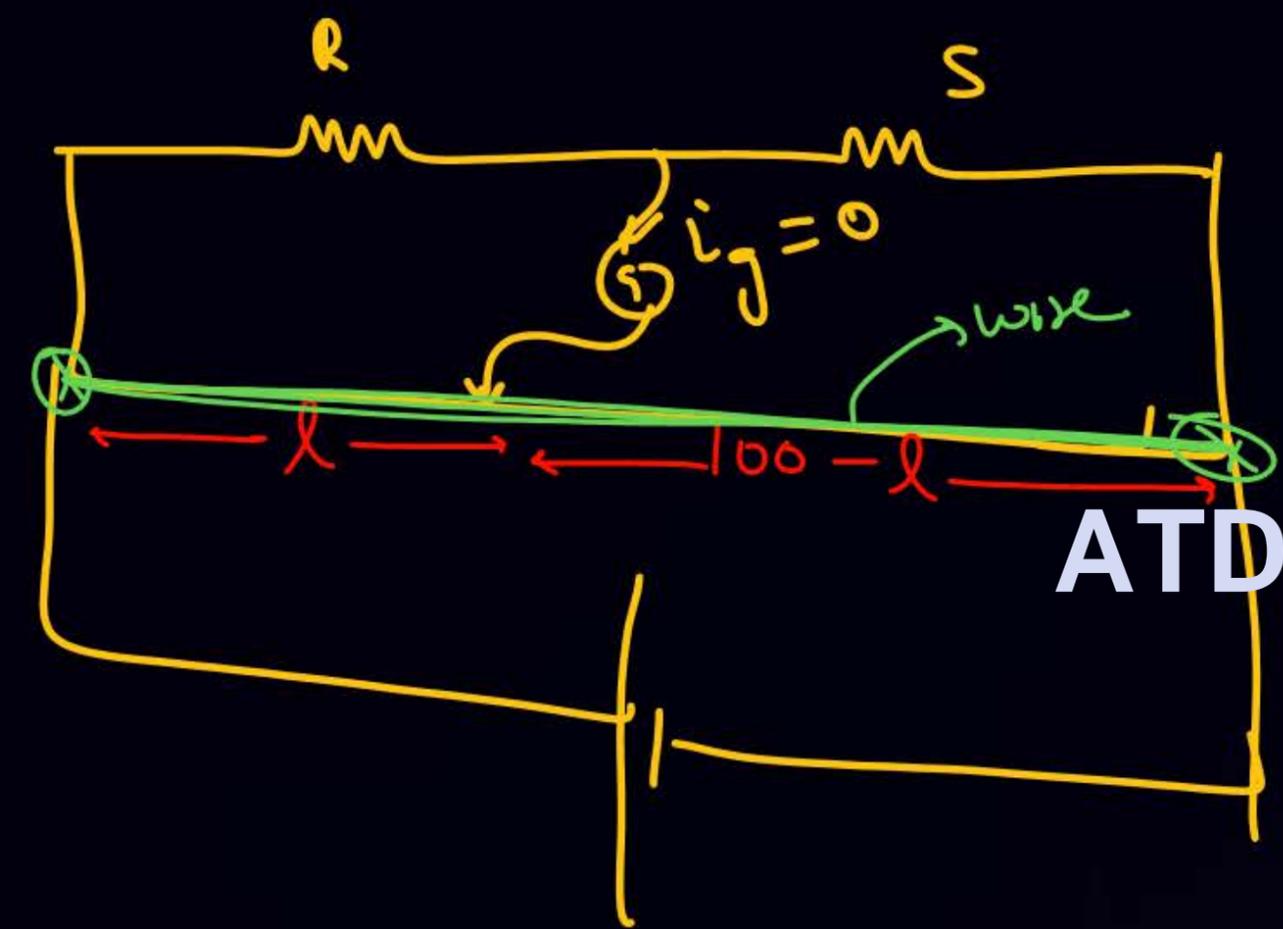

$$\frac{R}{S} = \frac{l}{100-l}$$

ATDB.uno

Meter Bridge

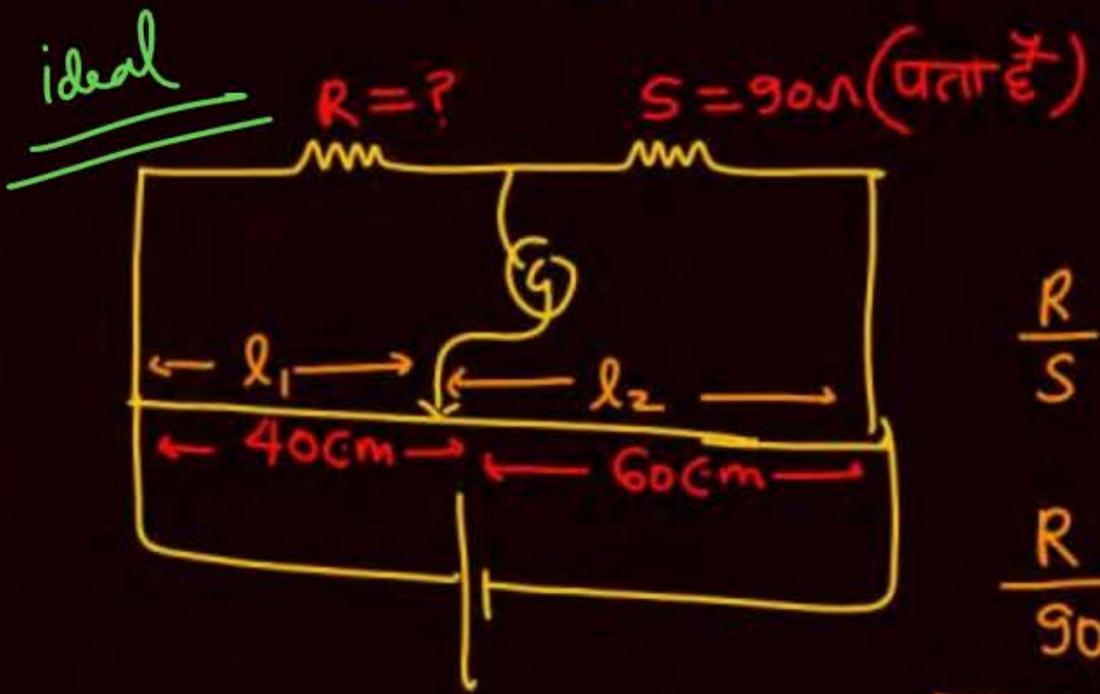


$$\frac{R}{S} = \frac{l_1}{l_2} = \frac{l}{100-l}$$

$$\frac{R}{90} = \frac{40}{60}$$

$$R = 60\Omega$$

$$\frac{R}{90} = \frac{40}{60}$$

$$R = 60\Omega$$

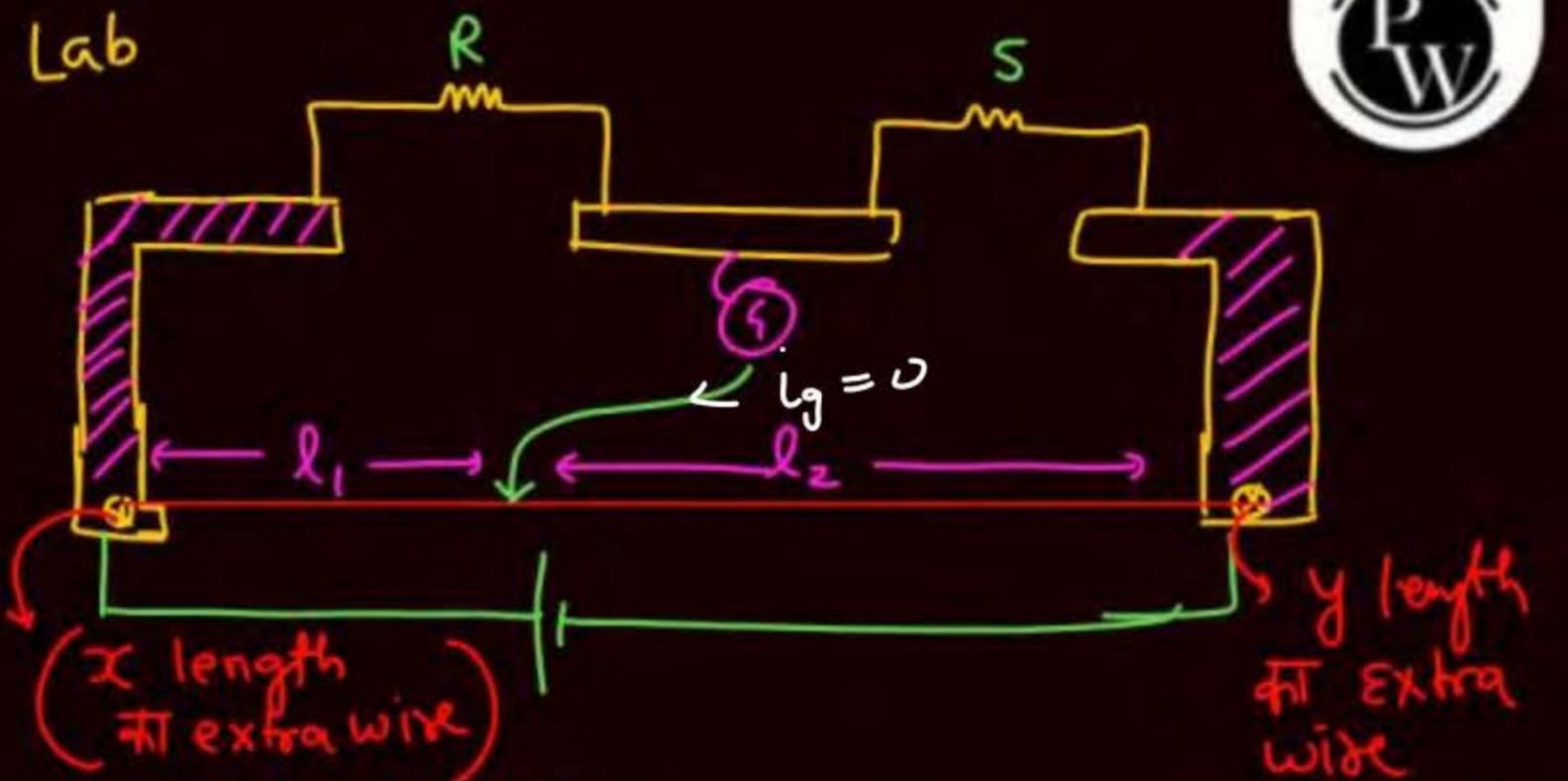

ATDB.uno end correction

परम $\Rightarrow \frac{R}{S} = \frac{l_1}{l_2}$


ideal

$$\frac{R}{S} = \frac{l_1 + x}{l_2 + y}$$

(end correction)

$$\frac{R}{S} = \frac{l + x}{(100 - l) + y}$$

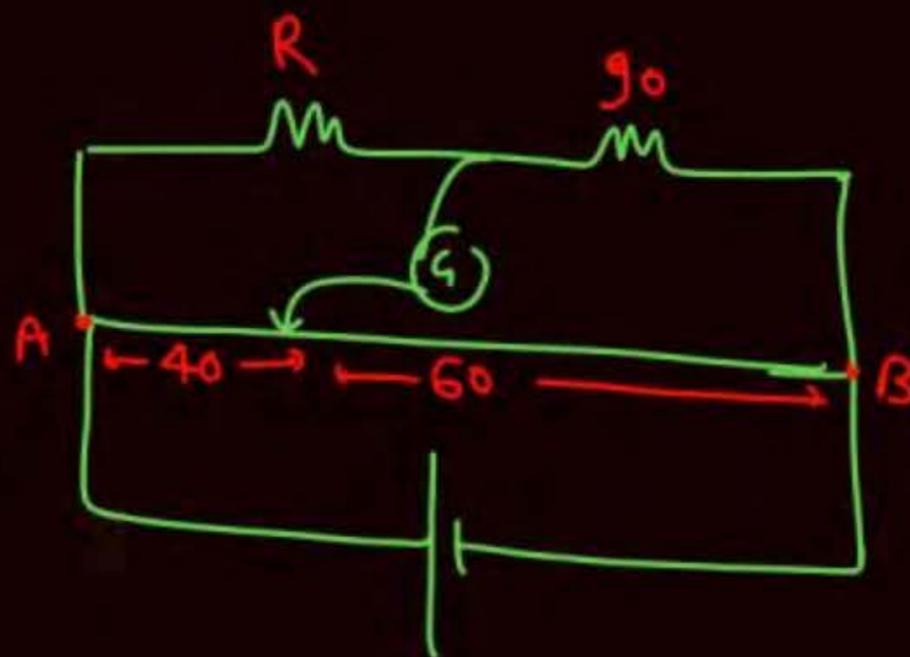Q In meter bridge find value of R if end correction are 1cm & 3cm .
at end A & end B



$$\frac{R}{90} = \frac{40+1}{60+3}$$

$$\frac{R}{90} = \frac{46+1}{60+3}$$


ATDB.uno



Q2



Q2

end corrects - are 1cm & 2cm at A & B.

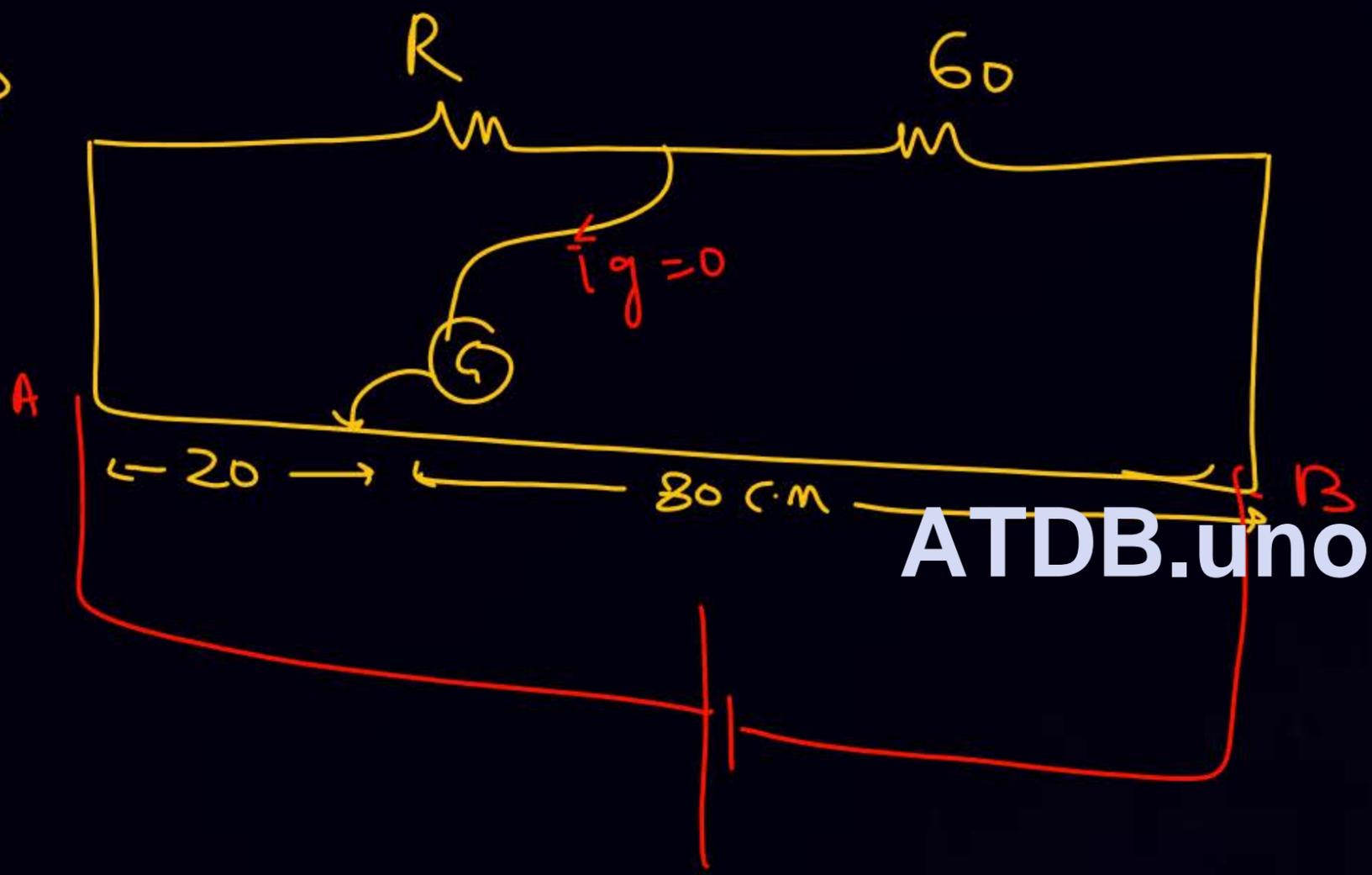

$$\frac{R}{60} = \frac{20 + 1}{80 + 2}$$

ATDB.uno

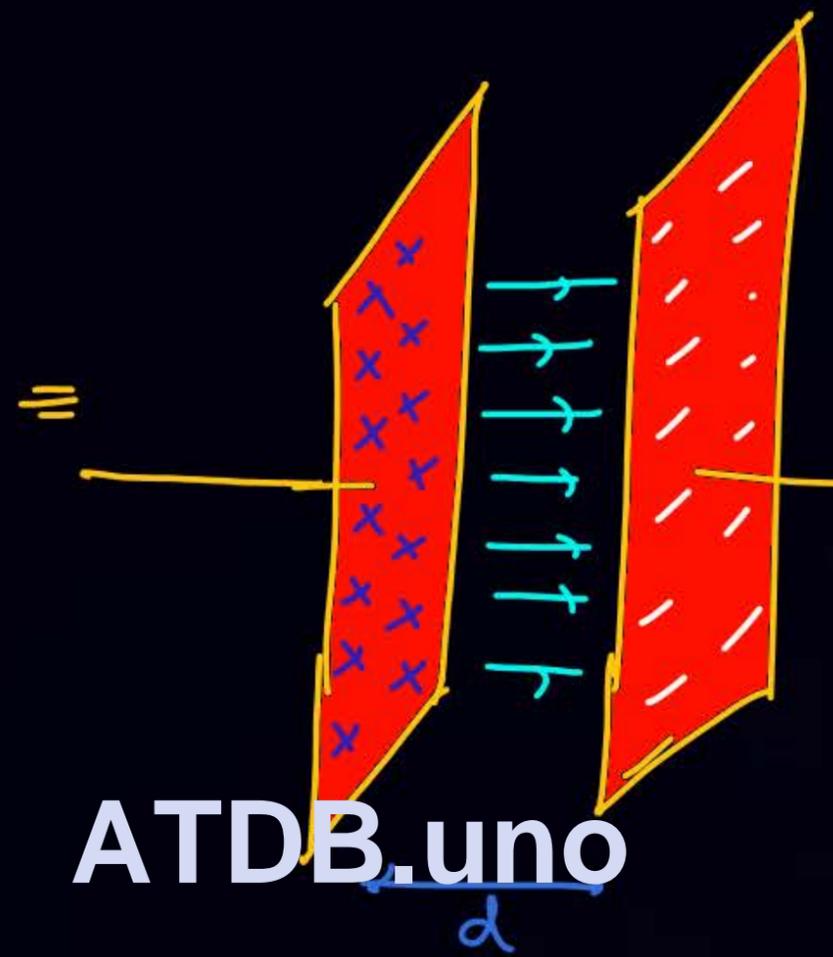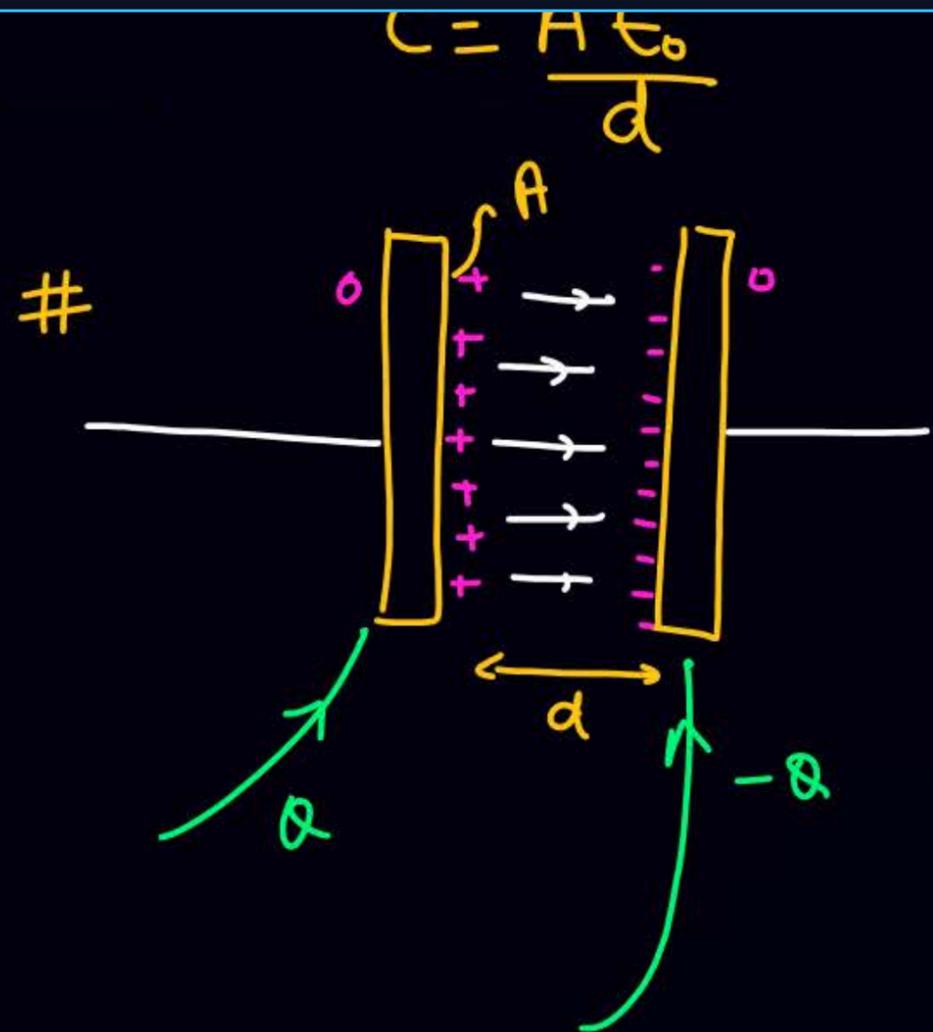

ATDB.uno

$\Delta V = \frac{Q}{C}$

$(0, R)$



$C = 4\pi\epsilon_0 R$




* Cylindrical capacitor

R·m

$$C = \frac{2\pi\epsilon_0 l}{\ln(R_2/R_1)}$$

ATDB.uno

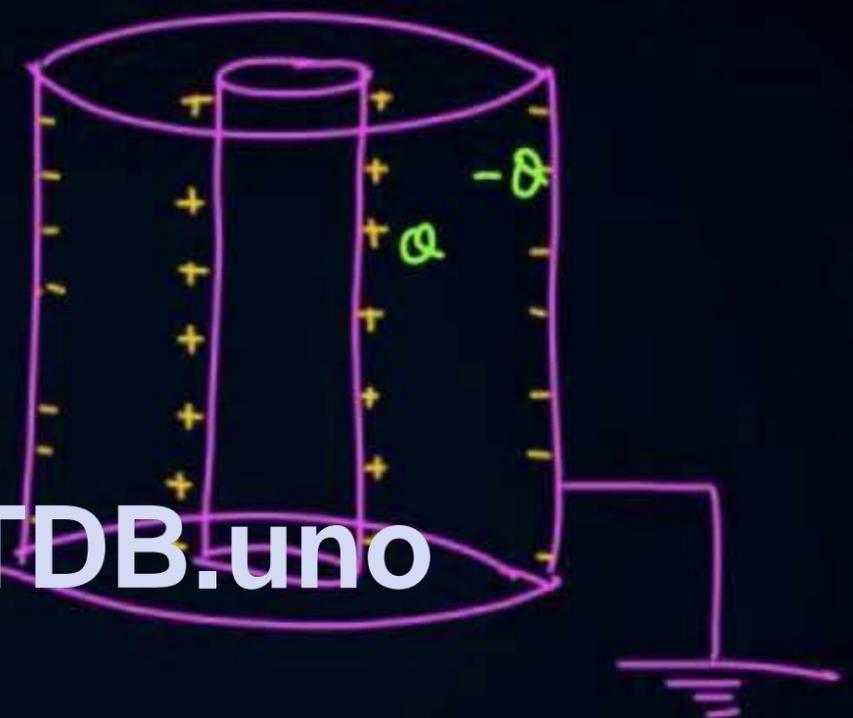



$$\leftarrow \Delta V = V \rightarrow$$



$$\Delta V = \frac{q}{C}$$

$$\Delta V = \frac{q}{C}$$

or


$$V = \frac{q}{C}$$

change on the capacitor \Rightarrow



capacitance

ATDB.uno


$$q = CV$$

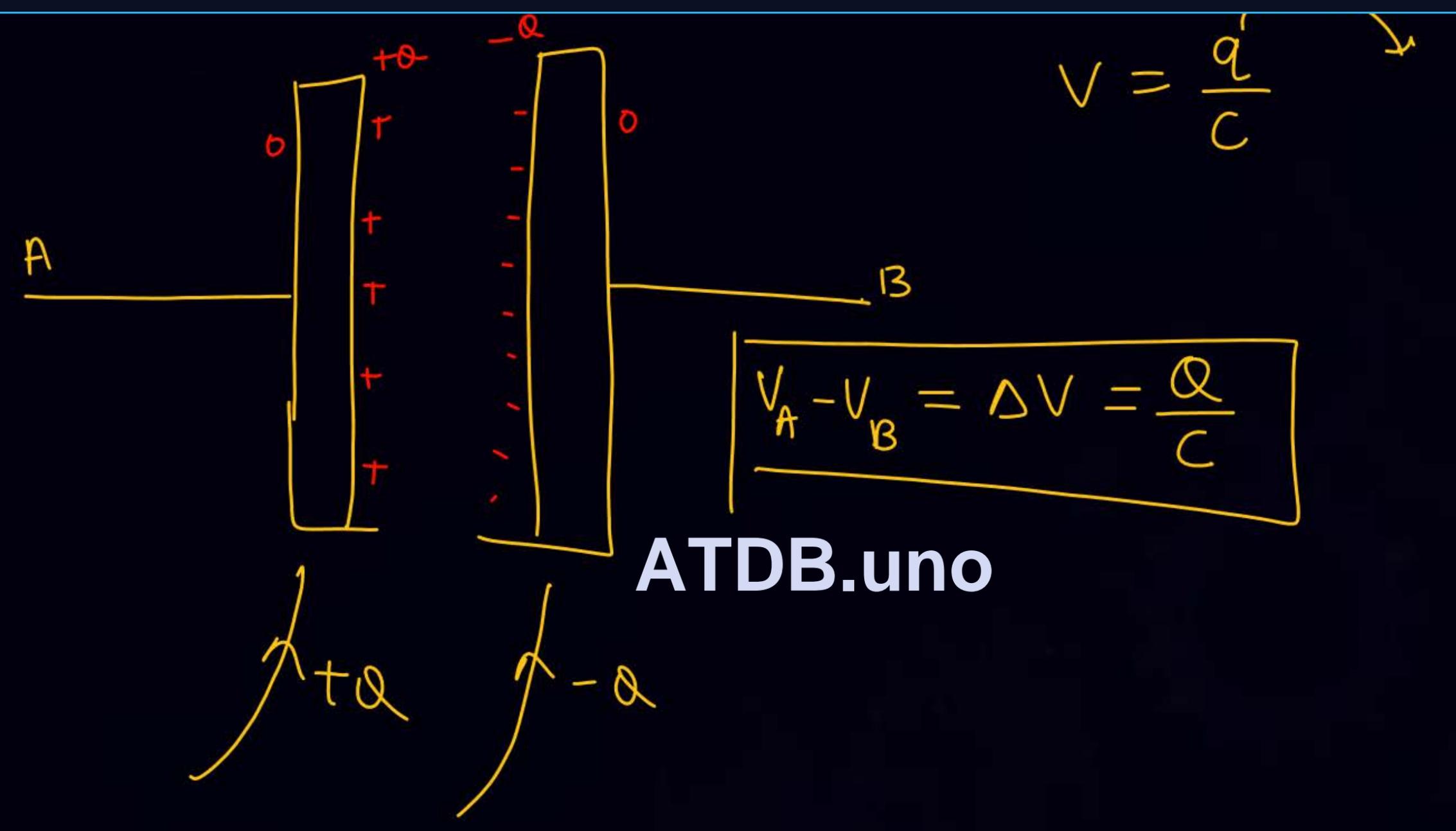


ATDB.uno

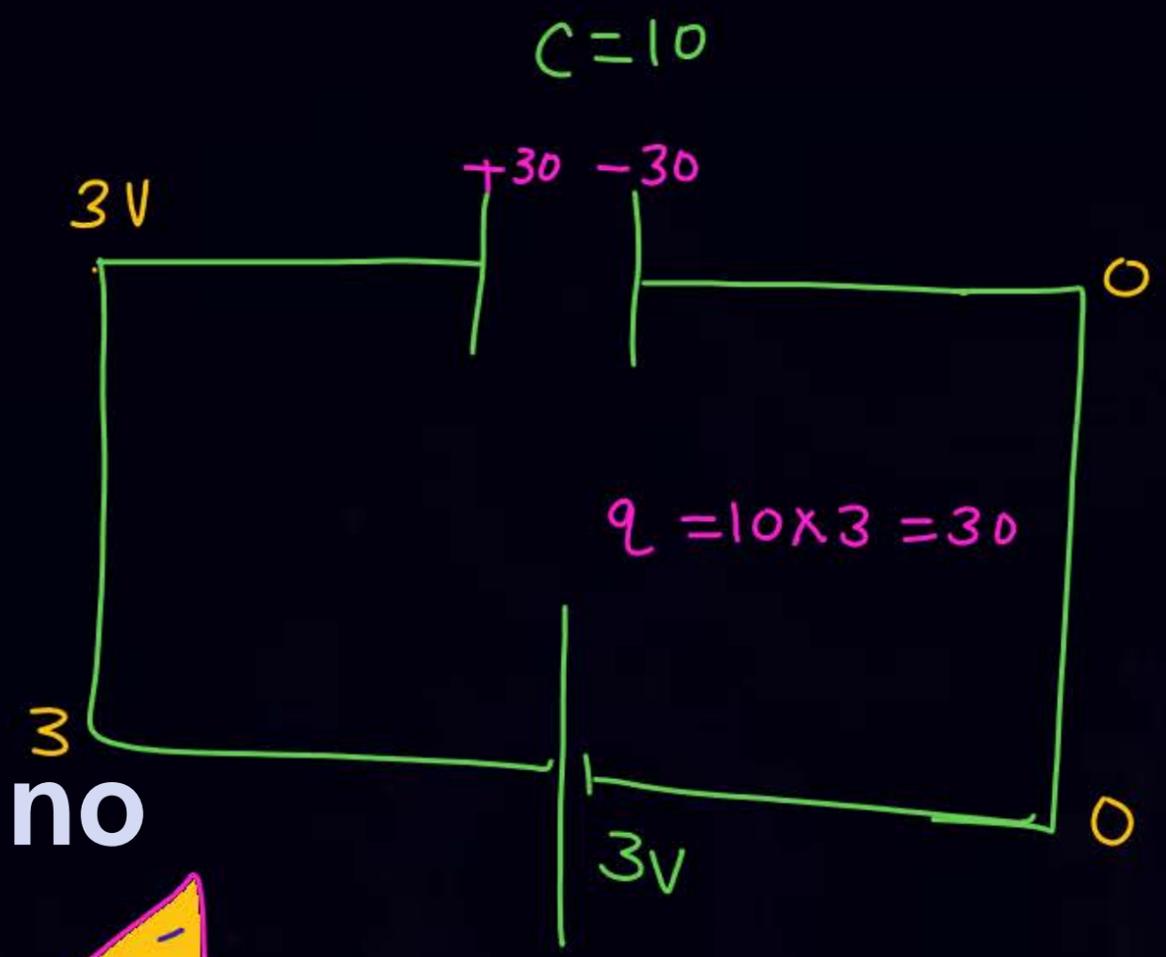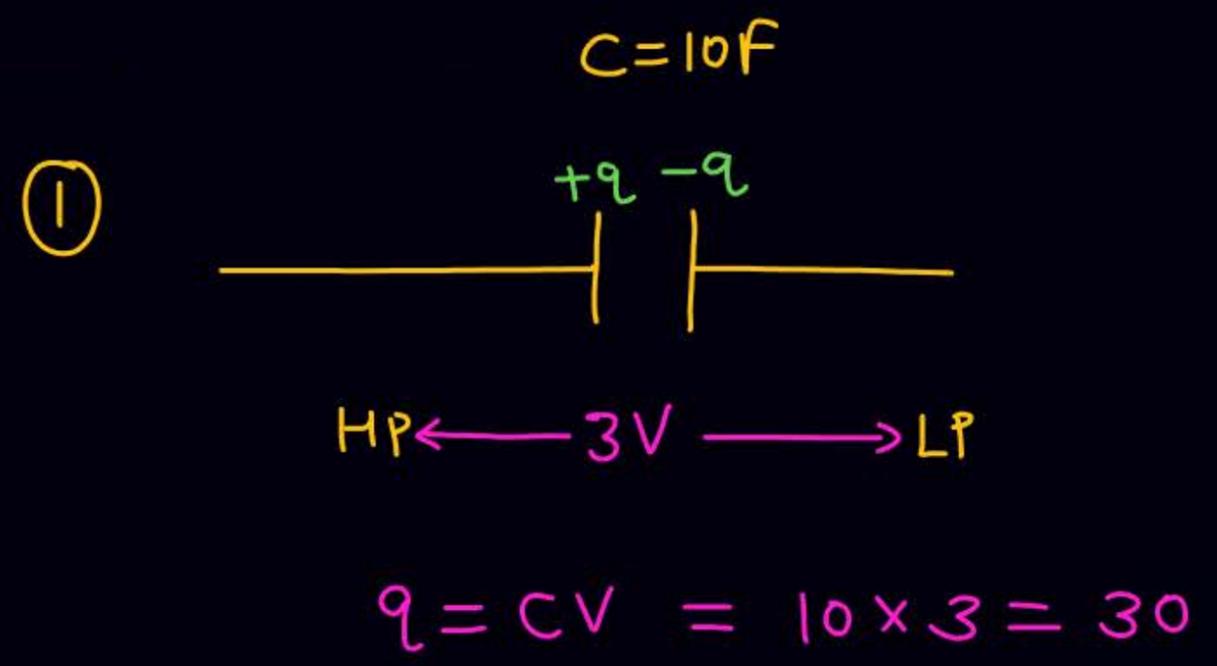


ATDB.uno

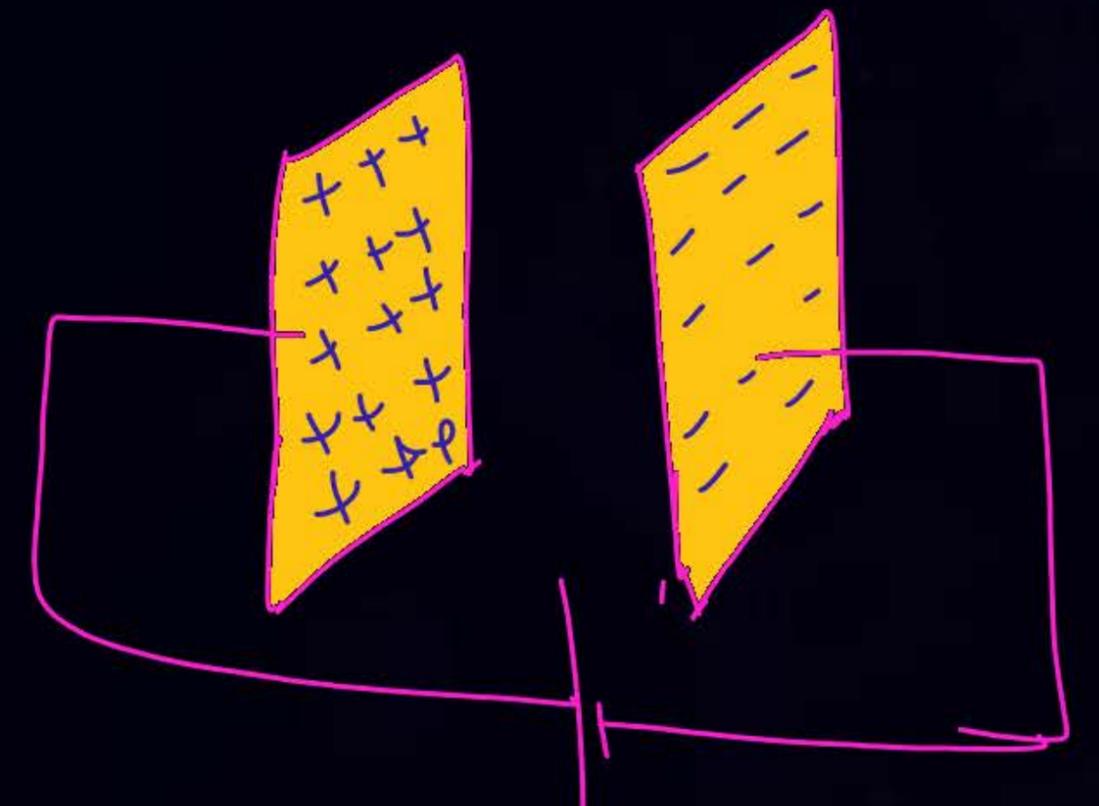

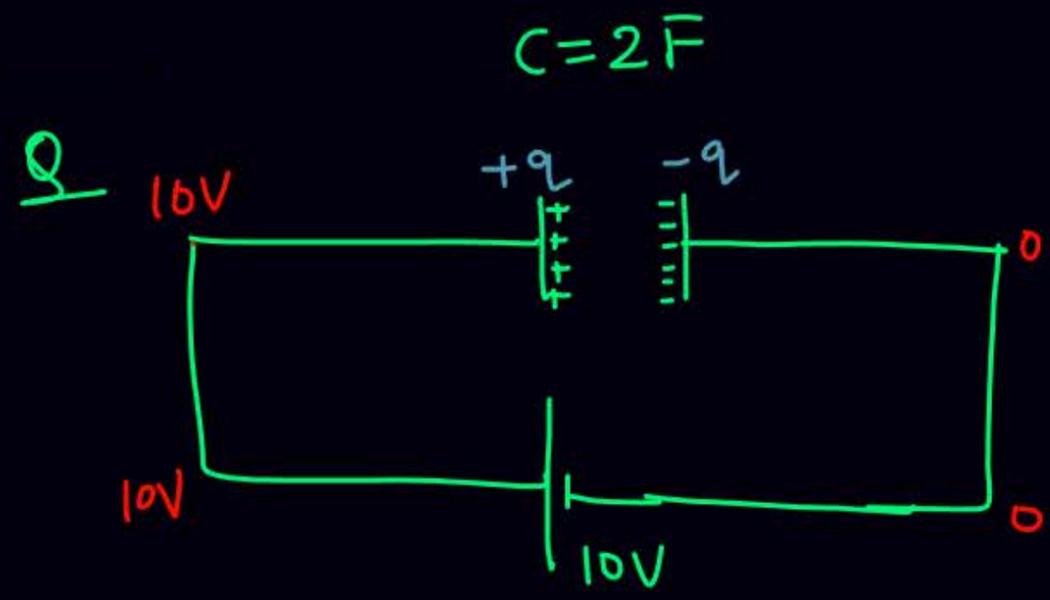

$q = CV$


$q = 2 \times 10 = 20$

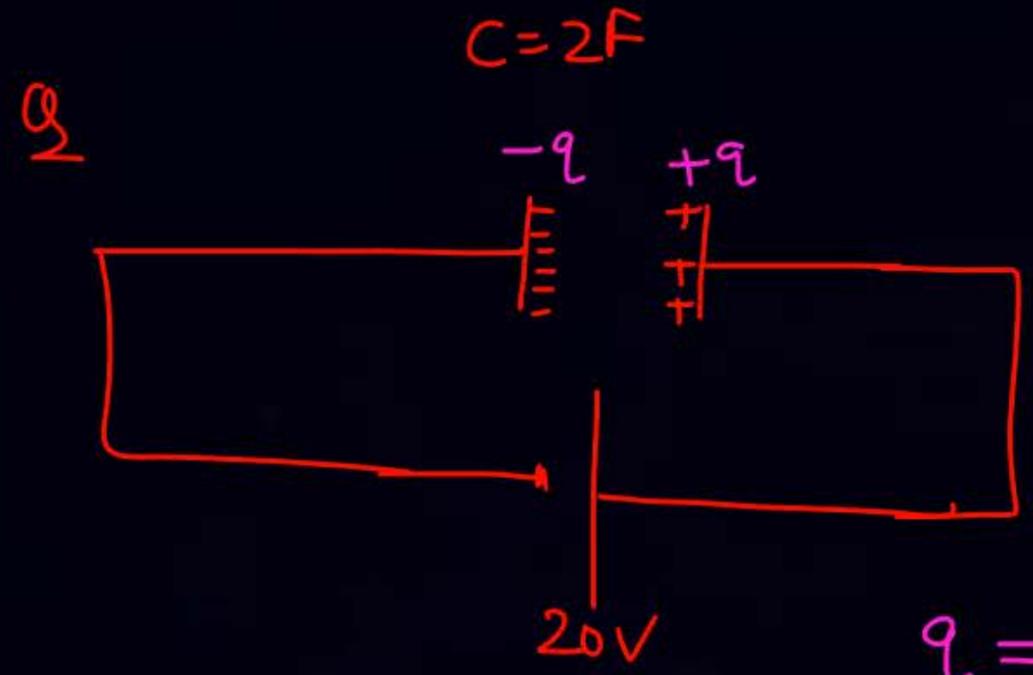


$q = 2 \times 20$

$q = 40$

ATDB.uno

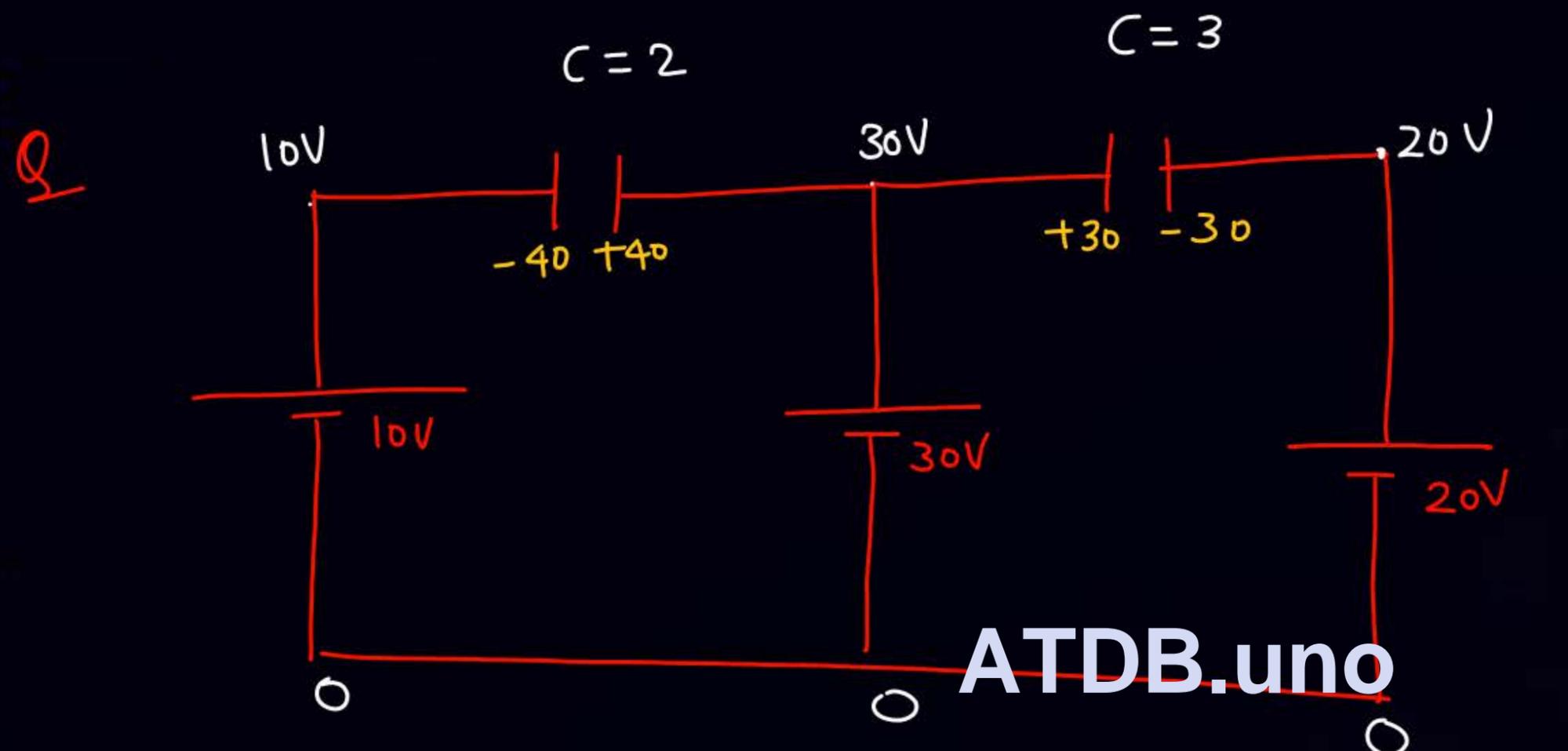


$$Q = CV$$

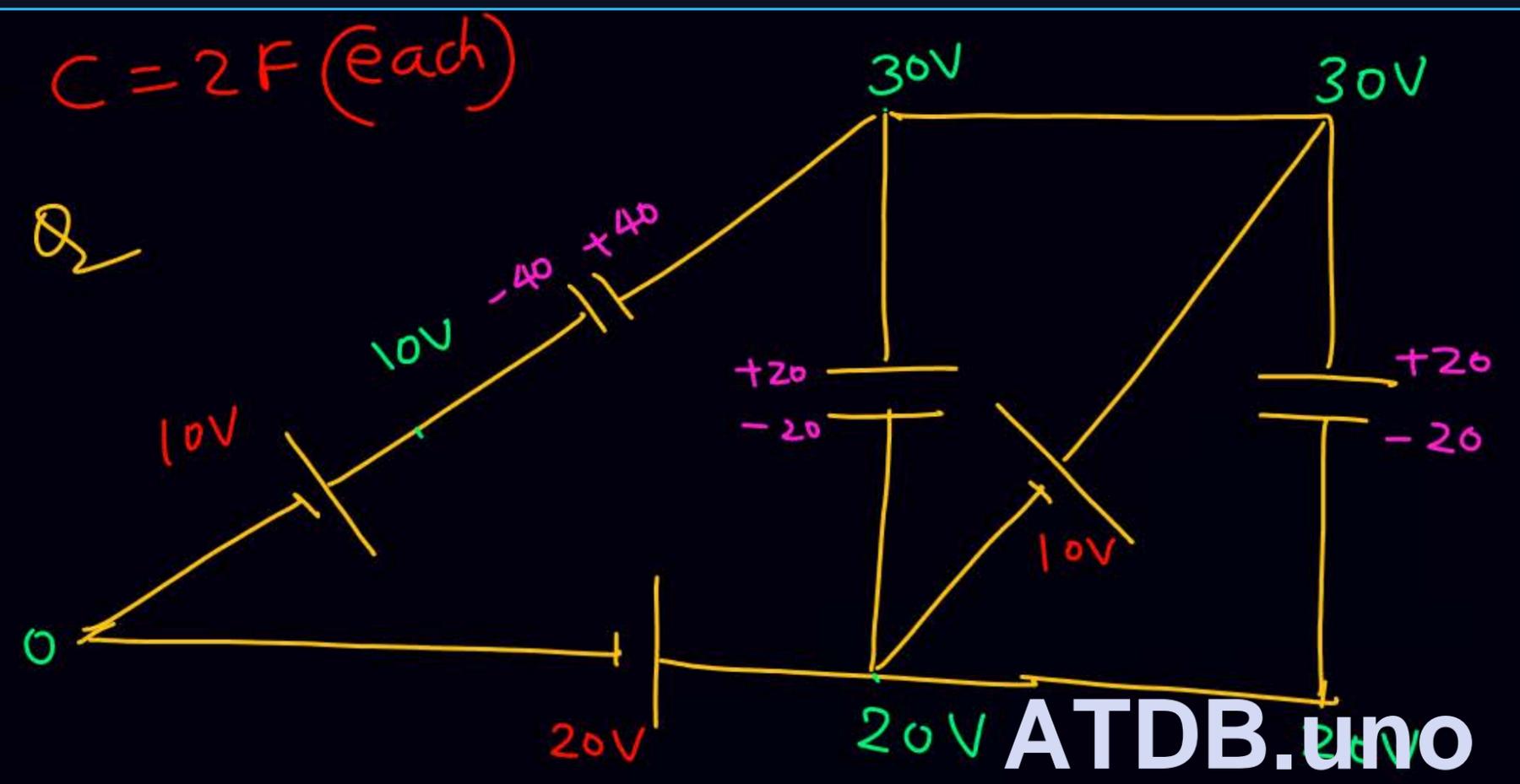



Q


$C = 2F$ (each)

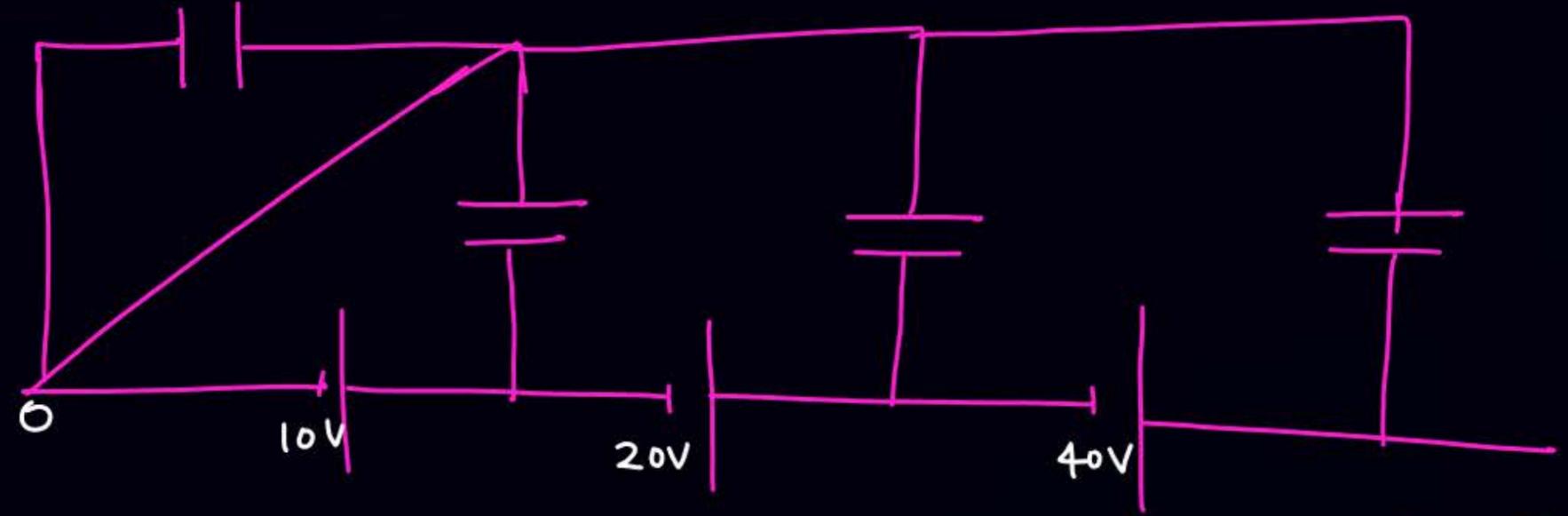


$$q = CV$$

ATDB.uno



वैचार

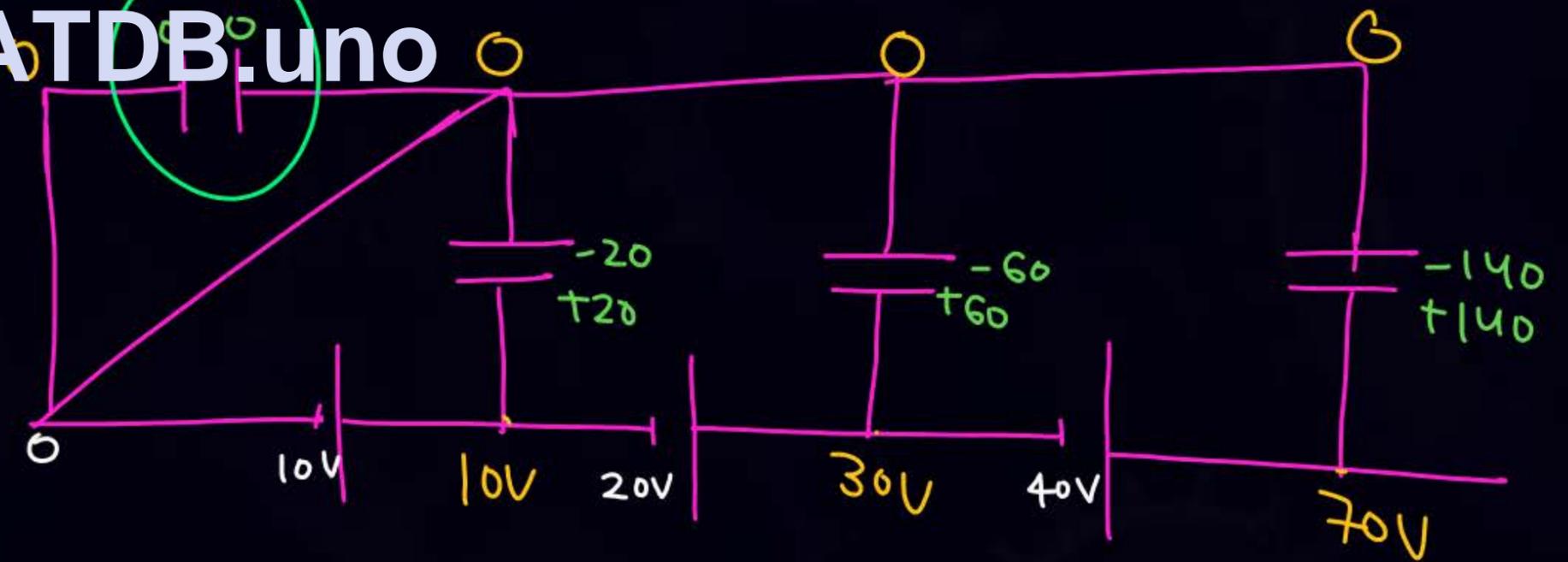


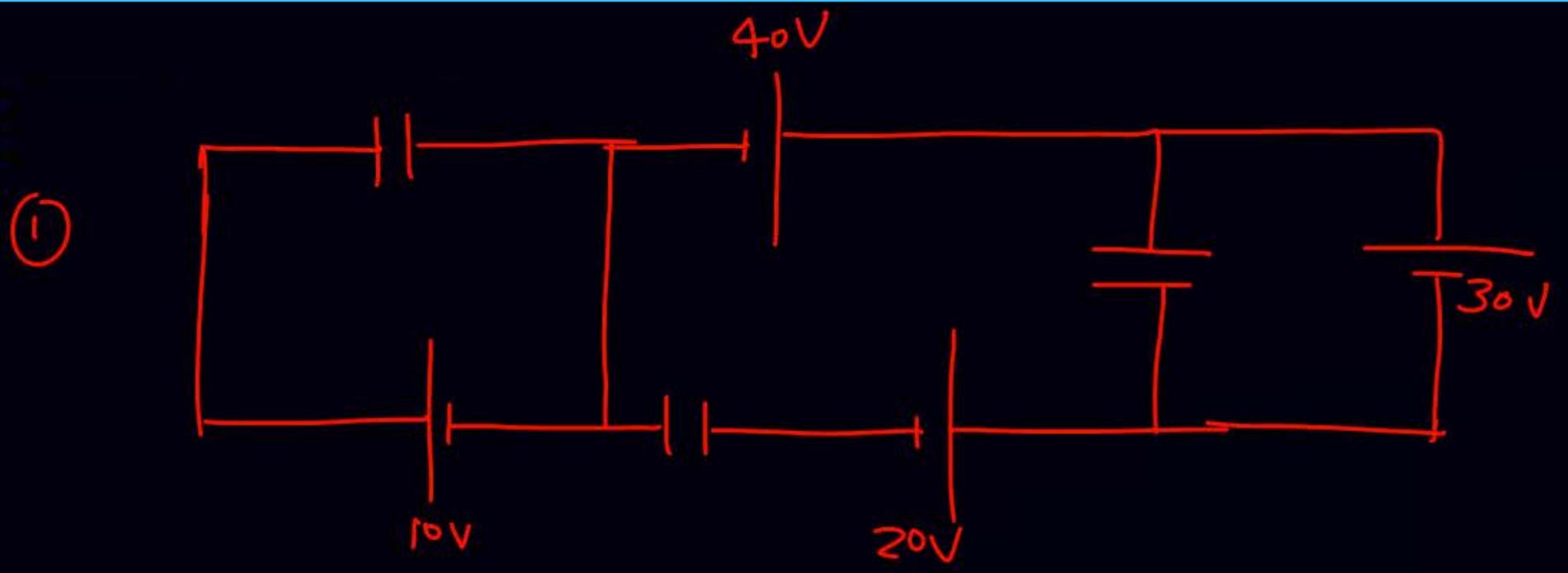

$C = 2.F(\text{each})$



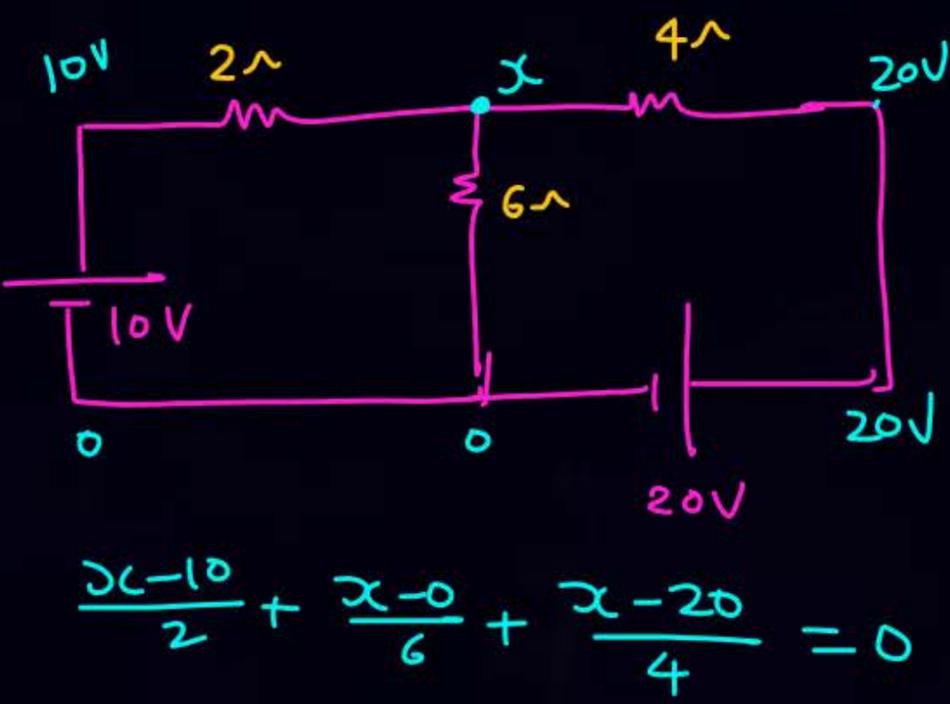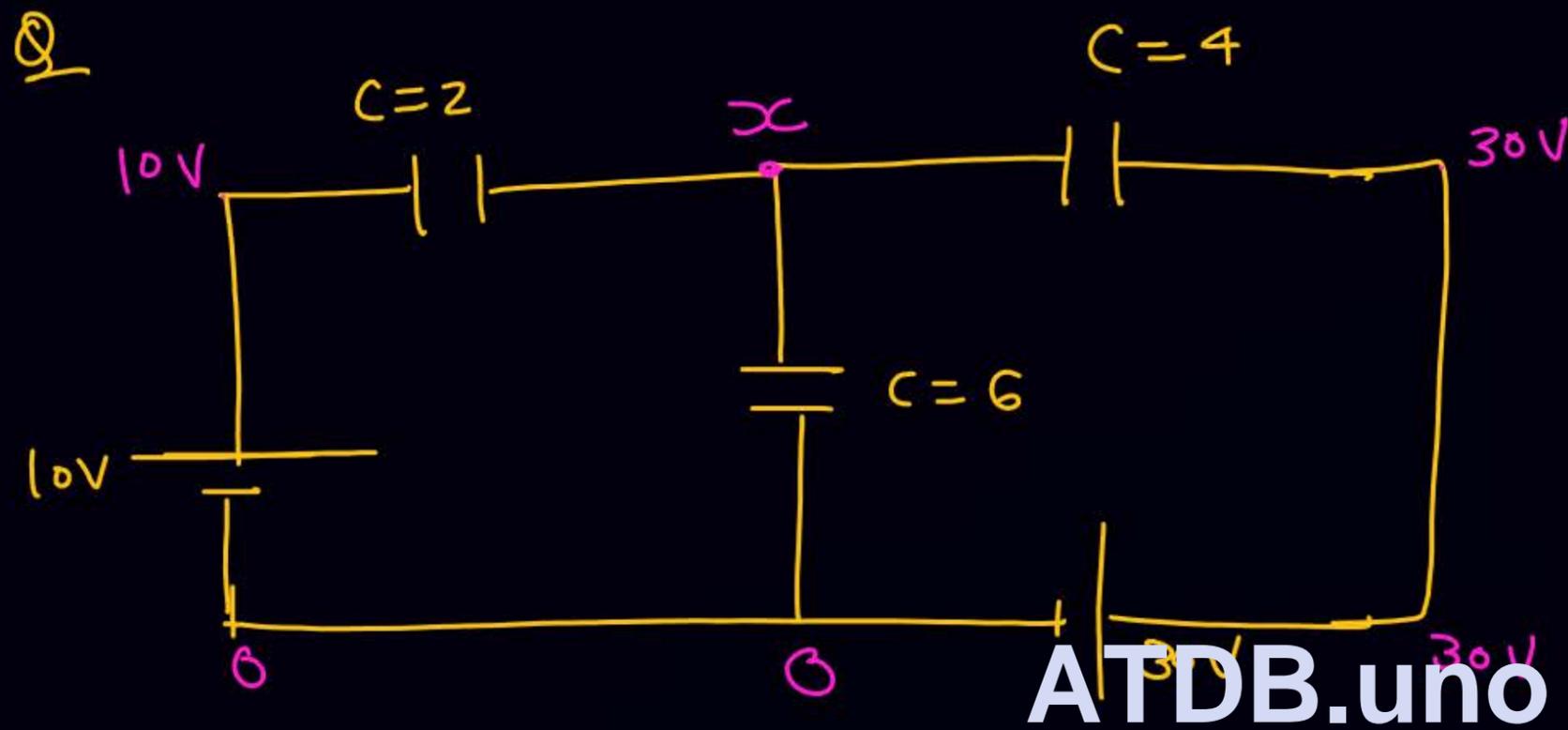

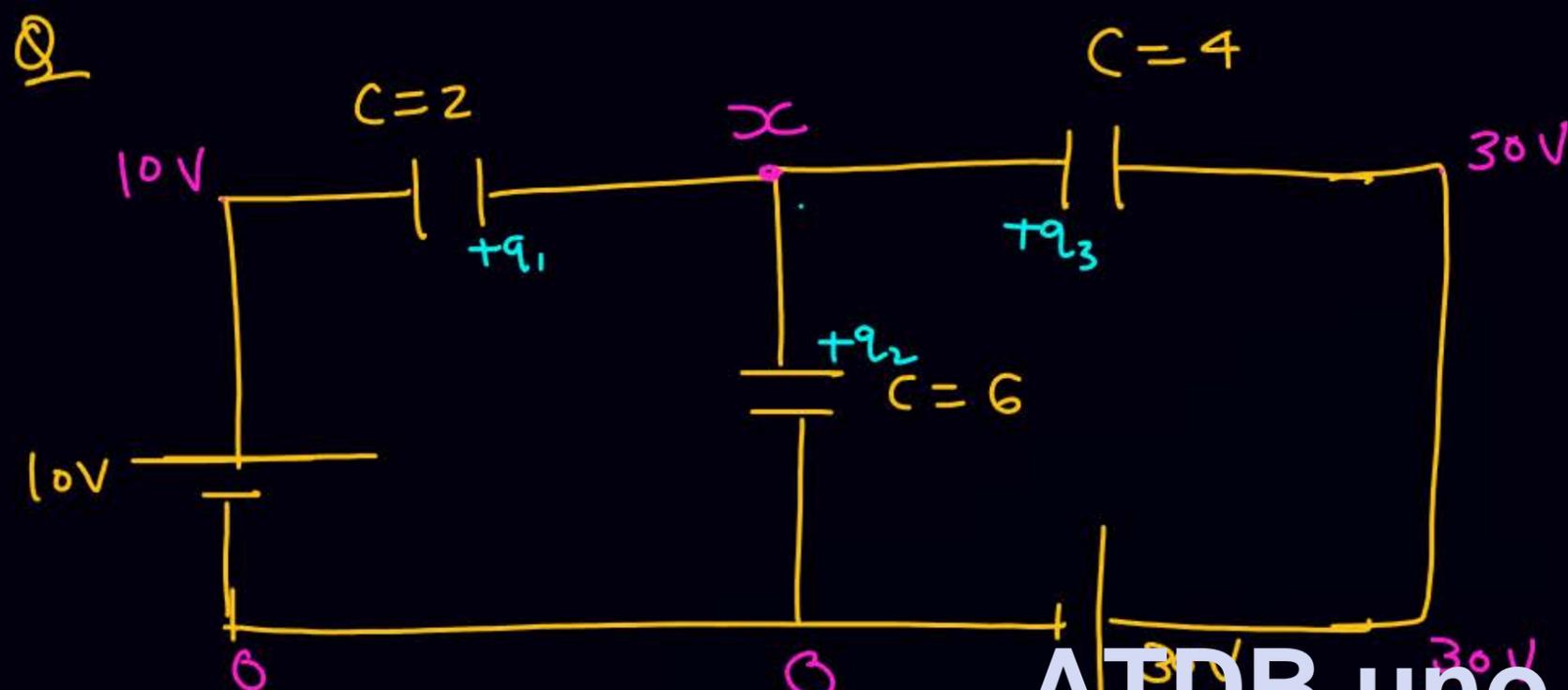

ATDB.uno


$$q_1 + q_2 + q_3 = 0$$

$$2(x-10) + 6(x-0) + 4(x-30) = 0$$


$$2x - 20 + 6x + 4x - 120 = 0$$

$$12x = 140$$

$$x = \checkmark$$

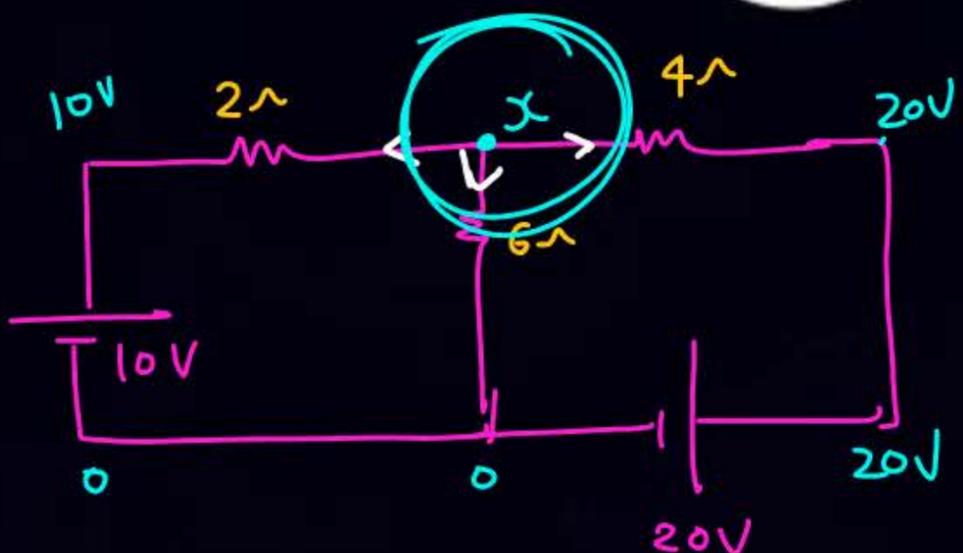

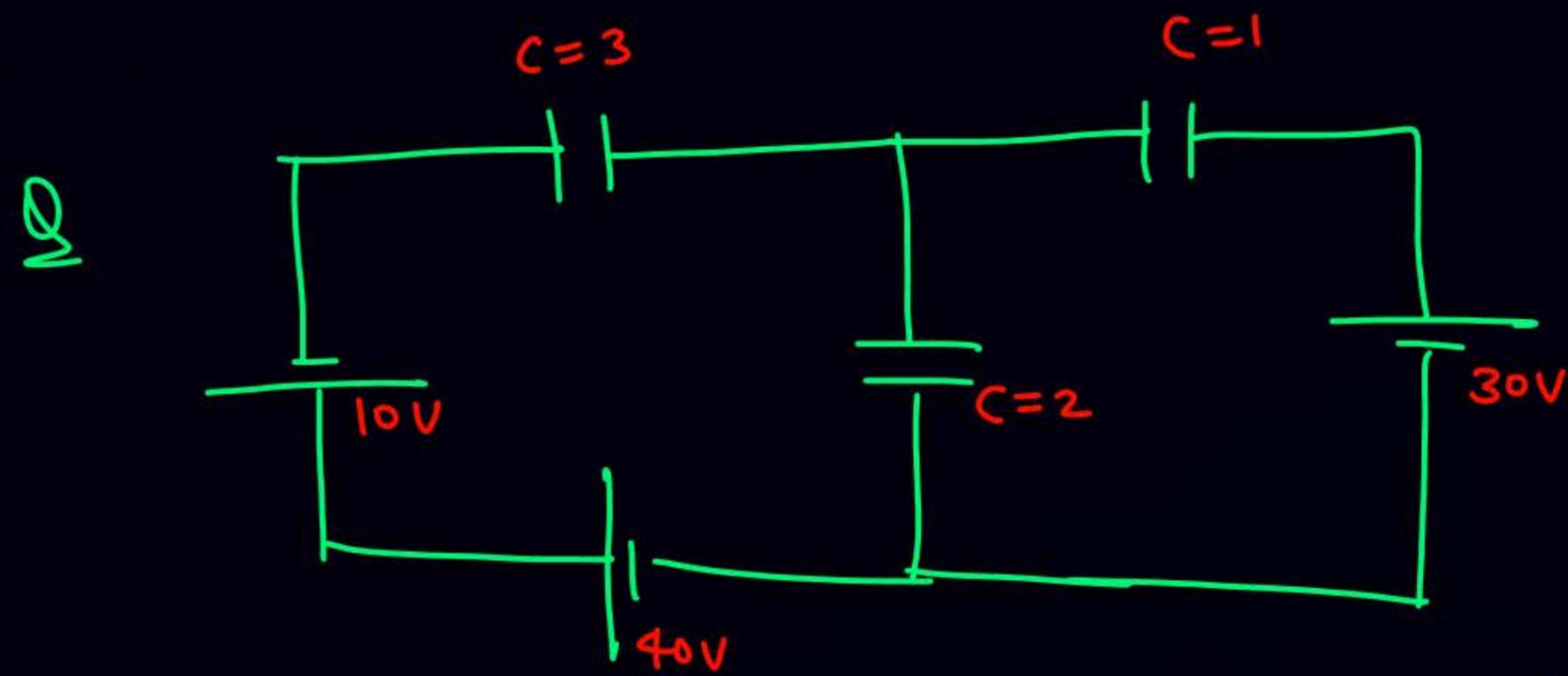
$$\frac{x-10}{2} + \frac{x-0}{6} + \frac{x-20}{4} = 0$$




$$3(x-30) + 2(x-0) + 1x(x-30) = 0$$


$$6x = 120 \quad \boxed{x = 20V}$$


ATDB.uno

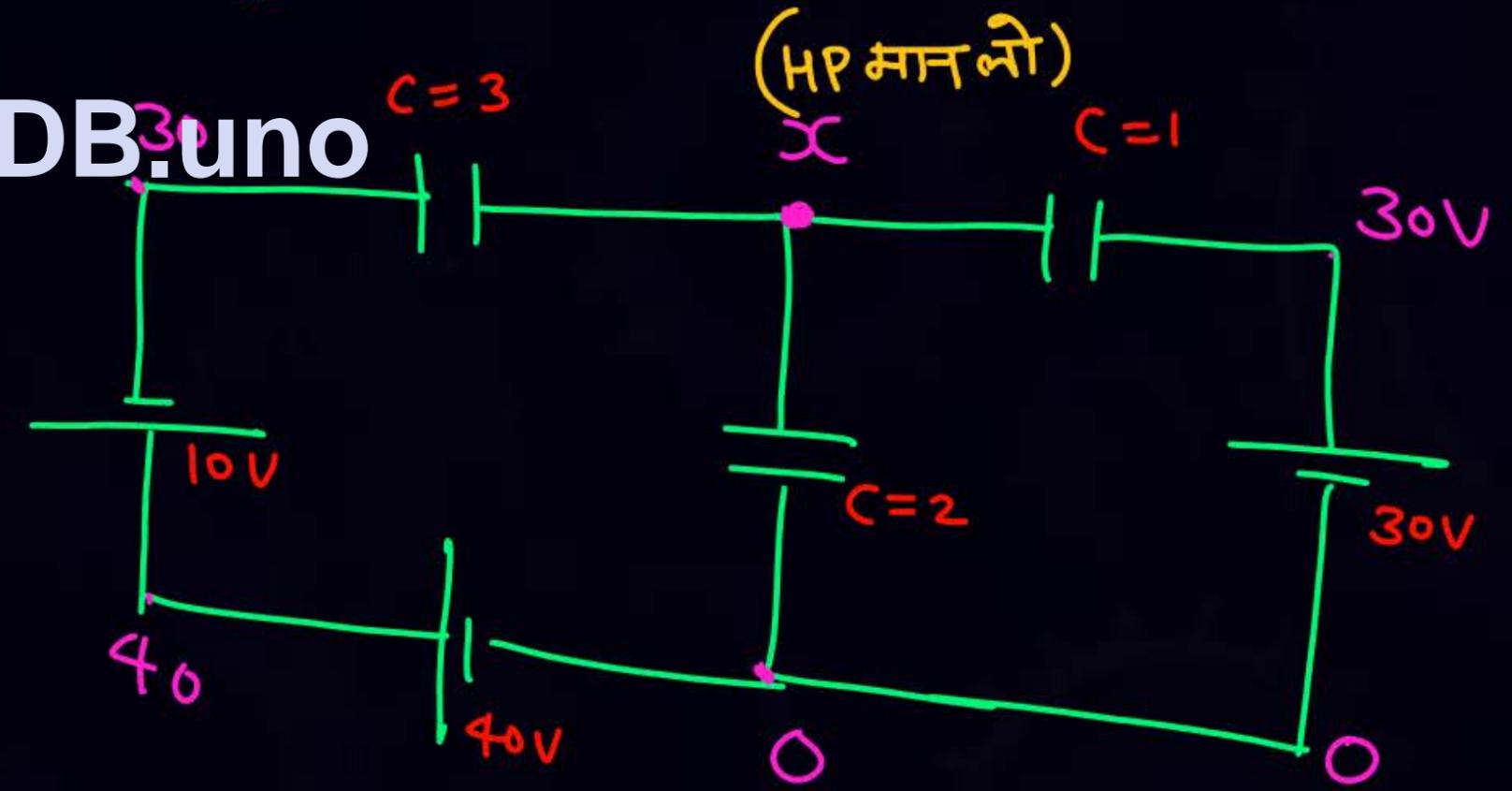

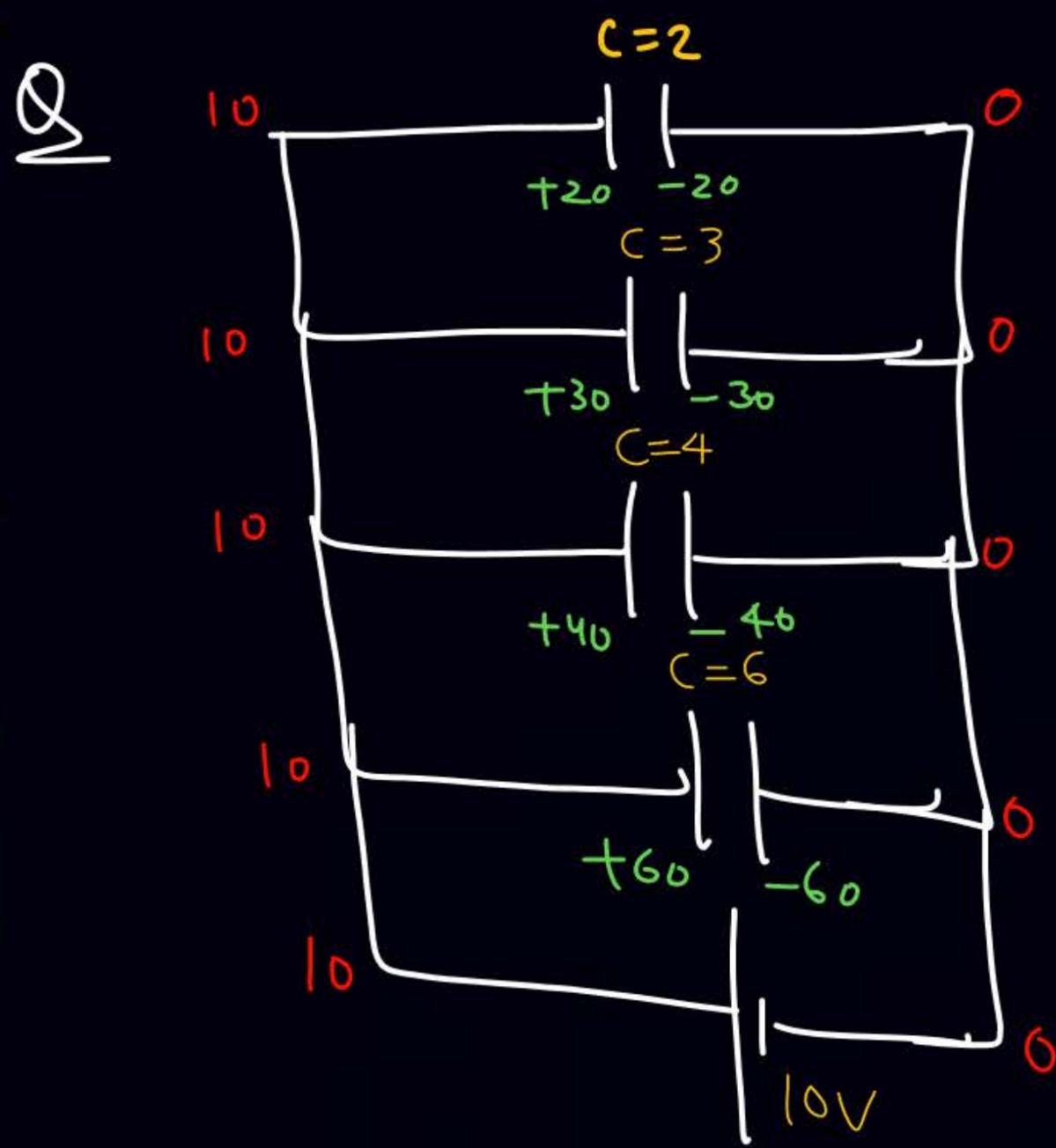

ATDB.uno

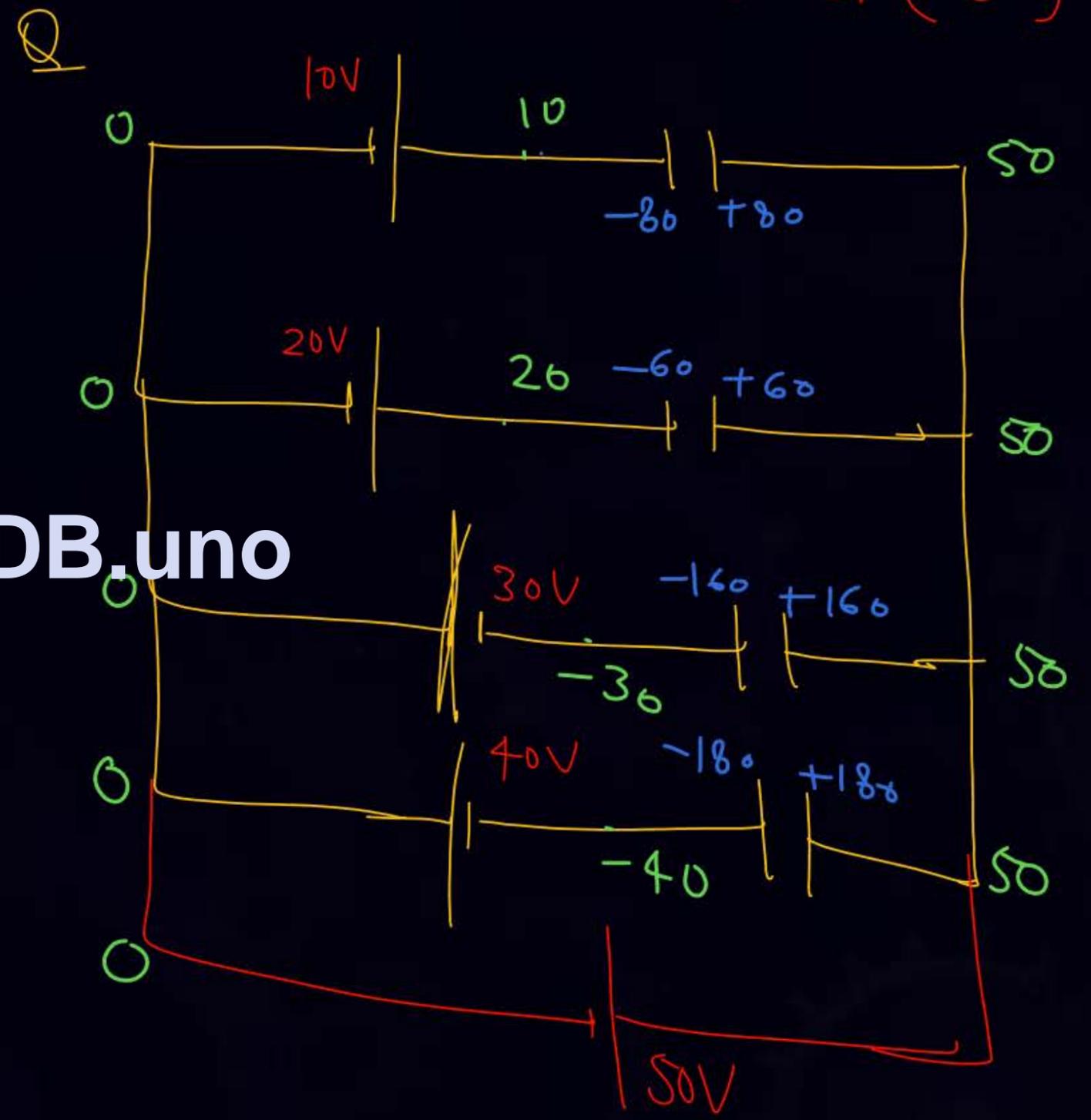

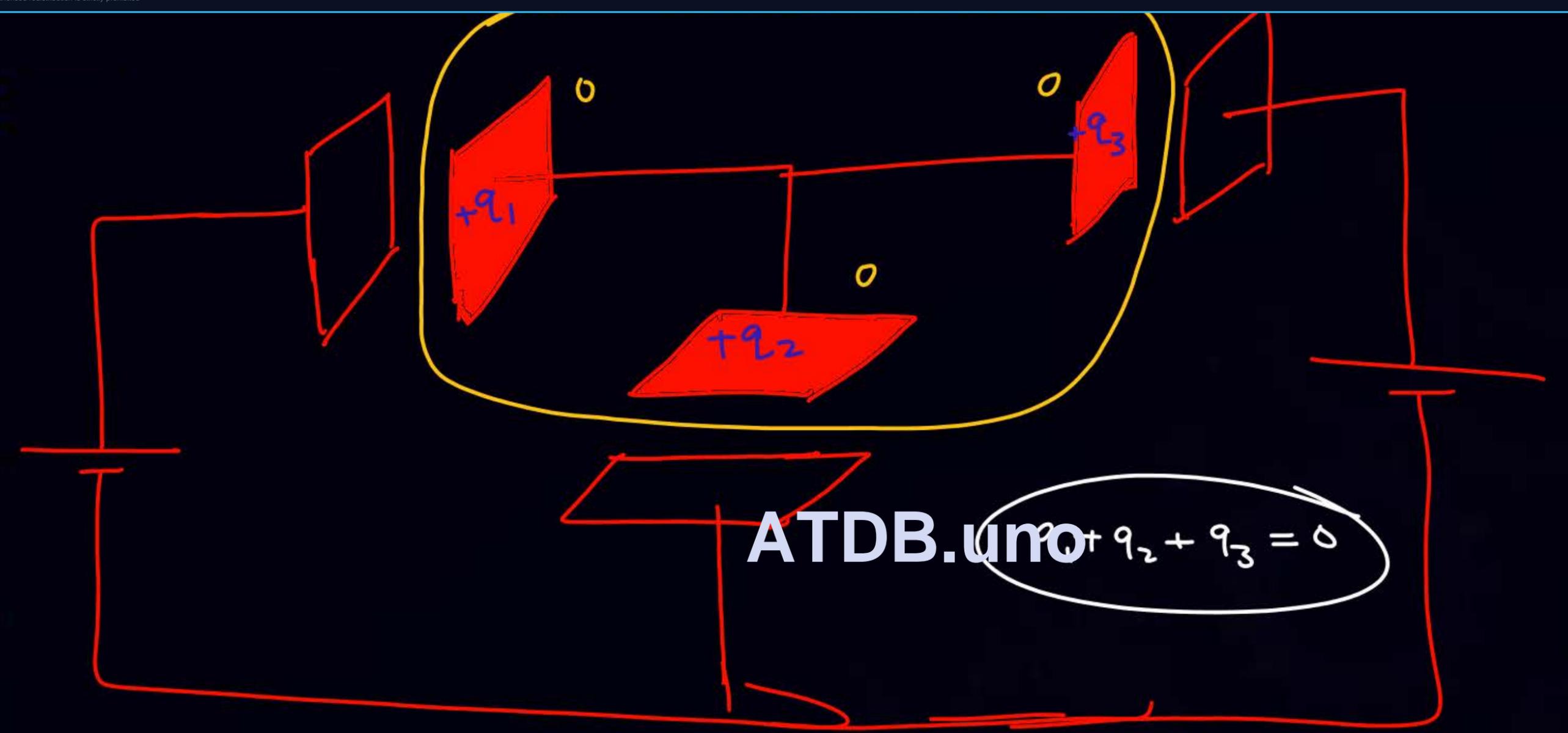

ATDB.uno $q_1 + q_2 + q_3 = 0$




Home Work Ques

(will upload vedio today)

ATDB.uno




①

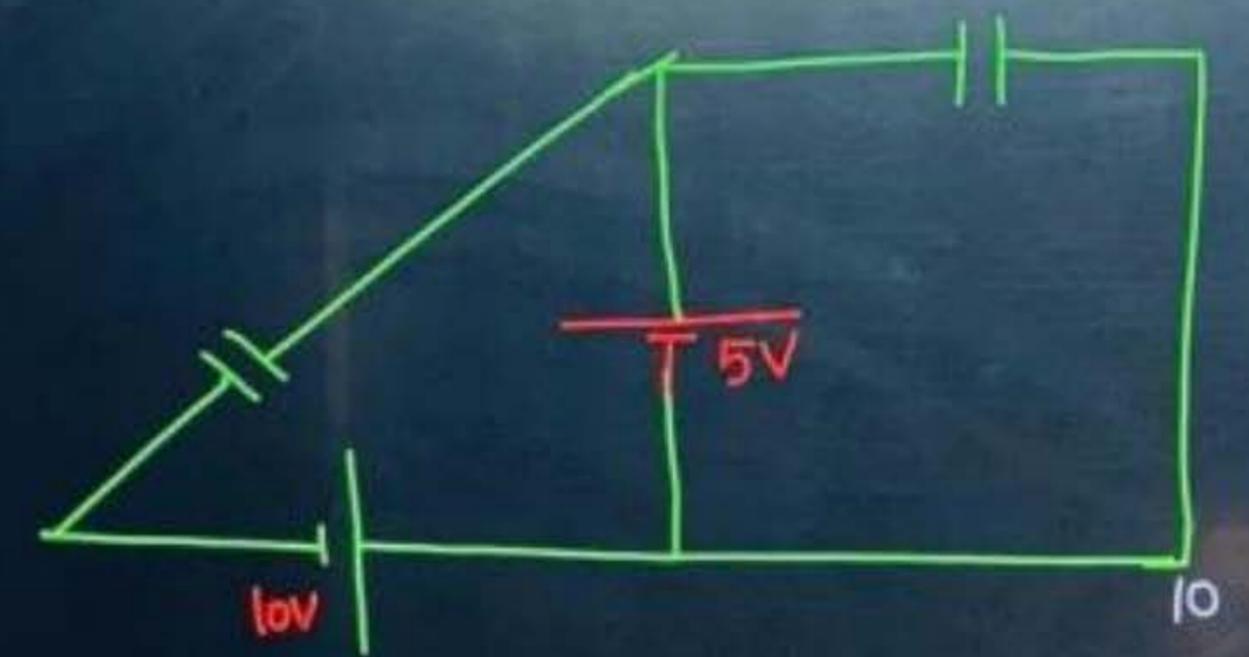

$C = 2F$ (each)

ATDB.uno

②

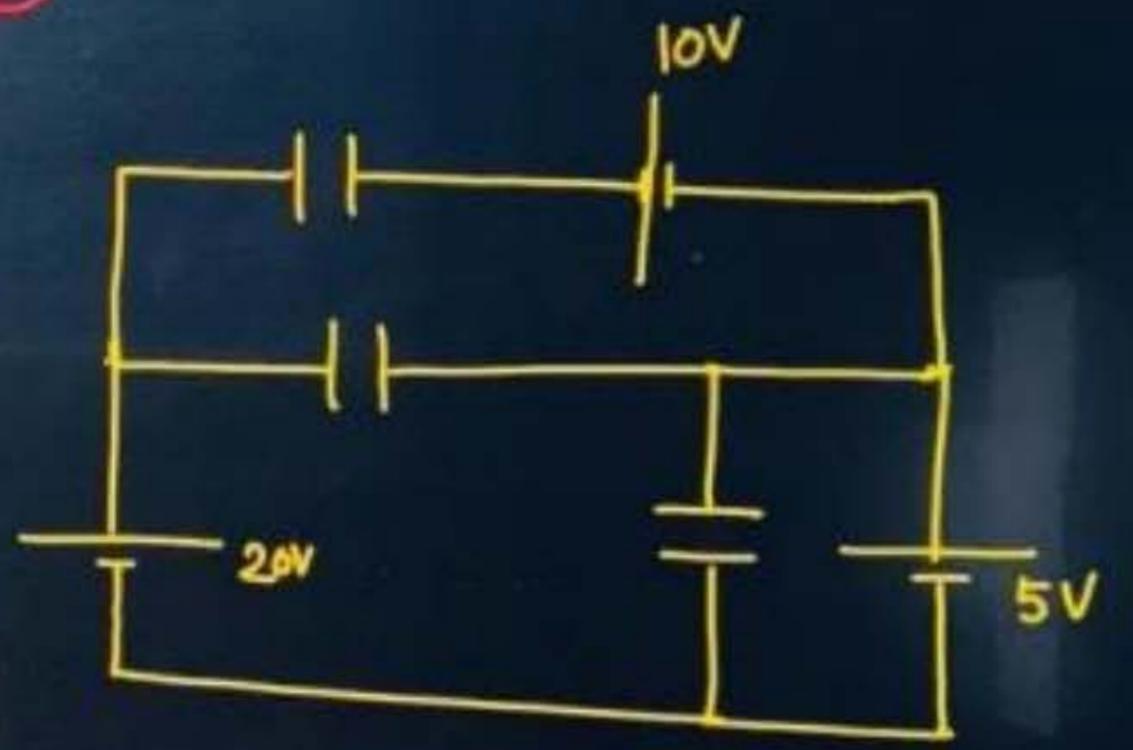


$C = 2F$ (each)

02.pdf



3

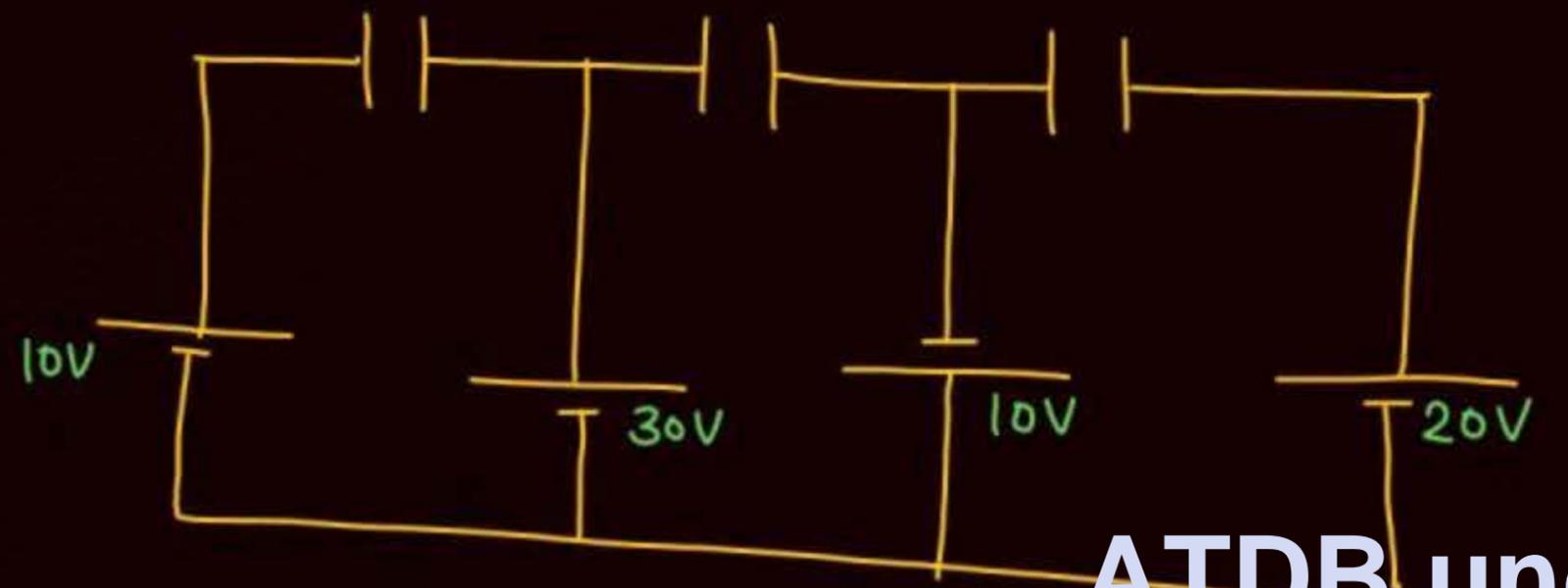




ATDB.uno

4

Q

$C = 2F$ (each)

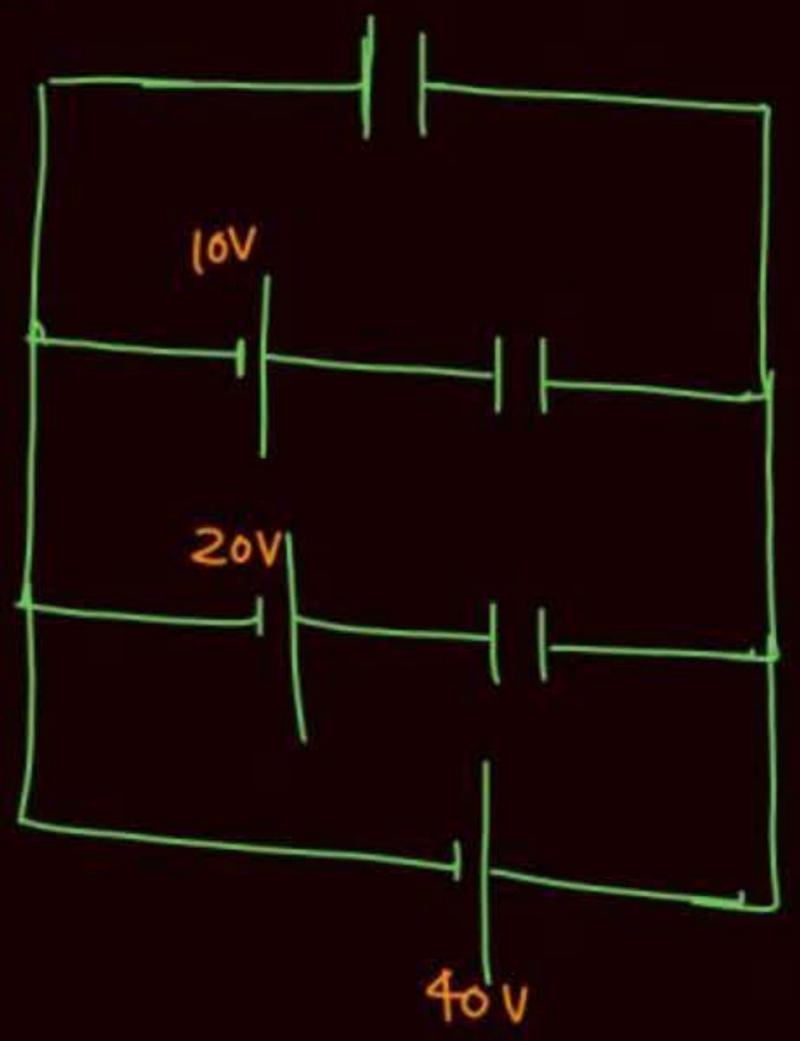

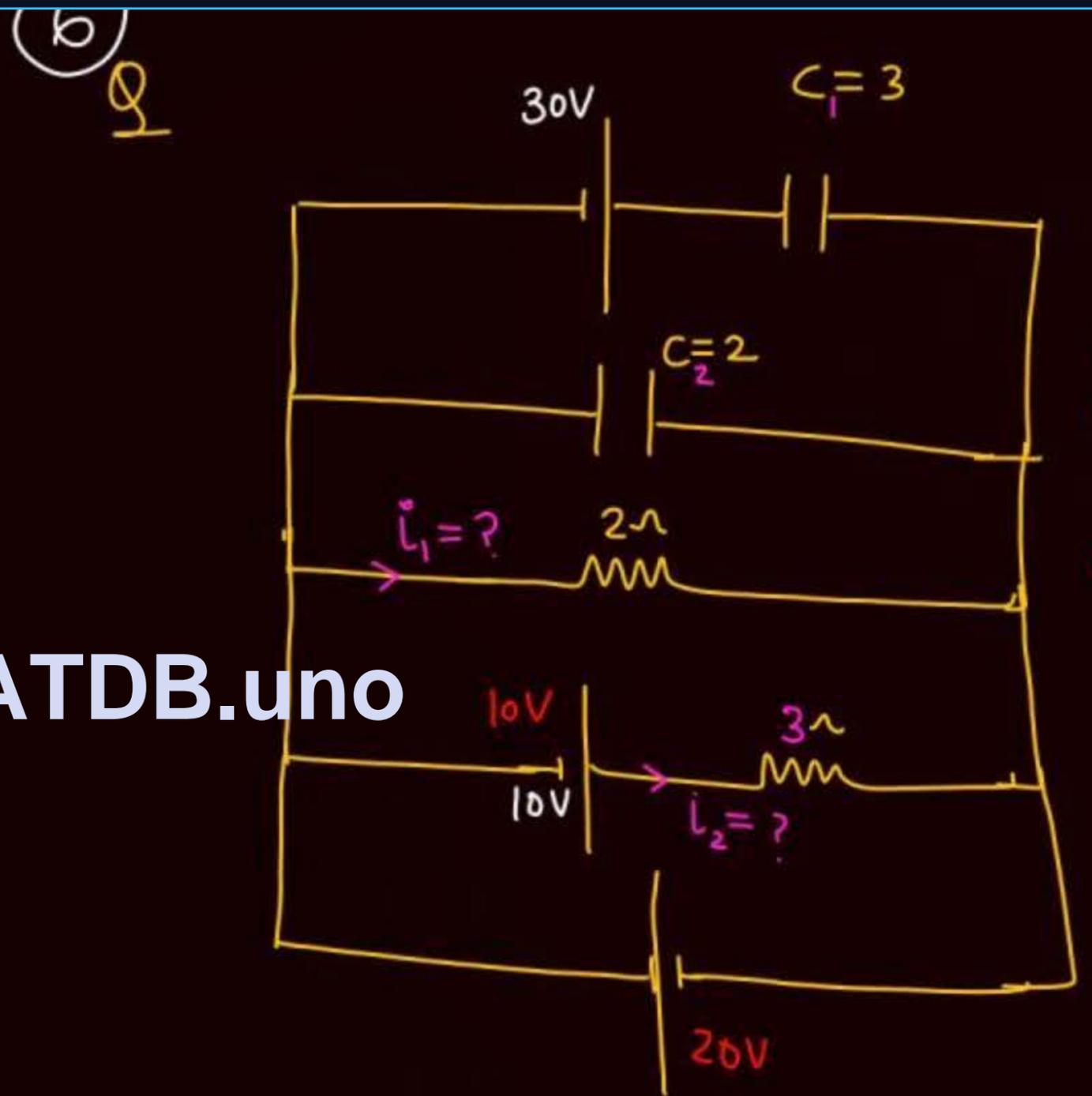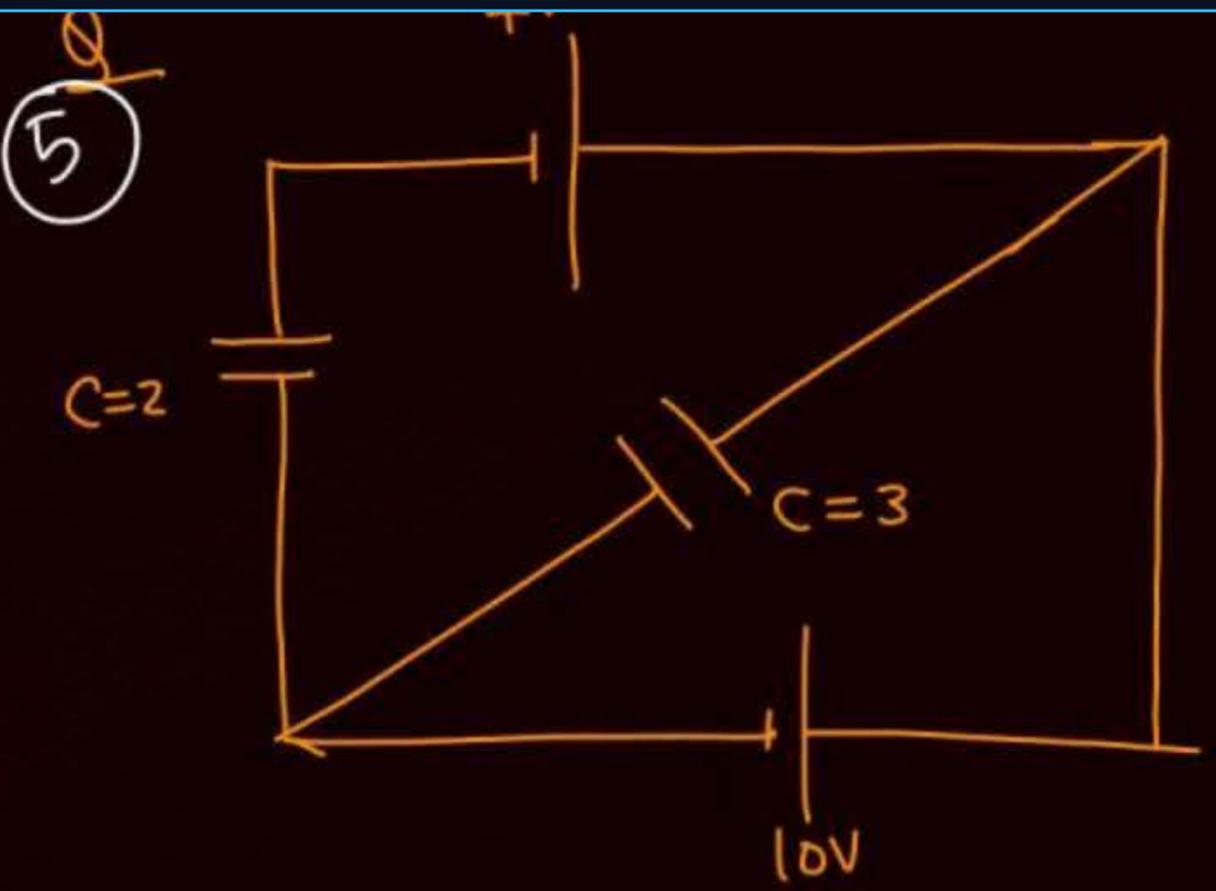


Find charge on capacitor C_1 & C_2 and current through 2Ω and 3Ω

ATDB.uno




7

Q

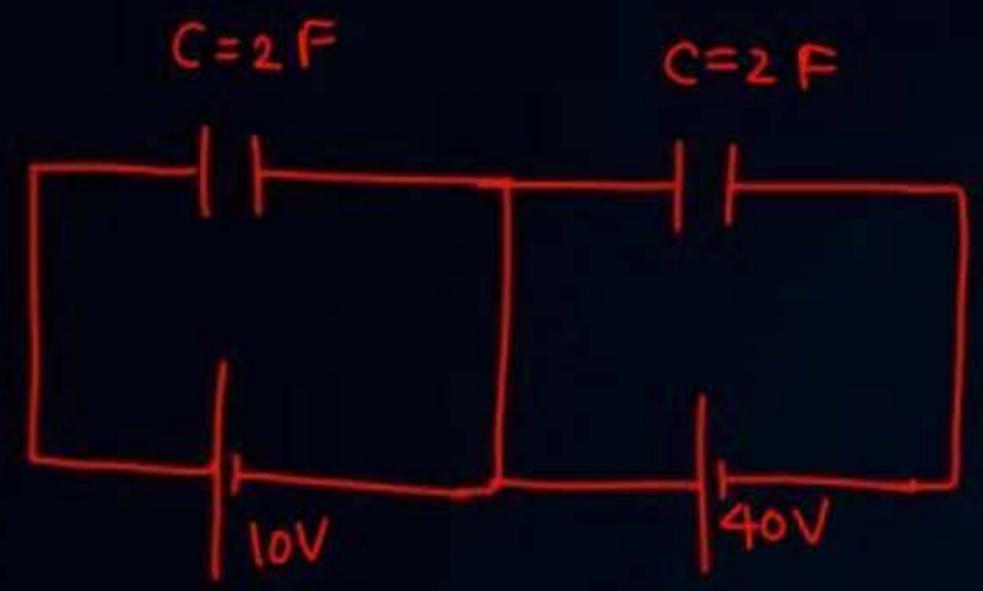

8

Q

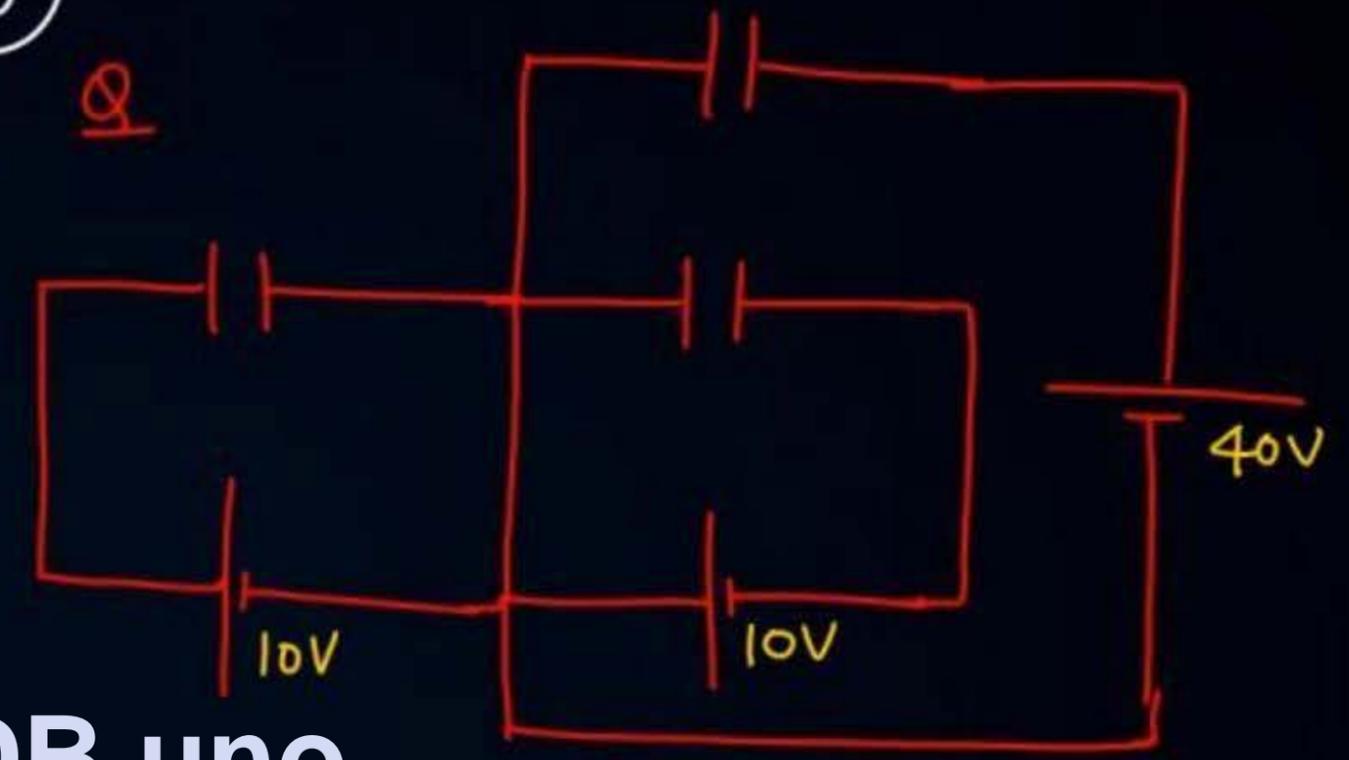


ATDB.uno

$C=2F$ (each)




9

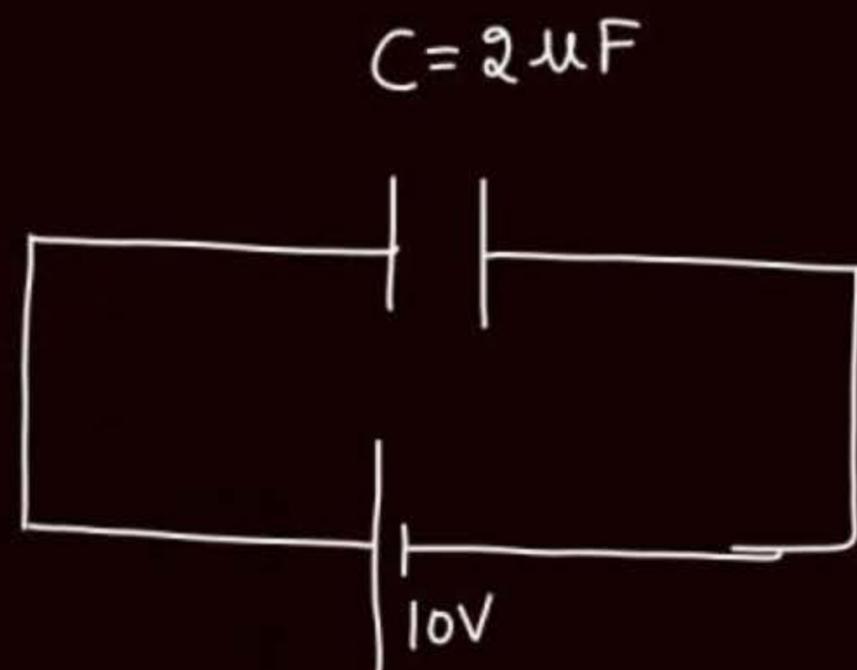

$$C = 2 \mu F = 2 \times 10^{-6} F$$


10

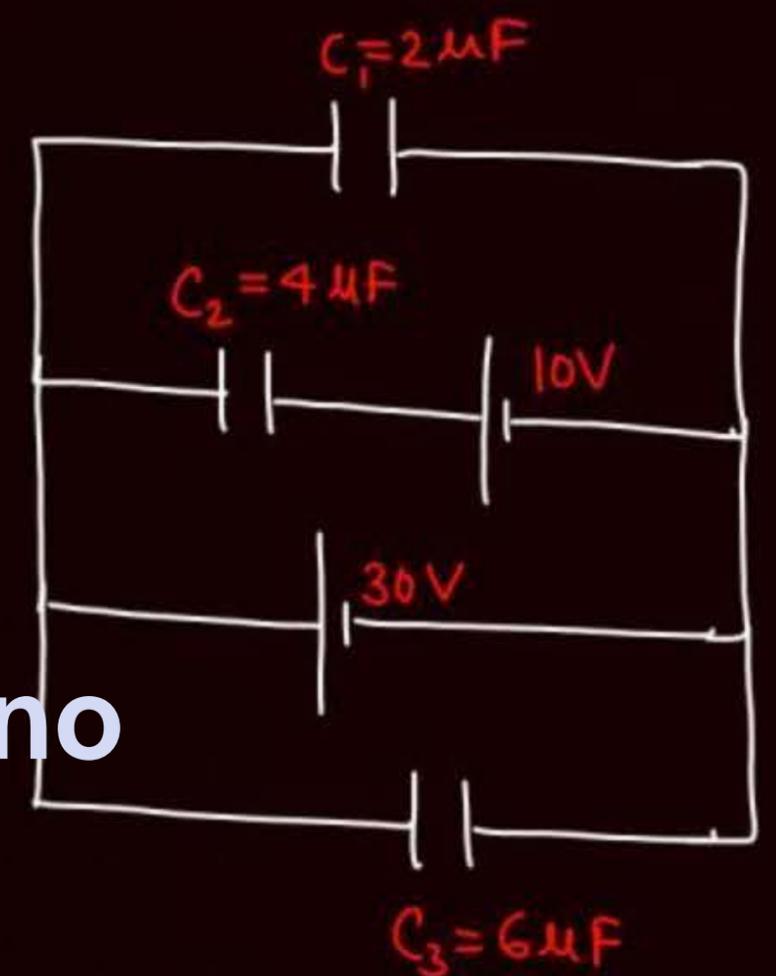

ATDB.uno




(12)

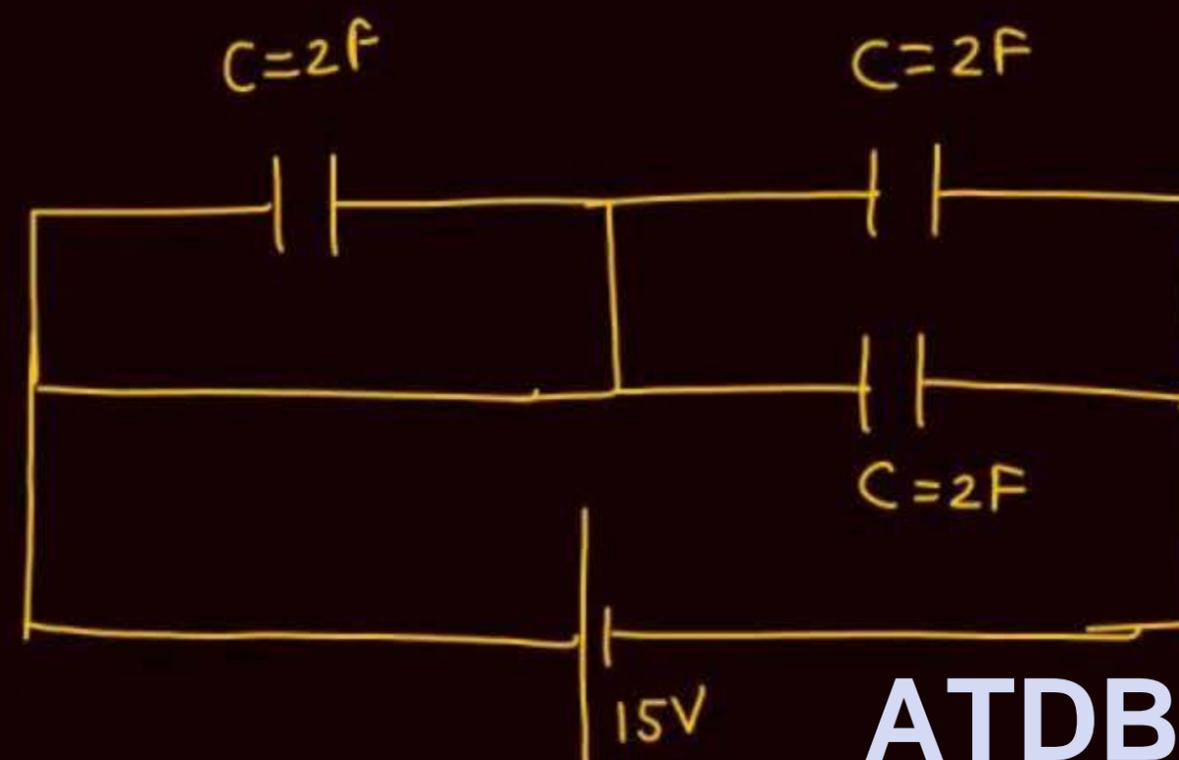

ATDB.uno


Q (13)

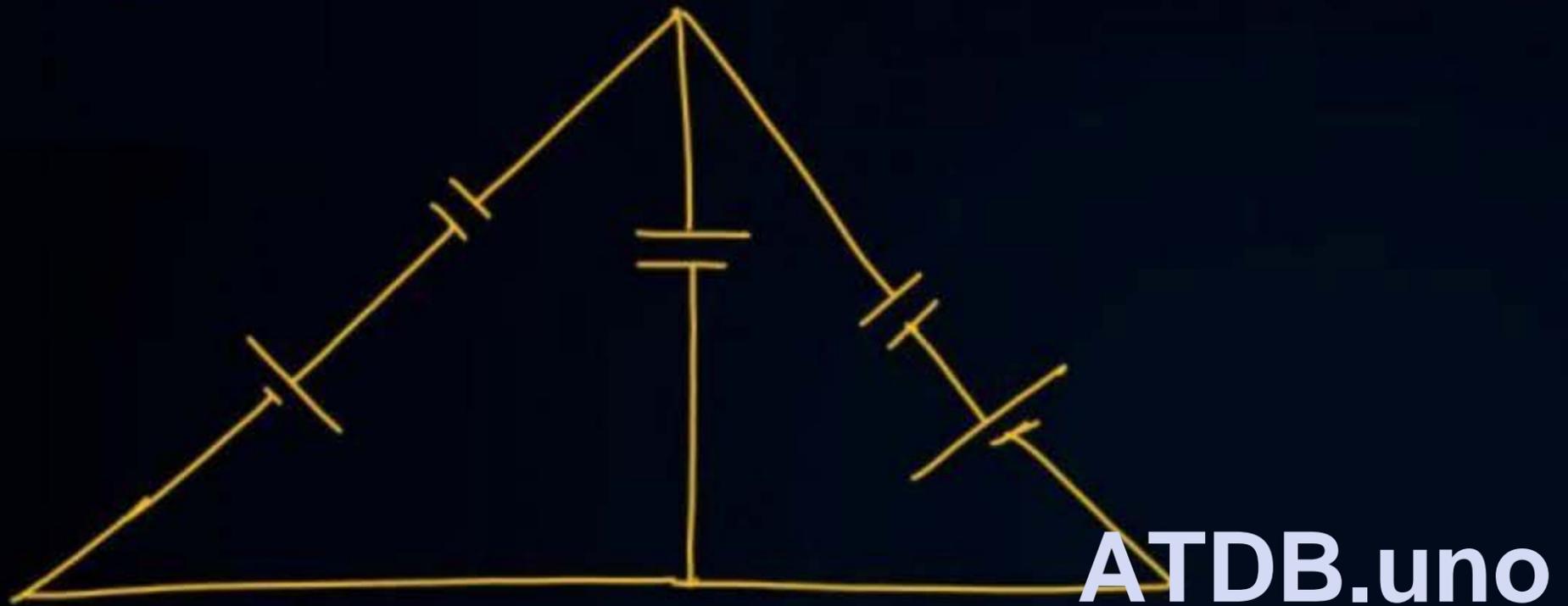




14

$C = 2F$ (each)

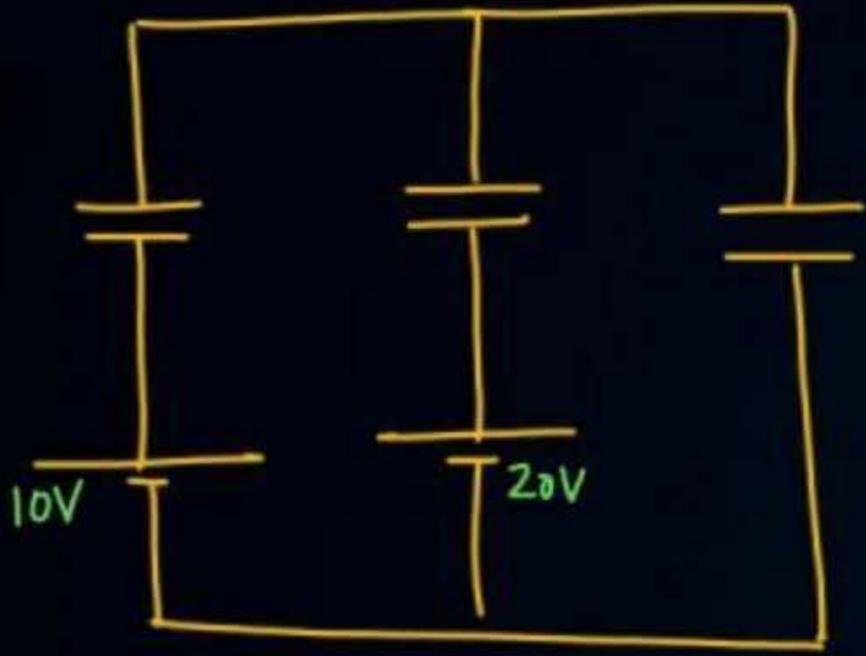

15


Q

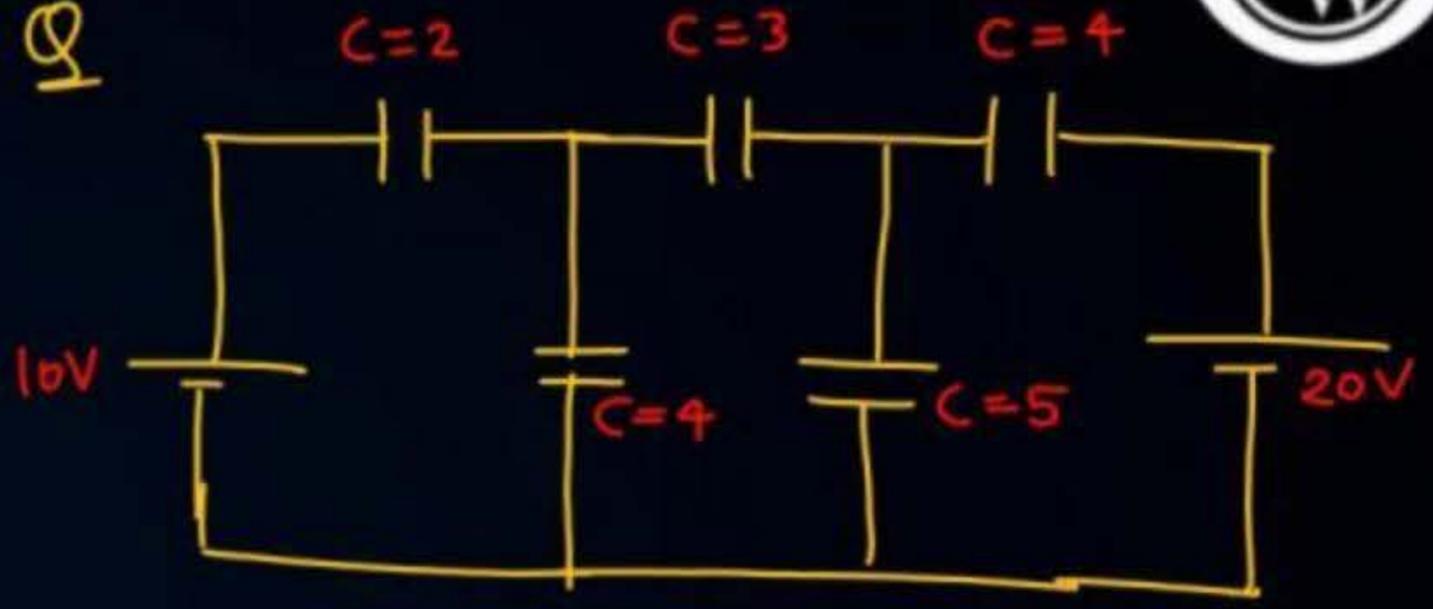

ATDB.uno



16

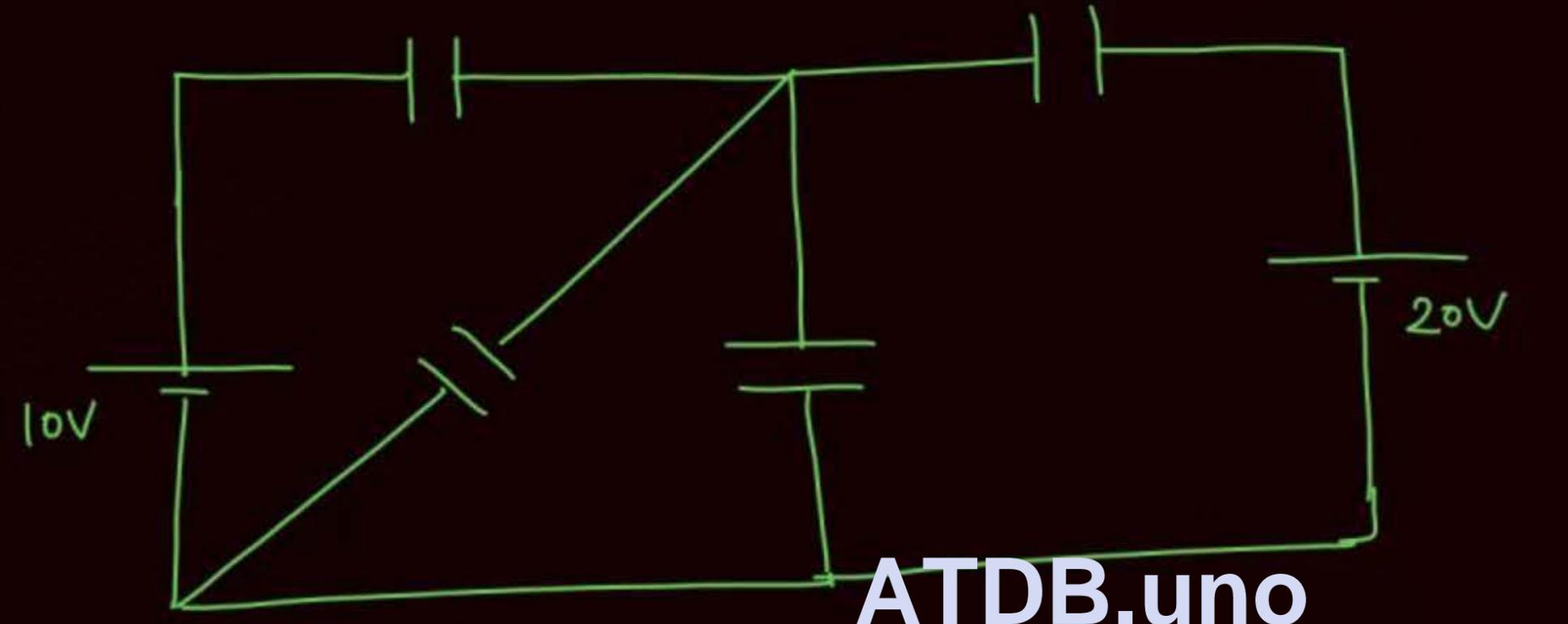


ATDB.uno

$C = 2 \mu F$ (each)




♥ $C = \frac{A\epsilon_0}{d}$

④

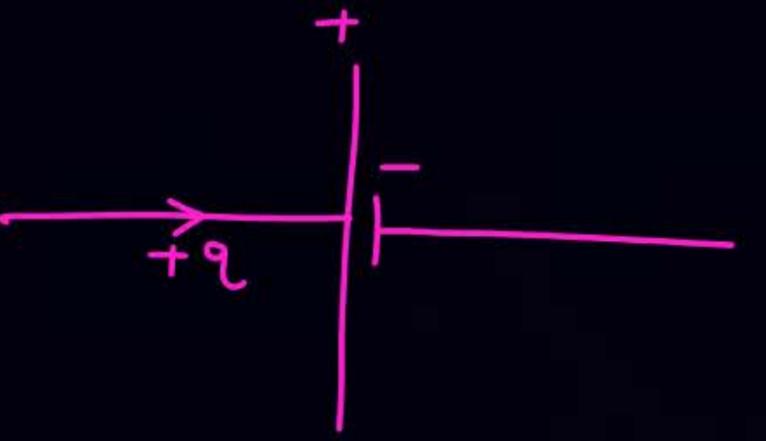

(wo) battery = $-Eq$


②

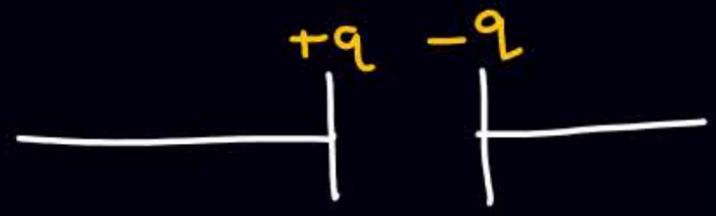


$q = CV$

⑤

ATDB.uno

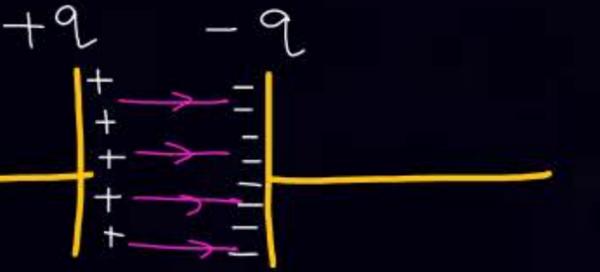


③

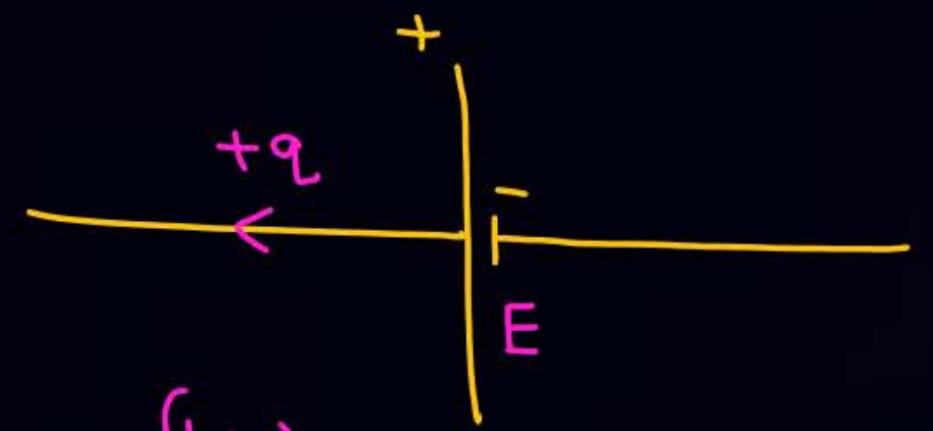

(wo) battery = $+Eq$

$U = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} CV^2$

$q = CV$

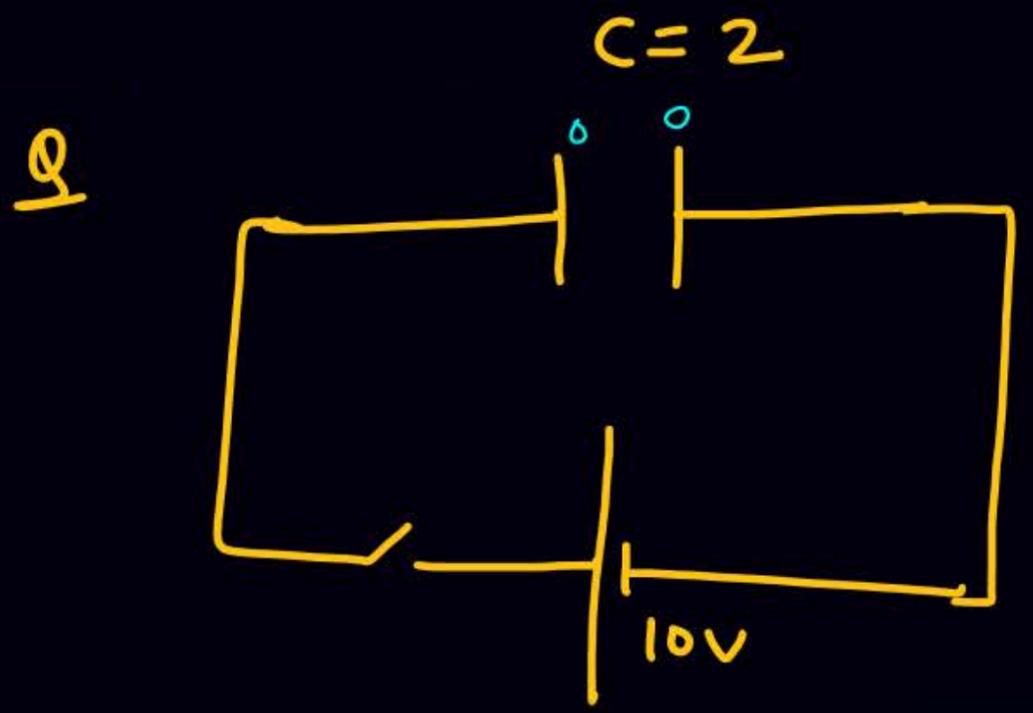

Switch
close



(WD) battery = $+20 \times 10 = \underline{\underline{+200}}$

or $U_f = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \times \frac{(20)^2}{2} = \underline{100}$

or $U_f = \frac{1}{2} CV^2 = \frac{1}{2} \times 2 \times (10)^2 = 100$

heat = $200 - 100 = 100$




Homework of the class soã pdf

ATDB.uno




1

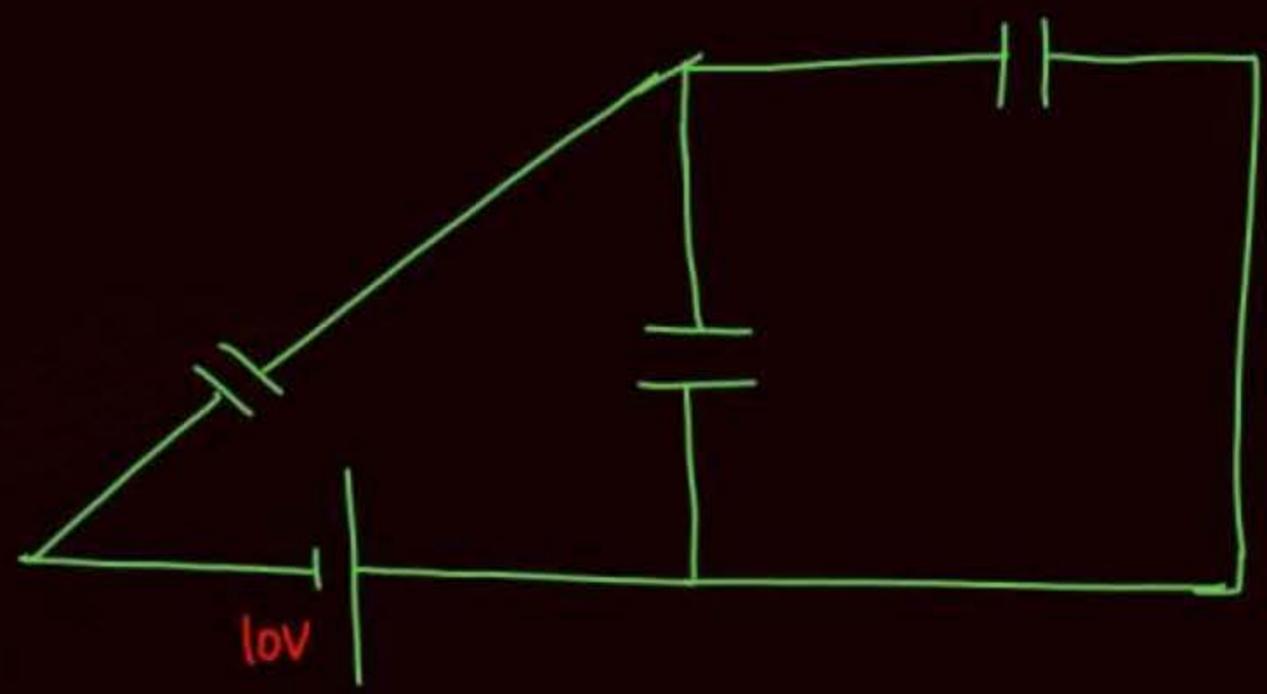

10V

$C = 2F$ (each)

2

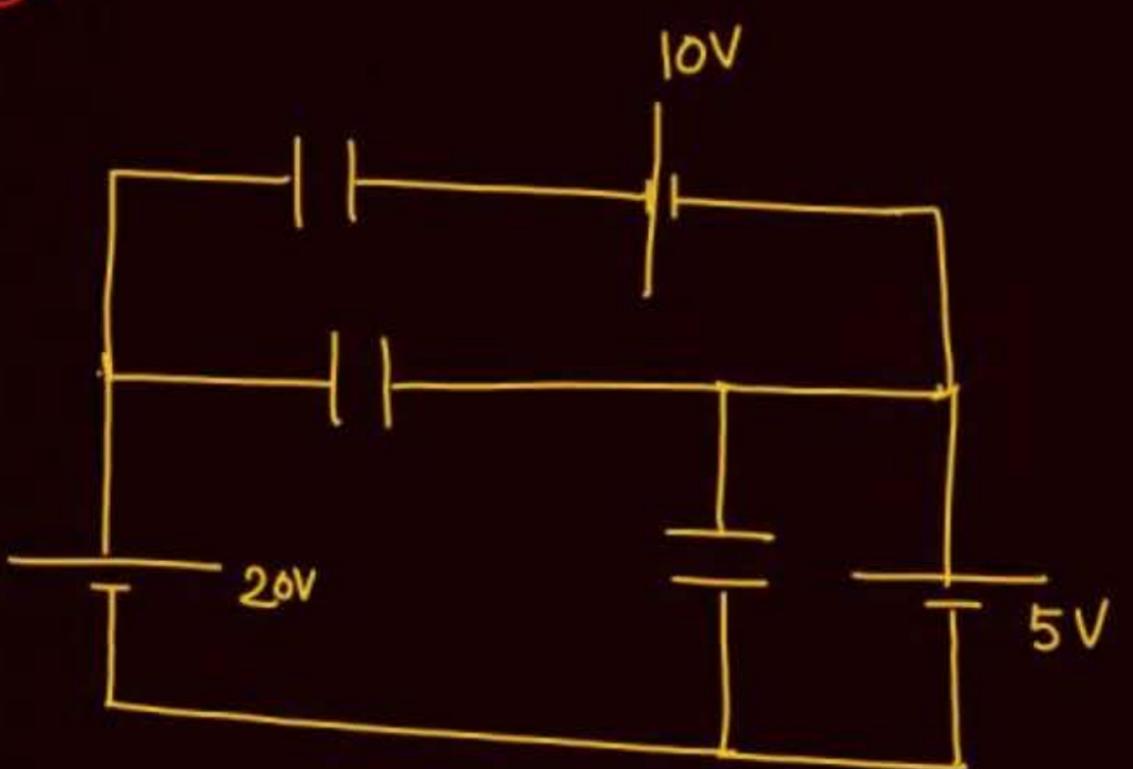


20V

10V

5V

$C = 2F$ (each)


ATDB.uno

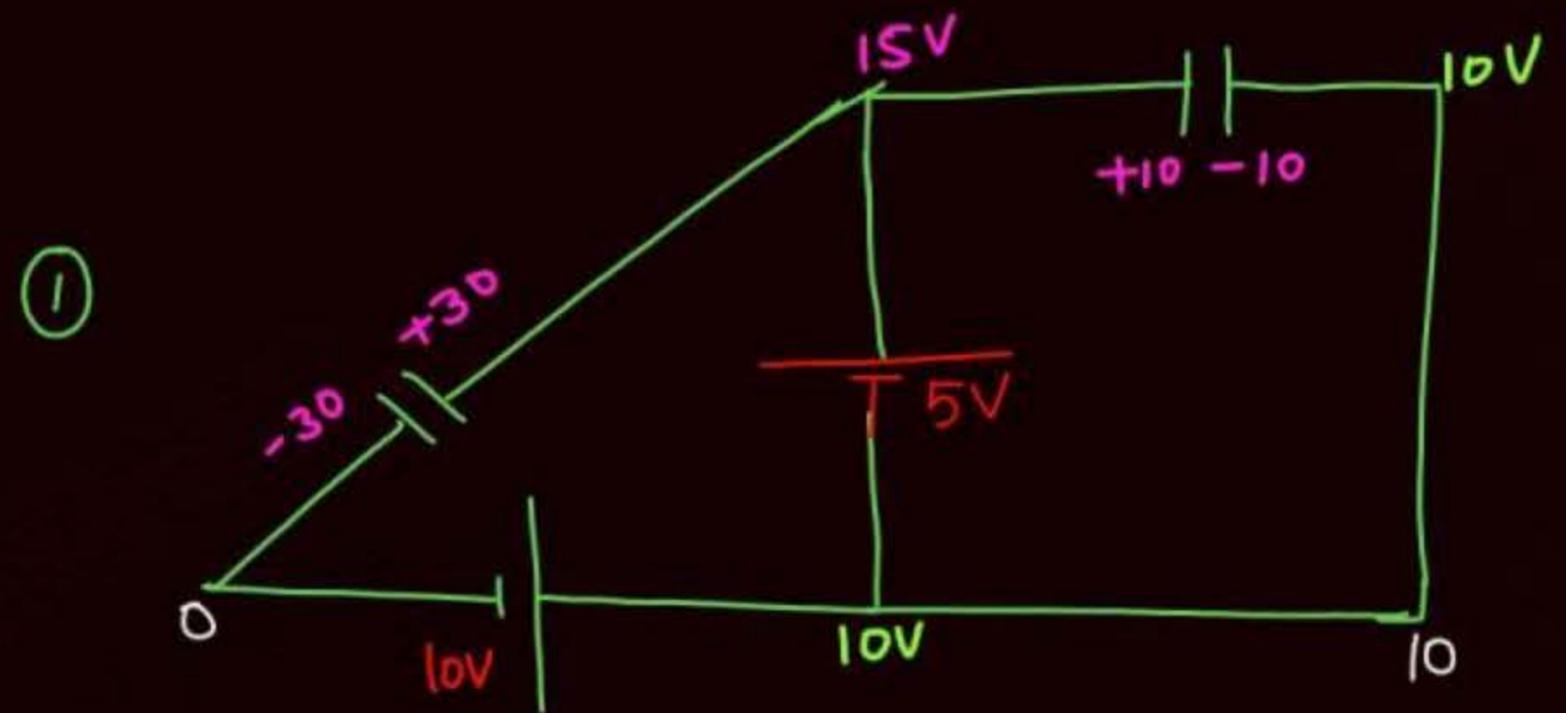

$C = 2F$ (each)

ATDB.uno


$\theta = CV$

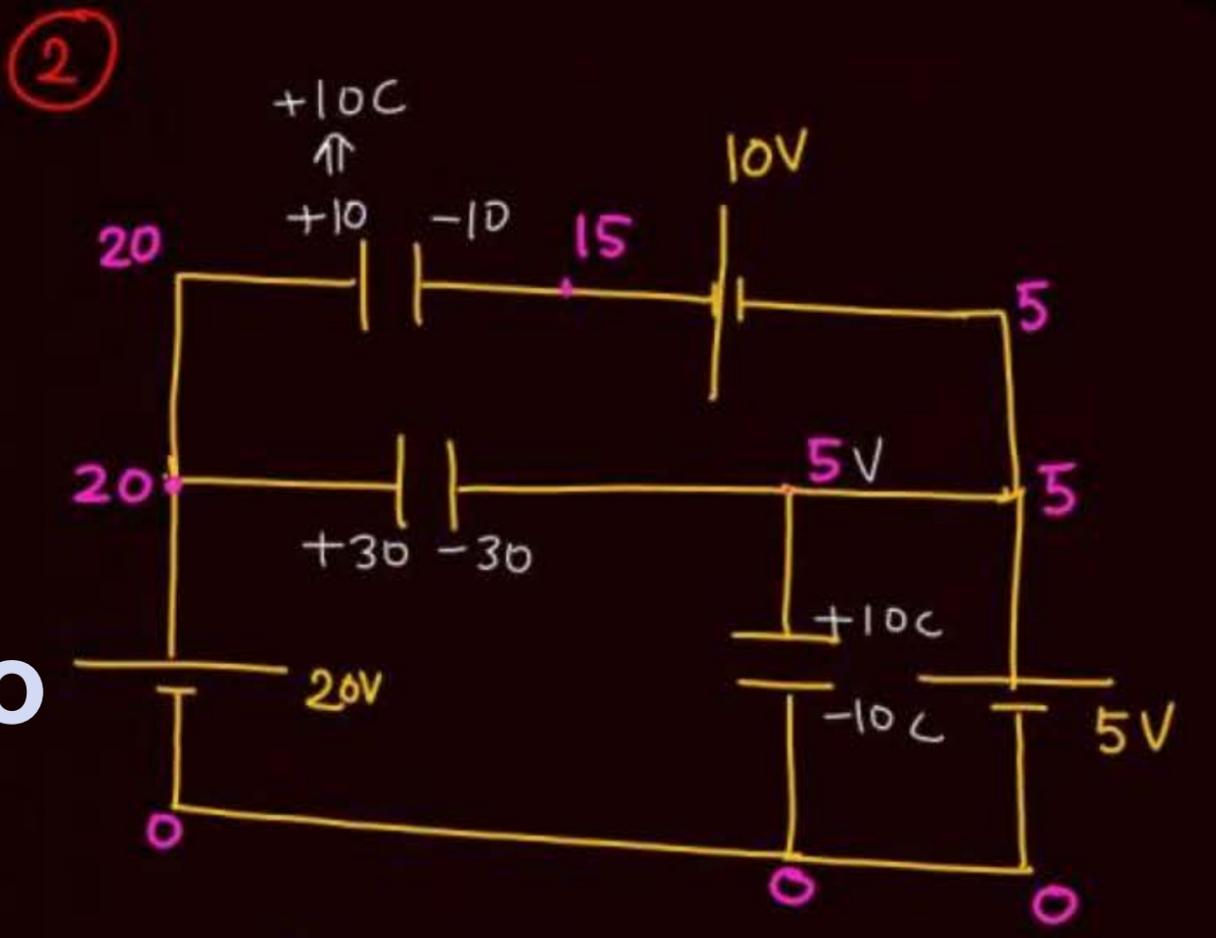

$C = 2F$ (each)



3

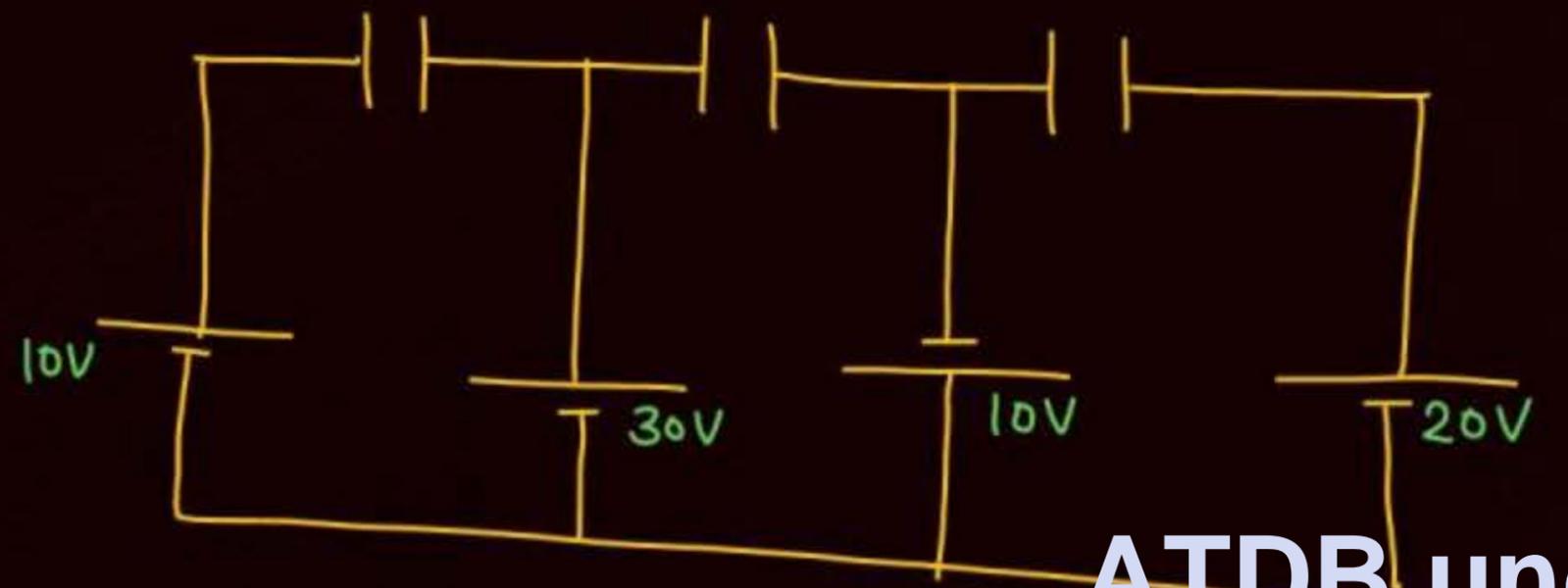


ATDB.uno

4

Q


$C = 2F$ (each)

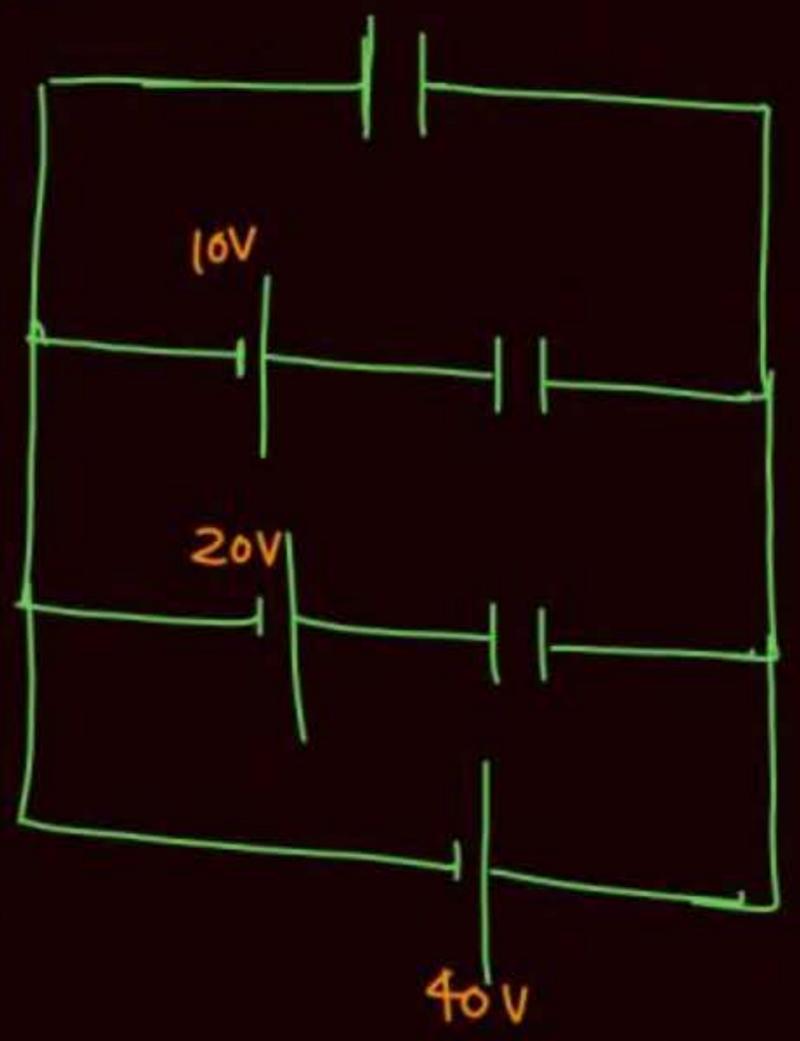



$C = 2F$
 $Q = CV$


3

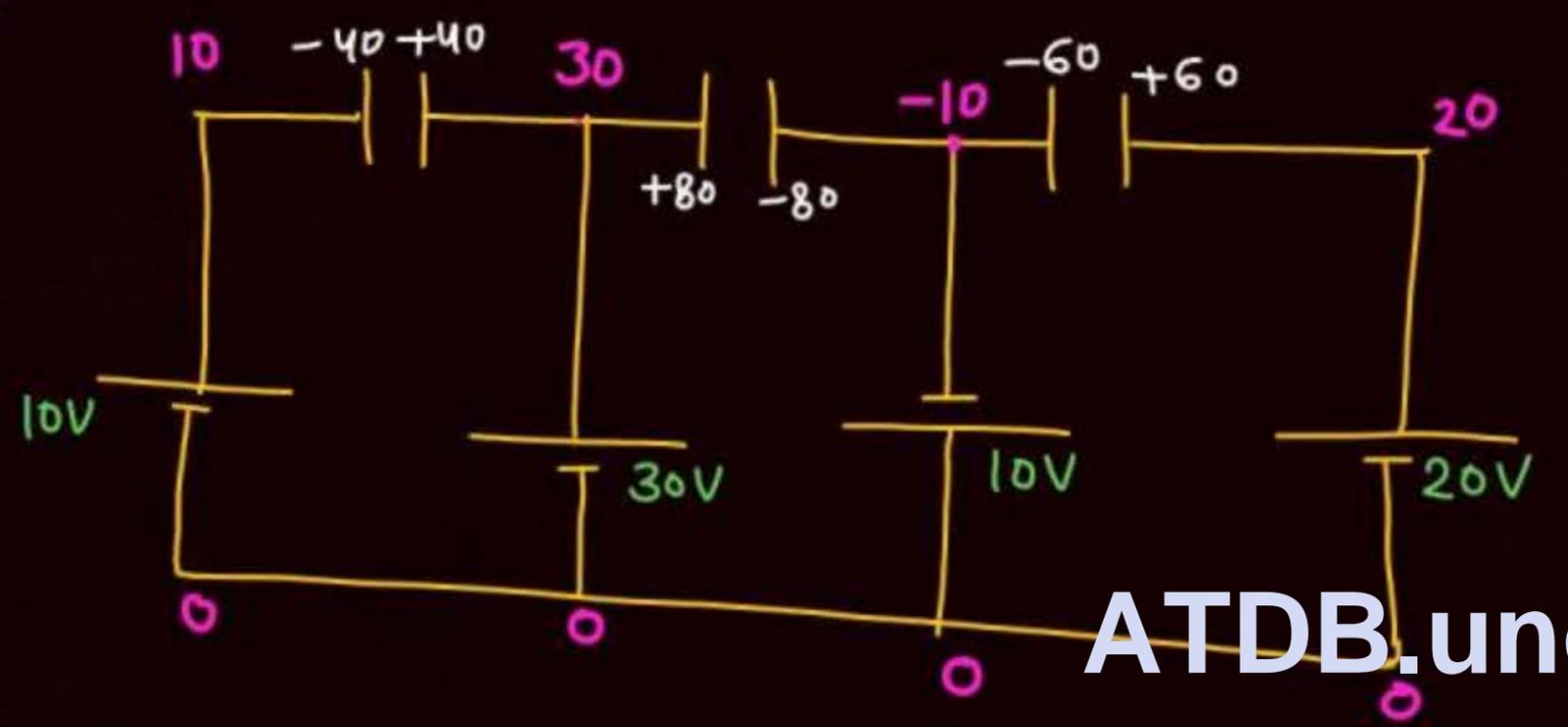


ATDB.uno

4

$C = 2F$ (each)

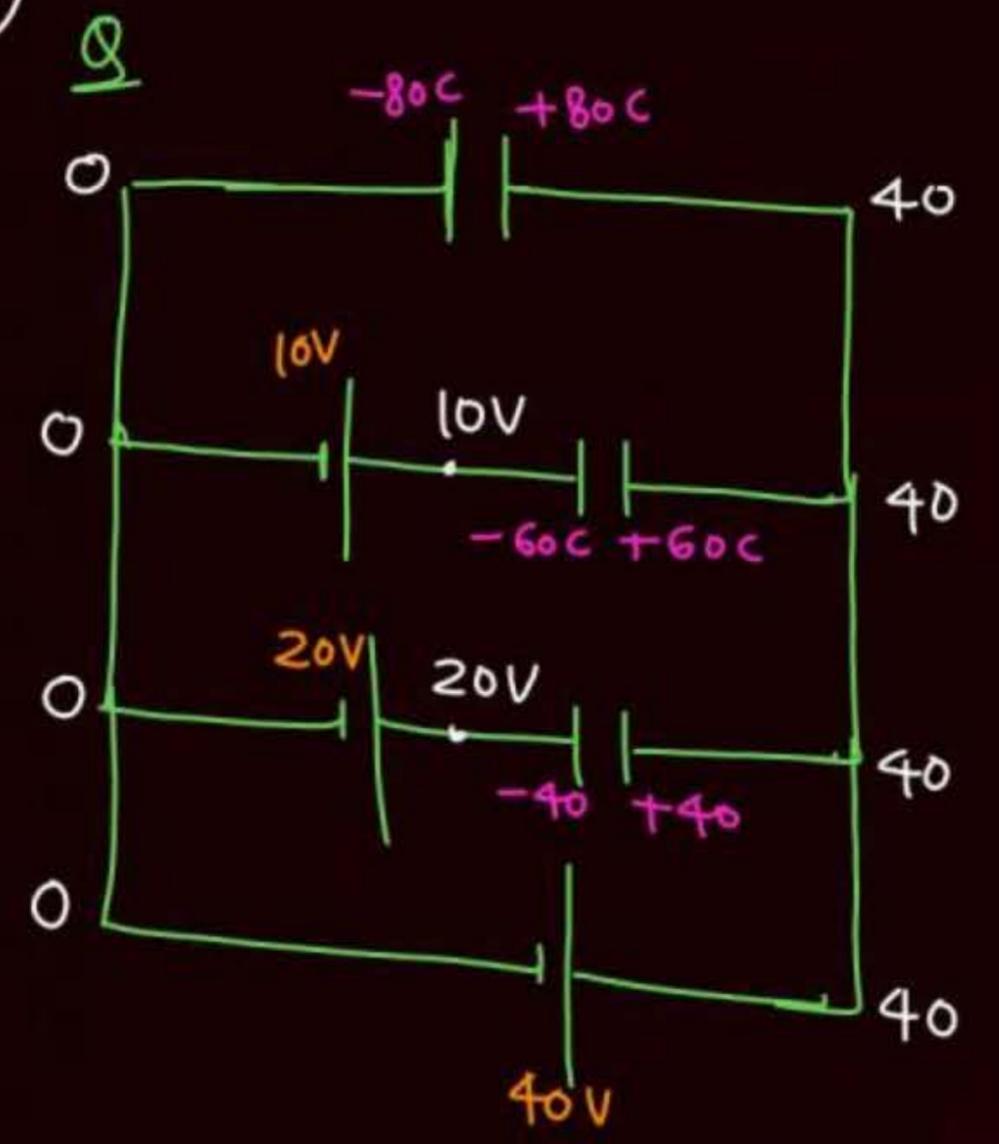

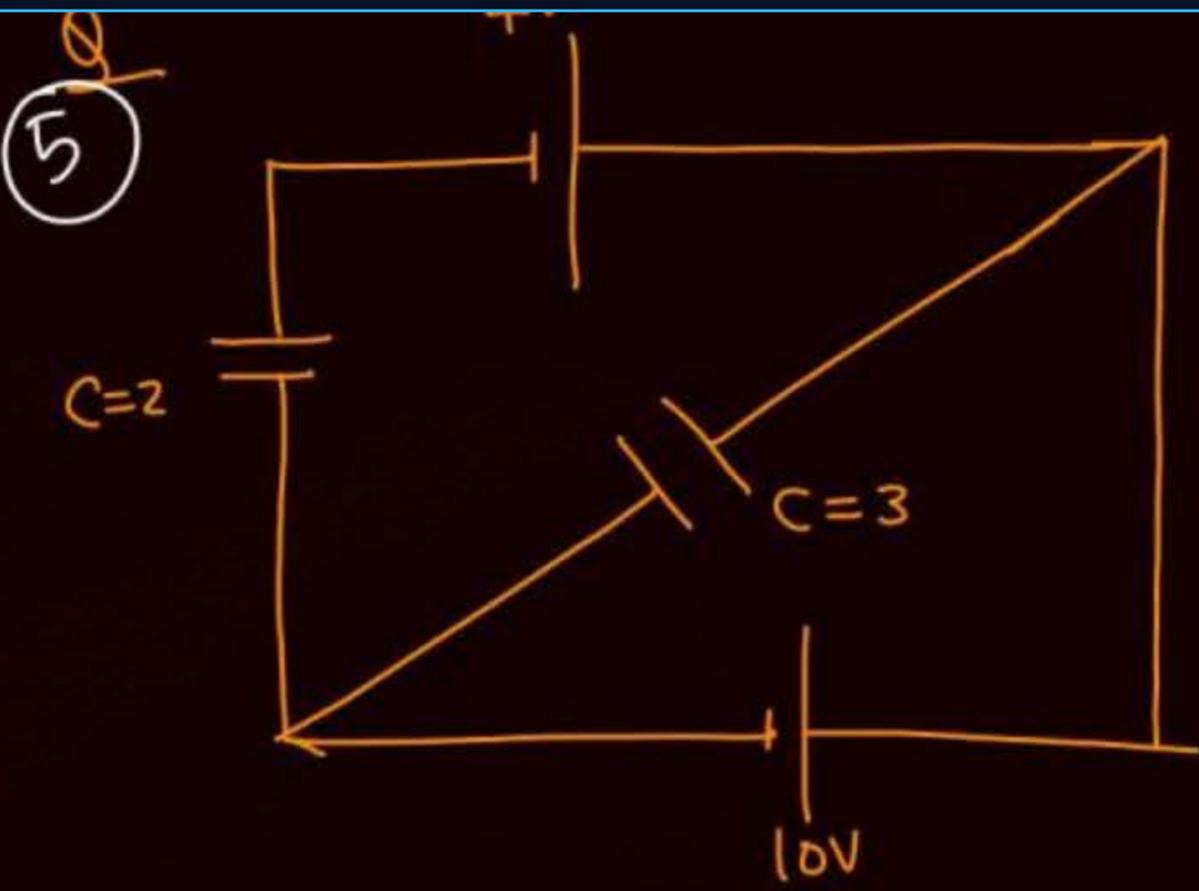


6




Find charge on capacitor C_1 & C_2 and current through 2Ω and 3Ω


ATDB.uno

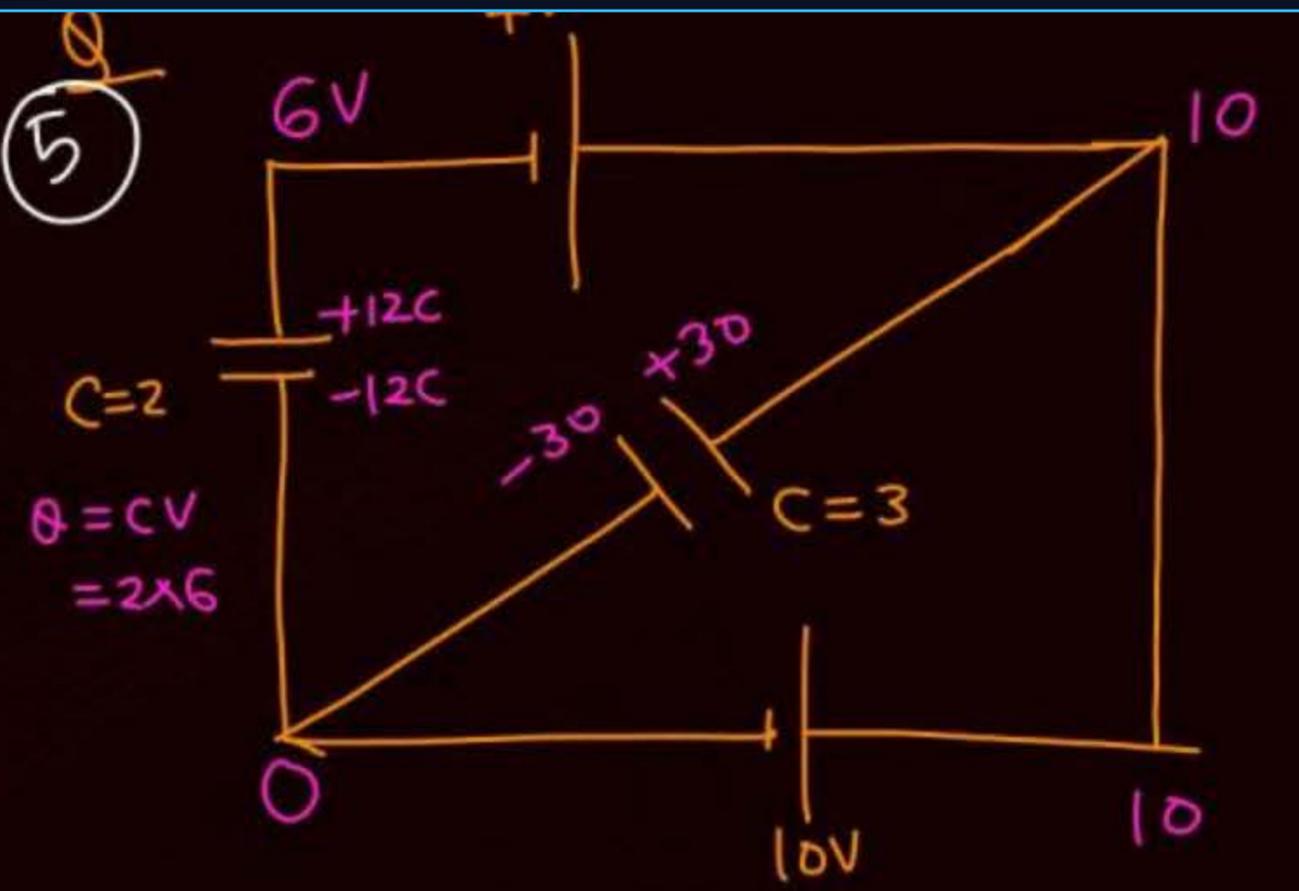

$Q = CV$
 $= 2 \times 6$

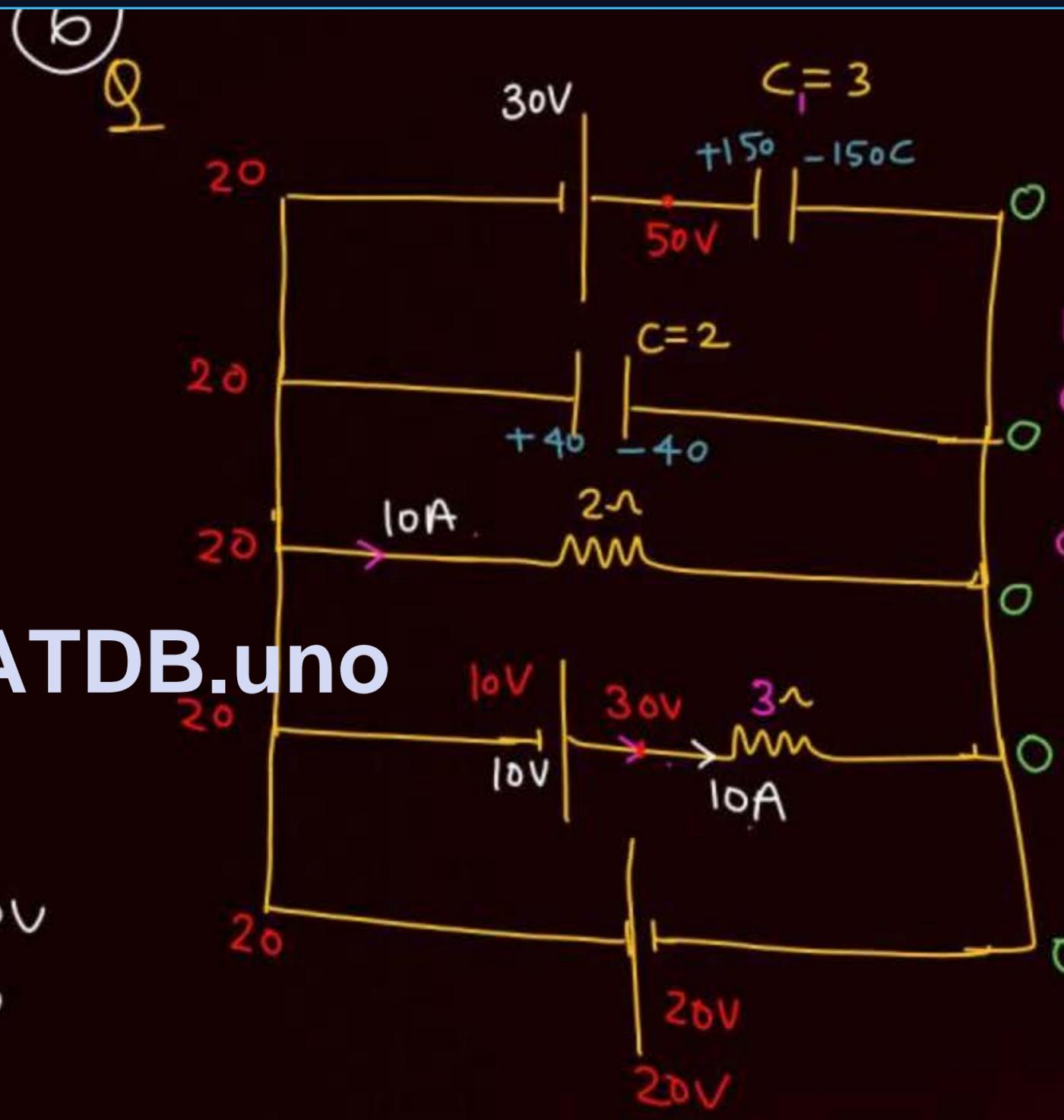

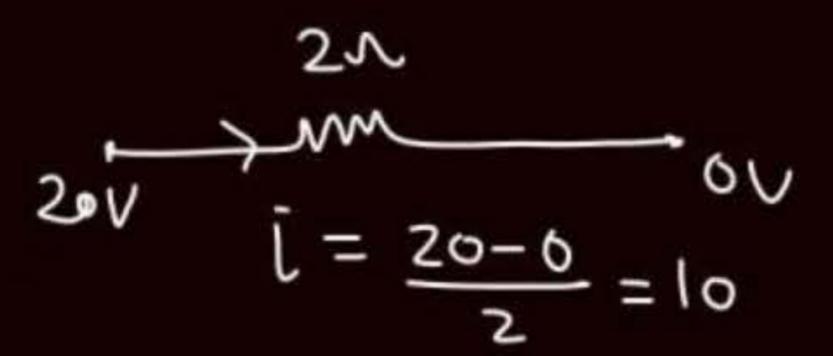Find charge on capacitor C_1 & C_2 and current through 2Ω and 3Ω




ATDB.uno




7

Q

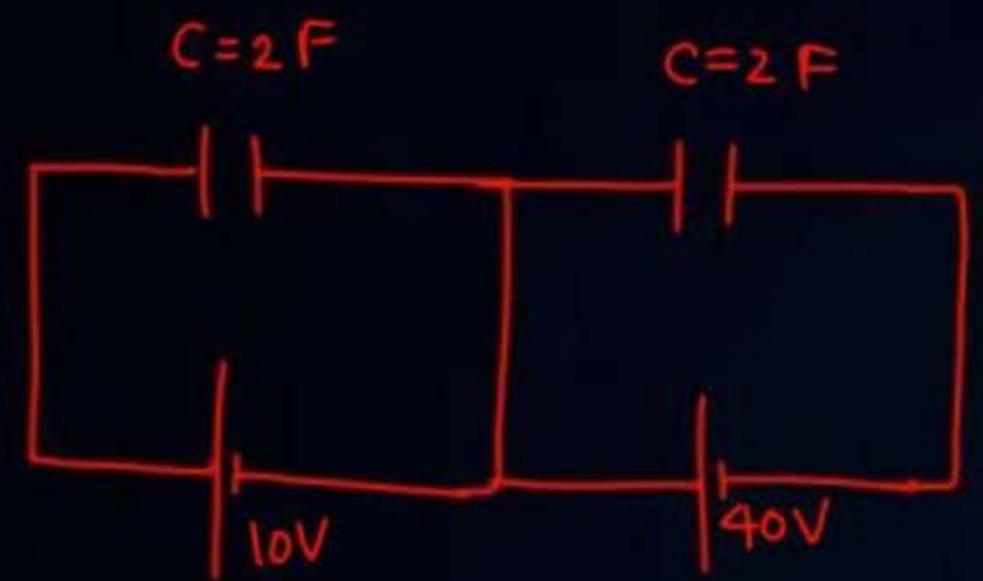

8

Q

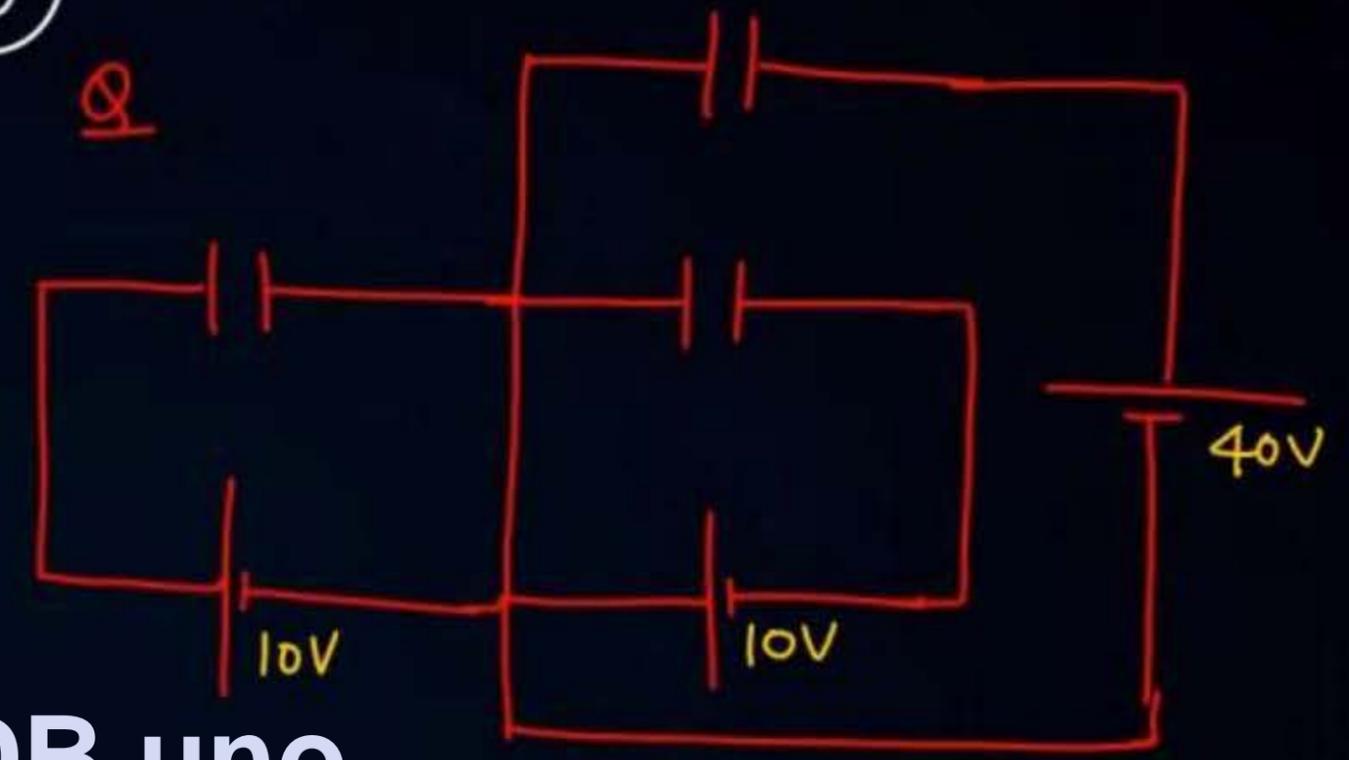


ATDB.uno

C=2F (each)




7

Q

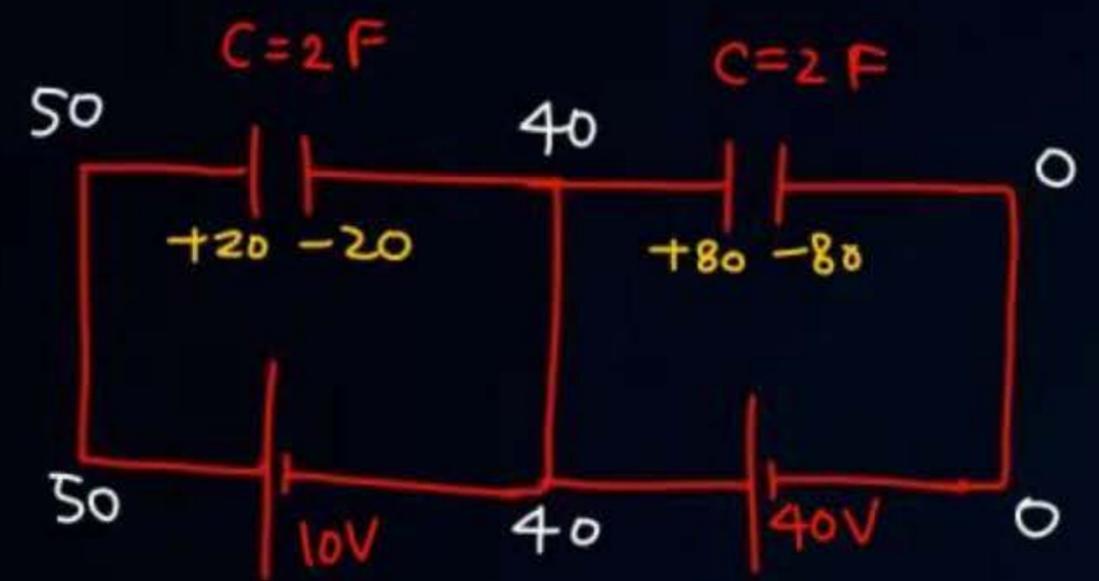

8

Q

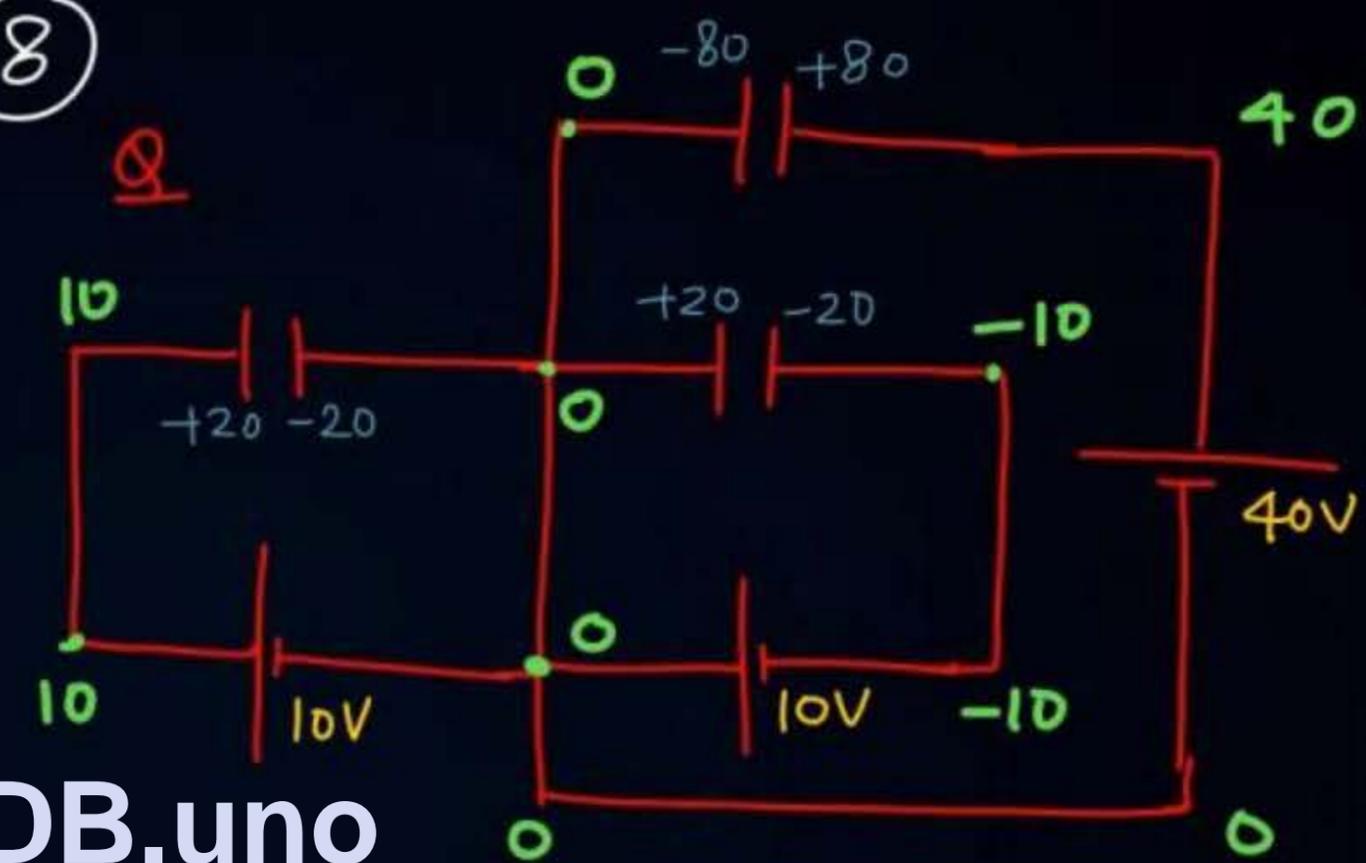


ATDB.uno

C=2F (each)




9

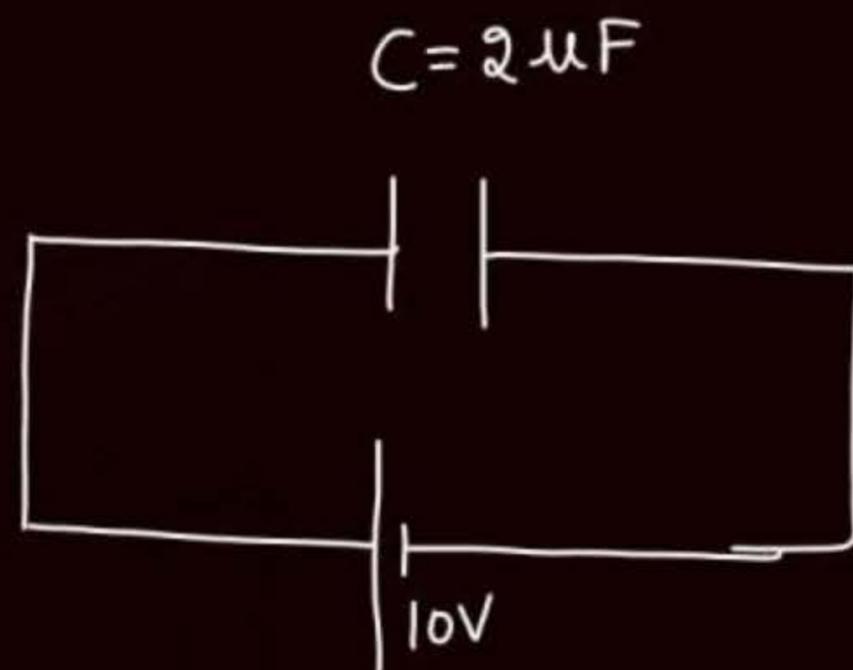


$$C = 2 \mu F = 2 \times 10^{-6} F$$

10

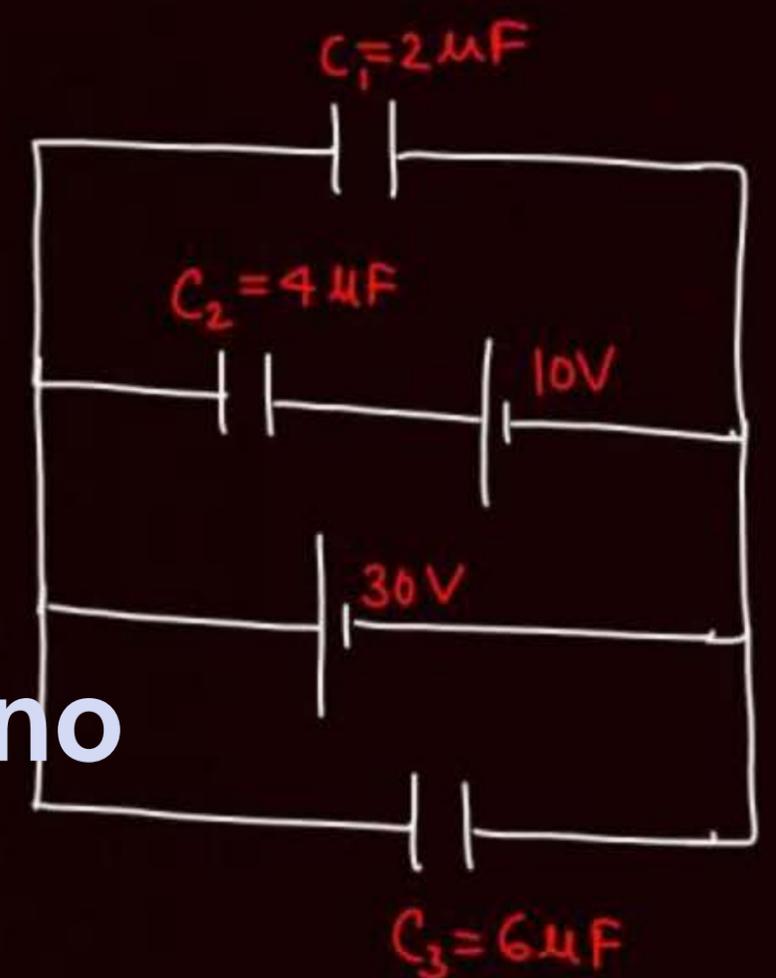

ATDB.uno

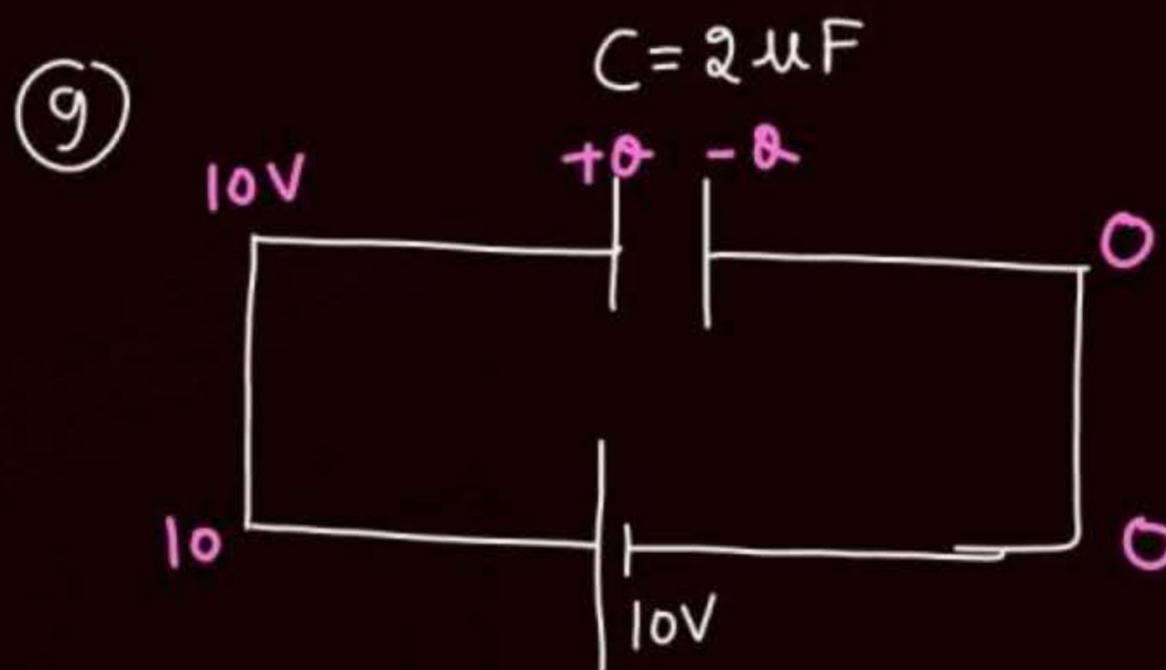


$$C = 2 \mu\text{F} = 2 \times 10^{-6} \text{ F}$$

$$Q = CV = 2 \times 10^{-6} \times 10$$

$$= 20 \times 10^{-6} \text{ Coulomb}$$

$$= 20 \mu\text{C}$$

ATDB.uno

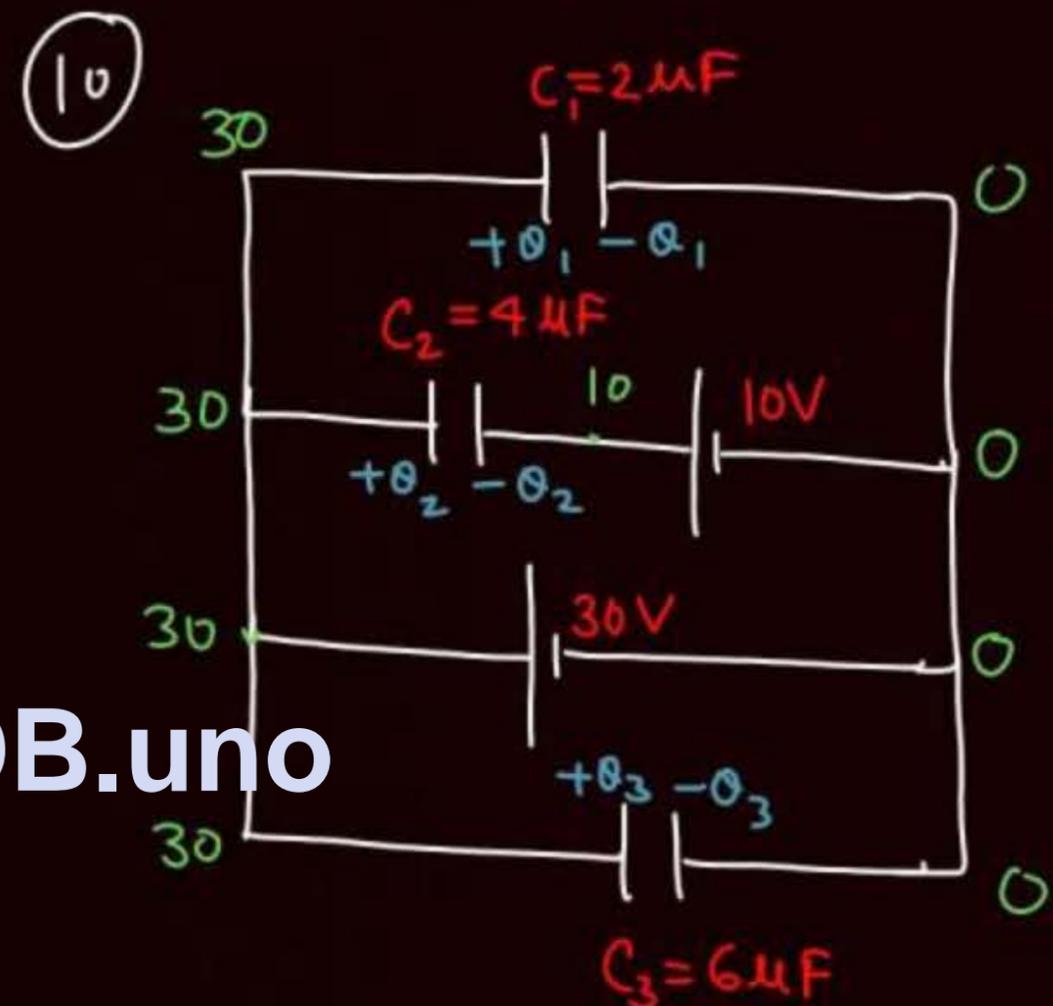


$$Q_1 = 2 \times 30 = 60 \mu\text{C}$$

$$Q_2 = 4 \times 20 = 80 \mu\text{C}$$

$$Q_3 = 6 \times 30 = 180 \mu\text{C}$$



(12)

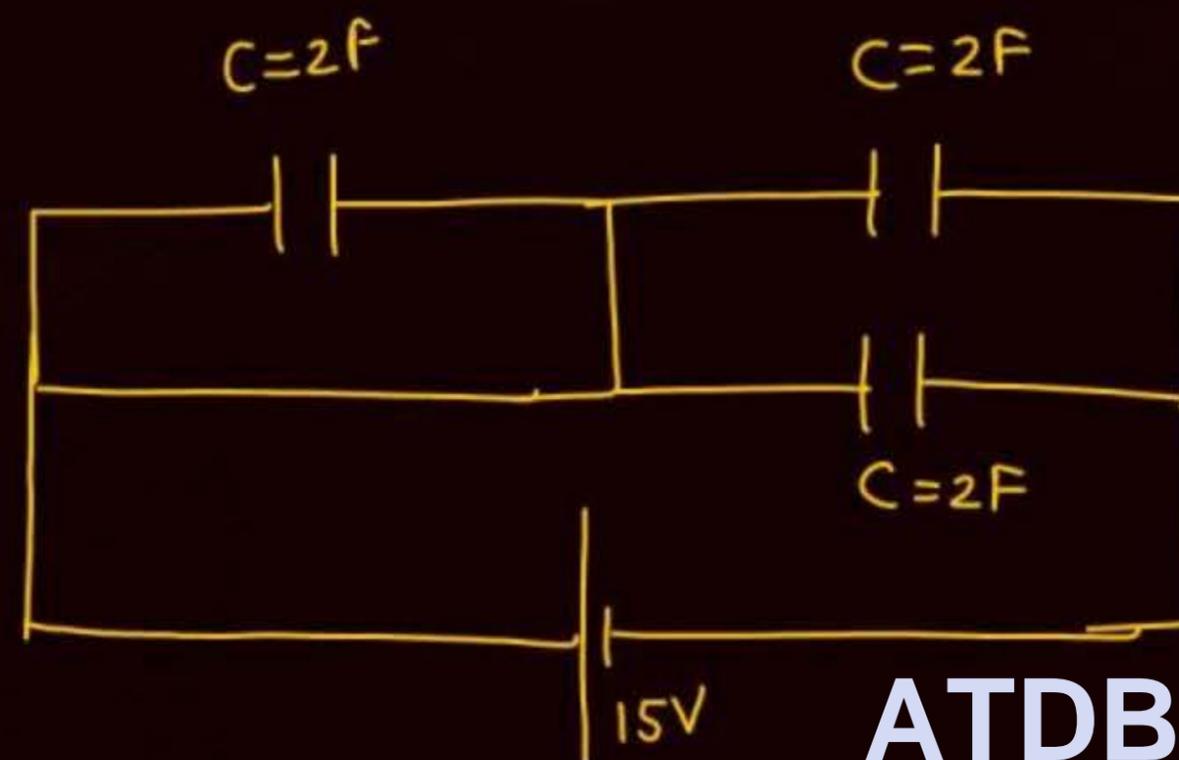

ATDB.uno




$Q = CV$

$C = 2F$

$C = 2F$


(12)

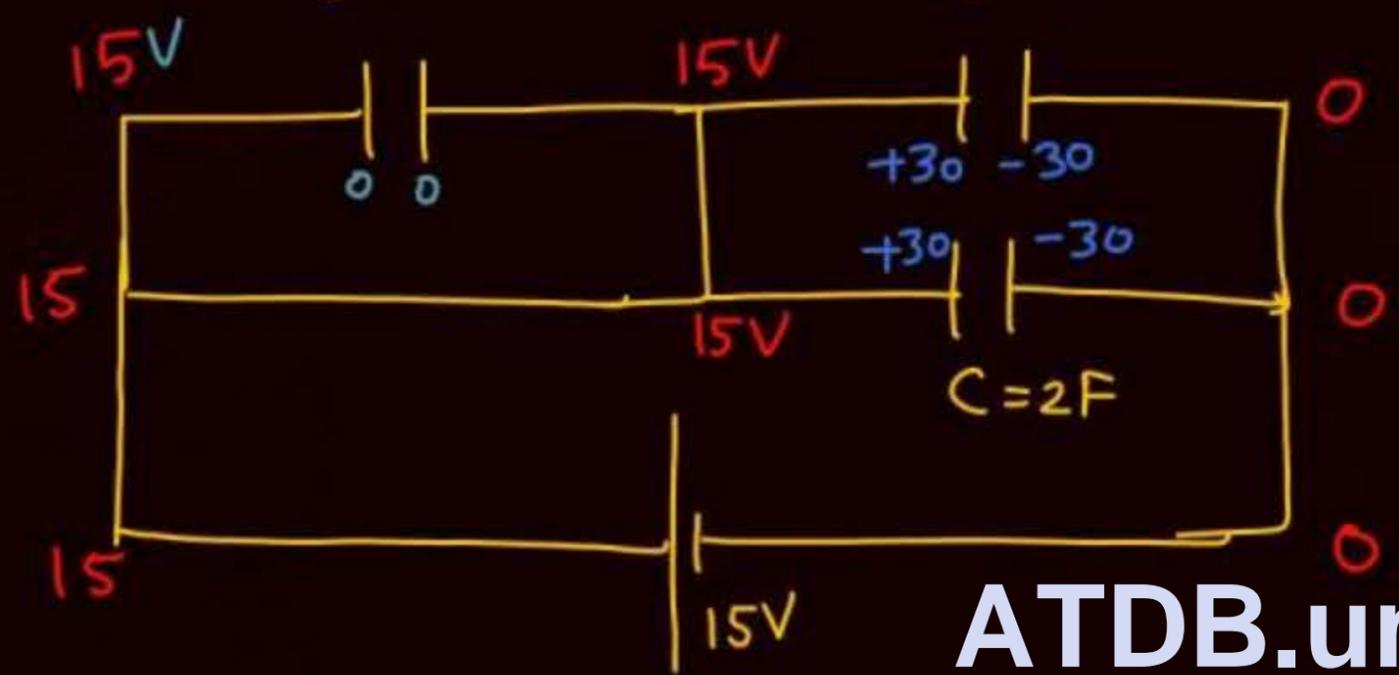

ATDB.uno




Q (13)

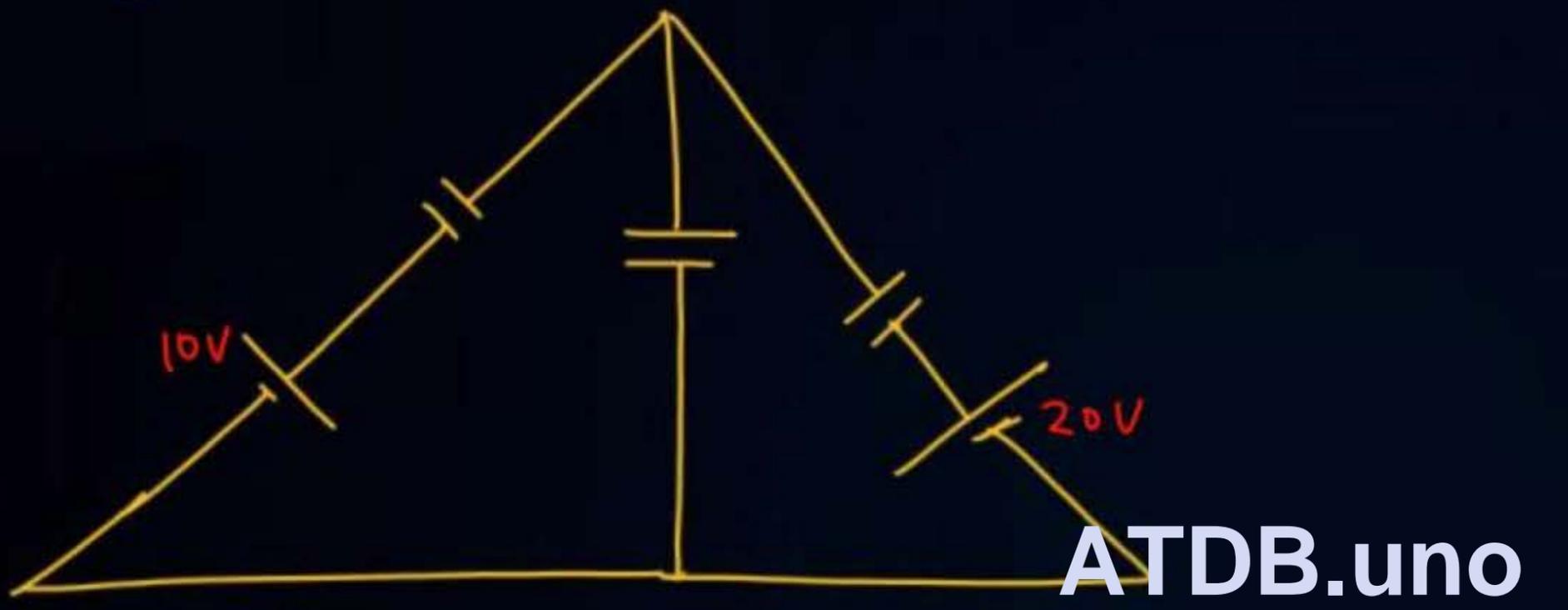


Q (13) Assume initially charge on all capacitors was zero

$C = 2F$ (each)

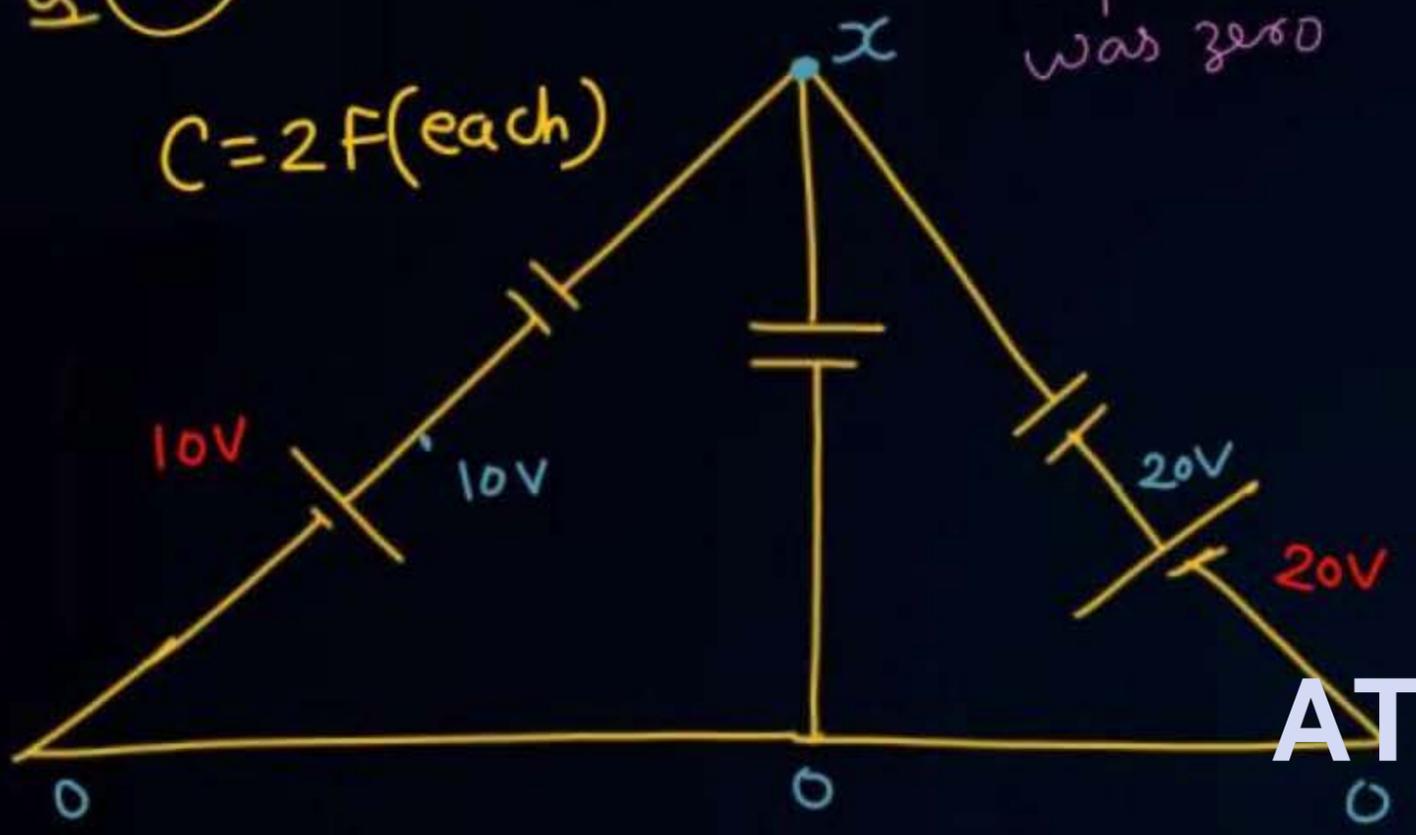

Junction Law

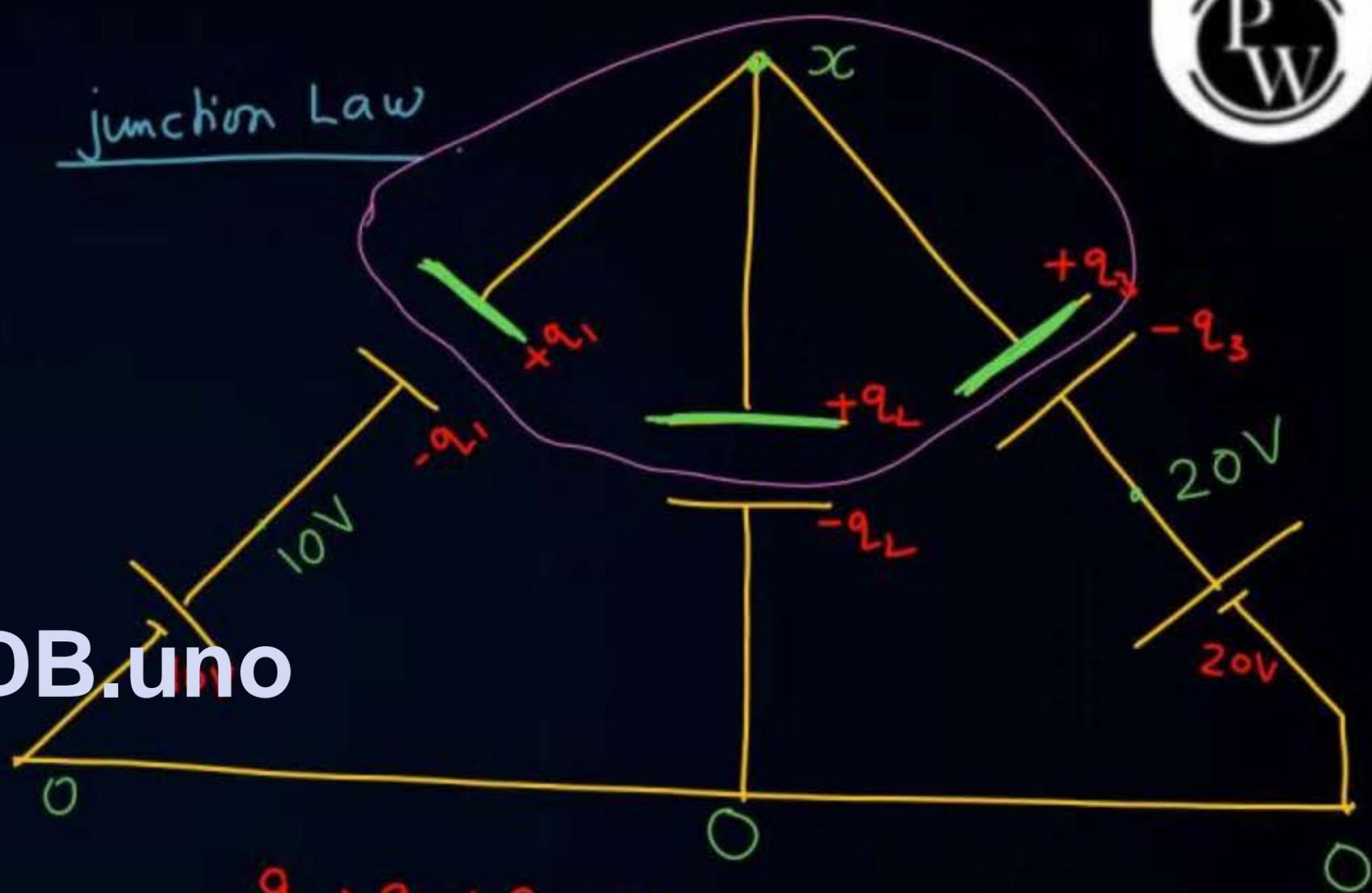

ATDB.uno

$$q_1 = 2 \times 0 = 0$$

$$q_2 = 2 \times 10 = 20$$

$$q_3 =$$



$$q_1 + q_2 + q_3 = 0$$

$$2 \times (x - 10) + 2 \times (x - 0) + 2 \times (x - 20) = 0$$

$$6x - 20 - 40 = 0$$

$$x = 10$$



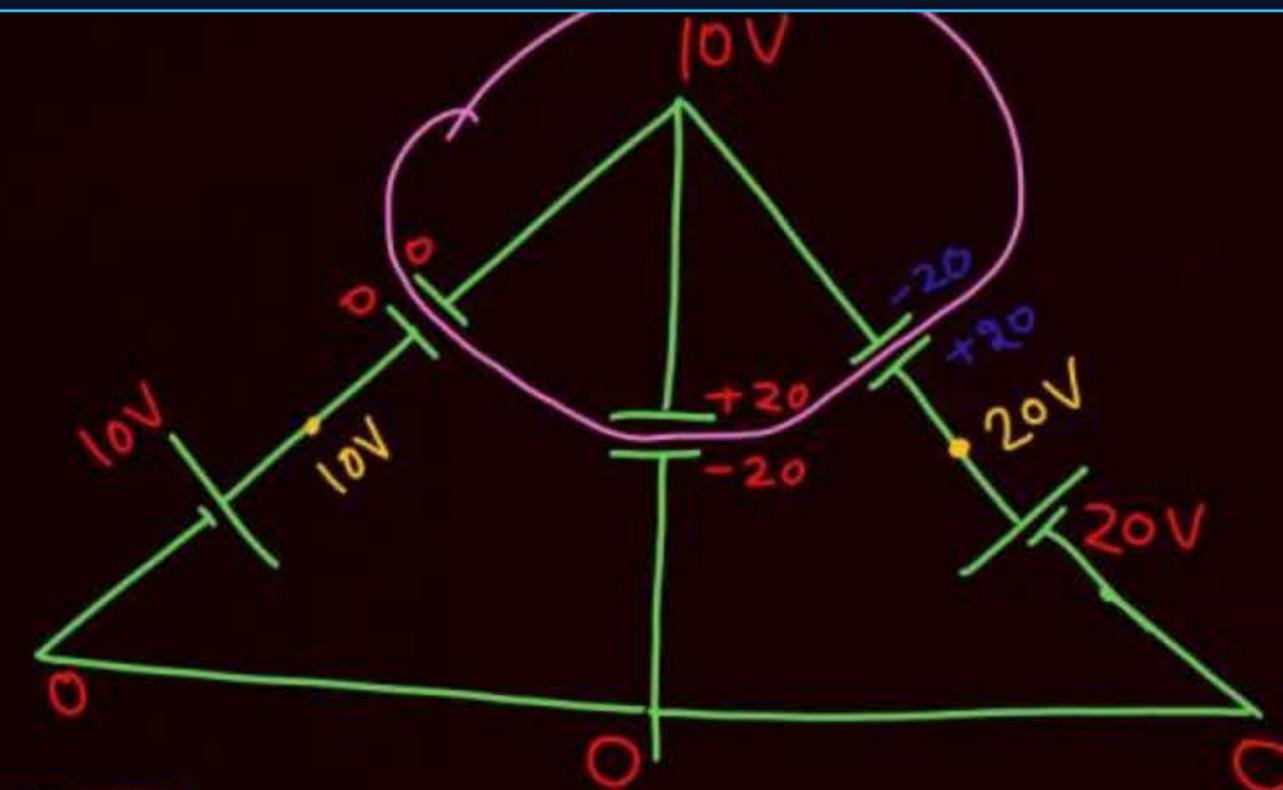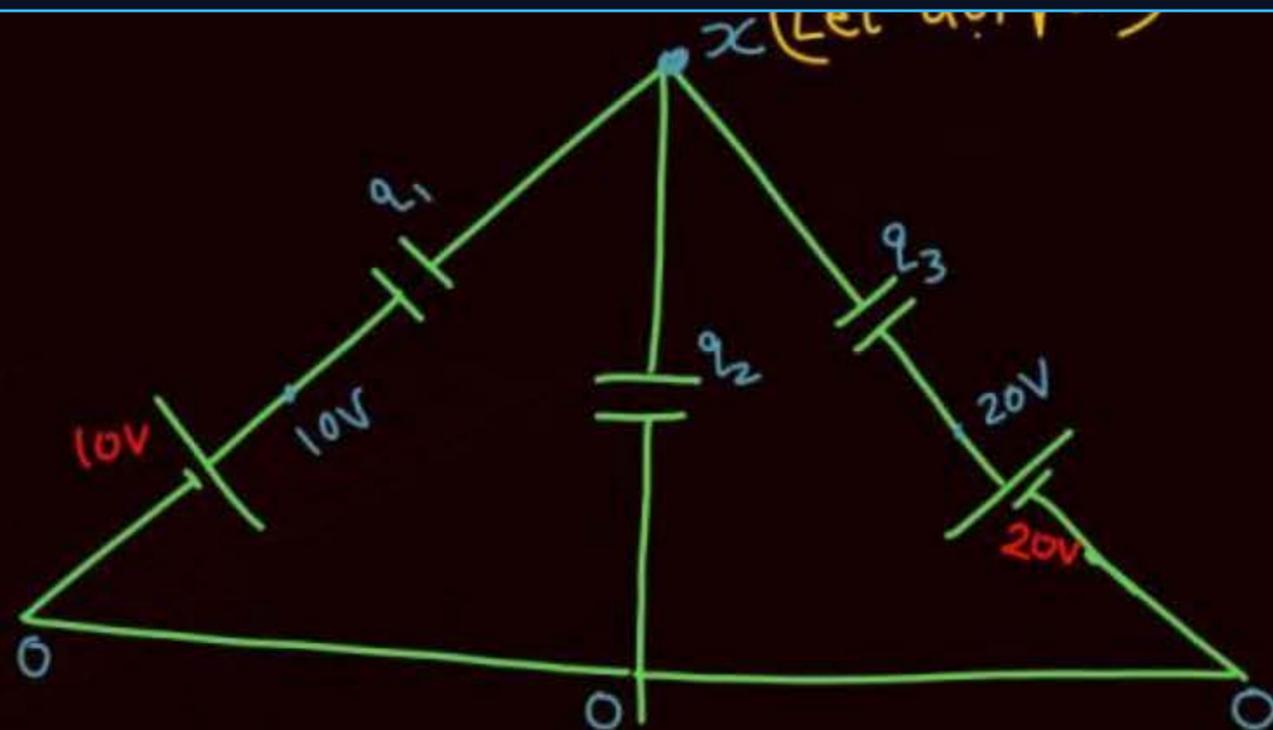

$$C = 2 \text{ F (each)}$$


$$q = CV = QC$$

$$q_1 + q_2 + q_3 = 0$$

$$(x-10) \times 2 + (x-0) \times 2 + (x-20) \times 2 = 0$$

$$6x = 60$$


$$x = 10 \text{ (matlab)}$$

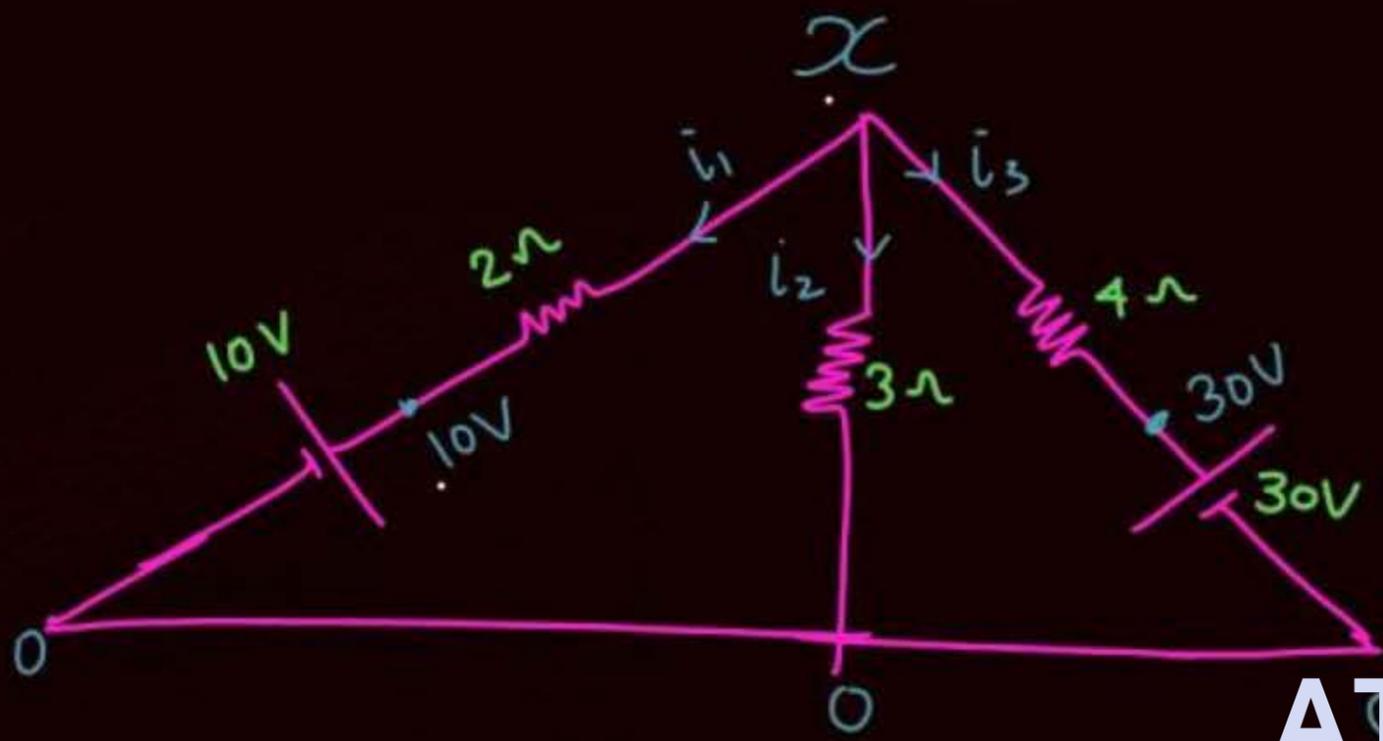

ATDB.uno

$$i_1 + i_2 + i_3 = 0$$
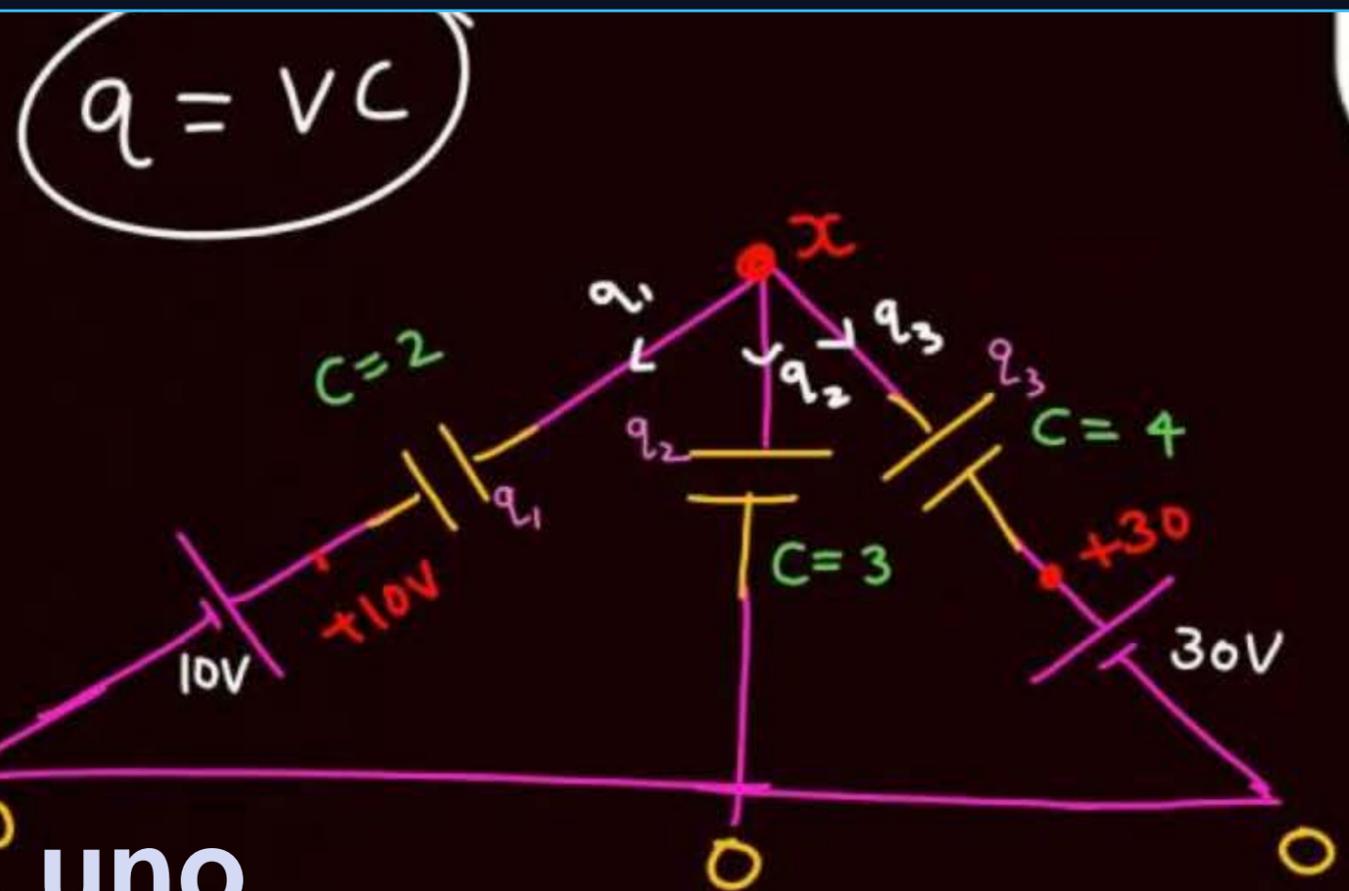
$$\frac{x-10}{2} + \frac{x-0}{3} + \frac{x-30}{4} = 0$$




$$q = VC$$

$$q_1 + q_2 + q_3 = 0$$

$$(x-10) \times 2 + (x-0) \times 3 + (x-30) \times 4 = 0$$



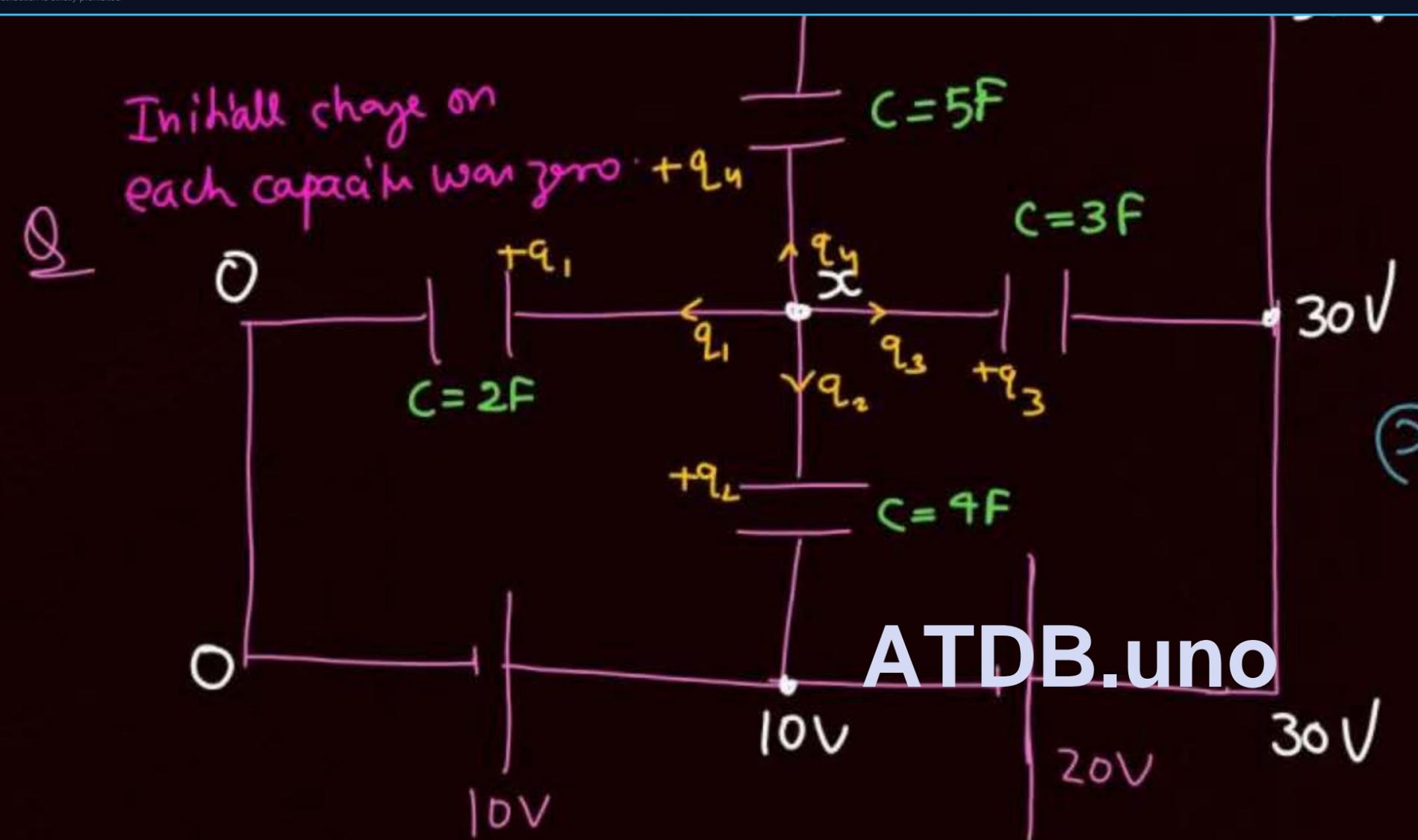Initial charge on each capacitor was zero



$$q_1 + q_2 + q_3 + q_4 = 0$$



$$(x - 0) \times 2 + (x - 10) \times 4 + (x - 30) \times 3 + (x - 30) \times 5 = 0$$

ATDB.uno



$Q = CV$

$C = 2F$

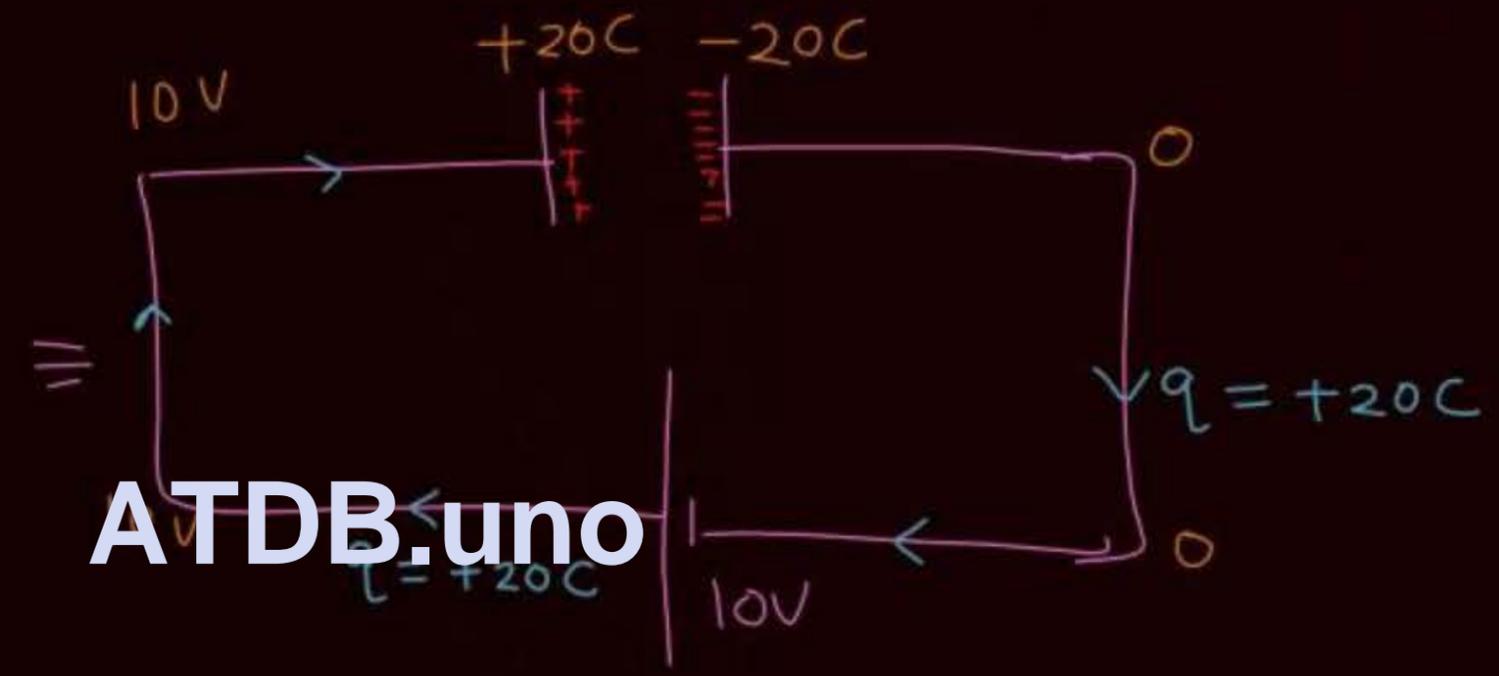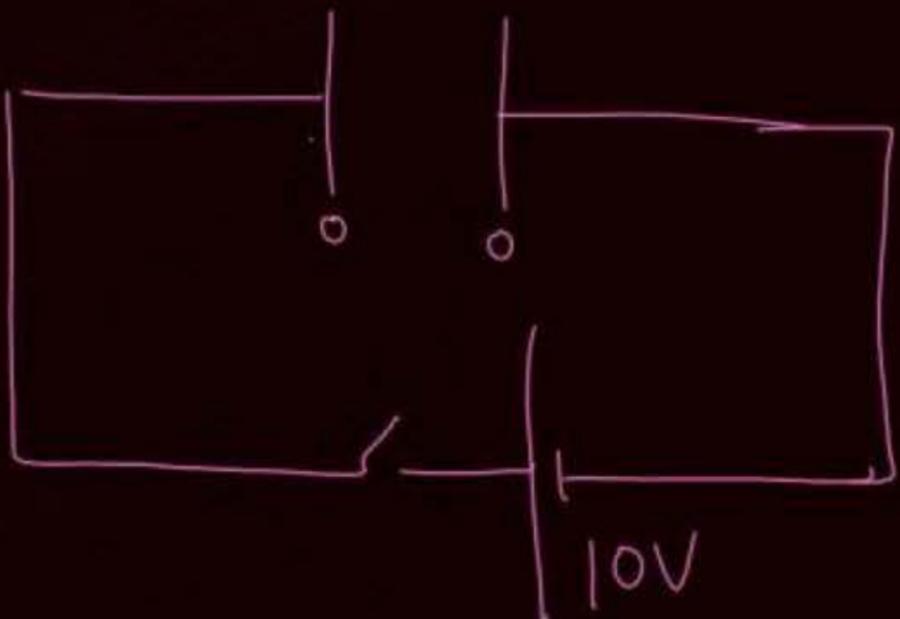


ATDB.uno



14


$C = 2F$ (each)

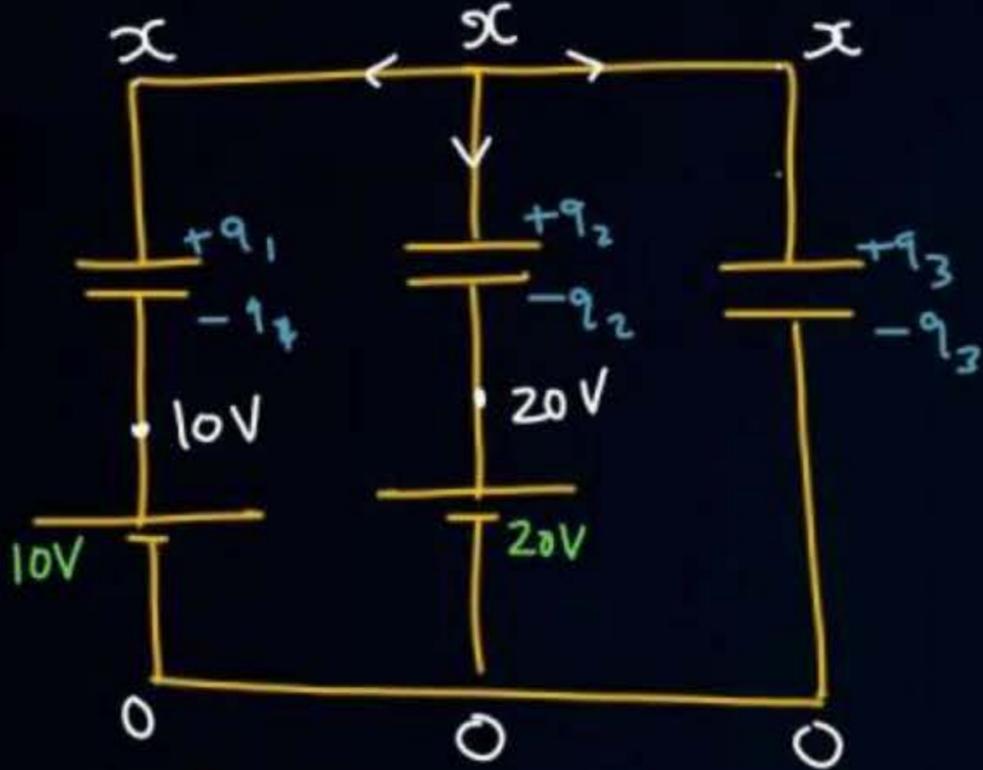

$$(x-10)^2 + (x-20)^2 + (x-0) \times 2 = 0$$

15

Q

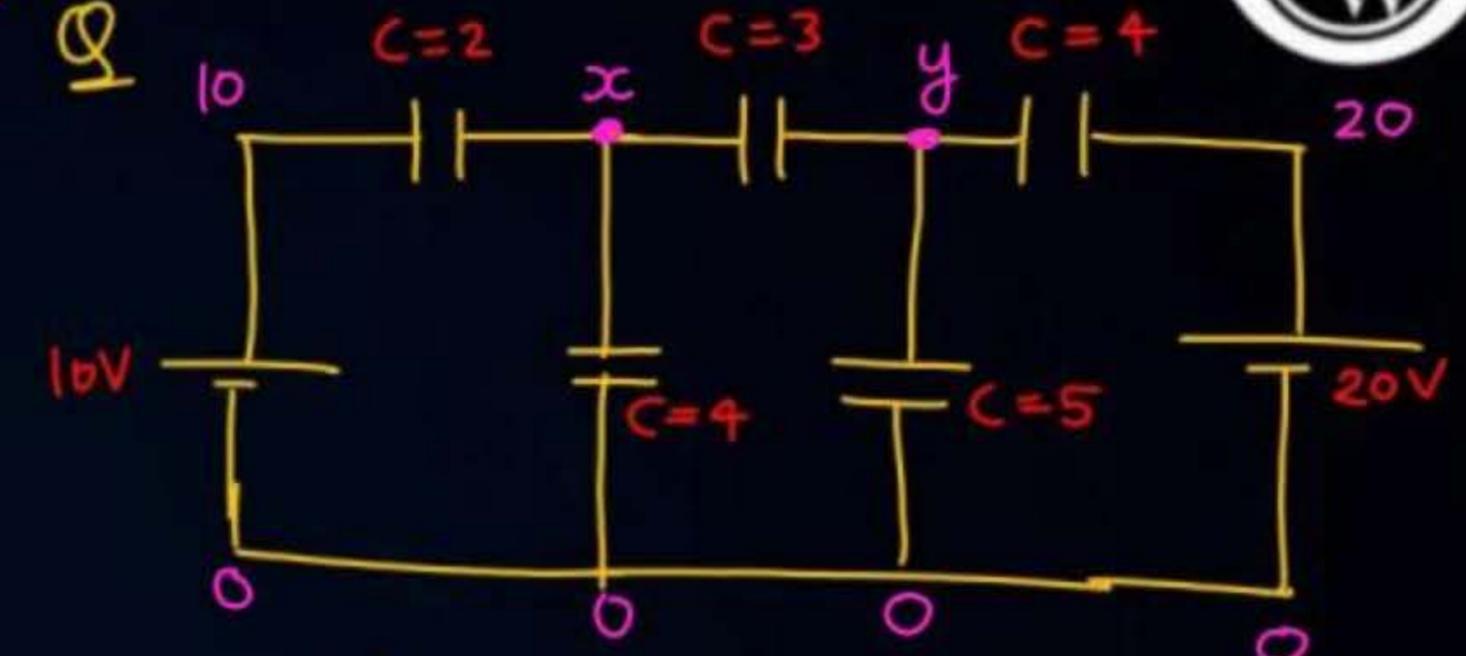

$$(x-10)^2 + (x-0)^4 + (x-y) \times 3 = 0$$


$$(y-x) \times 3 + (y-0) \times 5 + (y-20) \times 4 = 0$$

ATDB.uno




14

$C = 2F$ (each)

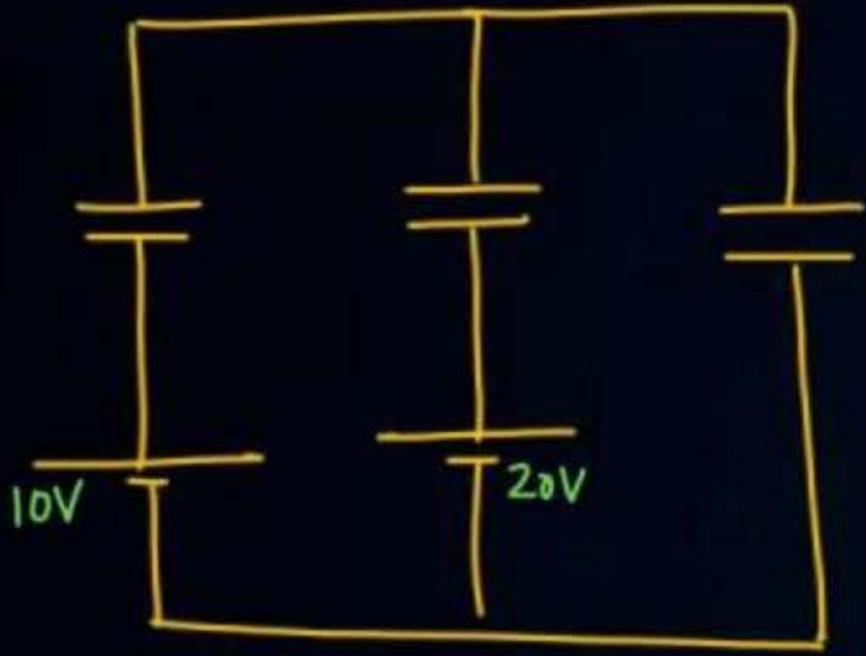


15

Q

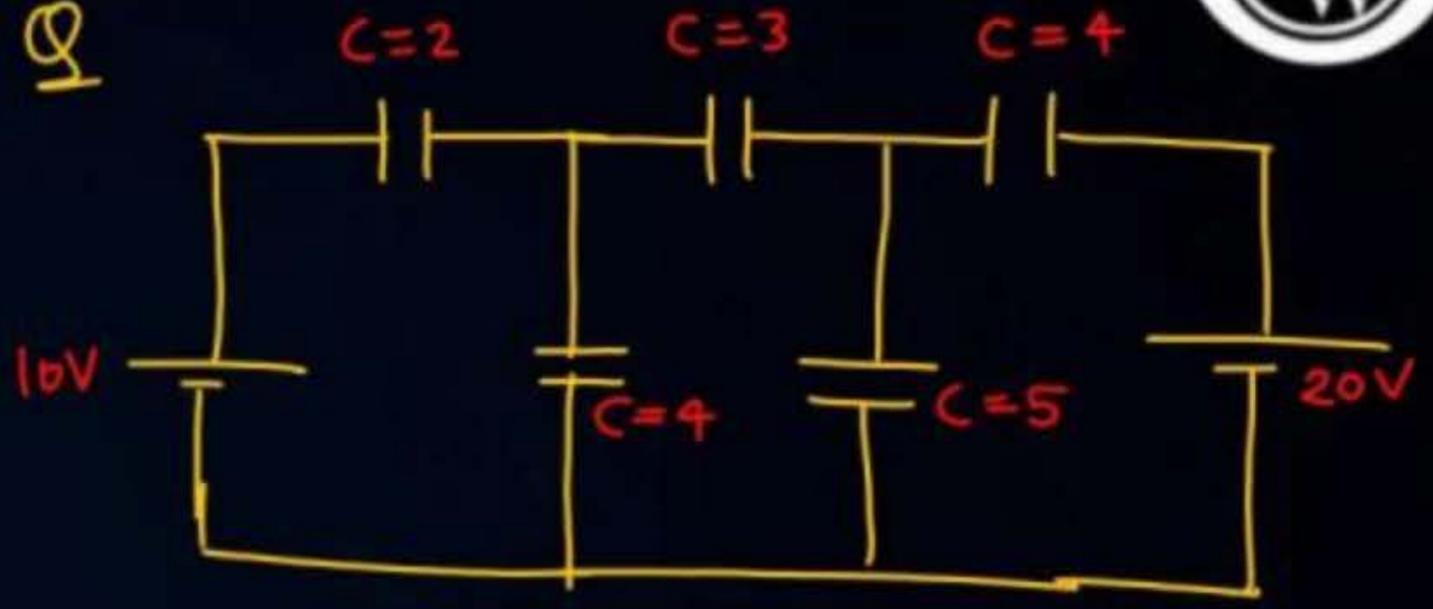


ATDB.uno

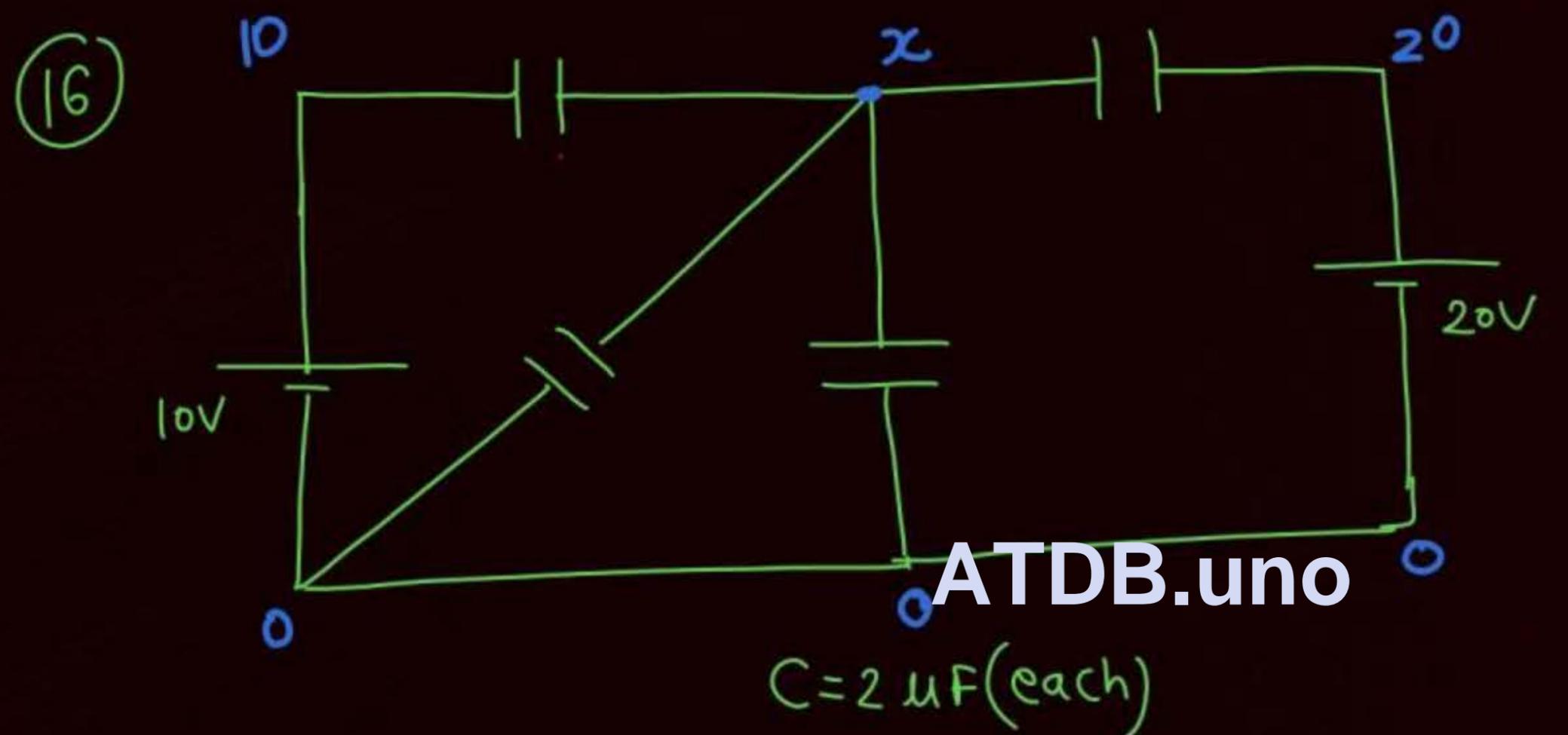

$$(x - 10)^2 + (x - 0) \times 2 + (x - 0) \times 2 + (20 - x) \times 2 = 0$$



16

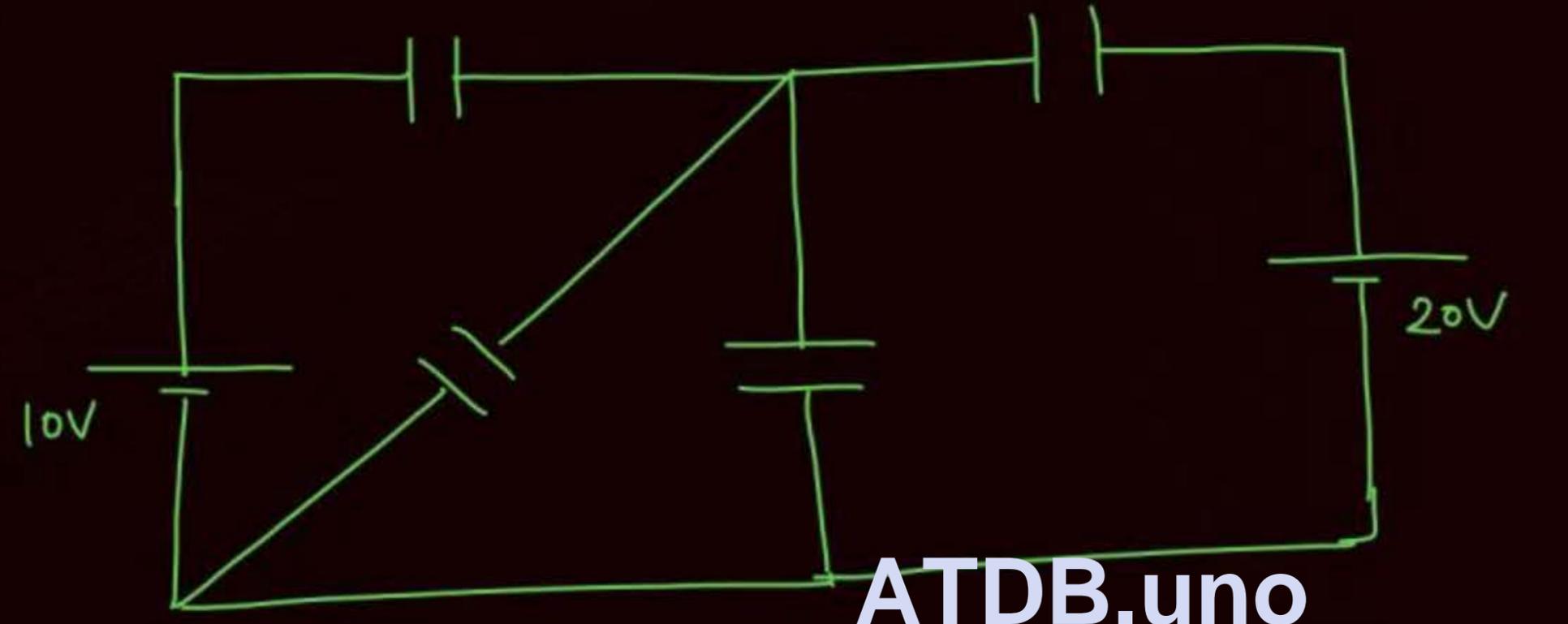

$C = 2 \mu F$ (each)



Home work

— PYQ (CE) module

ATDB.uno



THANK YOU

ATDB.uno

