

PRAYAS

JEE 2025



Lecture - 3

Physics

ATDB.uno

Capacitor

By- Saleem Ahmed Sir





Topics *to be covered*

1

C_{eq} , series-parallel

2

Slab inserted b/w Cap. band qus.


3

4

ATDB.uno



ATDB.uno

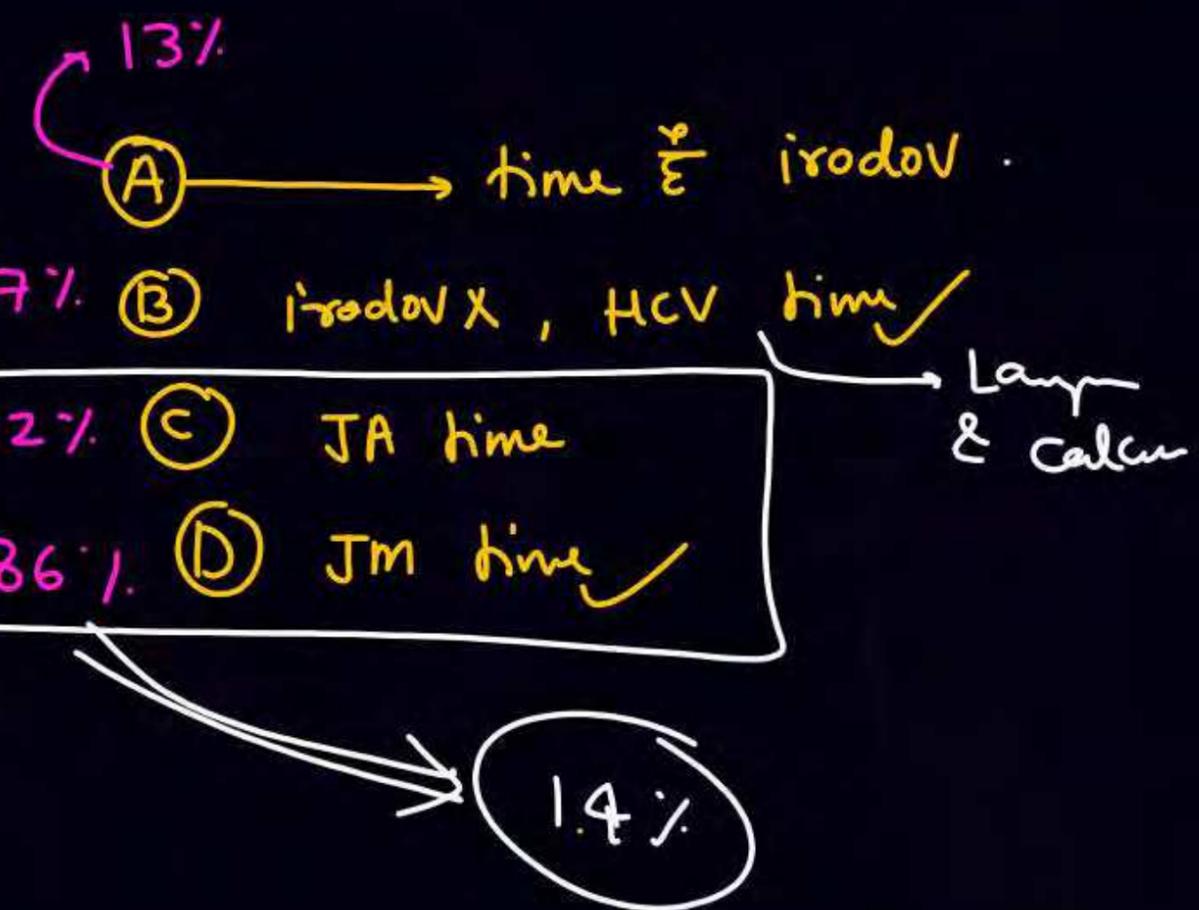





Resistance \Rightarrow series $R_{eq} = R_1 + R_2$
 parallel $R_{eq} = ?$
 $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

Capacitor parallel $\Rightarrow C_{eq} = C_1 + C_2 + C_3 + \dots$

Capacitor Series $\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$



1

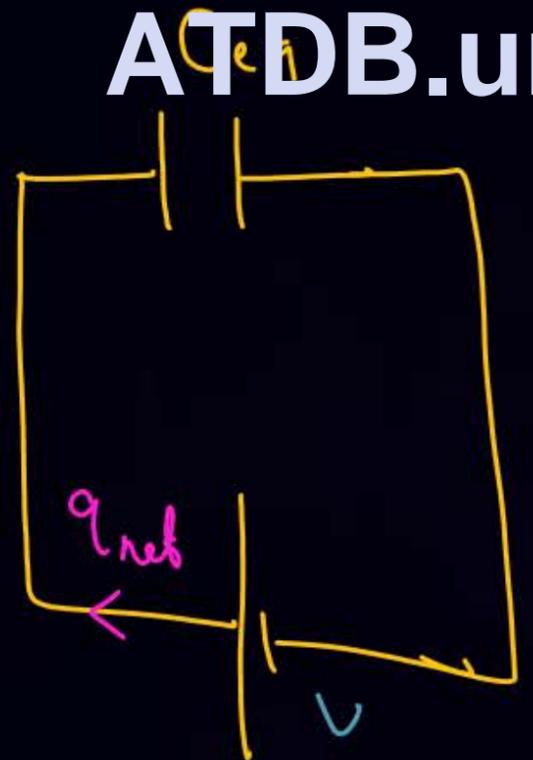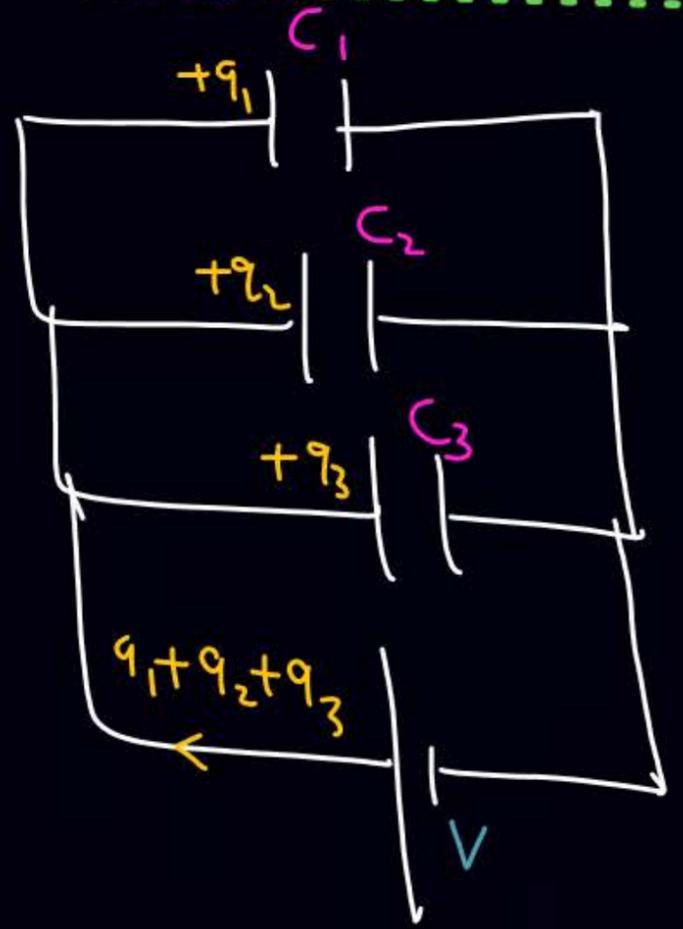

$$q_1 + q_2 + q_3 = C_1V + C_2V + C_3V = q_{net}$$

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$


$$= C_{eq} \cdot V$$

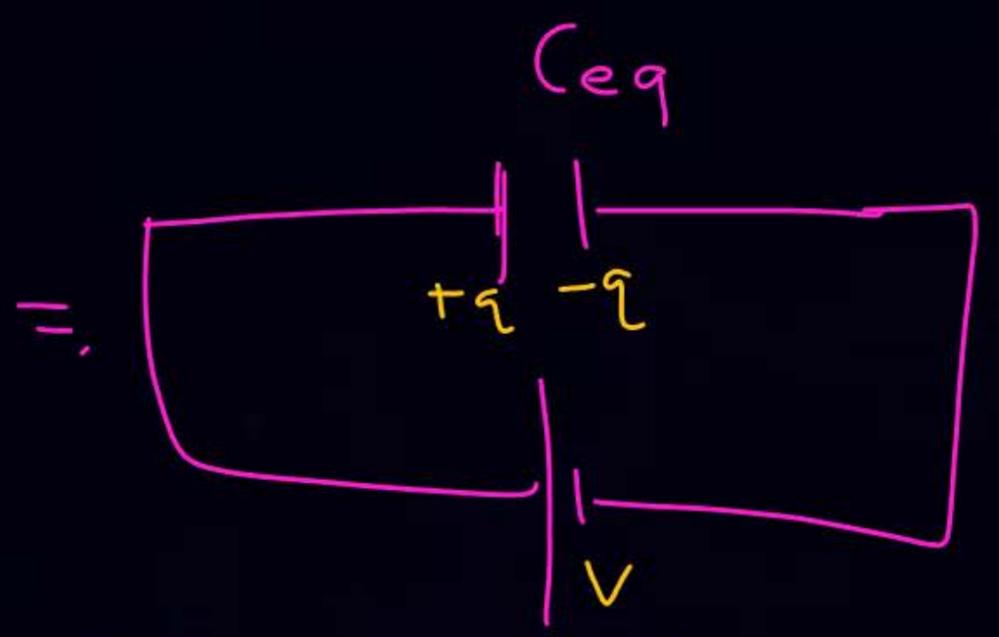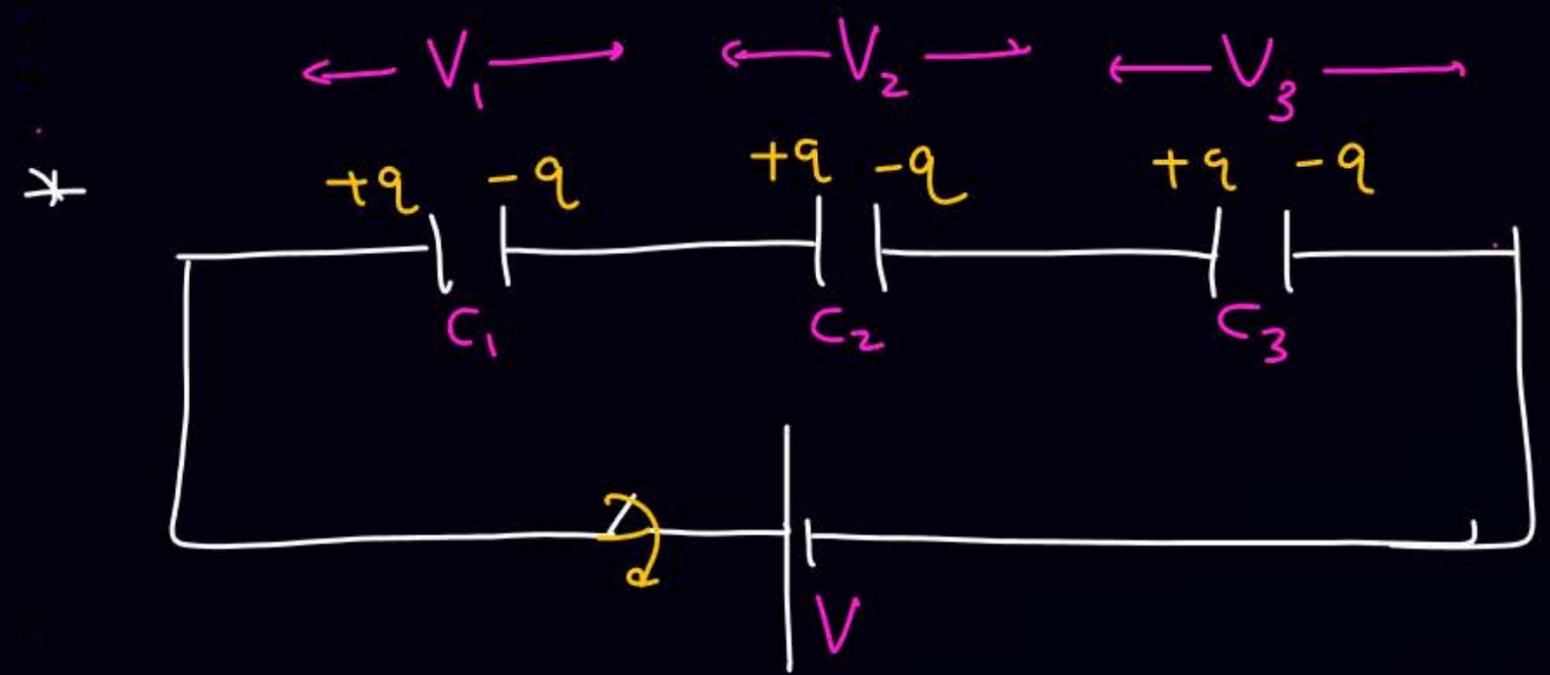


$$V = V_1 + V_2 + V_3 = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3} = \frac{q}{C_{eq}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

$$V = \frac{q}{C_{eq}}$$

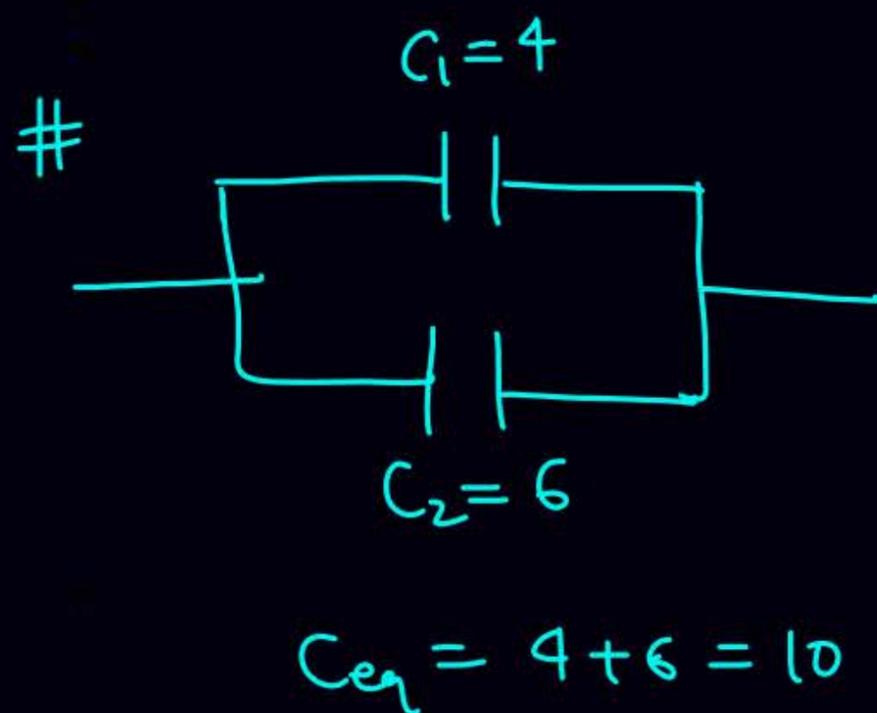


#

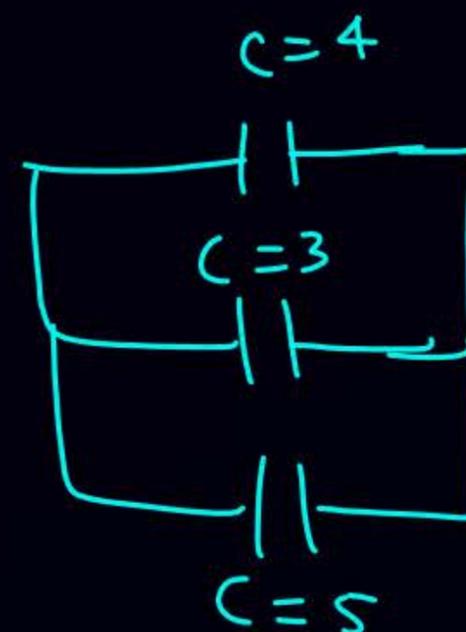


$C_{eq} = 12$

ATDB.uno


#

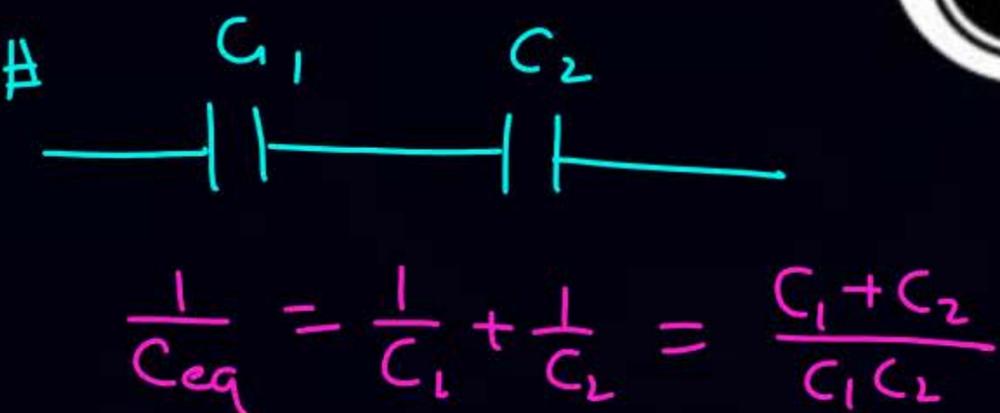

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

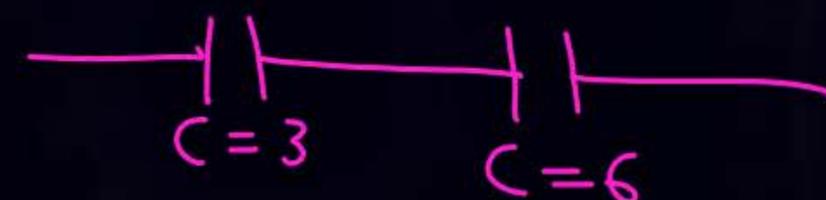

$$C_{eq} = \frac{18}{9} = 2$$

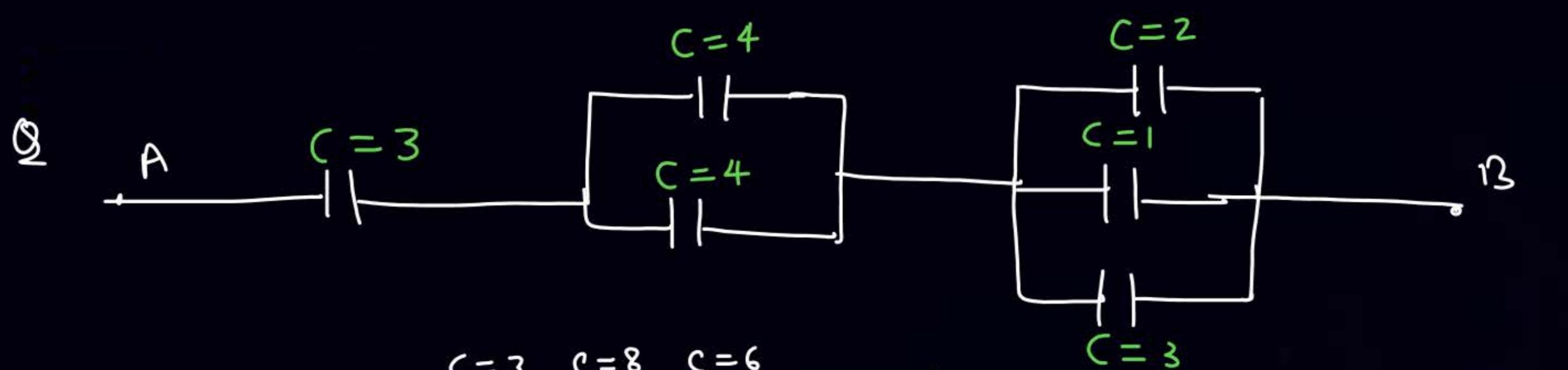

$(C_{eq})_{AB} = ?$





$C_{eq} = \frac{2 \times 8}{2 + 8} = 1.6$

ATDB.uno


Same

Q

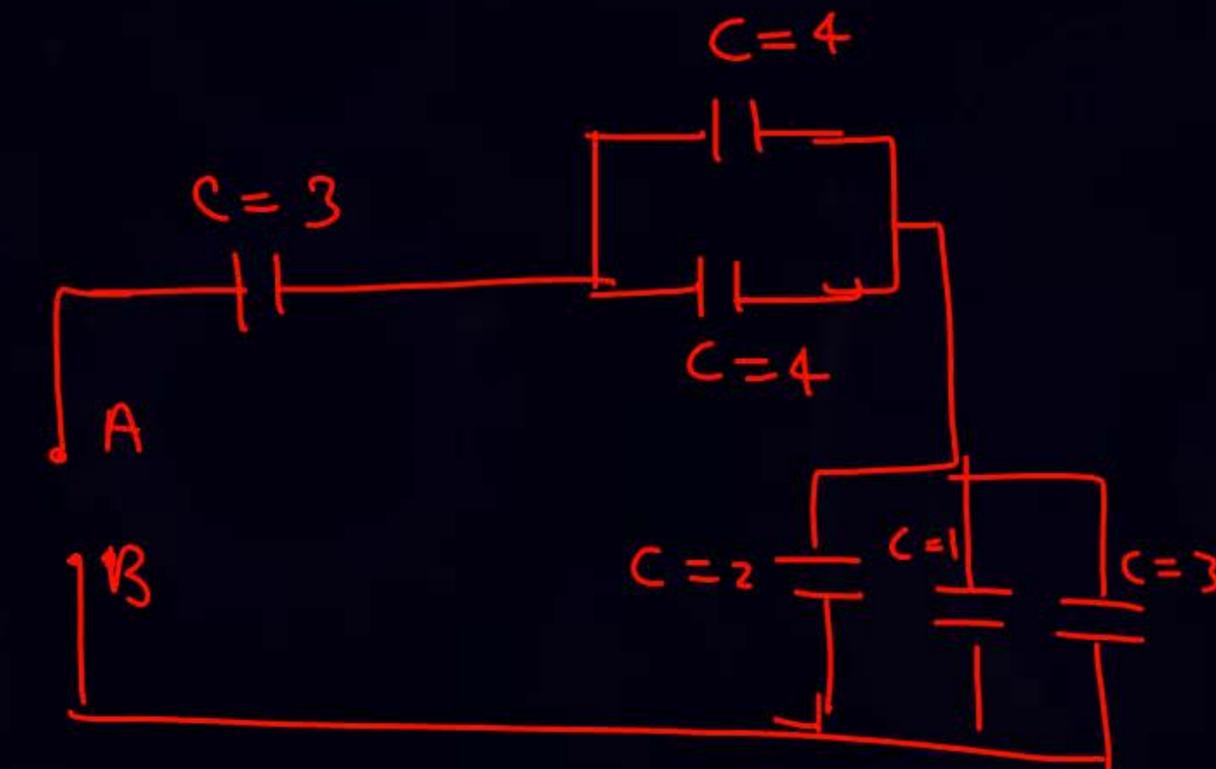


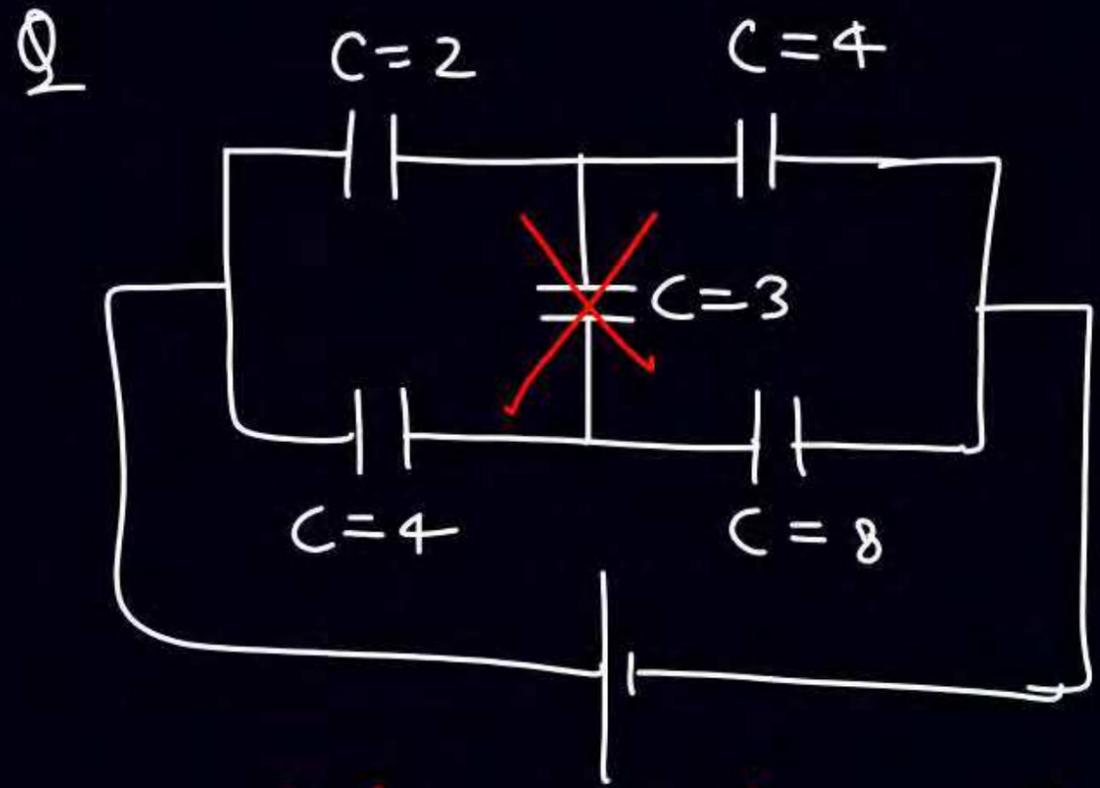

Balance wheatstone ✓

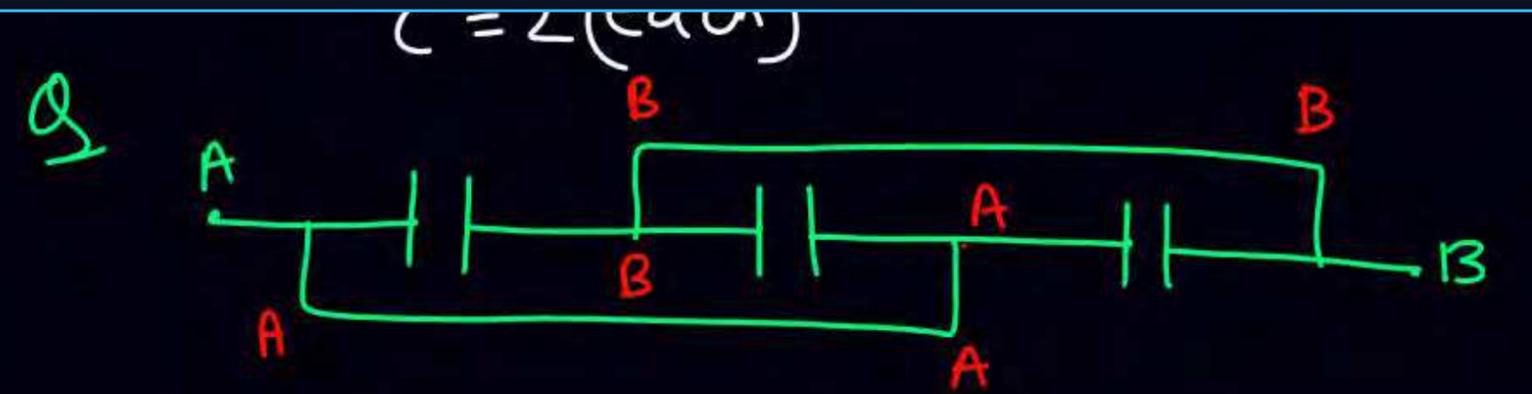


$C_{AB} = ?$

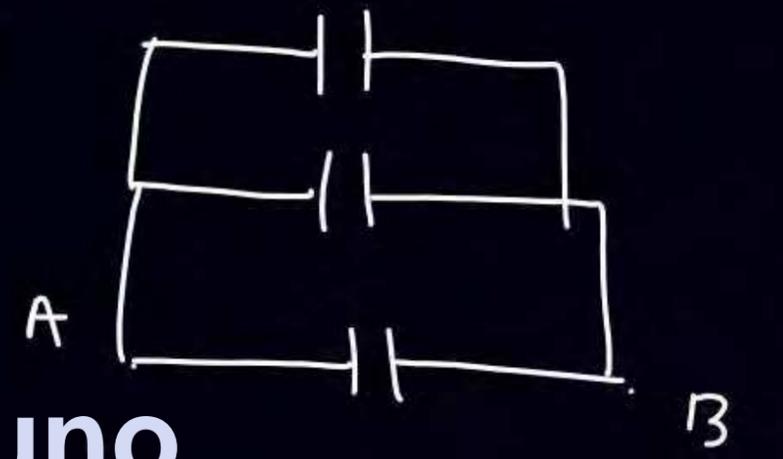


$C_{AB} = 2 + 2 + 2$


ATDB.uno

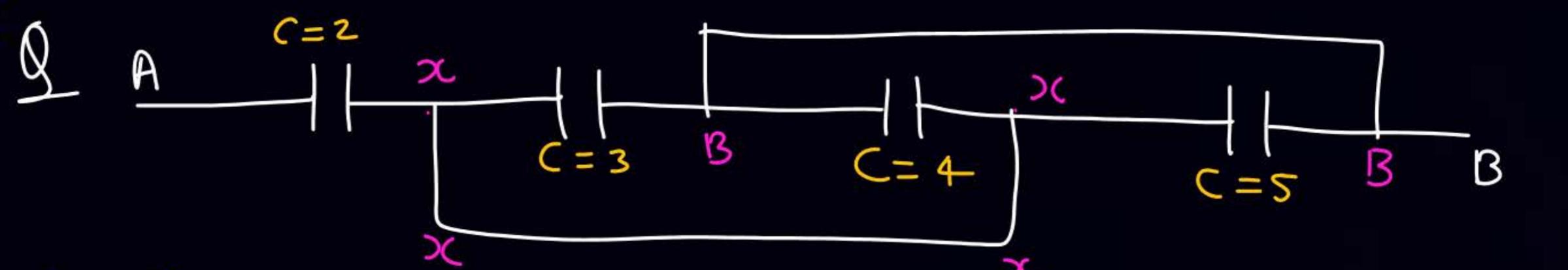


$C_{AB} = ?$


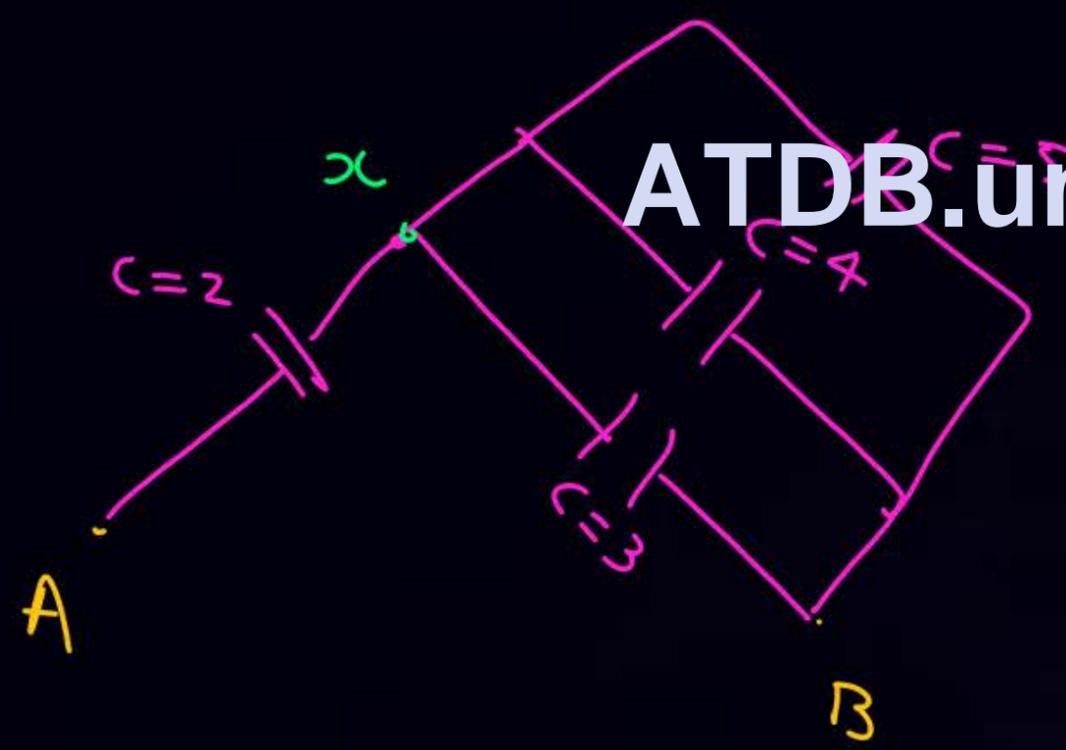


$$C_{AB} = \frac{24}{14}$$

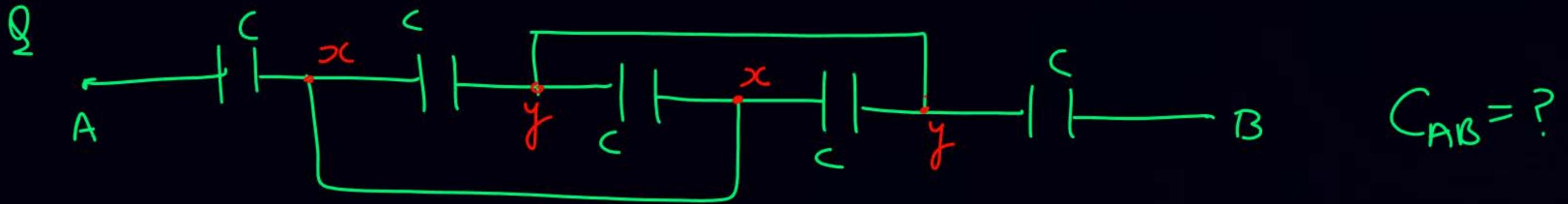

ATDB.uno

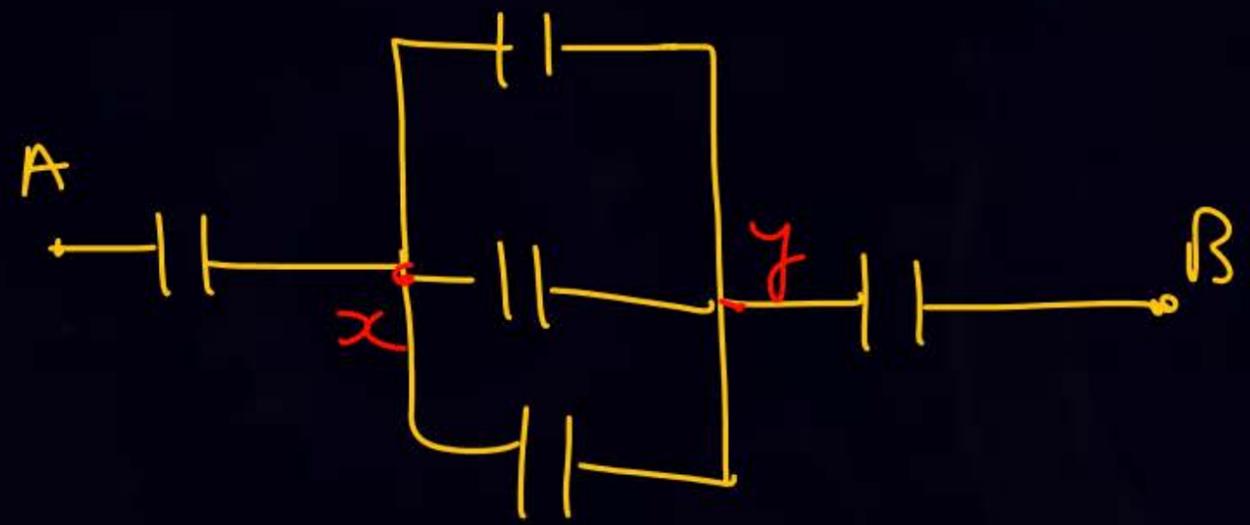


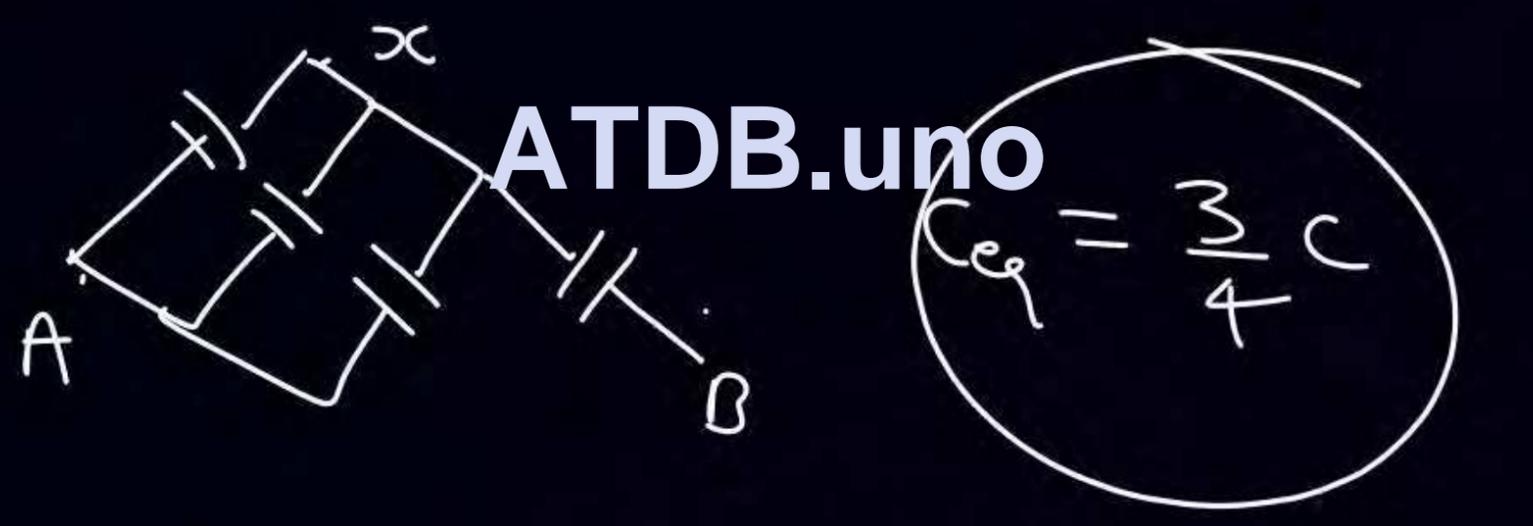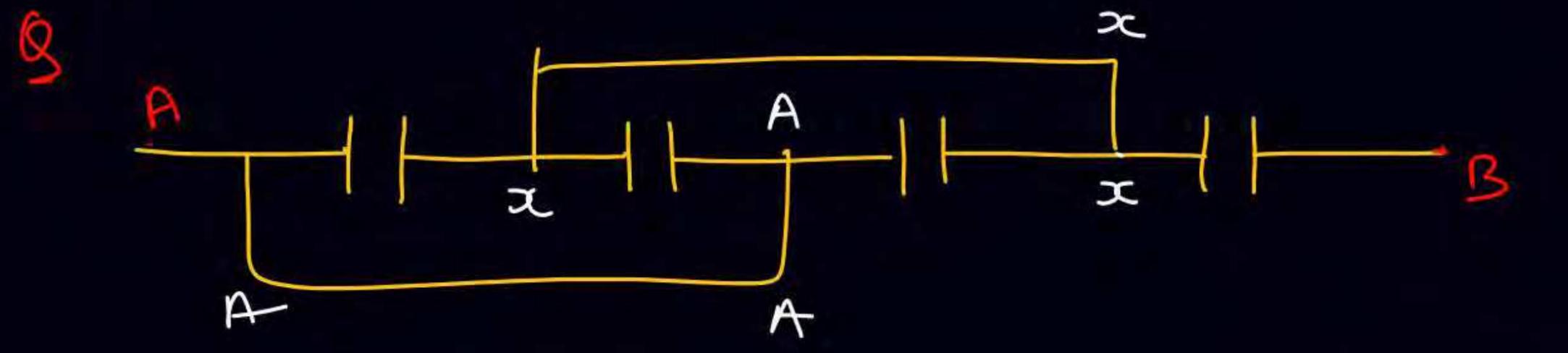


ATDB.uno



∞ Ladder

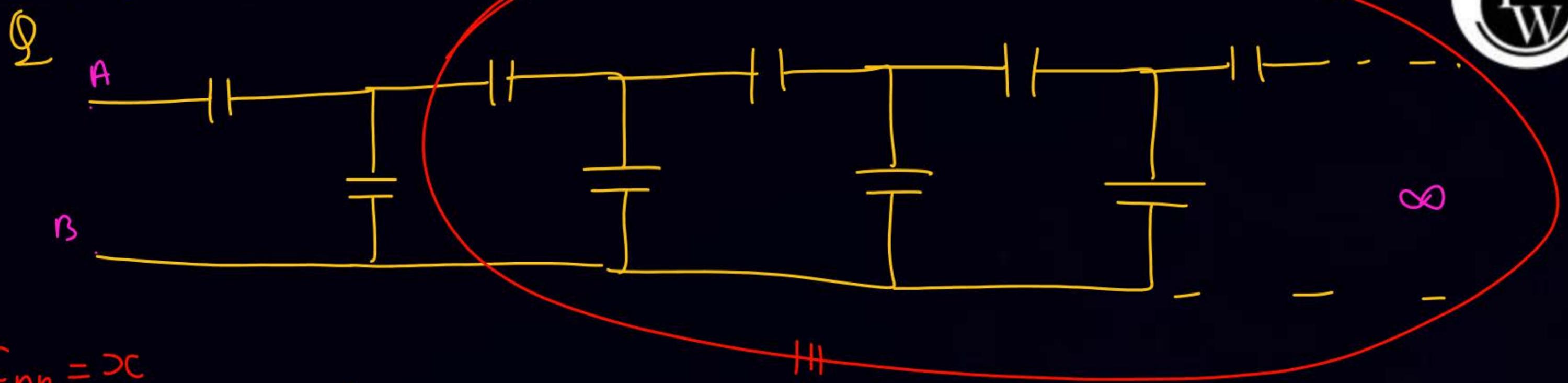

$C_{AB} = x$

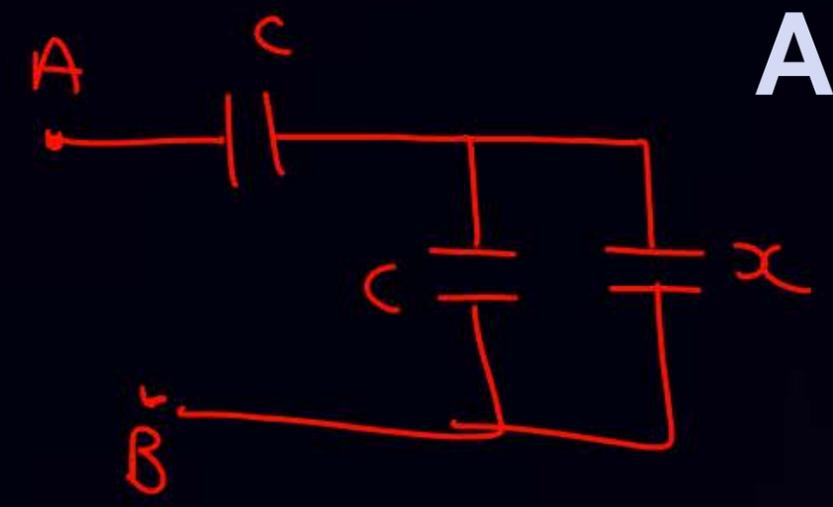

ATDB.uno

$$C_{AB} = \frac{(C+x) \cdot C}{(C+x) + C} = x$$


$$C^2 + xC = x(C+x) + Cx$$

$$x^2 + xC - C^2 = 0$$


$$x = \frac{-C + \sqrt{5C^2}}{2}$$




(parallel plate cap.)

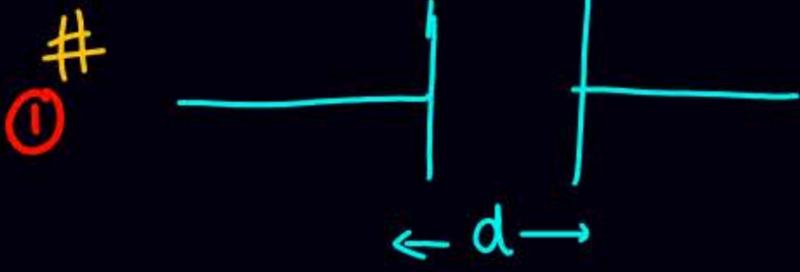


$$C = \frac{A \epsilon_0}{d}$$

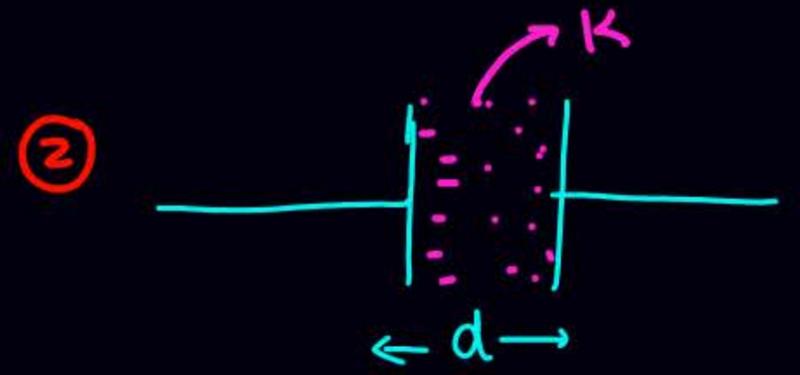
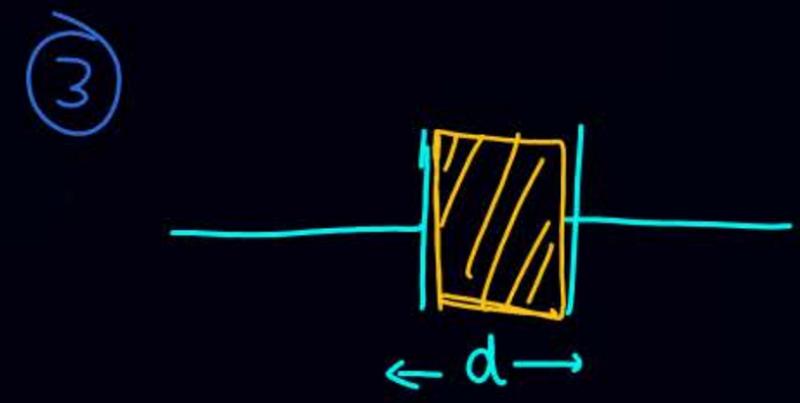
$$C_{\text{now}} = \frac{A \epsilon_0 K}{d} = KC$$


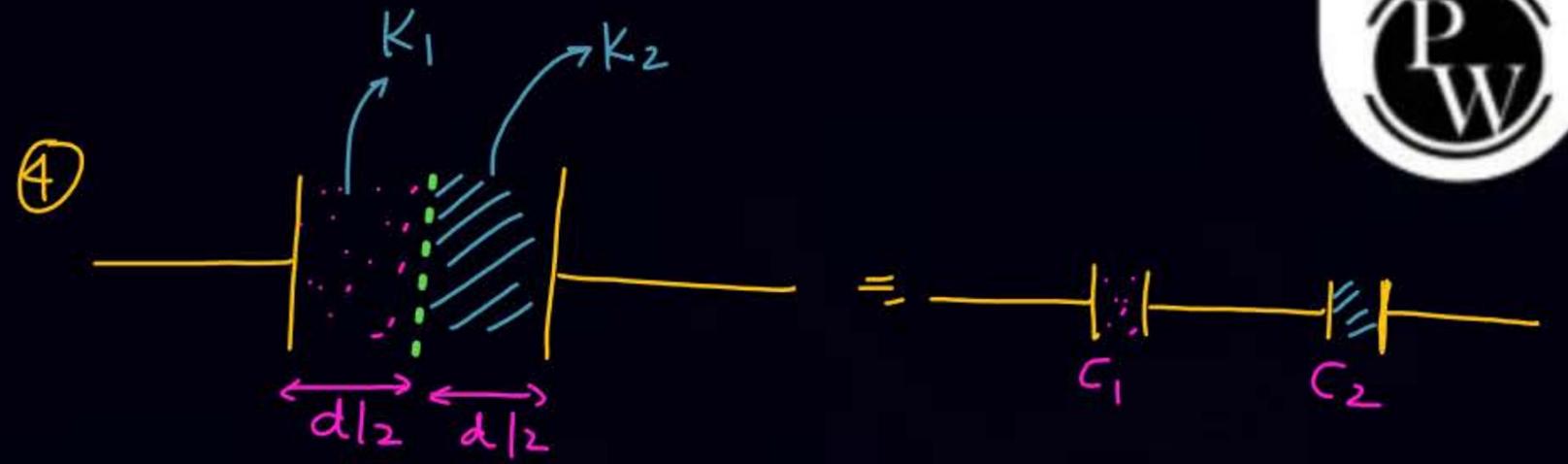
$$C_{\text{now}} = \frac{A \epsilon_0 K}{d} = KC$$



$$C_1 = \frac{A \epsilon_0 K_1}{(d/2)}$$

$$C_2 = \frac{A \epsilon_0 K_2}{(d/2)}$$


$$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$$

ATDB.uno



$$C_1 = \frac{A \epsilon_0 K_1}{d/3}$$

$$C_2 = \frac{A \epsilon_0 K_2}{2d/3}$$

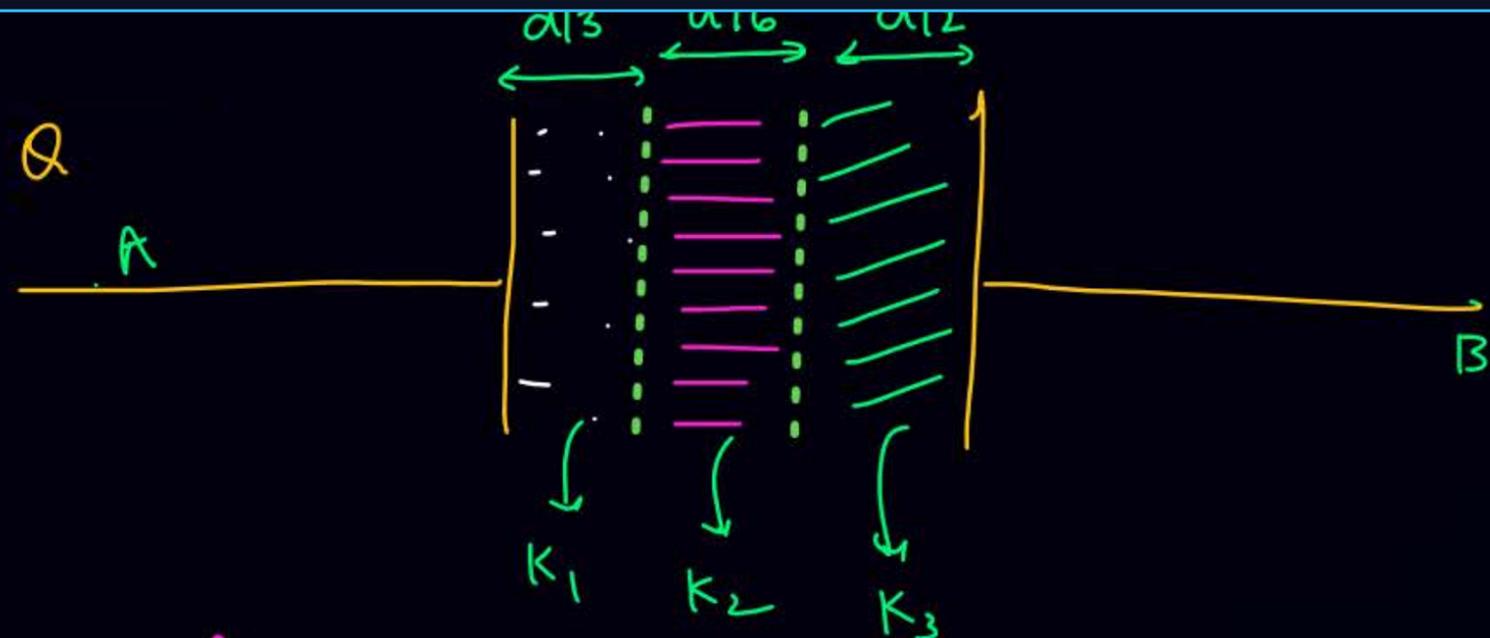


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_1 = \frac{A \epsilon_0 K_1}{d/3}$$

$$C_2 = \frac{A \epsilon_0 K_2}{d/6}$$


$$C_3 = \frac{A \epsilon_0 K_3}{d/2}$$

ATDB.uno

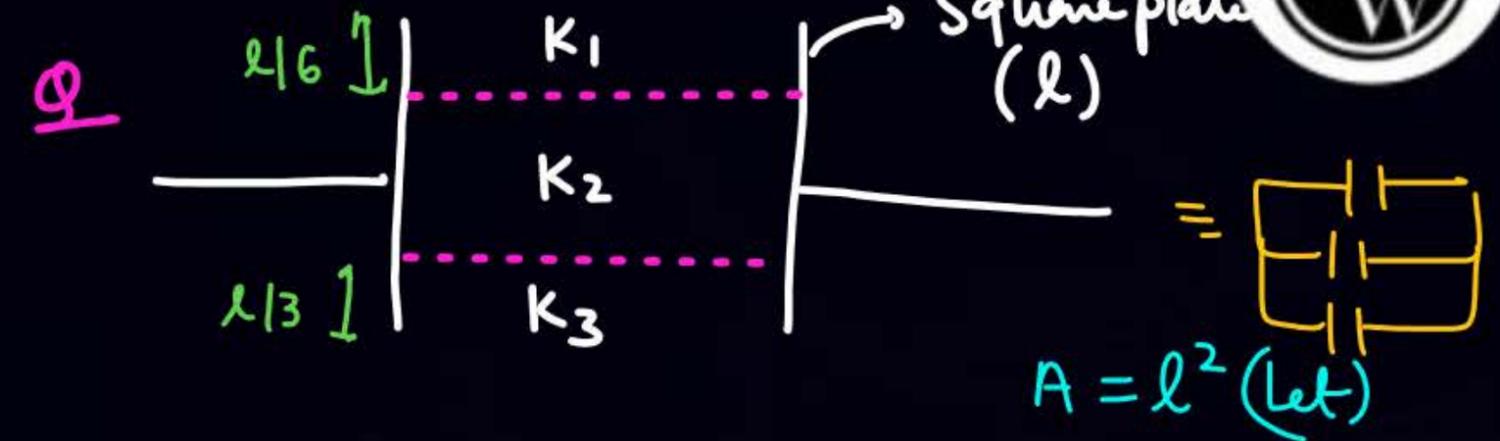


$$C_{eq} = C_1 + C_2 + C_3$$
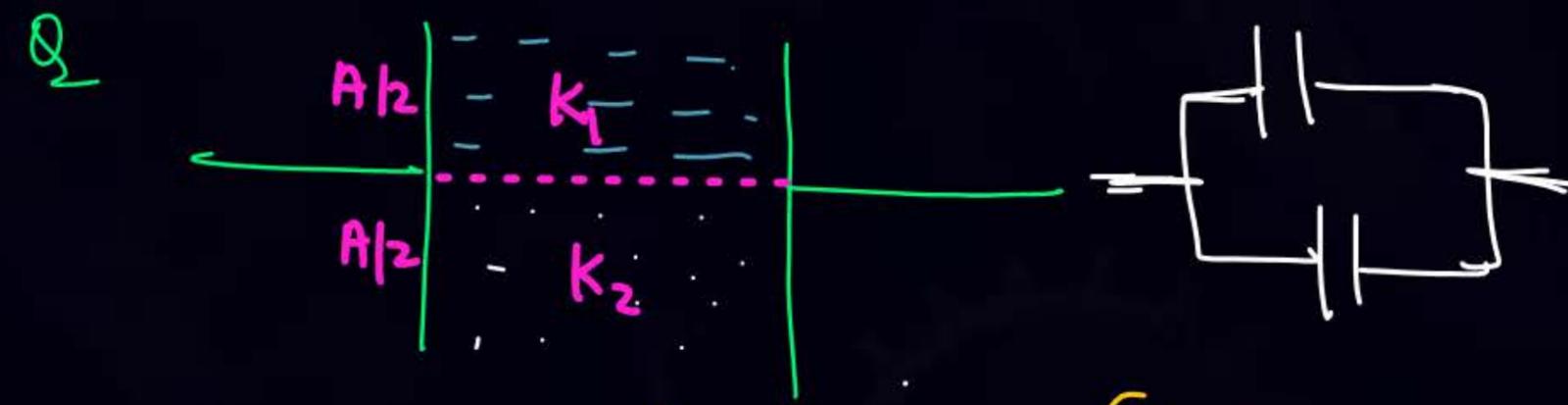
$$= \frac{\frac{A}{6} \epsilon_0 K_1}{d} + \frac{\frac{A}{2} \epsilon_0 K_2}{d} + \frac{\frac{A}{3} \epsilon_0 K_3}{d}$$


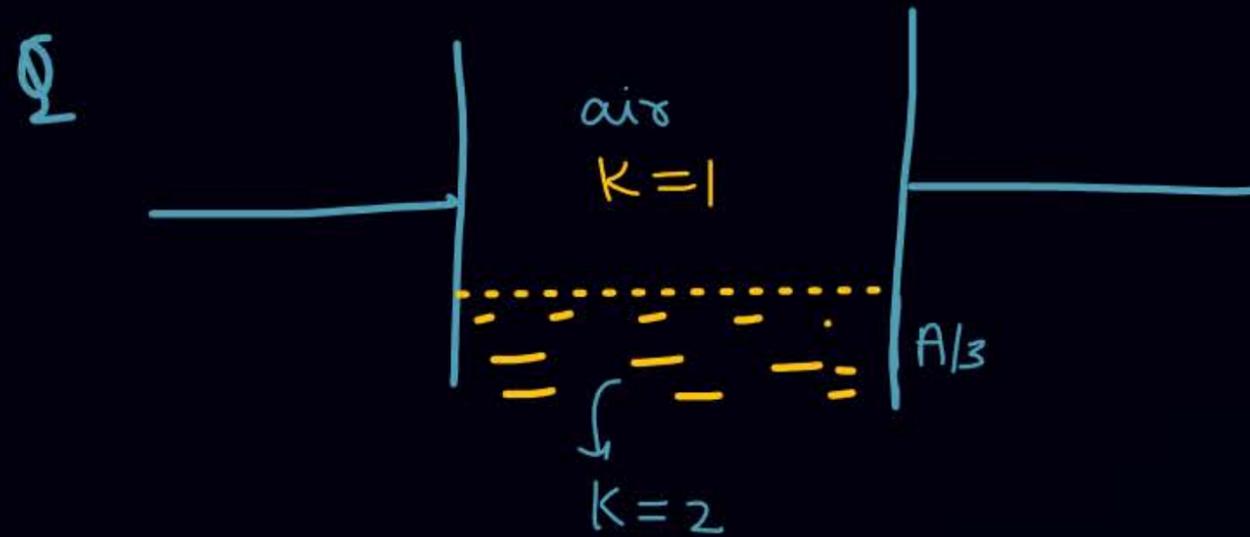
$$C_{eq} = C_1 + C_2 = \frac{(A/2) \epsilon_0 K_1}{d} + \frac{(A/2) \epsilon_0 K_2}{d}$$





$$C_{eq} = C_1 + C_2 = \frac{\frac{2A}{3} \epsilon_0}{d} + \frac{(A/3) \epsilon_0 \times 2}{d}$$

ATDB.uno

केसम Qus JEE

Q

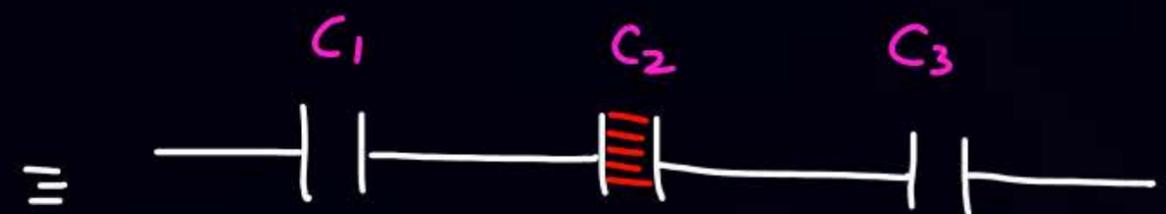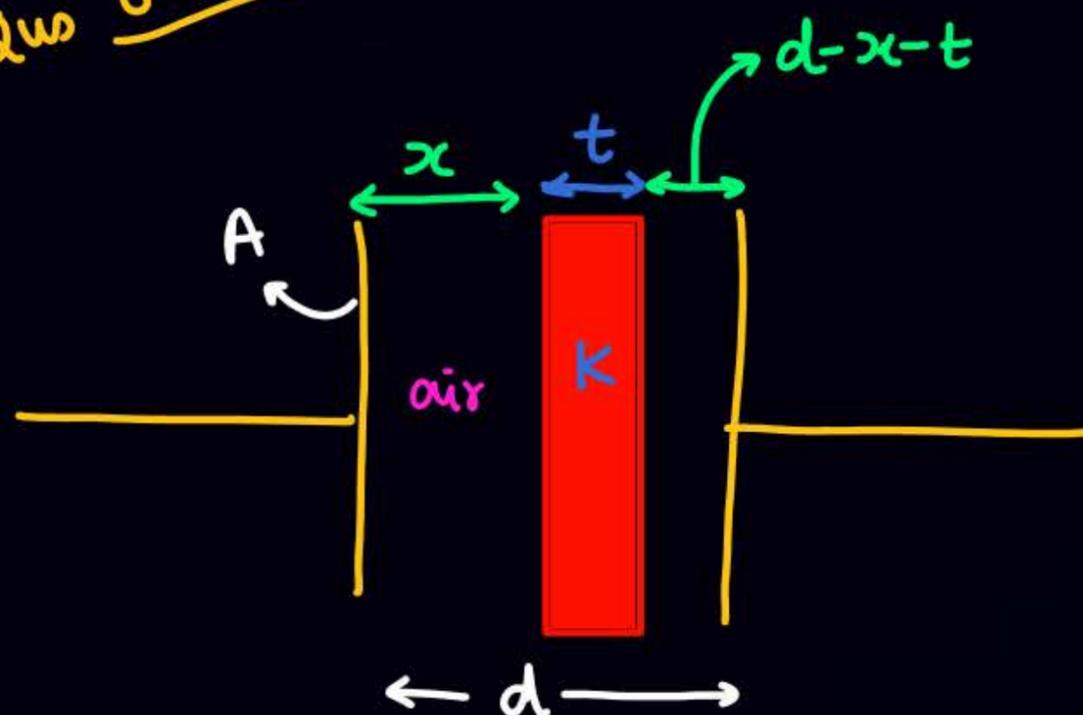


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

ATDB.uno

$$\frac{1}{C_{eq}} = \frac{1}{\left(\frac{A\epsilon_0}{x}\right)} + \frac{1}{\frac{A\epsilon_0 K}{t}} + \frac{1}{\frac{A\epsilon_0}{(d-x-t)}} = \frac{1}{A\epsilon_0} \left[\cancel{x} + \frac{t}{K} + d - \cancel{x} - t \right]$$
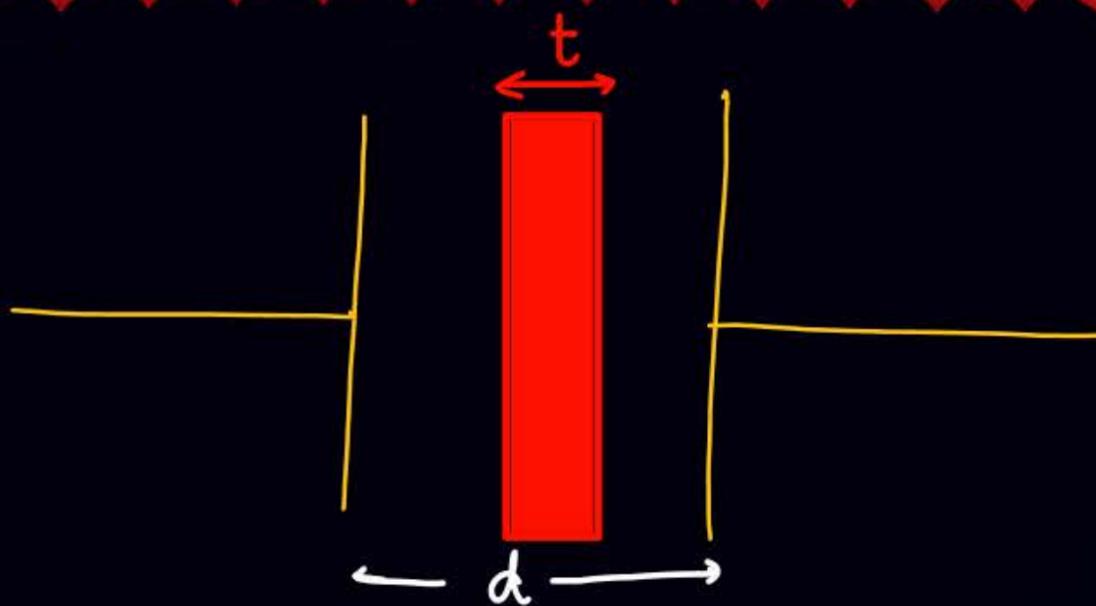
$$C_{eq} = \frac{A\epsilon_0}{\frac{t}{K} + d - t} = \frac{A\epsilon_0}{d - t \left(1 - \frac{1}{K}\right)}$$



$$C = \frac{A\epsilon_0}{d - t \left(1 - \frac{1}{k}\right)}$$

ATDB.uno

Q Between the parallel plate capacitor of capacitance C , (plate area A & distance b/w plate is d) a dielectric slab of dielectric const $k=3$ is inserted as shown in daigram.

If thickness of slab is $\frac{d}{4}$ find

Ratio of $\frac{C_{new}}{C_{old}} = ?$

A diagram of a parallel plate capacitor with a dielectric slab. The distance between the plates is 'd' and the thickness of the dielectric slab is 'd/4'.

Solⁿ

$$\frac{C_{new}}{A\epsilon_0/d} = \frac{C_{new}}{C_{old}} = \frac{12}{12-3+1} = \frac{12}{10} = \frac{6}{5}$$

$$C_{new} = \frac{A\epsilon_0}{d - \frac{d}{4} \left(1 - \frac{1}{3}\right)} = \frac{A\epsilon_0}{d \left[1 - \frac{1}{4} + \frac{1}{12}\right]}$$




$$C_1 = \frac{(A/2) \epsilon_0 k_1}{d/2}$$

$$C_2 = \frac{(A/2) \epsilon_0 k_2}{d/2}$$

ATDB.uno

$$C_3 = \frac{(A/2) \epsilon_0 k_3}{d}$$

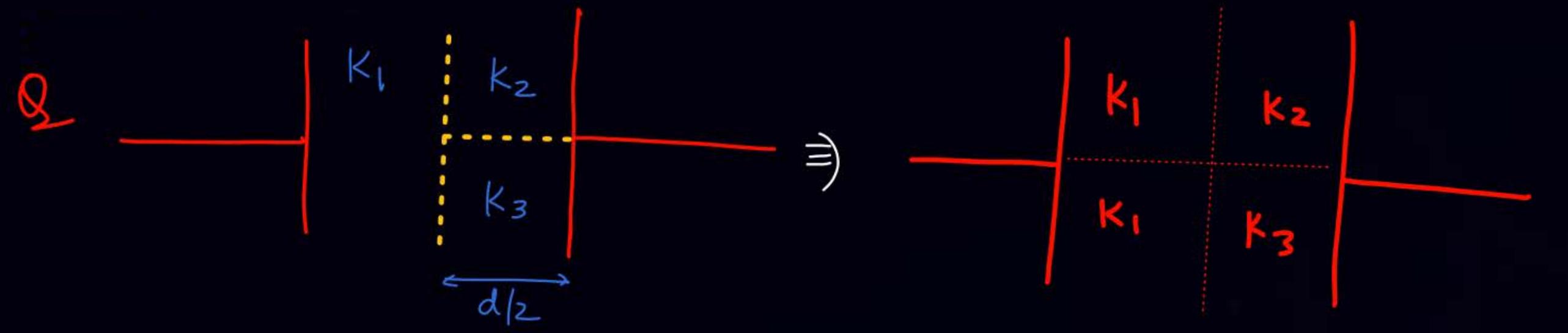

ATDB.uno

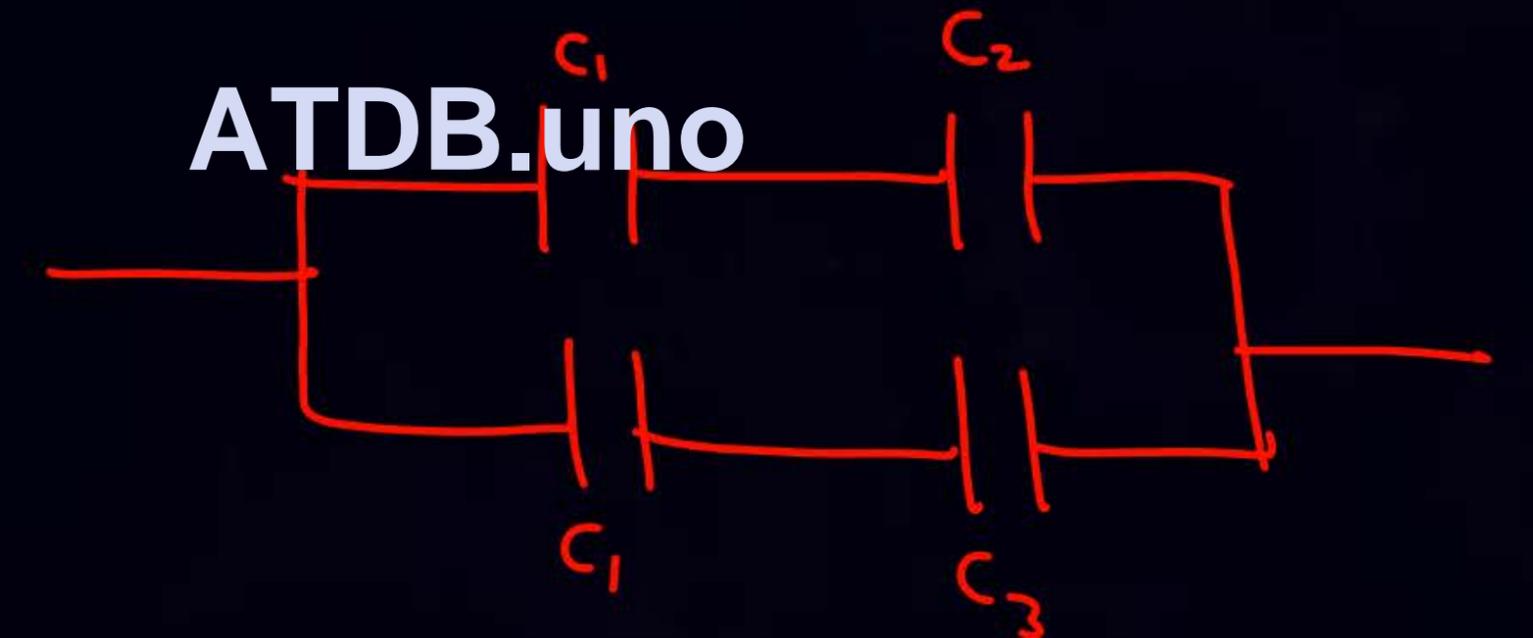
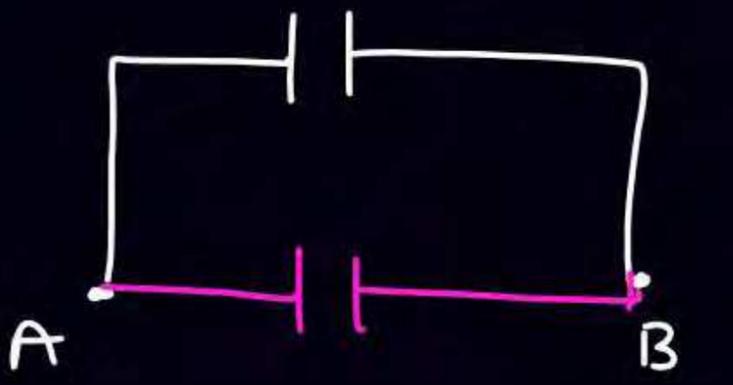


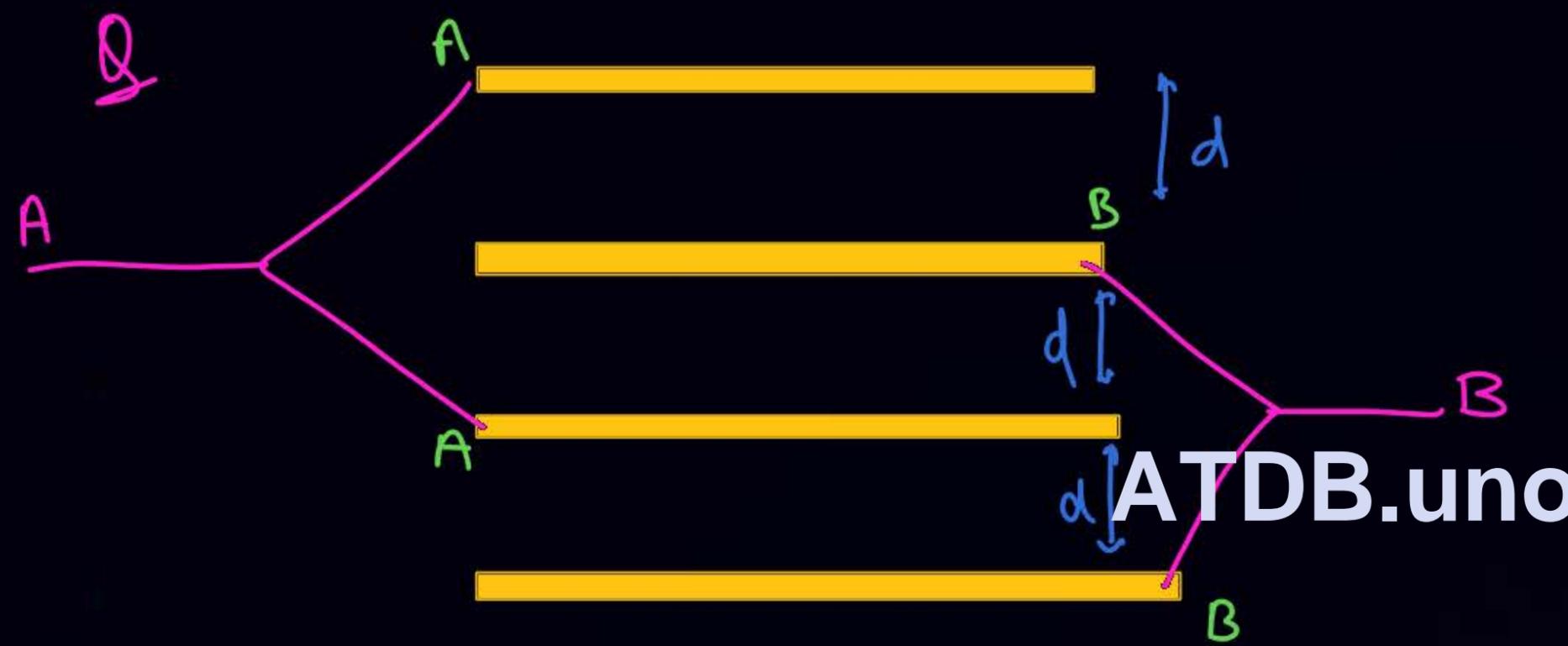


plate वाले Ques




ATDB.uno





ATDB.uno

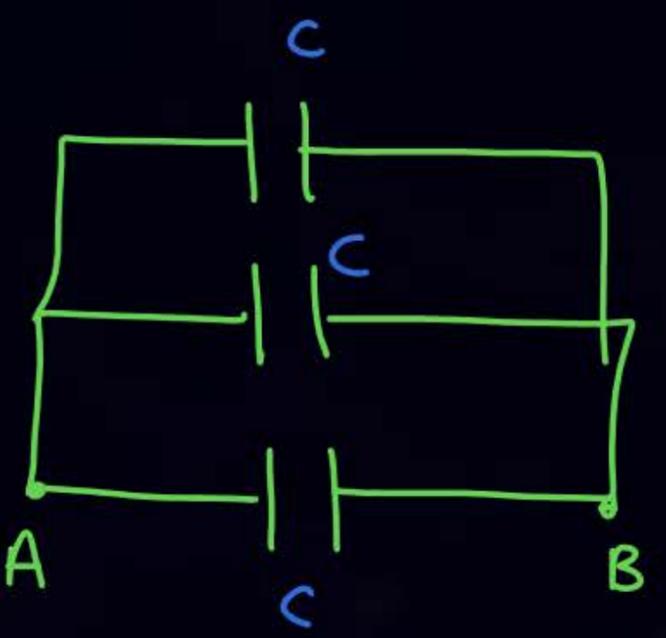


$$C = \frac{A\epsilon_0}{d}, \quad C_{eq} = 3C$$




$$C = \frac{A\epsilon_0}{d}$$





ATDB.uno

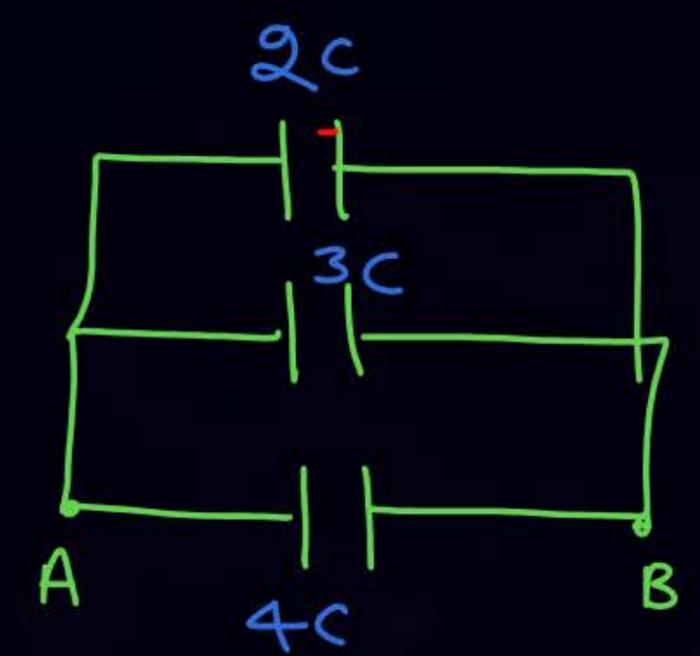
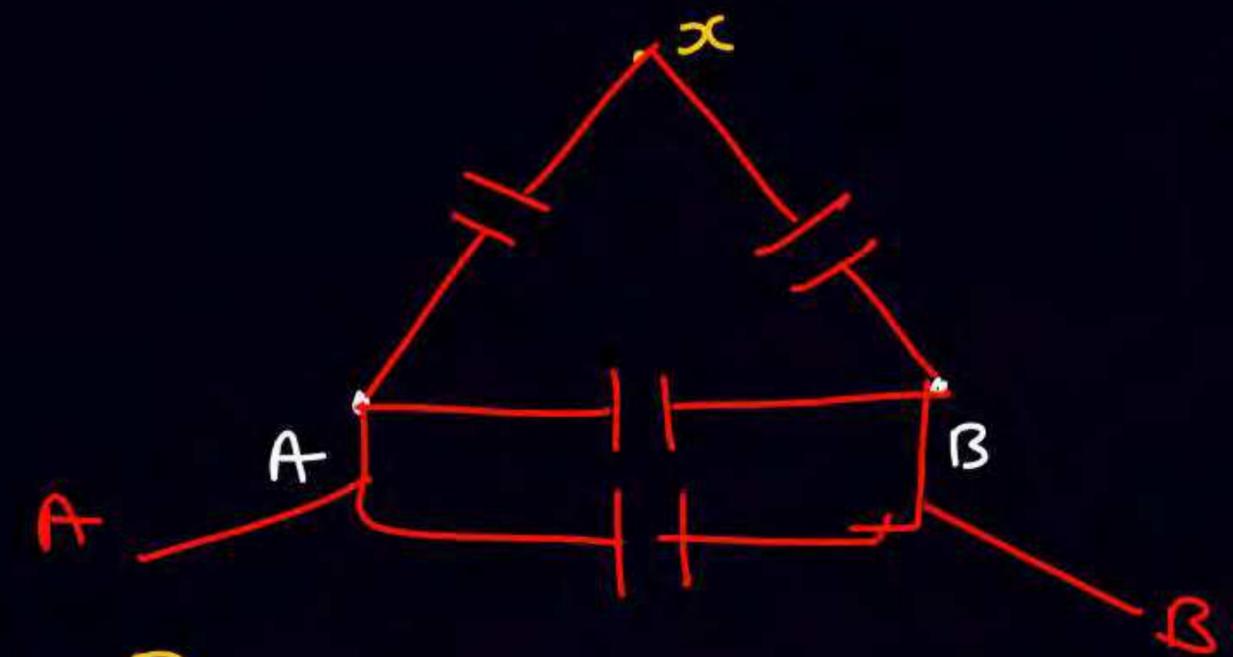
$$C = \frac{A\epsilon_0}{d}, \quad C_{eq} = 9C$$




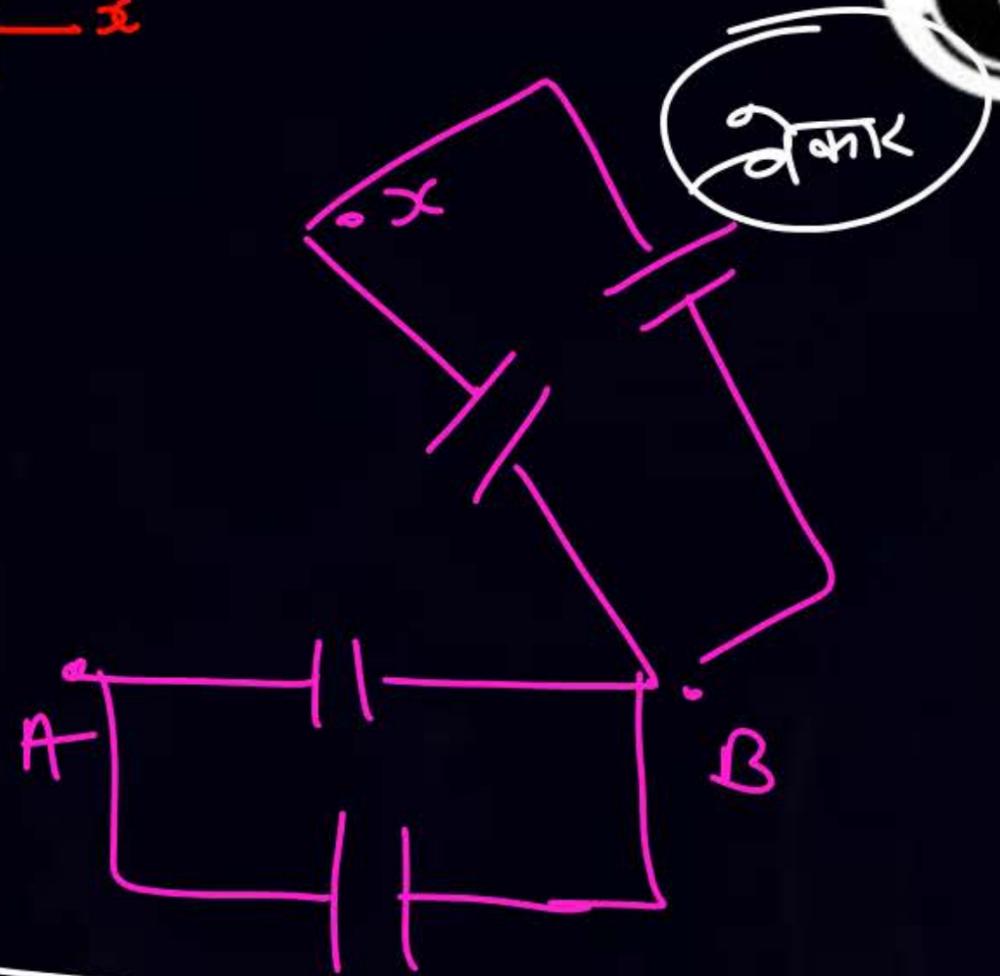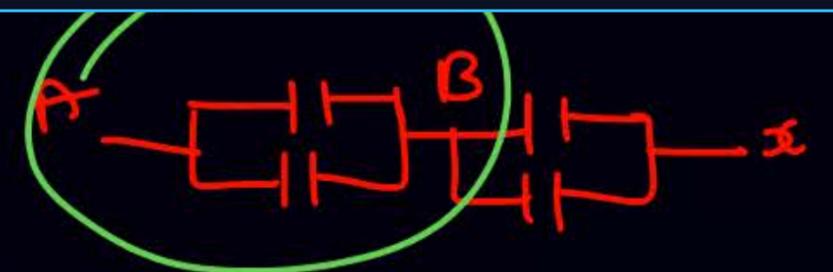


$C_{AB} = ?$

ATDB.uno

$C_{eq} = 2C$

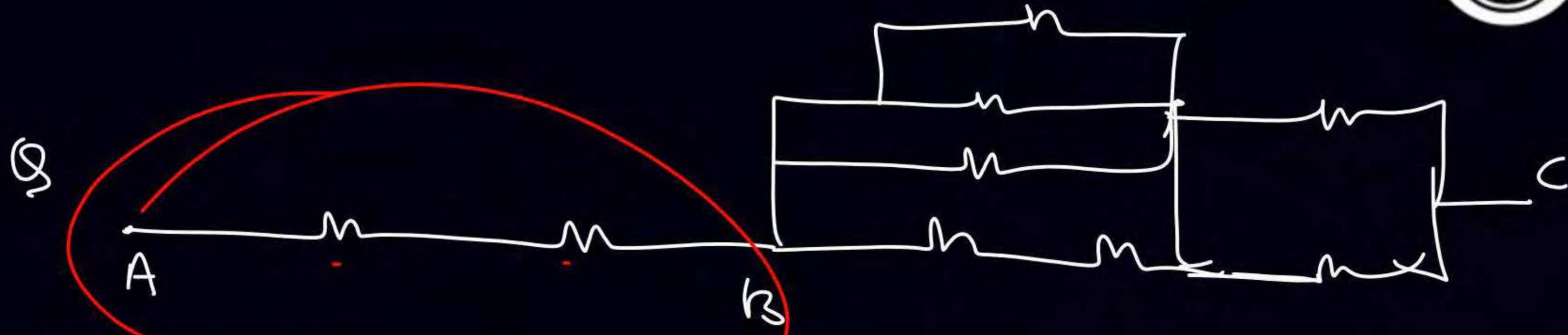

ATDB.uno

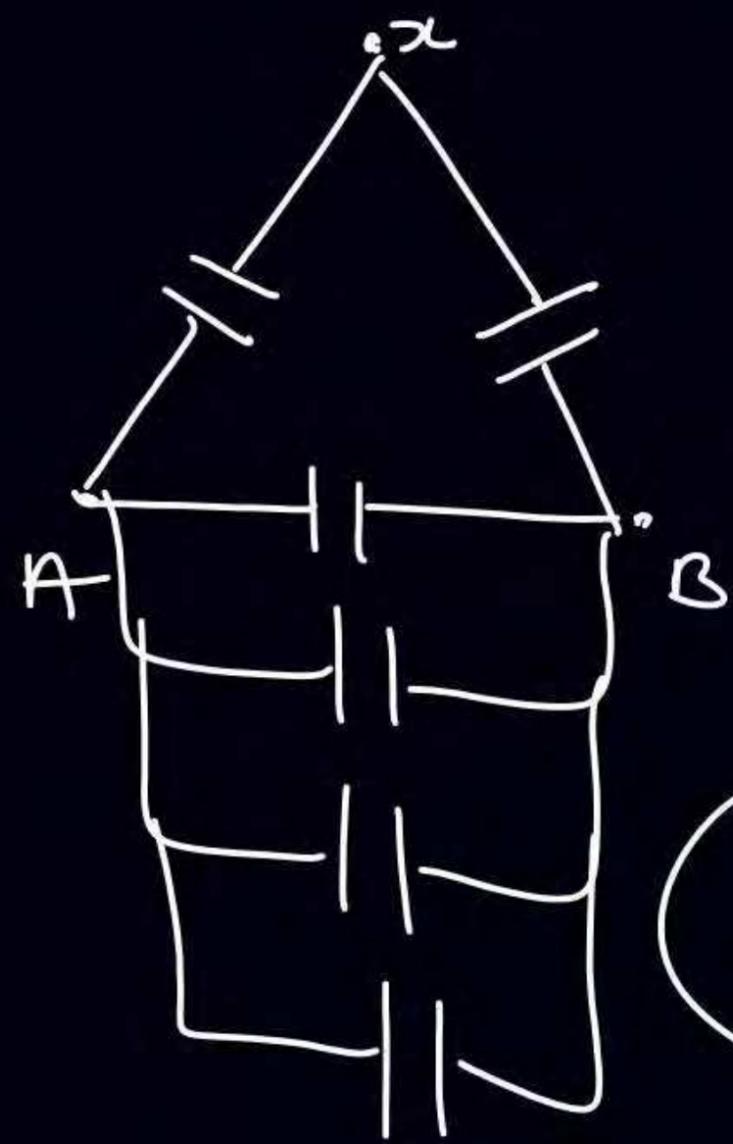

$$C_{eq} = 4.5C$$



ATDB.uno





$$\frac{A \parallel B}{2} = C$$




20

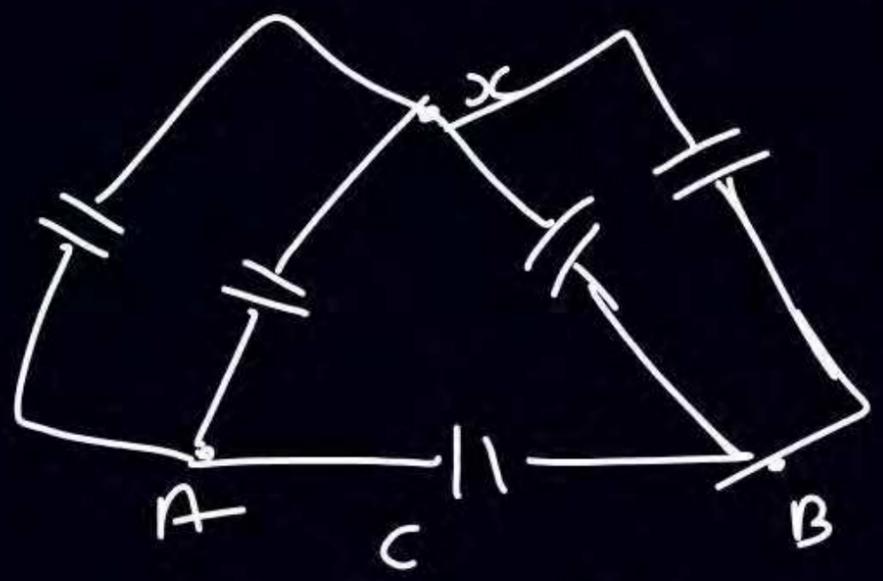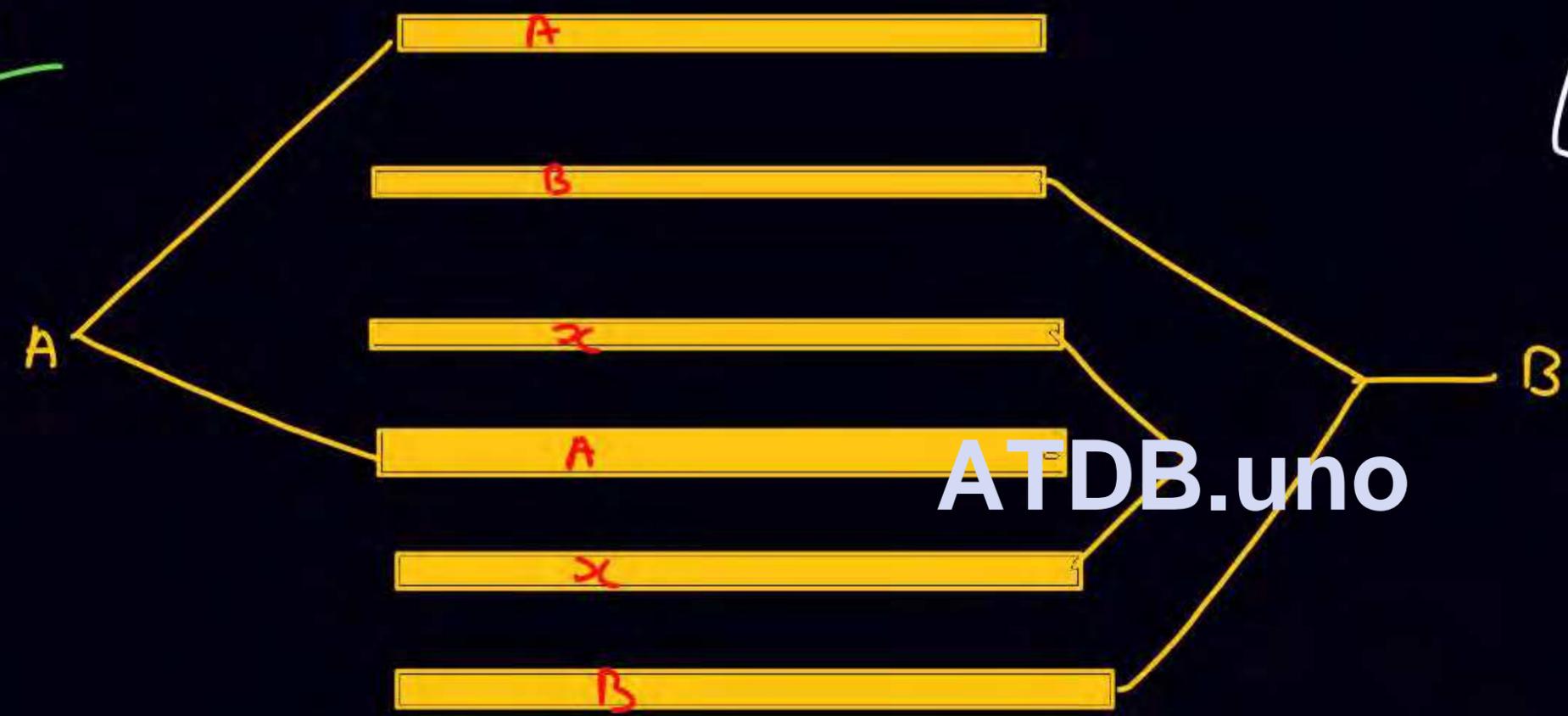

$$C_{eq} = 2C$$

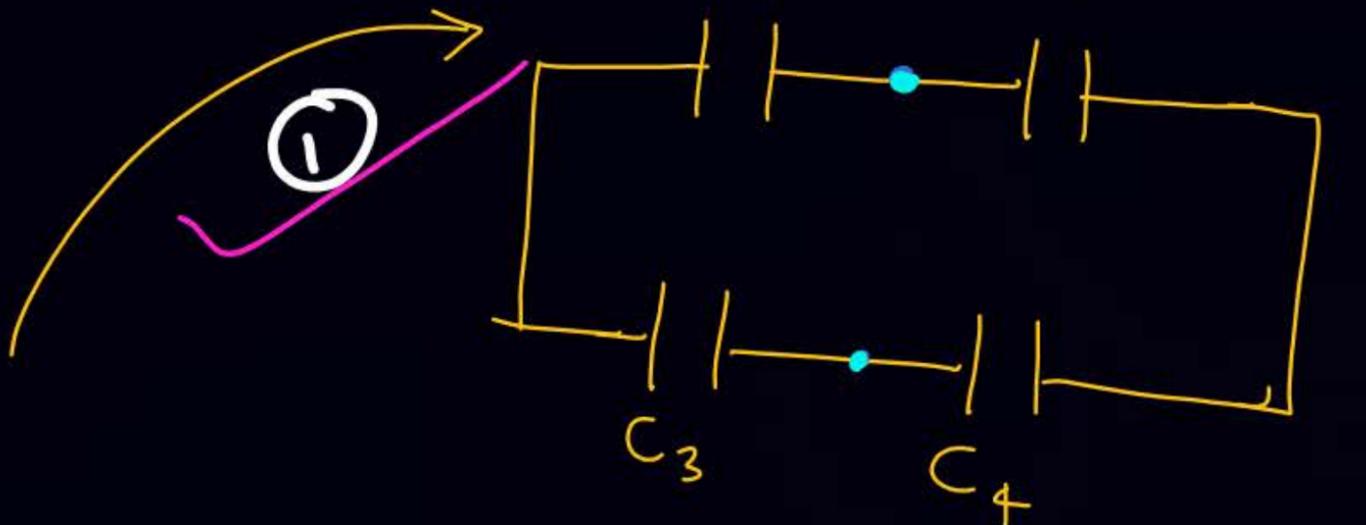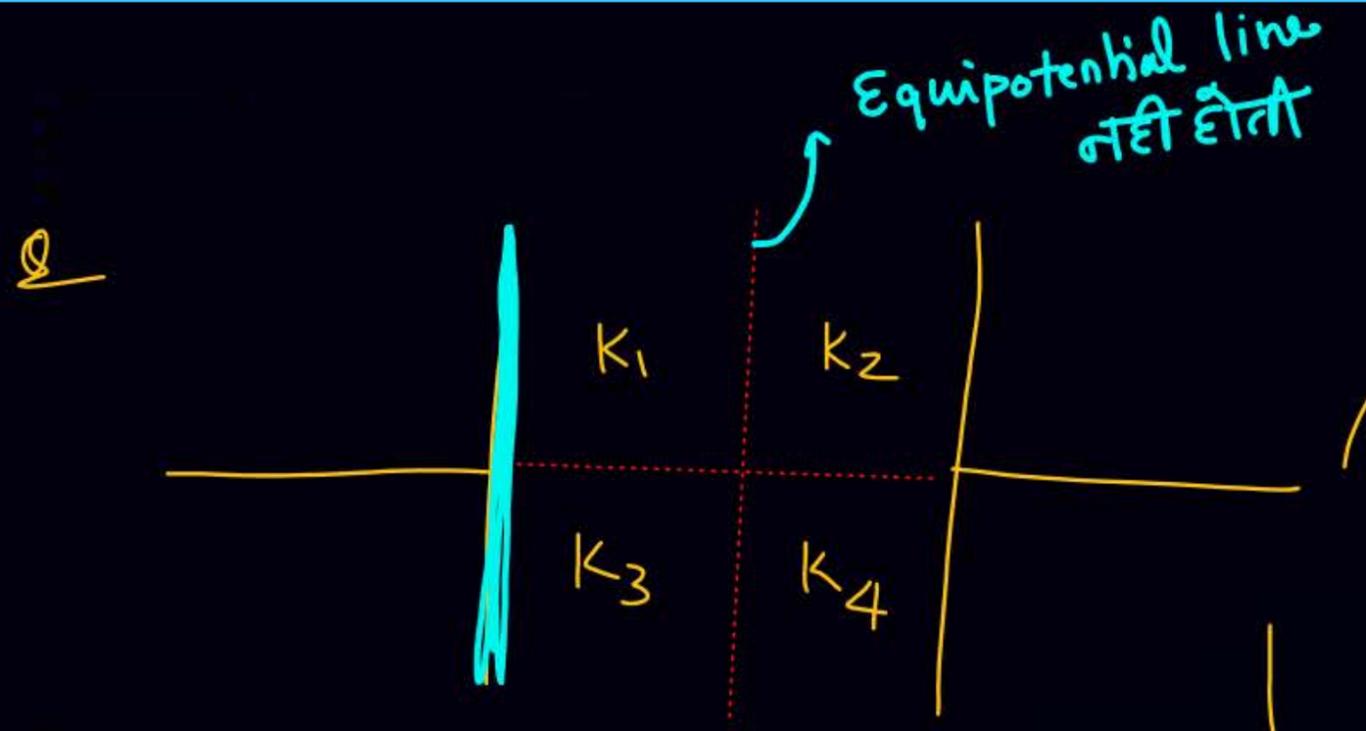

ATDB.uno

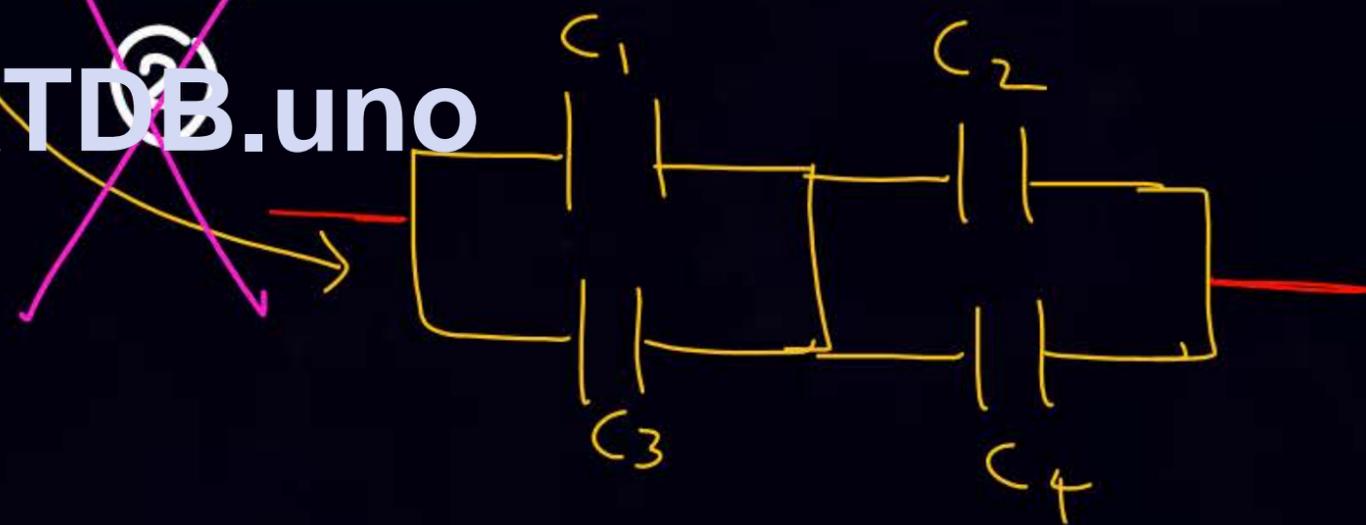



If two appliances with rating (w_1, V) & (w_2, V) are connected to 'V'

① In parallel \Rightarrow Total power dissipated = $w_1 + w_2$

② In series \Rightarrow " " " = w_{net} then $\frac{1}{w_{net}} = \frac{1}{w_1} + \frac{1}{w_2}$


ATDB.uno

$$** \quad P_{net} = \frac{V^2}{R_{eq}} \quad , \quad P_{net} = i^2 R_{eq}$$

Dissipated Dissipated



Q find $R_{eq} = ?$

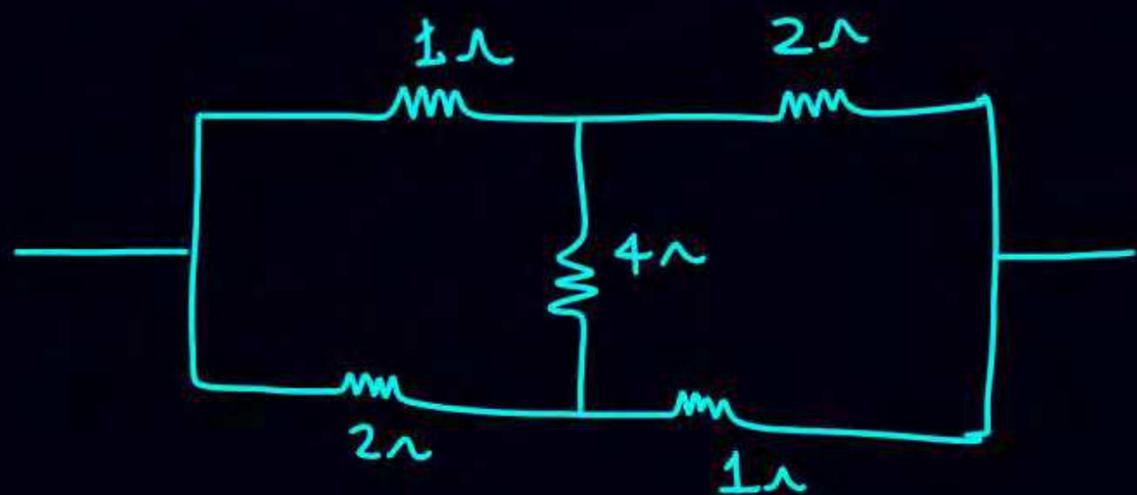

ATDB.uno


QUESTION -



In the circuit shown in the figure, the total charge is $750 \mu\text{C}$ and the voltage across capacitor C_2 is 20 V . Then the charge on capacitor C_2 is: **[JEE Mains-2020]**

- 1 $590 \mu\text{C}$
- 2 $450 \mu\text{C}$
- 3 $650 \mu\text{C}$
- 4 $160 \mu\text{C}$

ATDB.uno

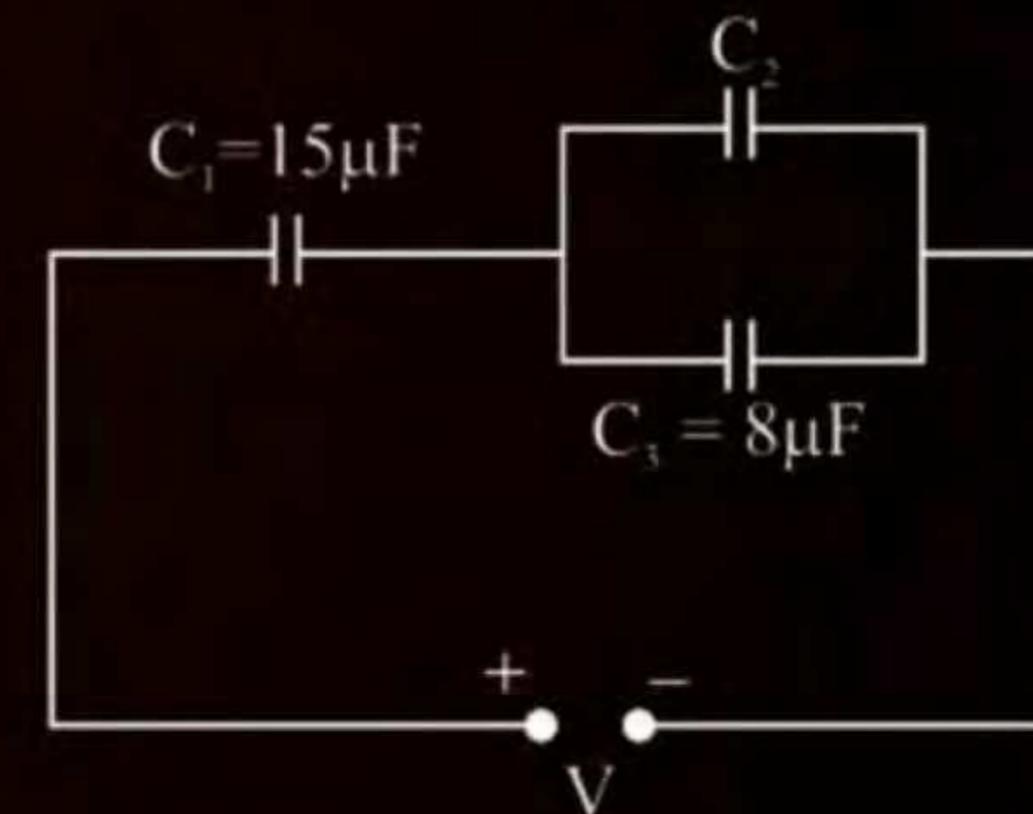

Ans. (1)


**QUESTION -**

In the circuit shown, charge on the $5\mu\text{F}$ capacitor is:

[JEE Mains-2020]

- 1 $5.45\mu\text{C}$
- 2 $16.36\mu\text{C}$
- 3 $10.90\mu\text{C}$
- 4 $18.00\mu\text{C}$

ATDB.uno

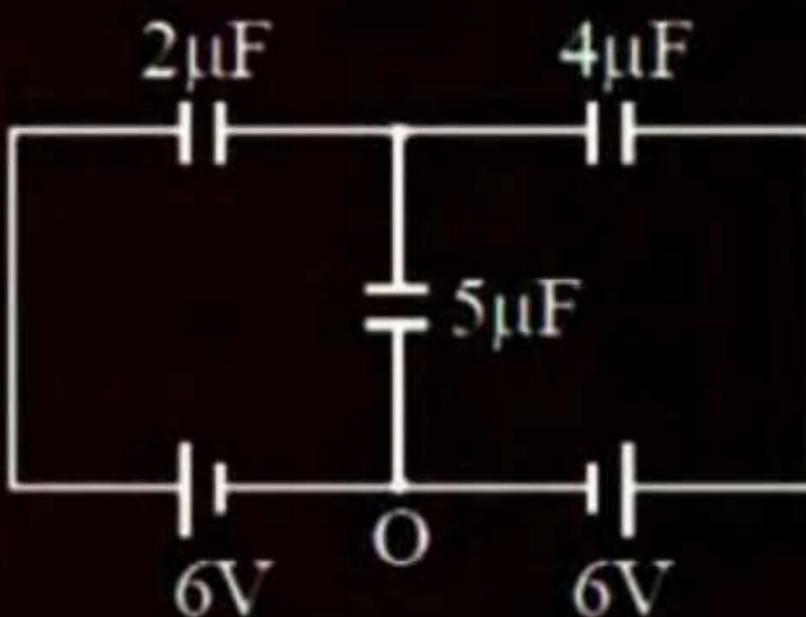


Ans. (2)

QUESTION -



Four identical rectangular plates with length, $l = 2$ cm and breadth, $b = \frac{3}{2}$ cm are arranged as shown in figure. The equivalent capacitance between A and C is $\frac{x\epsilon_0}{d}$. The value of x is _____. (Round off to the Nearest Integer) **[JEE Mains-2021]**


ATDB.uno

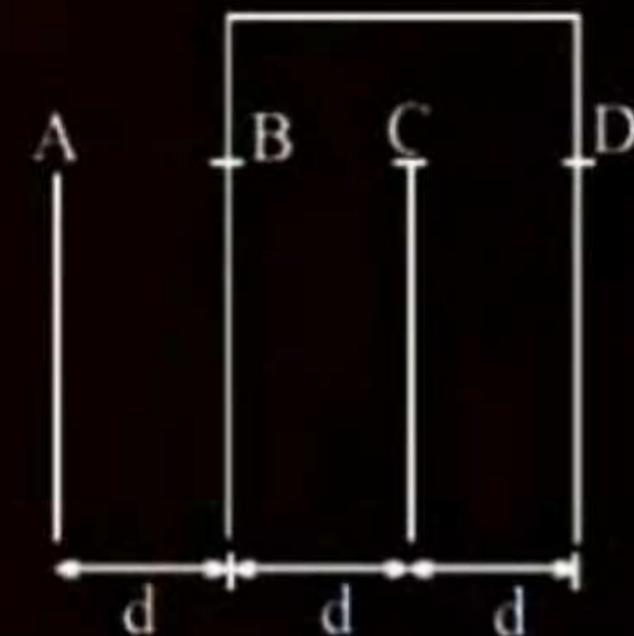

Ans. (2)

QUESTION -

A $2 \mu\text{F}$ capacitor C_1 is first charged to a potential difference of 10 V using a battery. Then the battery is removed and the capacitor is connected to an uncharged capacitor C_2 of $8 \mu\text{F}$. The charge in C_2 on equilibrium condition is _____ μC . (Round off to the Nearest Integer)

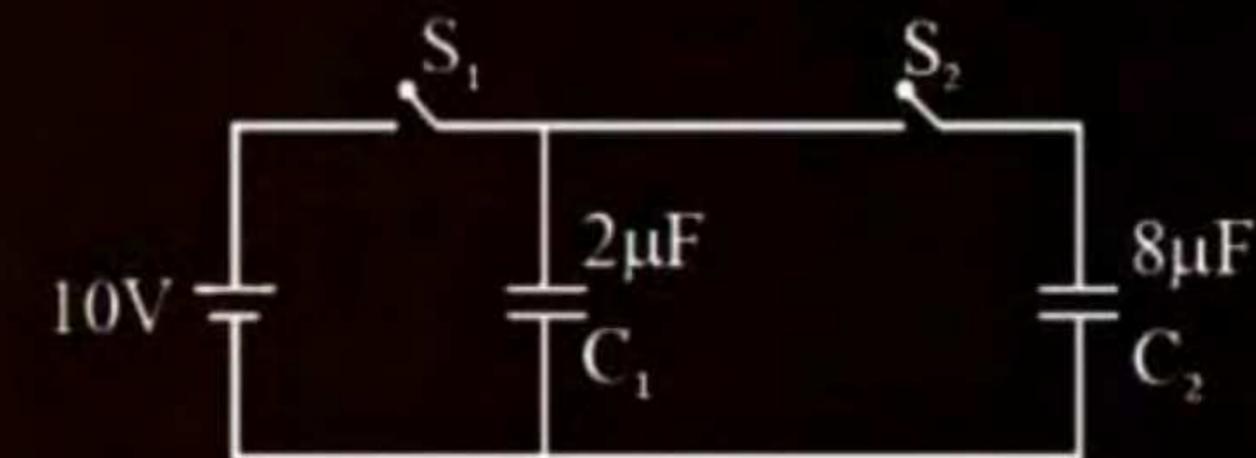
[JEE Mains-2021]**ATDB.uno****Ans. (16)**

QUESTION - 1



The equivalent capacitance between points A and B on below shown figure will be _____ μF

[JEE Mains-2022]

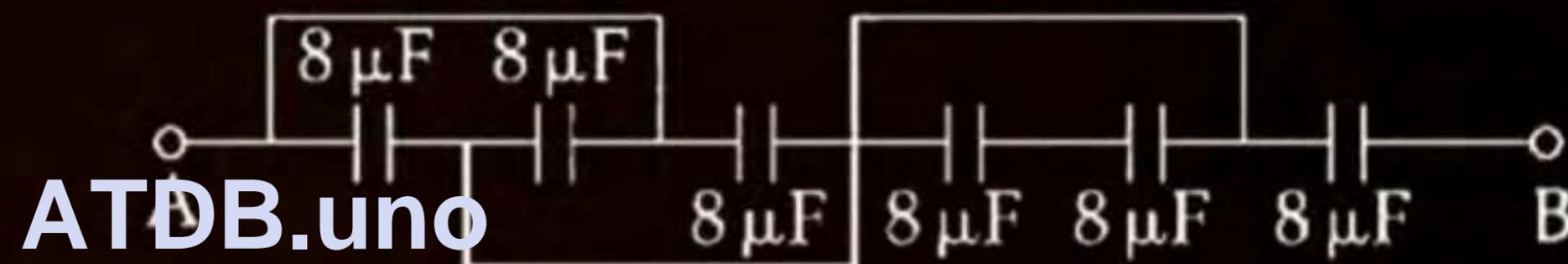

Ans. (6)


QUESTION -)



As shown in the figure, two parallel plate capacitors having equal plate area of 200 cm^2 are joined in such a way that $a \neq b$. The equivalent capacitance of the combination is $x\epsilon_0 \text{ F}$. The value of x is _____.

[06 April 2023 - Shift 2]

ATDB.uno

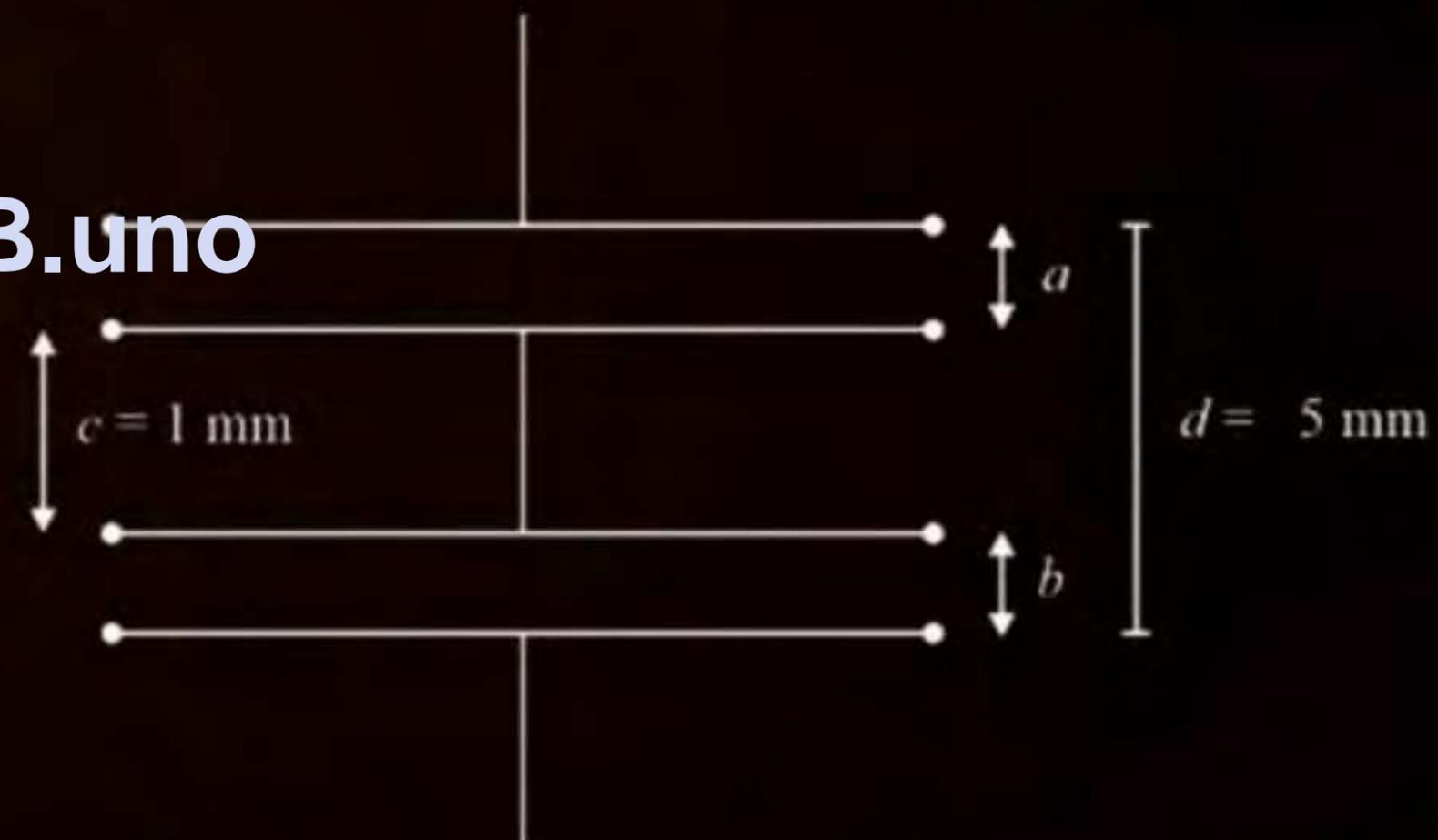

Ans : (5)

QUESTION -



The equivalent capacitance of the combination shown is

[10 April 2023 - Shift 1]


1 $2C$

2 $\frac{5}{3}C$

3 $\frac{C}{2}$

4 $4C$

ATDB.uno

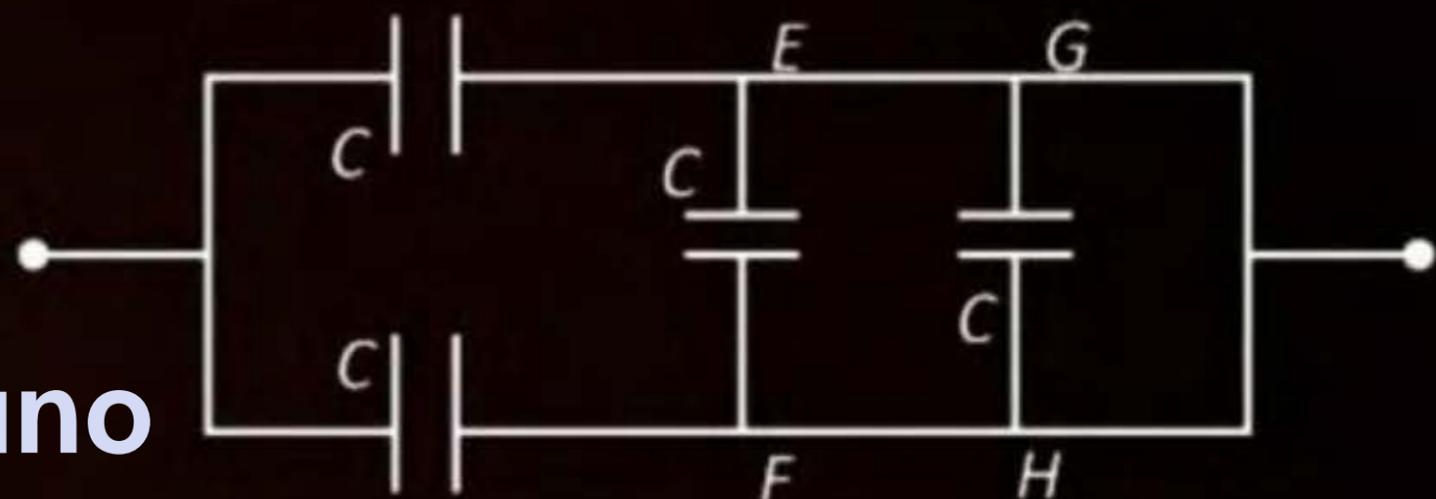


Ans. (1)

QUESTION -



In the given circuit. $C_1 = 2\mu\text{F}$, $C_2 = 0.2\mu\text{F}$, $C_3 = 2\mu\text{F}$, $C_4 = 4\mu\text{F}$, $C_5 = 2\mu\text{F}$, $C_6 = 2\mu\text{F}$. The charge stored on capacitor C_4 is _____ μC .
[11 April 2023 - Shift 2]

ATDB.uno

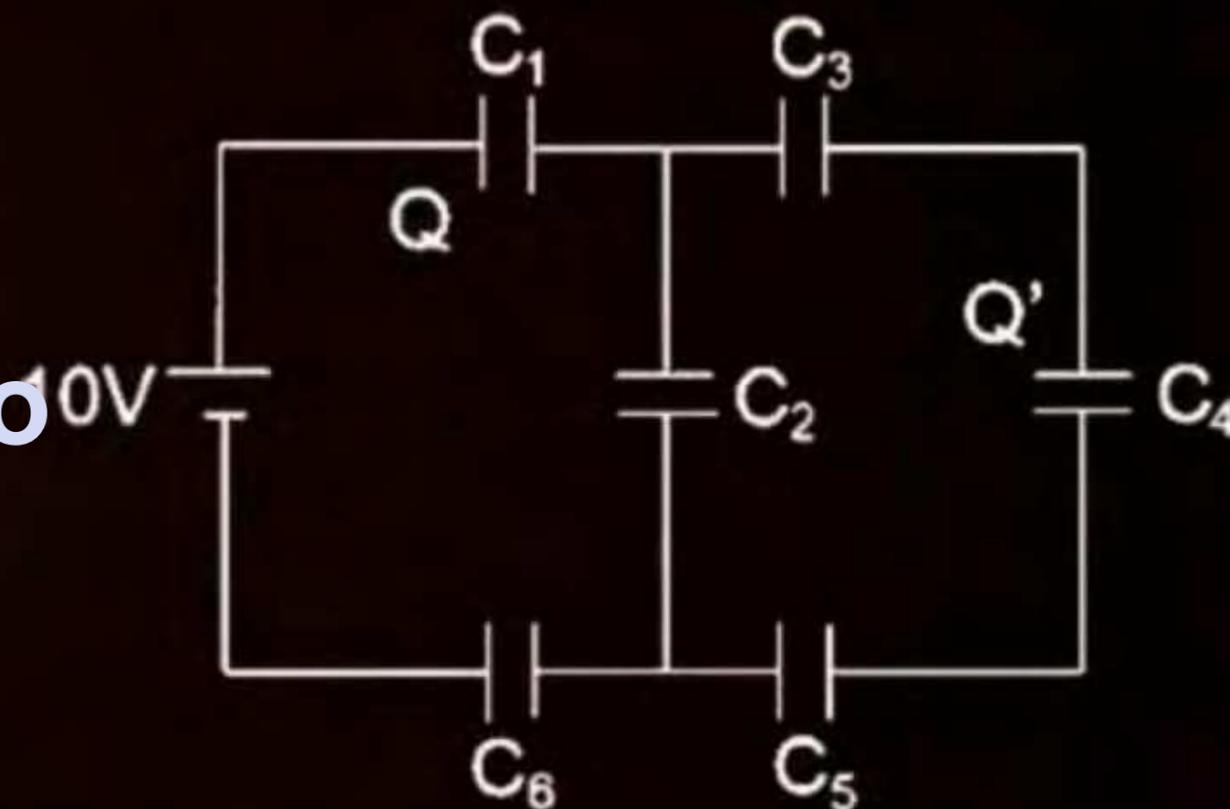

Ans. (4)


QUESTION -



In the given figure the total charge stored in the combination of capacitors is $100\mu\text{C}$.
The value of 'x' is _____.

[15 April 2023 - Shift 1]

ATDB.uno

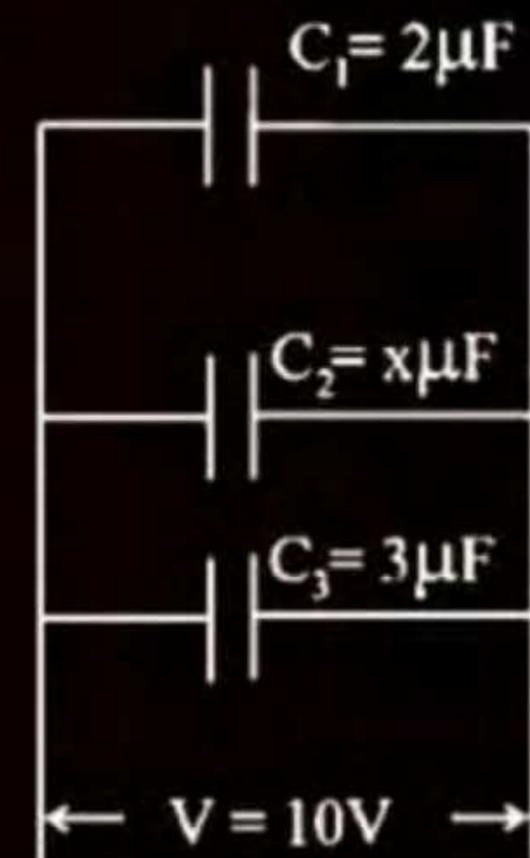

Ans. (5)

QUESTION - 1



The equivalent capacitance between points A and B on below shown figure will be _____ μF

[JEE Mains-2022]




Ans. (6)

QUESTION

ϵ



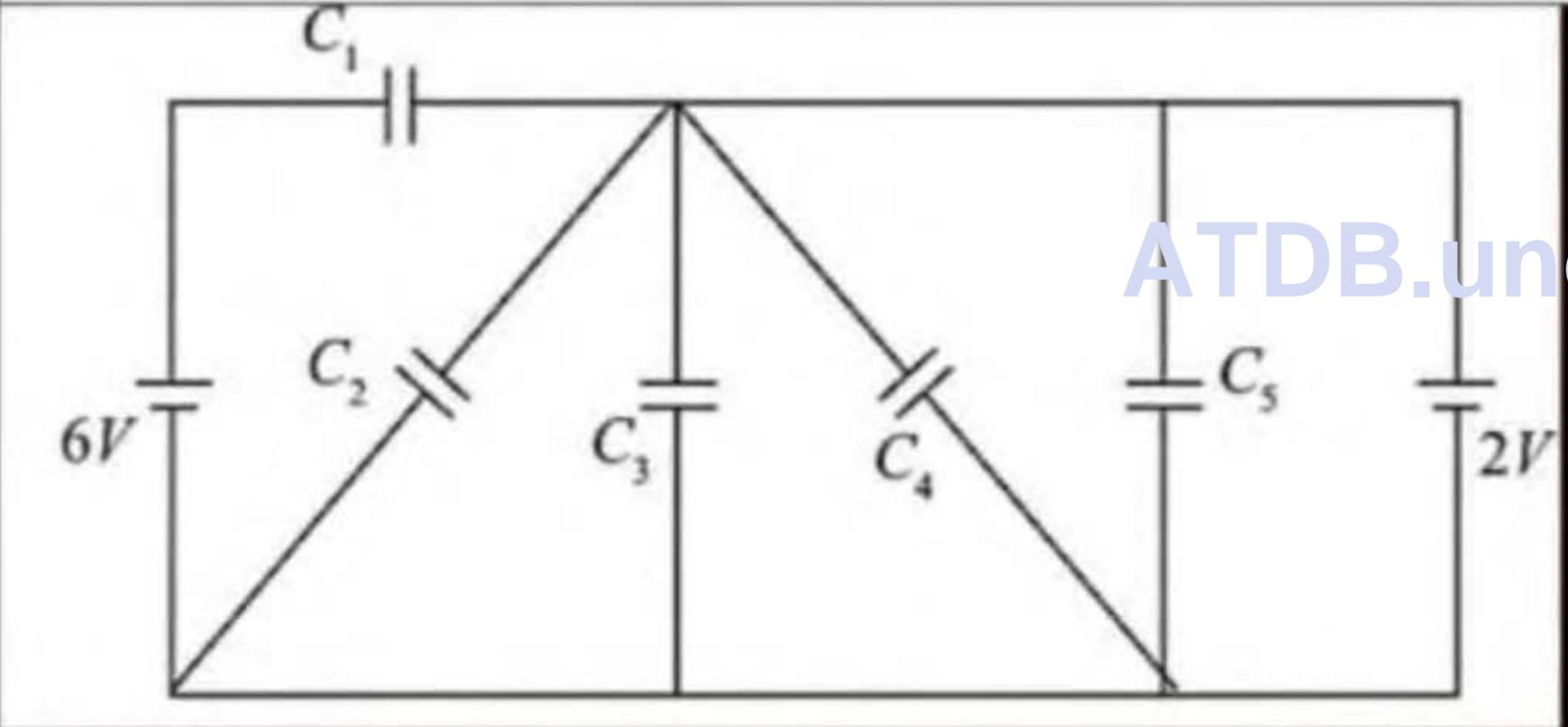12. In the following circuit $C_1 = 12\mu\text{F}$, $C_2 = C_3 = 4\mu\text{F}$ and $C_4 = C_5 = 2\mu\text{F}$. The charge stored in C_3 is _____ μC . (JEE Adv. 2022)



ATDB.uno

Ans. (8)


QUESTION

$$C_1 = \frac{A\epsilon_0}{d}$$



ϵ

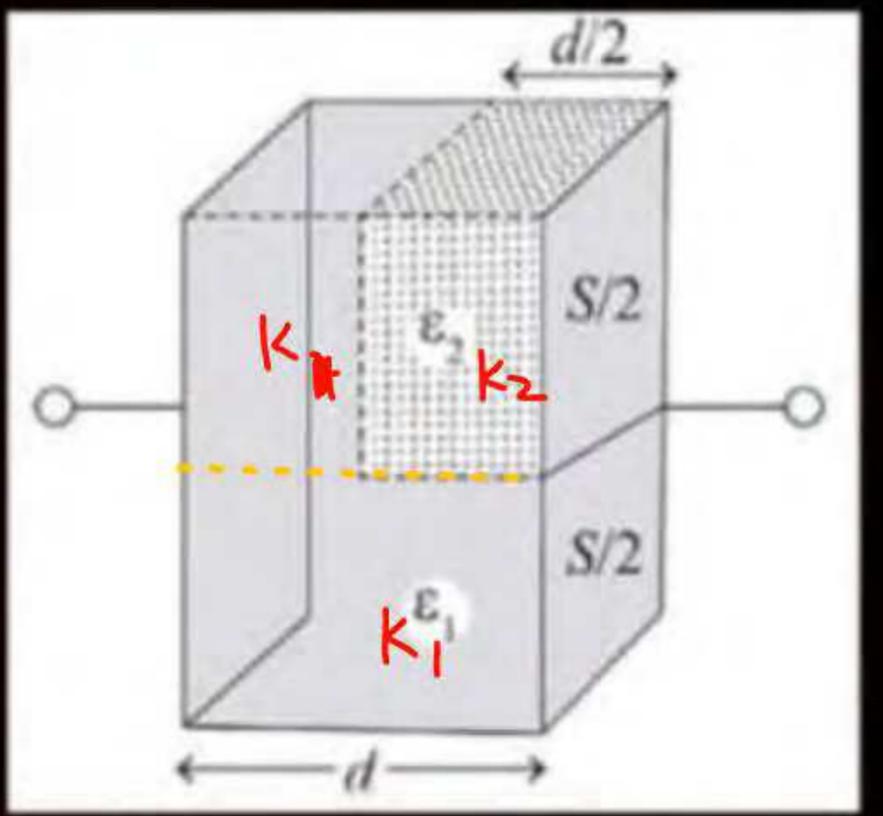14. A parallel plate capacitor having plates of area S and plate separation d , has capacitance C_1 in air. When two dielectrics of different relative permittivity's ($\epsilon_1 = 12$ and $\epsilon_2 = 4$) are introduced between the two plates as shown in the figure, the capacitance becomes C_2 . The ratio $\frac{C_2}{C_1}$ is (JEE Adv. 2015)



ATDB.uno





- | | |
|-------------------|-------------------|
| (1) $\frac{6}{5}$ | (2) $\frac{5}{3}$ |
| (3) $\frac{7}{5}$ | (4) $\frac{7}{3}$ |

Ans. (4)

QUESTION

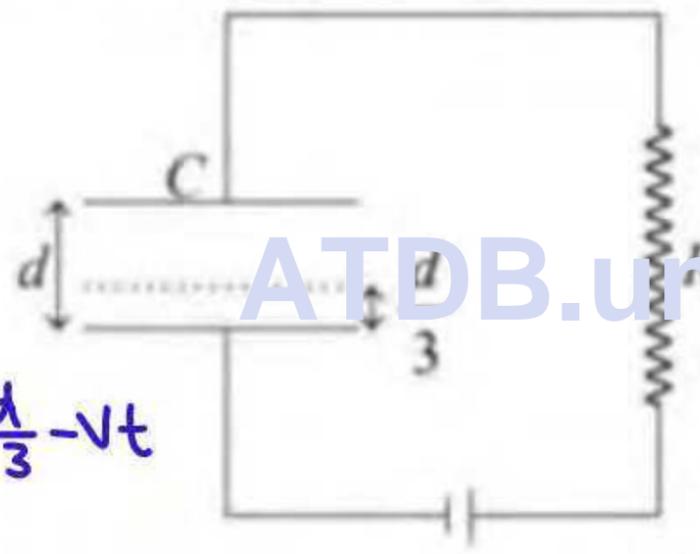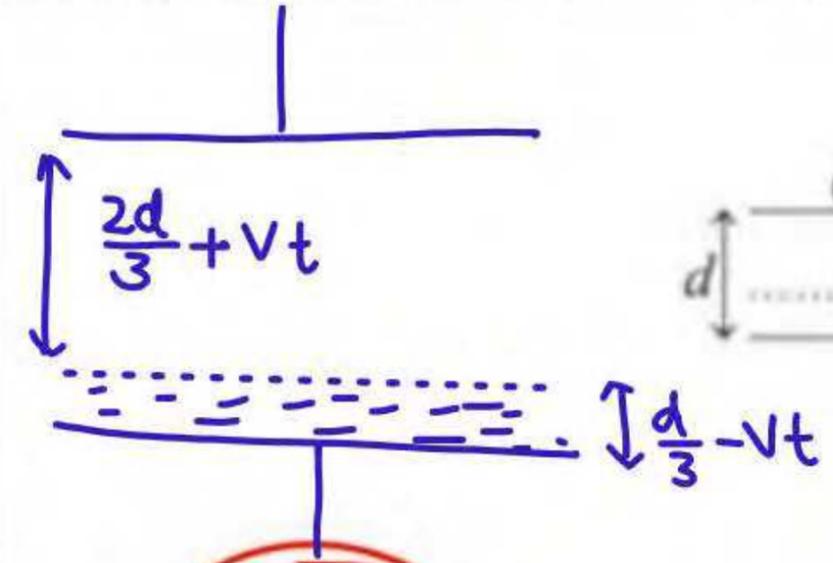26.

A parallel plate capacitor C with plates of unit area and separation d is filled with a liquid of dielectric constant $K = 2$. The level of liquid is $d/3$ initially. Suppose the liquid level decreases at a constant speed v , the time constant as a function of time t is (IIT-JEE 2008)



$\tau = RC_{eq}$

- (a) $\frac{6\epsilon_0 R}{5d + 3vt}$
- (c) $\frac{6\epsilon_0 R}{5d - 3vt}$

- (b) $\frac{(15d + 9vt)\epsilon_0 R}{2d^2 - 3dvt - 9v^2t^2}$
- (d) $\frac{(15d - 9vt)\epsilon_0 R}{2d^2 + 3dvt - 9v^2t^2}$

**QUESTION - 02**

In the circuit shown, charge on the $5\mu\text{F}$ capacitor is:

[JEE Mains-2020]

- 1 $5.45\mu\text{C}$
- 2 $16.36\mu\text{C}$
- 3 $10.90\mu\text{C}$
- 4 $18.00\mu\text{C}$

ATDB.uno



Ans. (2)

QUESTION - 03

Two equal capacitors are first connected in series and then in parallel. The ratio of the equivalent capacities in the two cases will be: **[JEE Mains-2021]**

1 4 : 1

2 2 : 1

3 1 : 4

4 1 : 2

ATDB.uno

Ans. (3)

QUESTION - 04

Consider the combination of 2 capacitors C_1 and C_2 , with $C_2 > C_1$, when connected in parallel, the equivalent capacitance is $\frac{15}{4}$ time the equivalent capacitance of the same connected in series. Calculate the ratio of capacitors, $\frac{C_2}{C_1}$.

[JEE Mains-2021]

- 1 $\frac{15}{11}$
- 2 $\frac{111}{80}$
- 3 $\frac{29}{15}$
- 4 None of these

ATDB.uno

Ans. (4)


QUESTION - 07



Four identical rectangular plates with length, $l = 2$ cm and breadth, $b = \frac{3}{2}$ cm are arranged as shown in figure. The equivalent capacitance between A and C is $\frac{x\epsilon_0}{d}$. The value of x is _____. (Round off to the Nearest Integer)

[JEE Mains-2021]

ATDB.uno

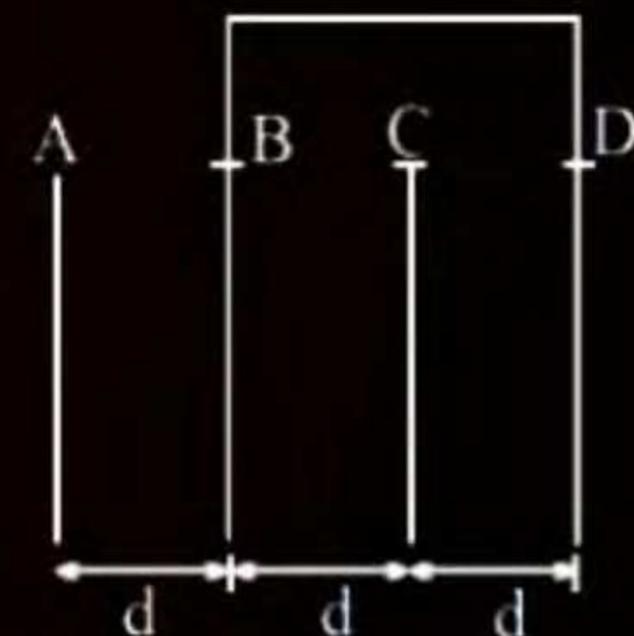


Ans. (2)

QUESTION - 08

A $2 \mu\text{F}$ capacitor C_1 is first charged to a potential difference of 10 V using a battery. Then the battery is removed and the capacitor is connected to an uncharged capacitor C_2 of $8 \mu\text{F}$. The charge in C_2 on equilibrium condition is _____ μC . (Round off to the Nearest Integer)

[JEE Mains-2021]

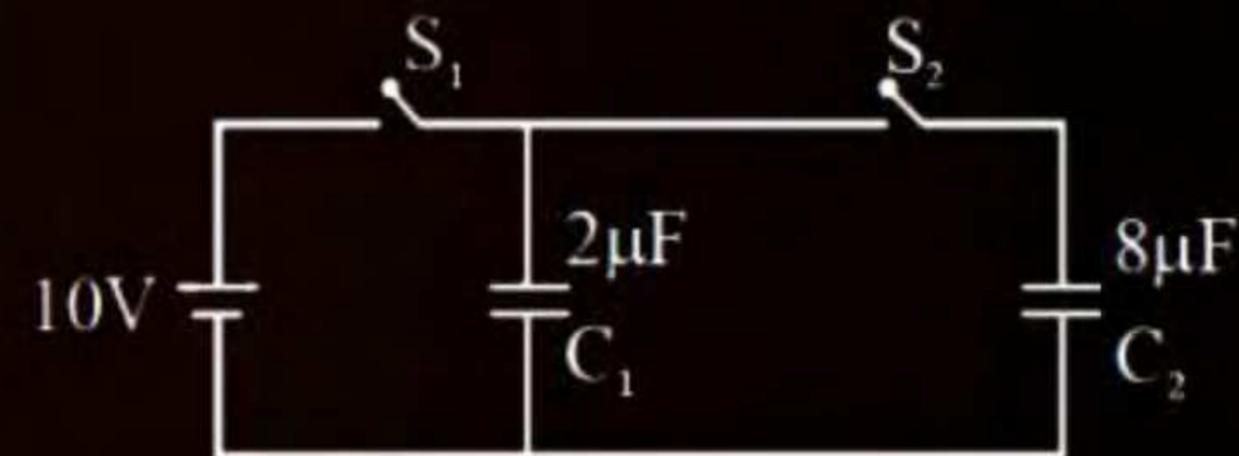ATDB.uno**Ans. (16)**

QUESTION - 12



Three capacitors $C_1 = 2 \mu\text{F}$, $C_2 = 6 \mu\text{F}$ and $C_3 = 12 \mu\text{F}$ are connected as shown in figure. Find the ratio of the charges on capacitors C_1 , C_2 and C_3 respectively: **[JEE Mains-2021]**


1 $2 : 1 : 1$

2 $2 : 3 : 3$

3 $1 : 2 : 2$

4 $3 : 4 : 4$

ATDB.uno

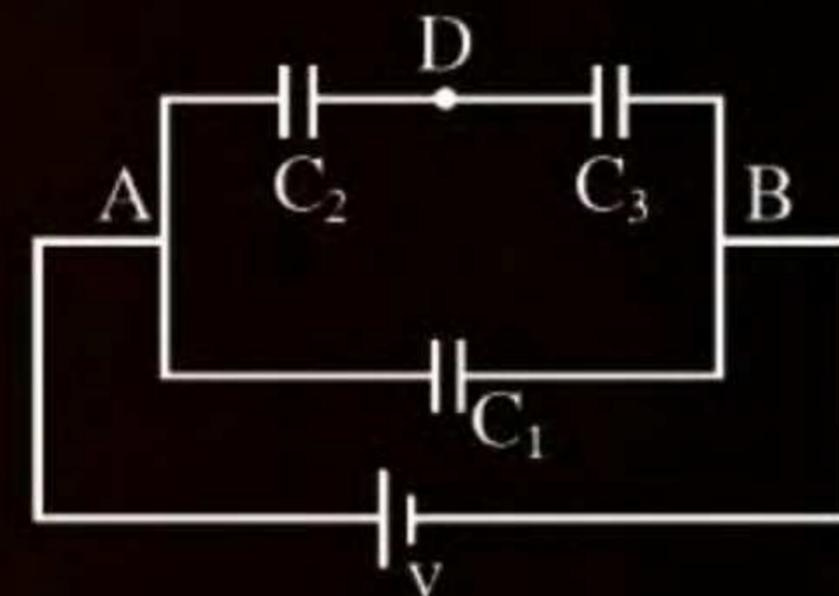

Ans. (3)

QUESTION - 15

The total charge on the system of capacitance $C_1 = 1\mu\text{F}$, $C_2 = 2\mu\text{F}$, $C_3 = 4\mu\text{F}$ and $C_4 = 3\mu\text{F}$ connected in parallel is (Assume a battery of 20V is connected to the combination)

[JEE Mains-2022]

1 $200\mu\text{C}$

2 200C

3 $10\mu\text{C}$

4 10C

ATDB.uno

Ans. (1)

QUESTION – 19

If the charge on a capacitor is increased by $2C$, the energy stored in increases by 44%.
The original charge on the capacitor is (in C): **[JEE Mains-2022]**

1 10

2 20

3 30

4 40

ATDB.uno

Ans. (1)

QUESTION - 20



The equivalent capacitance between points A and B on below shown figure will be _____ μF

[JEE Mains-2022]



Ans. (6)

QUESTION - 21

Two metallic plates form a parallel plate capacitor. The distance between the plates is 'd'. A metal sheet of thickness $\frac{d}{2}$ and of area equal to area of each plate is introduced between the plates. What will be the ratio of the new capacitance to the original capacitance of the capacitor?

[JEE Mains-2022]

1 2 : 1

2 1 : 3

3 1 : 4

4 4 : 1

ATDB.uno

Ans. (1)


**QUESTION - 22**

The charge on capacitor of capacitance $15\mu\text{F}$ in the figure given below is :

[JEE Mains-2022]

- 1** $60\mu\text{C}$
- 2** $130\mu\text{C}$
- 3** $260\mu\text{C}$
- 4** $585\mu\text{C}$

ATDB.uno

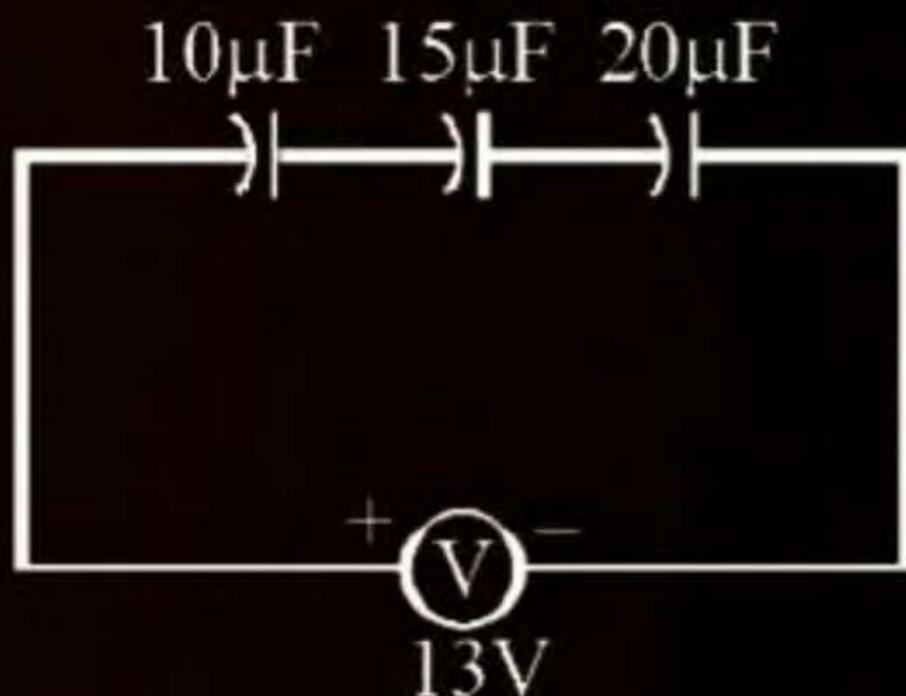

Ans. (1)

QUESTION - 23

A parallel plate capacitor with plate area A and plate separation $d = 2$ m has a capacitance of $4 \mu\text{F}$. The new capacitance of the system if half of the space between them is filled with a dielectric material of dielectric constant $K = 3$ (as shown in figure) will be :

[JEE Mains-2022]

1 $2\mu\text{F}$

2 $32\mu\text{F}$

3 $6\mu\text{F}$

4 $8\mu\text{F}$

ATDB.uno**Ans. (3)**

QUESTION - 24

A force of 10N acts on a charged particle placed between two plates of a charged capacitor. If one plate of capacitor is removed, then the force acting on that particle will be: **[JEE Mains-2022]**

1 5 N

2 10 N

3 20 N

4 Zero

ATDB.uno

Ans. (1)

QUESTION - 25

A parallel plate capacitor filled with a medium of dielectric constant 10, is connected across a battery and is charged. The dielectric slab is replaced by another slab of dielectric constant 15. Then the energy of capacitor will: **[JEE Mains-2022]**

- 1 increase by 50%
- 2 decrease by 15%
- 3 increase by 25%
- 4 increase by 33%

ATDB.uno**Ans. (1)**



QUESTION - 40

In the reported figure, a capacitor is formed by placing a compound dielectric between the plates of parallel plate capacitor. The expression for the capacity of the said capacitor will be: (Given area of plate = A)

[JEE Mains-2021]


1 $\frac{15 K\epsilon_0 A}{34 d}$

2 $\frac{15 K\epsilon_0 A}{6 d}$

3 $\frac{25 K\epsilon_0 A}{6 d}$

4 $\frac{9 K\epsilon_0 A}{6 d}$

ATDB.uno

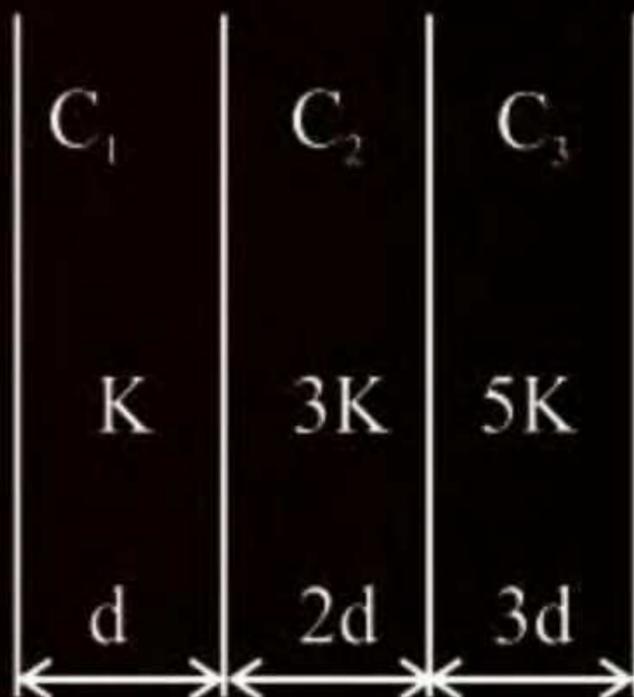

Ans. (1)

QUESTION - 49



A composite parallel plate capacitor is made up of two different dielectric materials with different thickness (t_1 and t_2) as shown in figure. The two different dielectric material are separated by a conducting foil F. The voltage of the conducting foil is _____ V.

[JEE Mains-2022]

ATDB.uno



Ans. (60)

QUESTION - 59

A parallel plate capacitor with air between the plate has a capacitance of 15 pF. The separation between the plate becomes twice and the space between them is filled with a medium of dielectric constant 3.5. Then the capacitance becomes $\frac{x}{4}$ pF. The value of x is:

[24 January 2023 - Shift 2]

ATDB.uno

Ans. (105)

QUESTION - 60

A parallel plate capacitor has plate area 40cm^2 and plates separation 2 mm . The space between the plates is filled with a dielectric medium of a thickness 1 mm and dielectric constant 5 . The capacitance of the system is:

[25 January 2023 - Shift 1]

1 $24\epsilon_0\text{ F}$

2 $\frac{3}{10}\epsilon_0\text{ F}$

3 $\frac{10}{3}\epsilon_0\text{ F}$

4 $10\epsilon_0\text{ F}$

ATDB.uno

Ans. (3)

QUESTION - 61

A capacitor has capacitance $5 \mu\text{F}$ when its parallel plates are separated by air medium of thickness d . A slab of material of dielectric constant 1.5 having area equal to that of plates but thickness $\frac{d}{2}$ is inserted between the plates. Capacitance of the capacitor in the presence of slab will be _____ μF .

[25 January 2023 - Shift 2]

ATDB.uno

Ans. (6)

QUESTION - 67



The equivalent capacitance of the combination shown is

[10 April 2023 - Shift 1]


1 $2C$

2 $\frac{5}{3}C$

3 $\frac{C}{2}$

4 $4C$

ATDB.uno

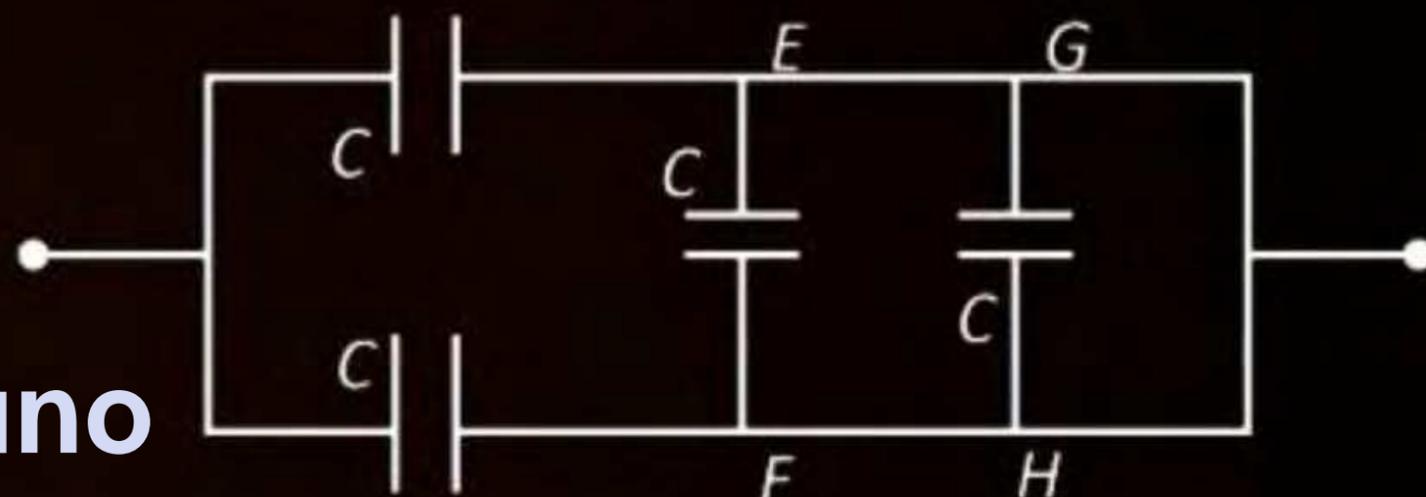

Ans. (1)

QUESTION - 68

The distance between two plates of a capacitor is d and its capacitance is C_1 , when air is the medium between the plates. If a metal sheet of thickness $\frac{2d}{3}$ and of the same area as plate is introduced between the plates, the capacitance of the capacitor becomes C_2 . The ratio $\frac{C_2}{C_1}$ is.

[10 April 2023 - Shift 2]

1 3 : 1

2 2 : 1

3 4 : 1

4 1 : 1

ATDB.uno

Ans. (1)

QUESTION - 71

A capacitor of capacitance C is charged to a potential V . The flux of the electric field through a closed surface enclosing the positive plate of the capacitor is:

[11 April 2023 - Shift 2]

- 1 $\frac{CV}{\epsilon_0}$
- 2 Zero
- 3 $\frac{2CV}{\epsilon_0}$
- 4 $\frac{CV}{2\epsilon_0}$


ATDB.uno

Ans. (1)

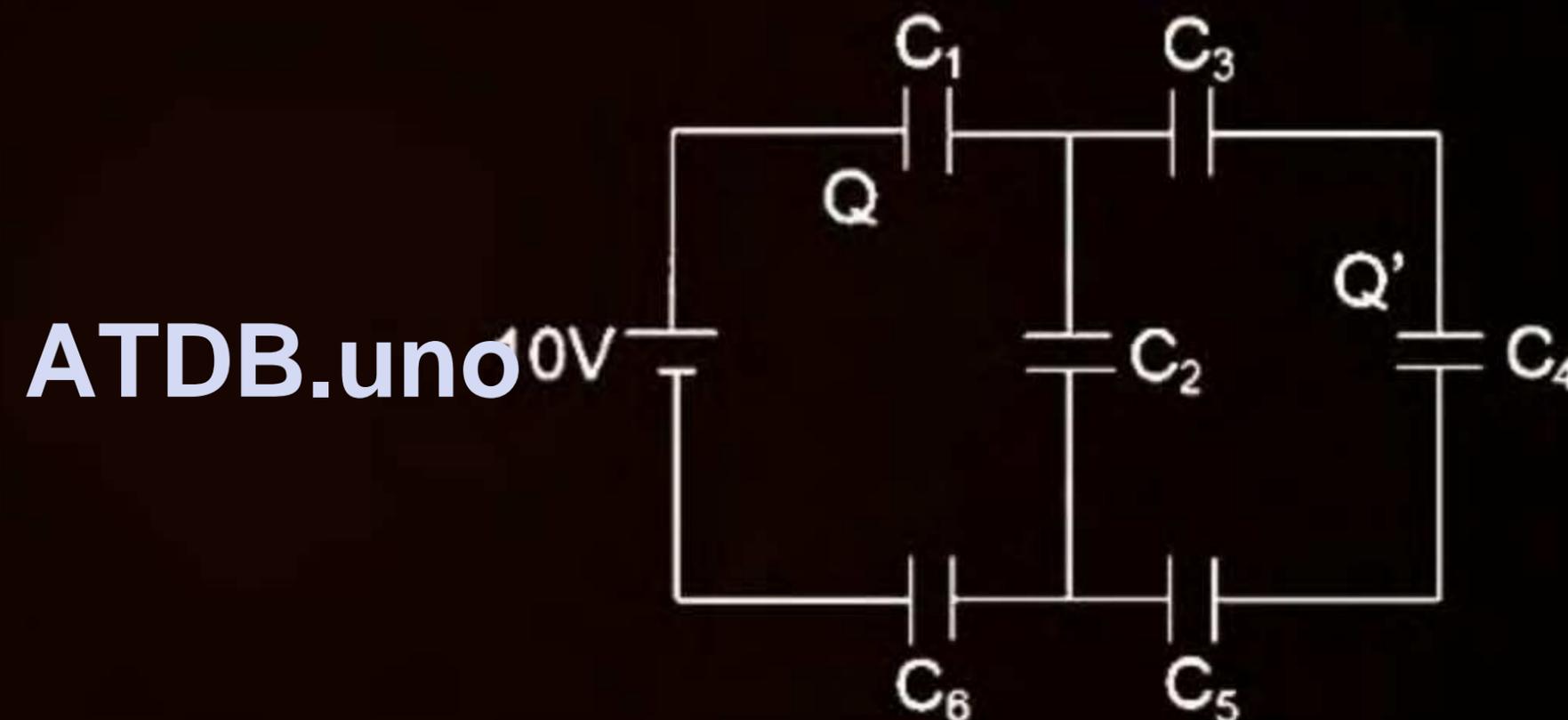QUESTION - 72



In the given circuit. $C_1 = 2\mu\text{F}$, $C_2 = 0.2\mu\text{F}$, $C_3 = 2\mu\text{F}$, $C_4 = 4\mu\text{F}$, $C_5 = 2\mu\text{F}$, $C_6 = 2\mu\text{F}$. The charge stored on capacitor C_4 is _____ μC .
[11 April 2023 - Shift 2]




Ans (4)

QUESTION



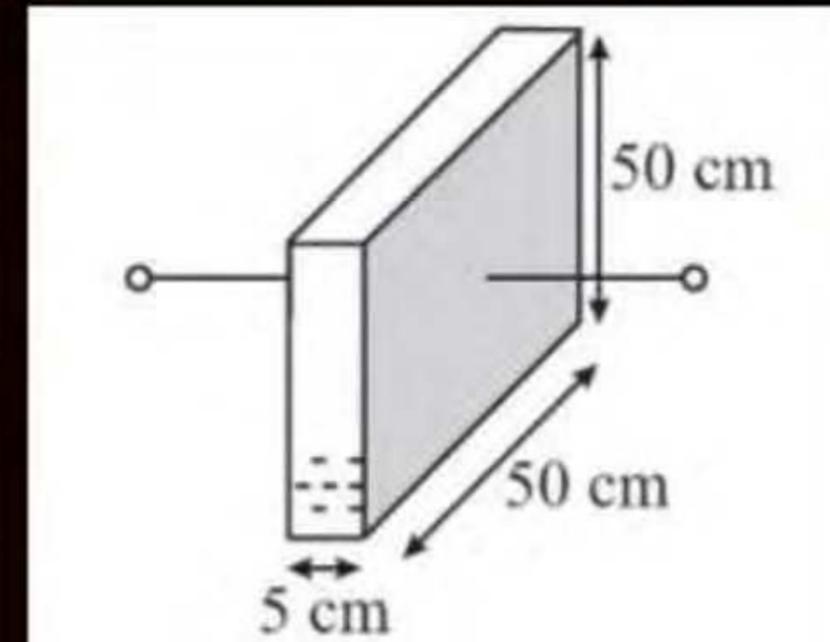8. A container has a base of $50 \text{ cm} \times 5 \text{ cm}$ and height 50 cm , as shown in the figure. It has two parallel electrically conducting walls each of area $50 \text{ cm} \times 50 \text{ cm}$. The remaining walls of the container are thin and non-conducting. The container is being filled with a liquid of dielectric constant 3 at a uniform rate of $250 \text{ cm}^3 \text{ s}^{-1}$. What is the value of the capacitance of the container after 10 seconds? [Given: Permittivity of free space $\epsilon_0 = 9 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$, the effects of the non-conducting walls on the capacitance are negligible] (JEE Adv. 2023)




- (1) 27 pF (2) 63 pF
(3) 81 pF (4) 135 pF

Ans. (2)

QUESTION



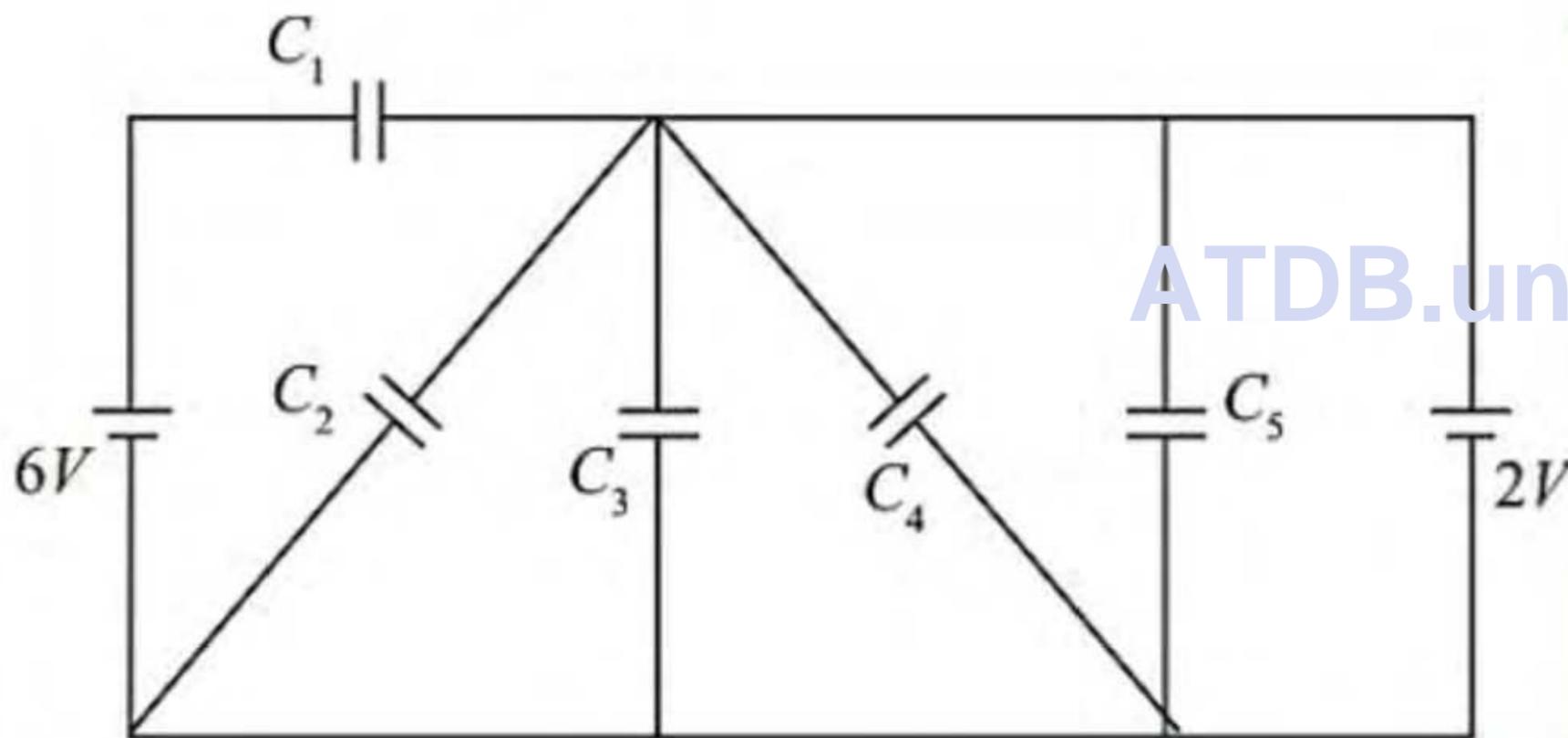12. In the following circuit $C_1 = 12\mu\text{F}$, $C_2 = C_3 = 4\mu\text{F}$ and $C_4 = C_5 = 2\mu\text{F}$. The charge stored in C_3 is _____ μC . (JEE Adv. 2022)




Ans. (8)

QUESTION



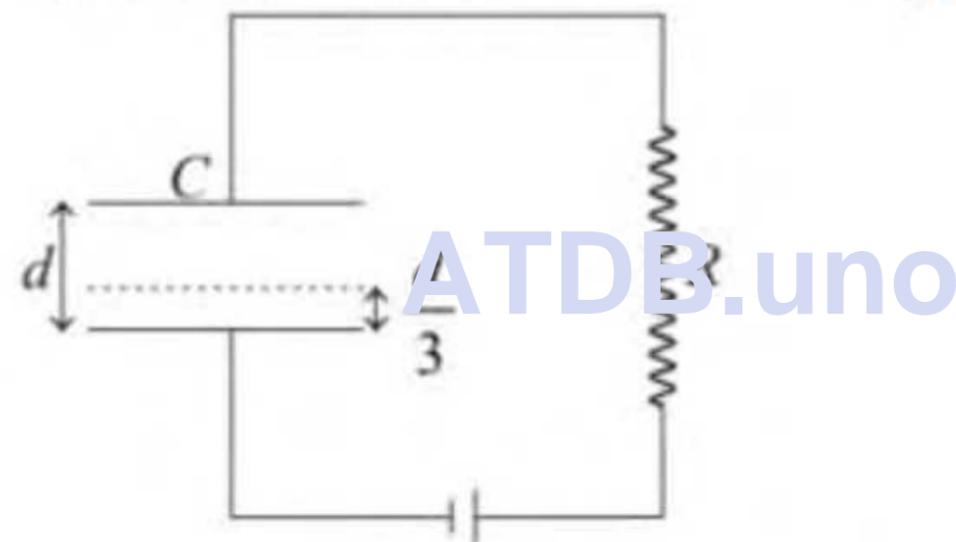26. A parallel plate capacitor C with plates of unit area and separation d is filled with a liquid of dielectric constant $K = 2$. The level of liquid is $d/3$ initially. Suppose the liquid level decreases at a constant speed v , the time constant as a function of time t is **(IIT-JEE 2008)**



(a) $\frac{6\epsilon_0 R}{5d + 3vt}$

(b) $\frac{(15d + 9vt)\epsilon_0 R}{2d^2 - 3dvt - 9v^2 t^2}$

(c) $\frac{6\epsilon_0 R}{5d - 3vt}$

(d) $\frac{(15d - 9vt)\epsilon_0 R}{2d^2 + 3dvt - 9v^2 t^2}$

Ans : (a)



HCV Ques

ATDB.uno



9. The negative plate of a parallel plate capacitor is given a charge of -20×10^{-8} C. Find the charges appearing on the four surfaces of the capacitor plates.

ATDB.uno

Ans. $Q = 10 \times 10^{-8}$ C.



13. Find the capacitance of the infinite ladder shown in figure (31-W11).

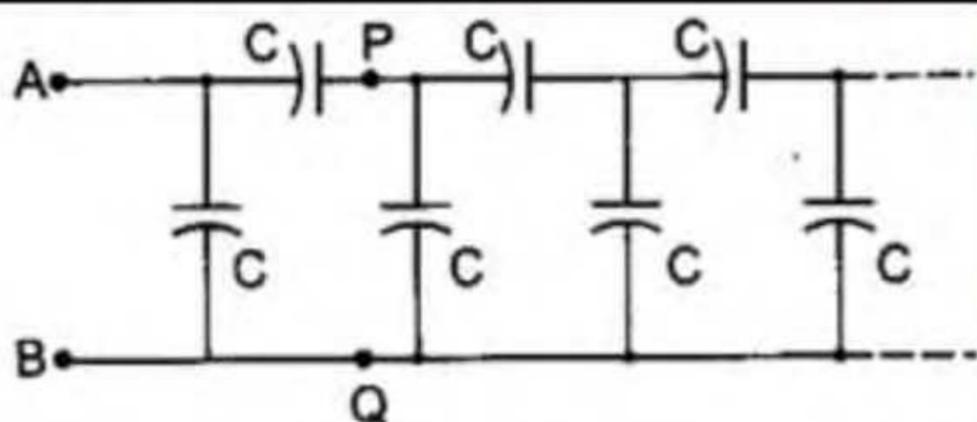


Figure 31-W11

ATDB.uno

Ans. $C = \frac{C + \sqrt{C^2 + 4C^2}}{2} = \frac{1 + \sqrt{5}}{2} C$



14. Find the energy stored in the electric field produced by a metal sphere of radius R containing a charge Q .

ATDB.uno

Ans. $U = \frac{Q^2}{8\pi\epsilon_0 R} = \frac{Q^2}{8\pi\epsilon_0 R}$



16. *An uncharged capacitor is connected to a battery. Show that half the energy supplied by the battery is lost as heat while charging the capacitor.*

ATDB.uno

Ans. $U = \frac{1}{2} CV^2 = \frac{1}{2} QV.$



19. The space between the plates of a parallel-plate capacitor of capacitance C is filled with three dielectric slabs of identical size as shown in figure (31-W13). If the dielectric constants of the three slabs are K_1 , K_2 and K_3 , find the new capacitance.

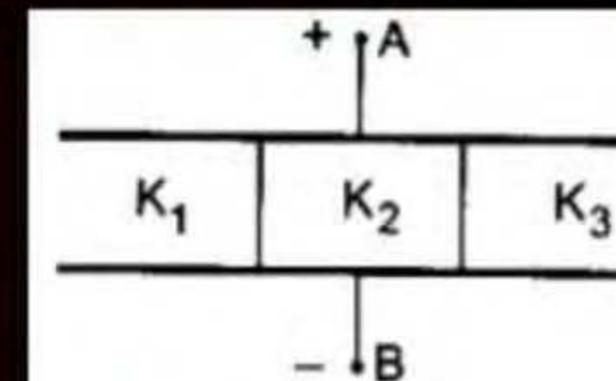


Figure 31-W13

ATDB.uno

Ans. *

EXERCISES

1. When 1.0×10^{12} electrons are transferred from one conductor to another, a potential difference of 10 V appears between the conductors. Calculate the capacitance of the two-conductor system.

ATDB.uno

Ans. 1.6×10^{-8} F



2. The plates of a parallel-plate capacitor are made of circular discs of radii 5.0 cm each. If the separation between the plates is 1.0 mm, what is the capacitance ?

ATDB.uno

Ans. $6.95 \times 10^{-5} \mu\text{F}$



4. A parallel-plate capacitor having plate area 25 cm^2 and separation 1.00 mm is connected to a battery of 6.0 V . Calculate the charge flown through the battery. How much work has been done by the battery during the process ?

ATDB.uno

Ans. $1.33 \times 10^{-10} \text{ C}$, $8.0 \times 10^{-10} \text{ J}$



6. Find the charges on the three capacitors connected to a battery as shown in figure (31-E1). Take $C_1 = 2.0 \mu\text{F}$, $C_2 = 4.0 \mu\text{F}$, $C_3 = 6.0 \mu\text{F}$ and $V = 12$ volts.

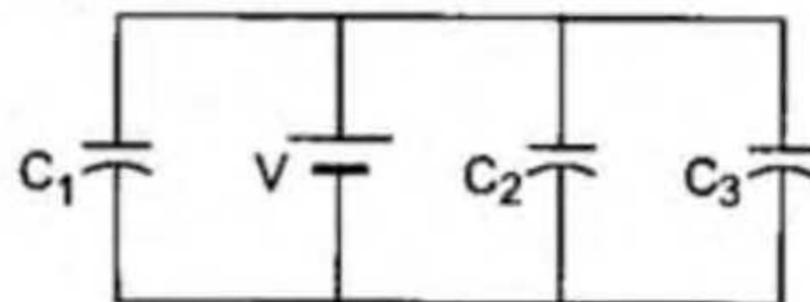


Figure 31-E1

ATDB.uno

Ans. $24 \mu\text{C}$, $48 \mu\text{C}$, $72 \mu\text{C}$



8. Find the charge appearing on each of the three capacitors shown in figure (31-E2).

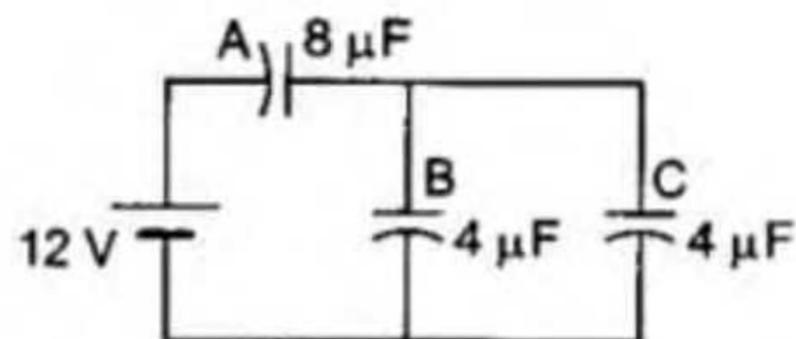


Figure 31-E2

ATDB.uno

Ans. $48 \mu\text{C}$ on the $8 \mu\text{F}$ capacitor and $24 \mu\text{C}$ on each of the



9. Take $C_1 = 4.0 \mu\text{F}$ and $C_2 = 6.0 \mu\text{F}$ in figure (31-E3). Calculate the equivalent capacitance of the combination between the points indicated.

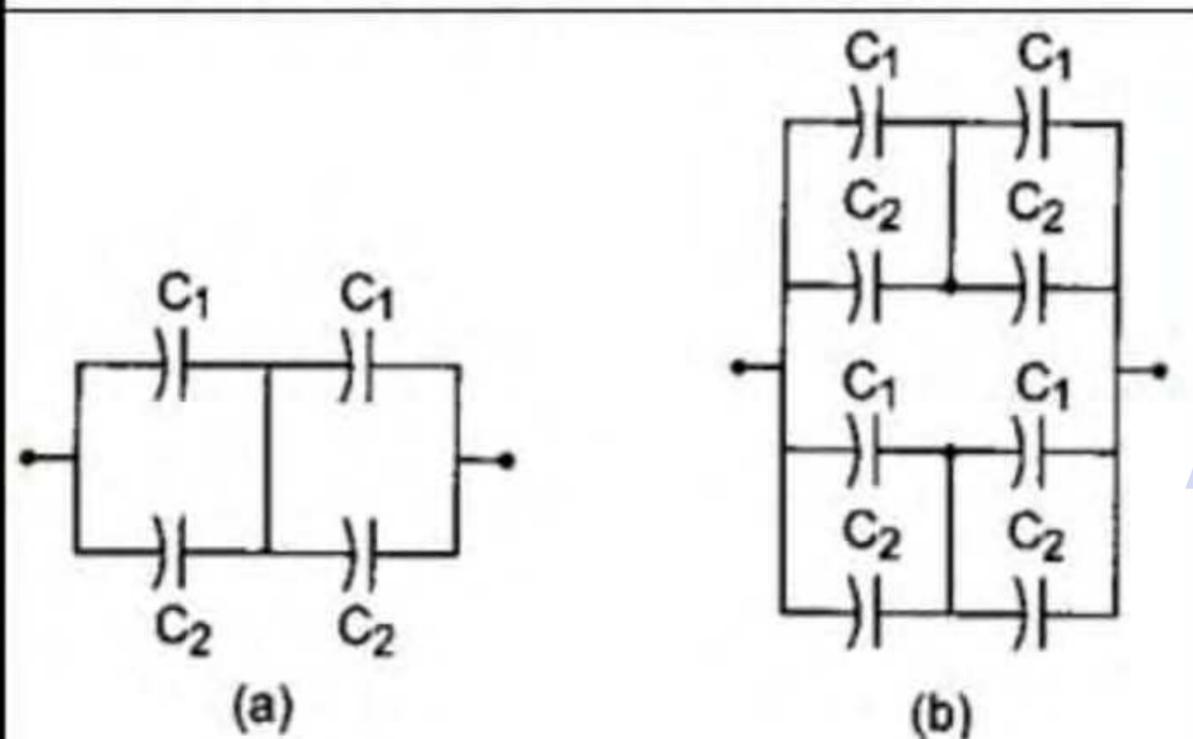


Figure 31-E3

ATDB.uno

Ans. (a) $5 \mu\text{F}$, (b) $10 \mu\text{F}$



10. Find the charge supplied by the battery in the arrangement shown in figure (31-E4).

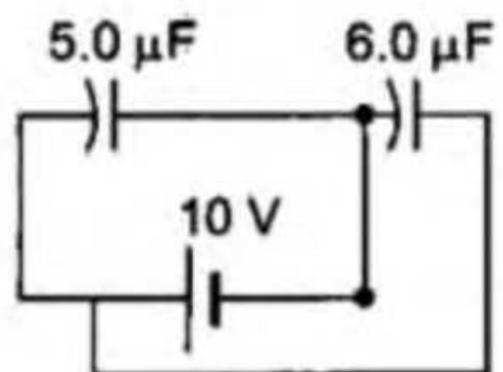


Figure 31-E4

ATDB.uno

Ans. $110 \mu\text{C}$



16. Find the equivalent capacitance of the system shown in figure (31-E8) between the points a and b .

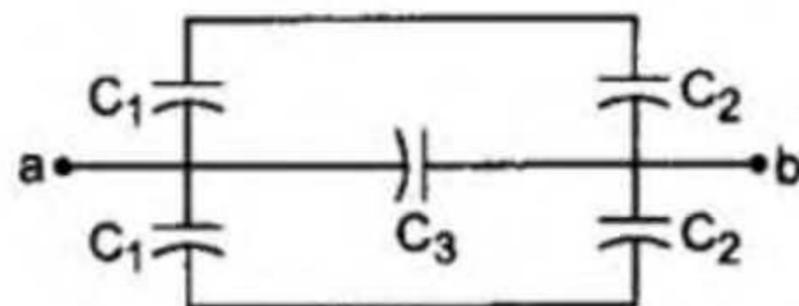


Figure 31-E8

ATDB.uno

Ans. $C_1 + \frac{2C_1C_2}{C_1 + C_2}$



20. Each capacitor shown in figure (31-E10) has a capacitance of $5.0 \mu\text{F}$. The emf of the battery is 50 V . How much charge will flow through AB if the switch S is closed?

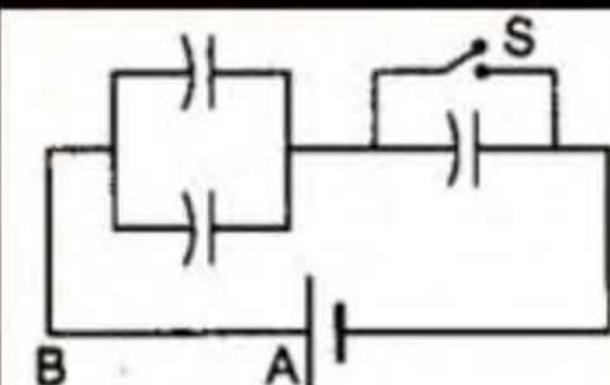



Figure 31-E10

ATDB.uno


Ans. $3.3 \times 10^{-4} \text{ C}$



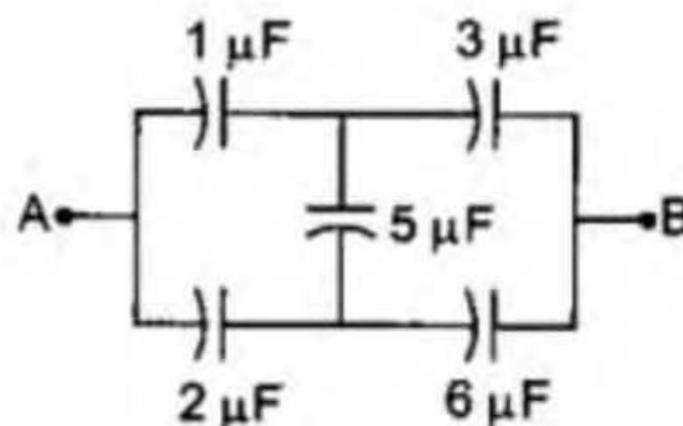
24. Convince yourself that parts (a), (b) and (c) of figure (31-E13) are identical. Find the capacitance between the points *A* and *B* of the assembly.



(a)

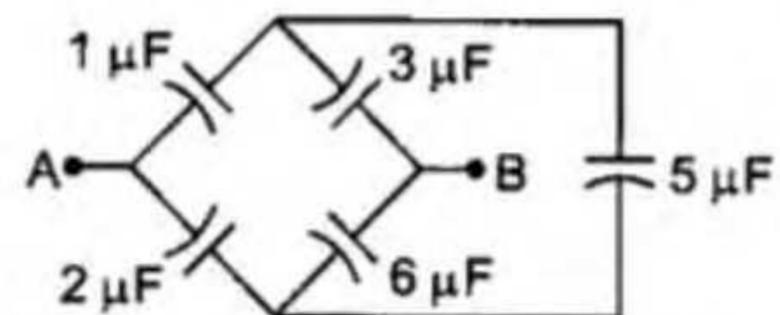

(b)

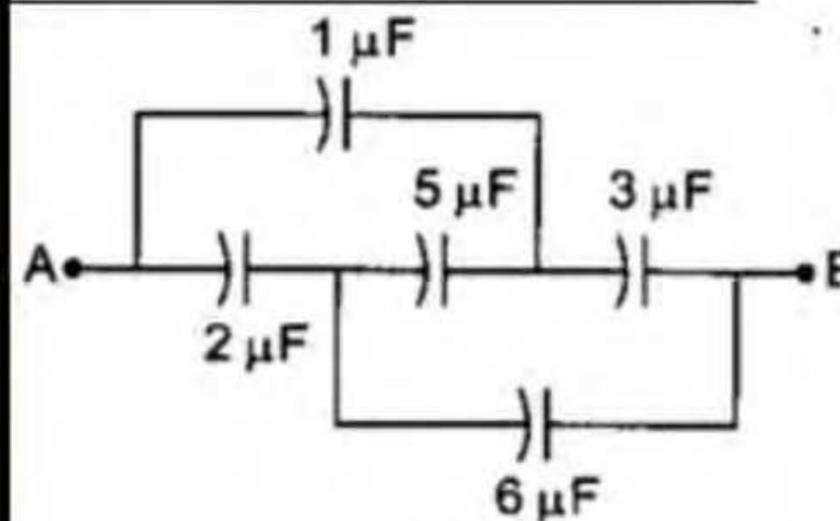

(c)

Ans. $2.25\ \mu\text{F}$



25. Find the potential difference $V_a - V_b$ between the points a and b shown in each part of the figure (31-E14).


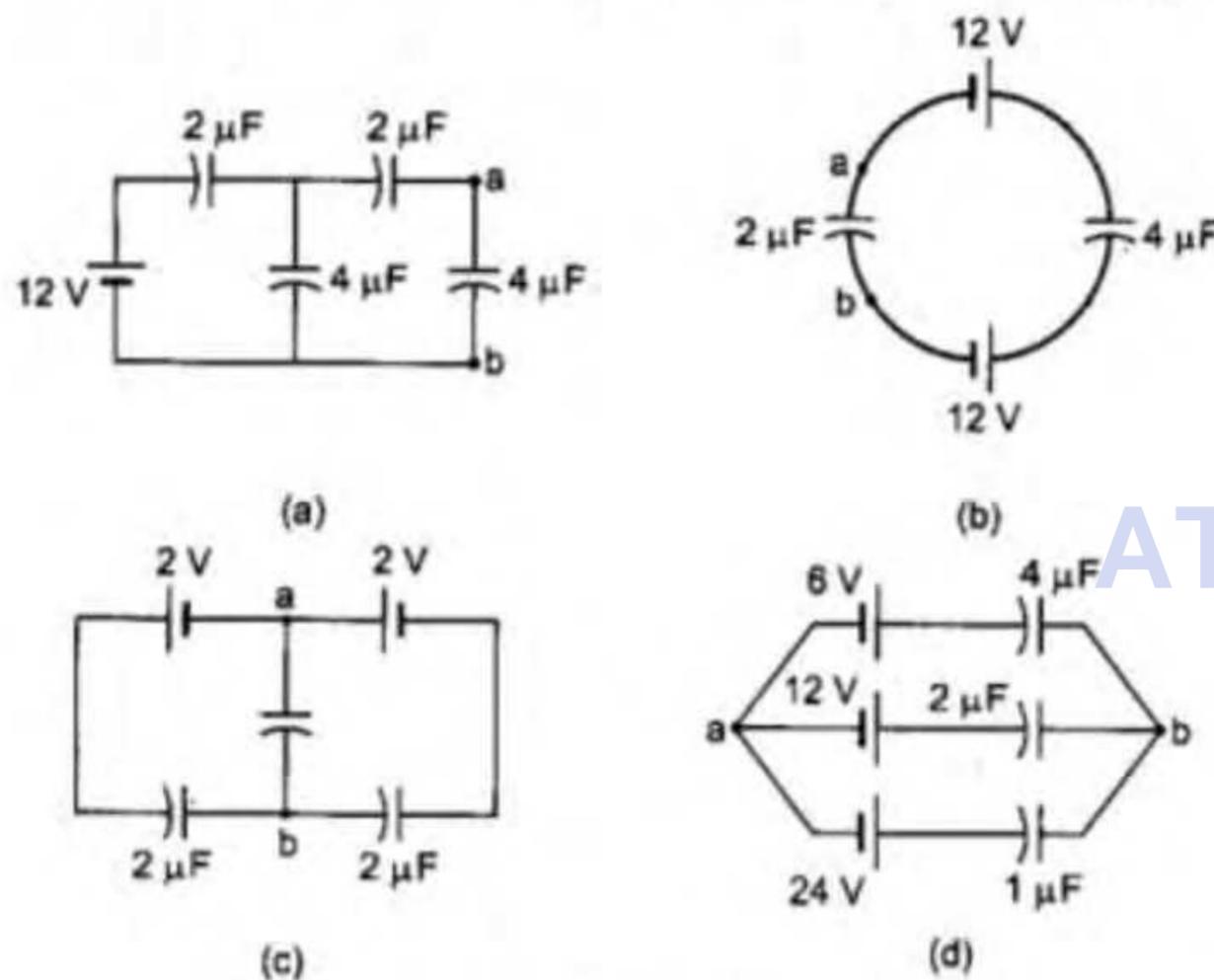


Figure 31-E14

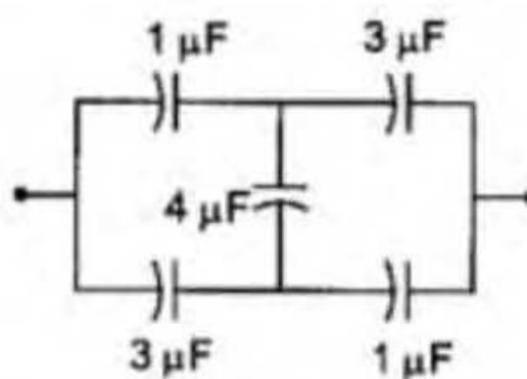
Ans. (a) $\frac{12}{11}$ V (b) -8 V (c) zero (d) -10.3 V




26. Find the equivalent capacitances of the combinations shown in figure (31-E15) between the indicated points.




(a)

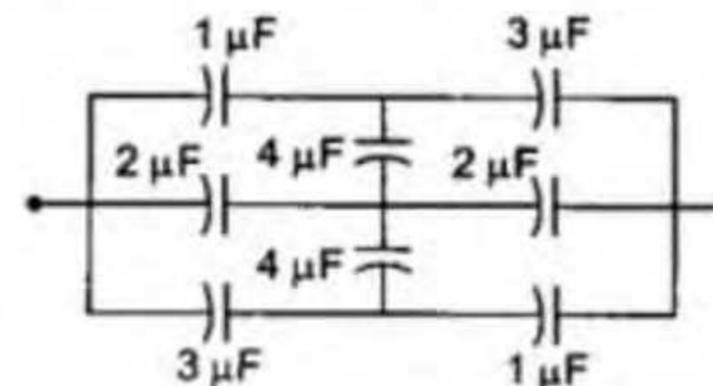

(b)

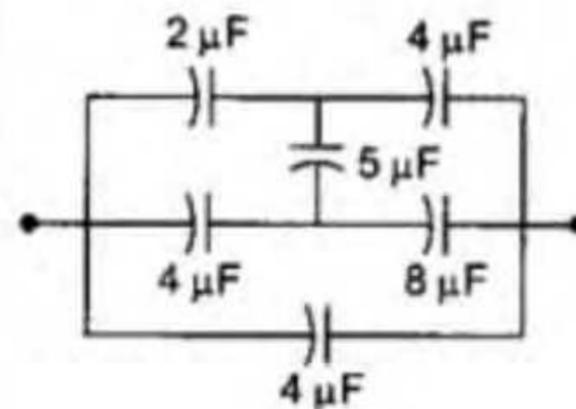

(c)

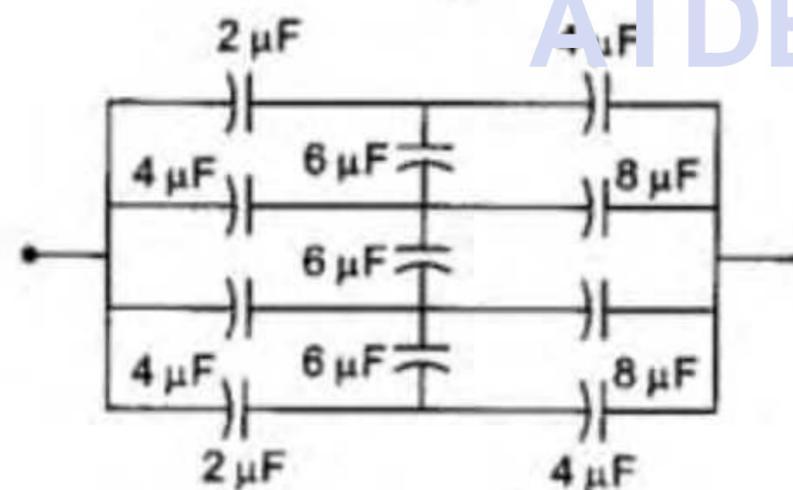

(d)

Figure 31-E15

Ans (a) $\frac{11}{2} \mu\text{F}$ (b) $\frac{11}{2} \mu\text{F}$ (c) $8 \mu\text{F}$ (d) $8 \mu\text{F}$



27. Find the capacitance of the combination shown in figure (31-E16) between A and B .

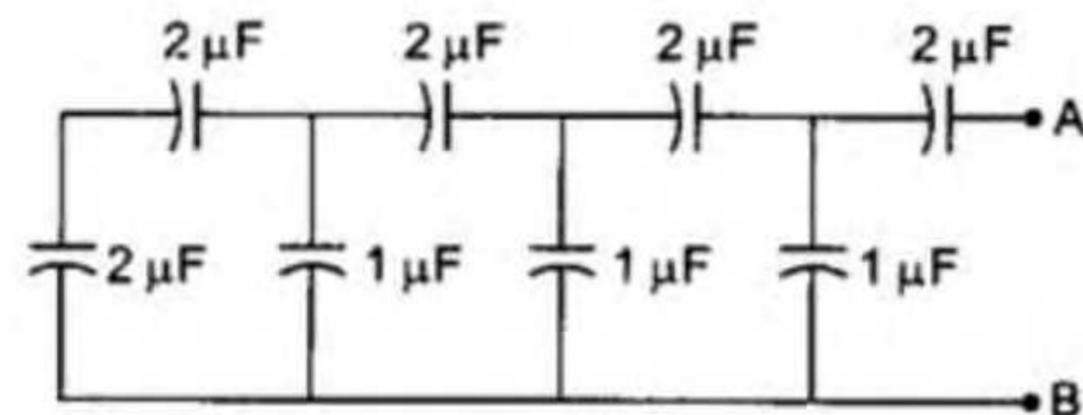


Figure 31-E16

ATDB.uno

Ans. $1 \mu\text{F}$



28. Find the equivalent capacitance of the infinite ladder shown in figure (31-E17) between the points A and B .

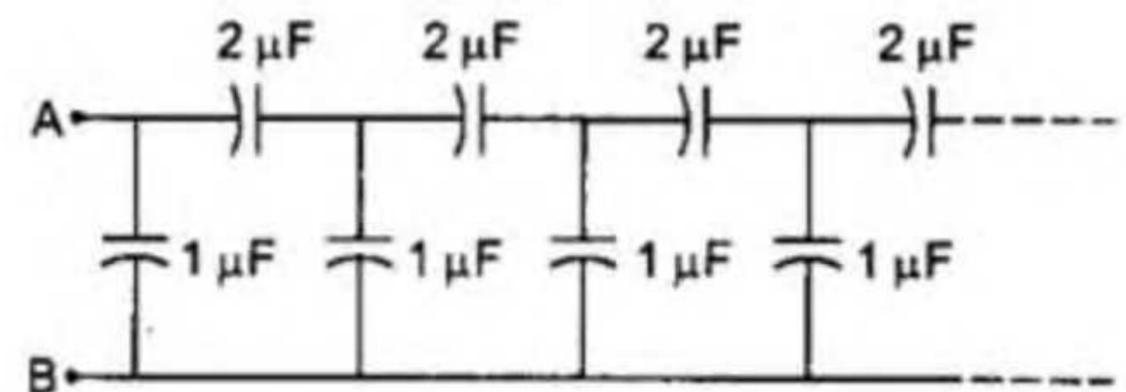


Figure 31-E17

ATDB.uno

Ans. $2 \mu\text{F}$



32. A charge of $1 \mu\text{C}$ is given to one plate of a parallel-plate capacitor of capacitance $0.1 \mu\text{F}$ and a charge of $2 \mu\text{C}$ is given to the other plate. Find the potential difference developed between the plates.

ATDB.uno

Ans. 5 V



THANK YOU

ATDB.uno

