



PRAYAS

JEE 2025

ATDB.uno

Lecture - 06

Physics

(Mini Lecture)

Capacitor



By- Saleem Ahmed Sir



Topics *to be covered*


1 Two Capacitor Connection

ATDB.uno


2

3

4

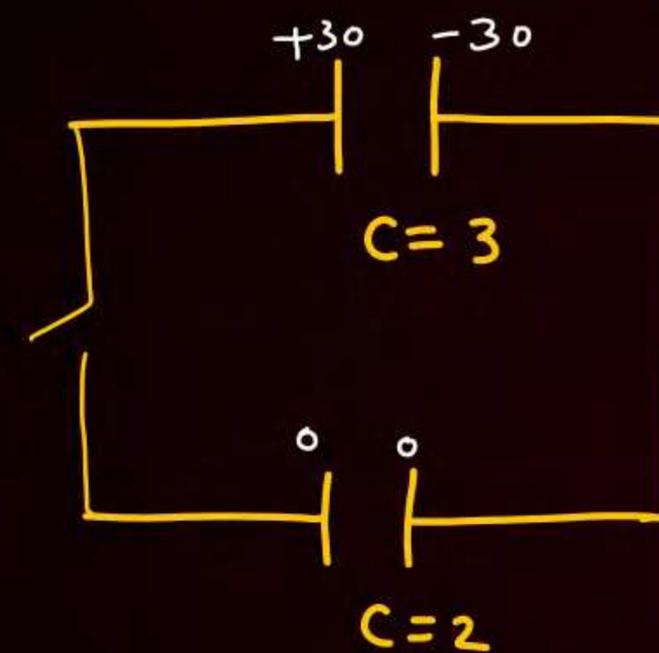

switch close

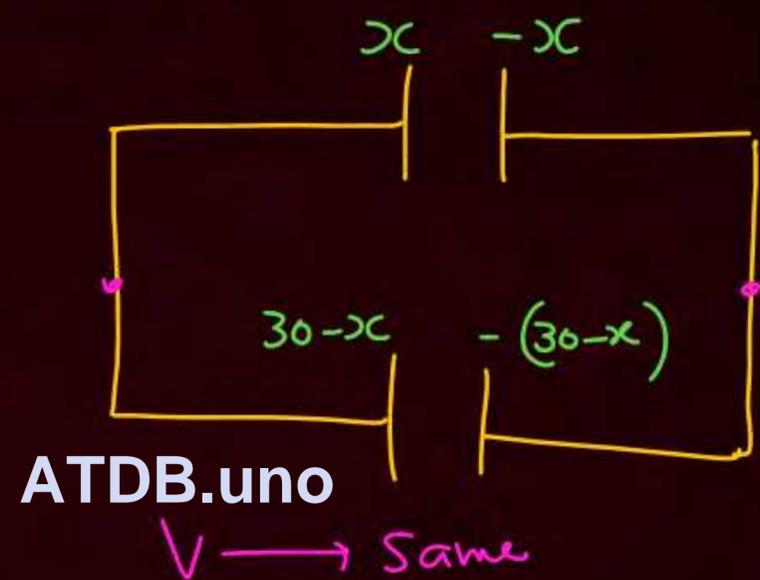


ATDB.uno

$V \rightarrow$ Same

$$V = \frac{x}{3} = \frac{30-x}{2}$$

$$2x = 90 - 3x$$

$$x = 18$$

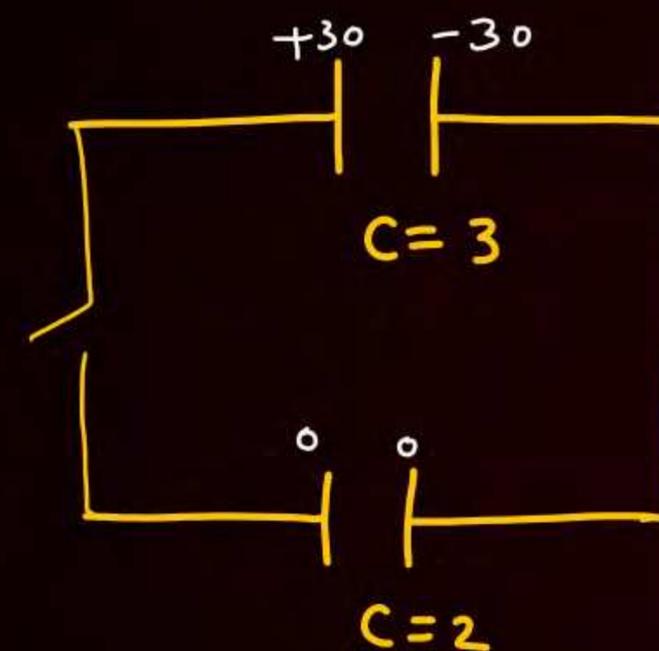

switch close



ATDB.uno

$V = V_{\text{common potential}}$


$$q_1 + q_2 = 30$$

$$3V + 2V = 30$$


$$V = 6$$

$$q_1 = 3 \times 6 = 18$$

$$q_2 = 2 \times 6 = 12$$

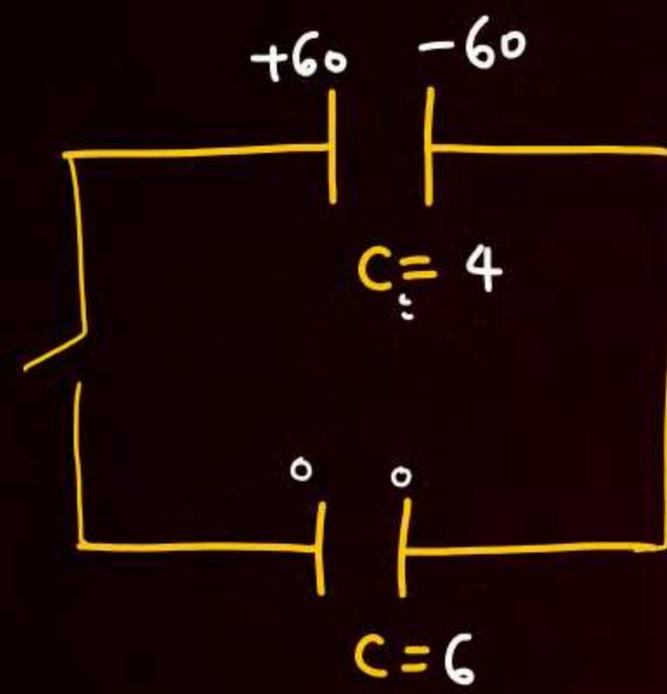


switch close

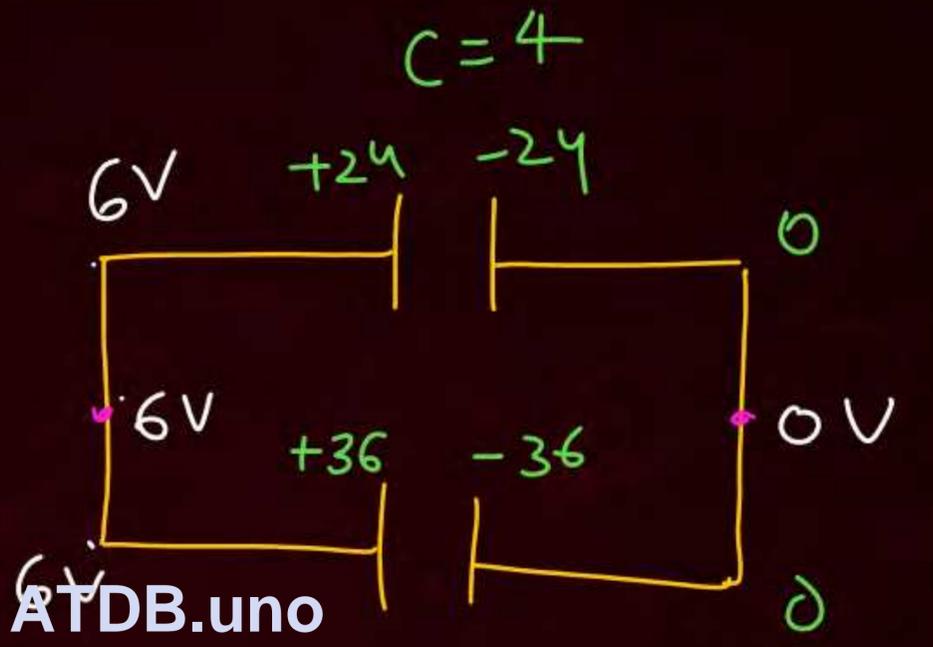


$$60 = 10 \times V_C$$

$$V_C = 6$$

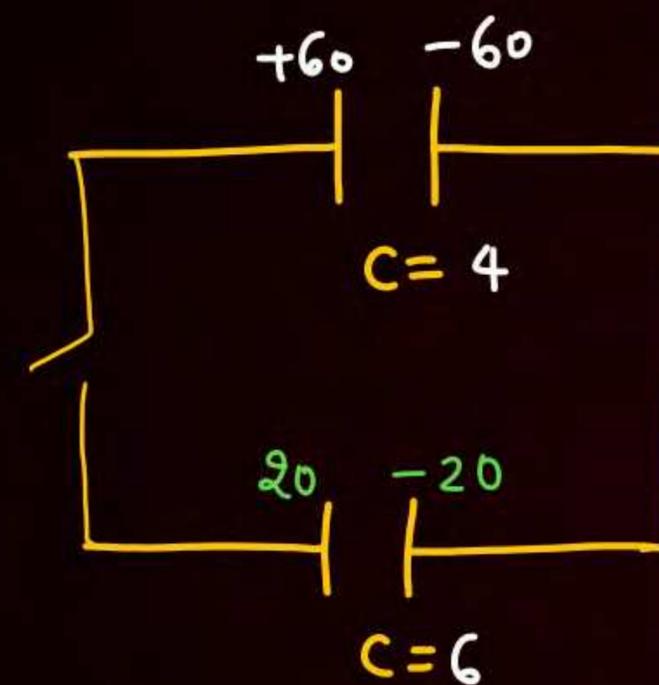

switch close

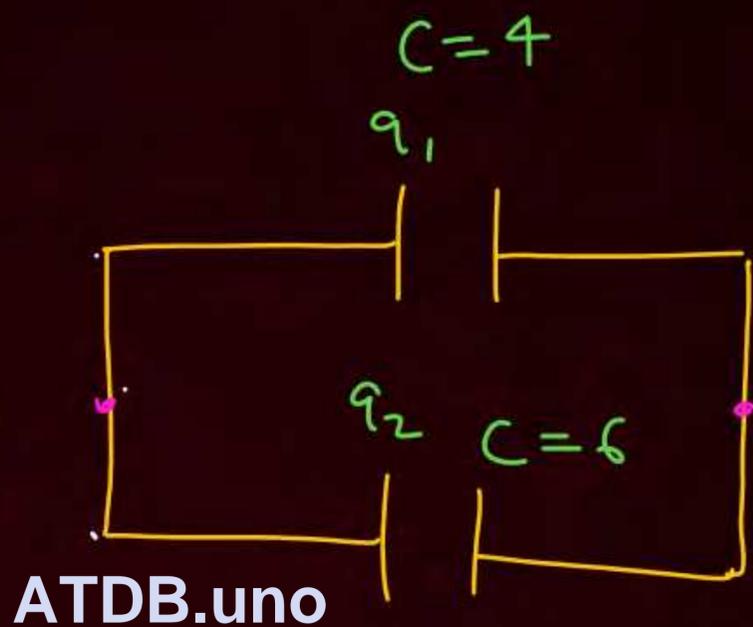


$$60 + 20 = (6 + 4) V$$


$$V = 8$$

$$q_1 = 32$$

$$q_2 = 48$$

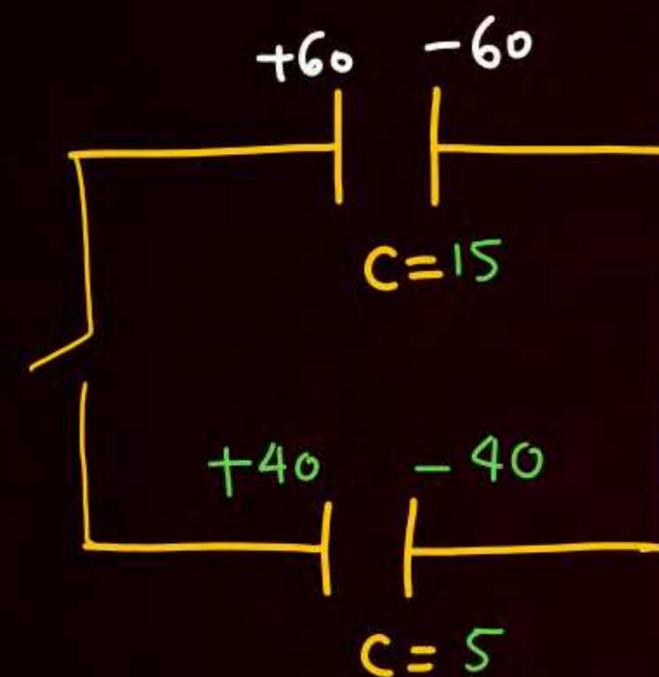


switch close

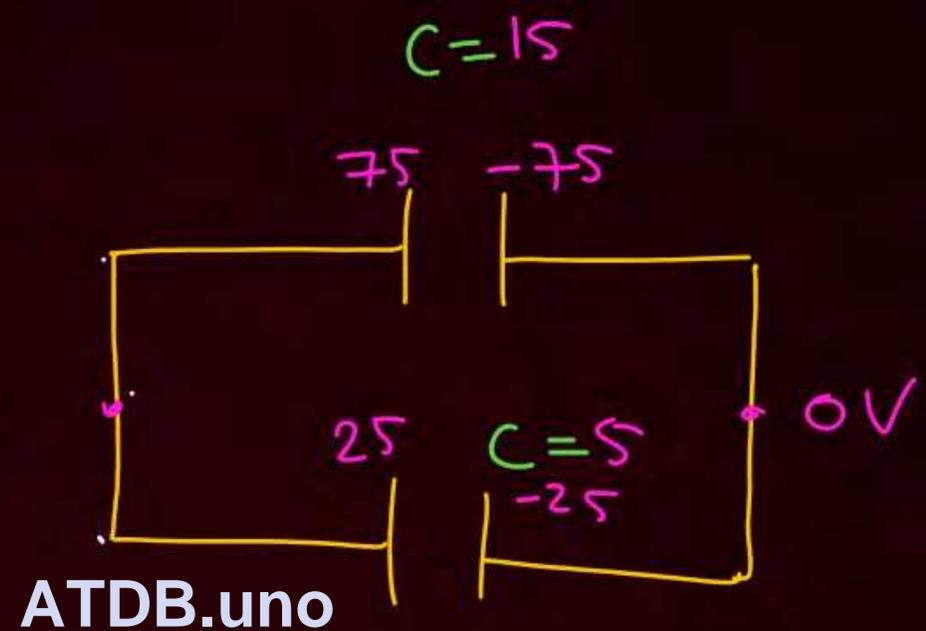

$$60 + 40 = 100 = (15 + 5) V$$

$$V = -5$$

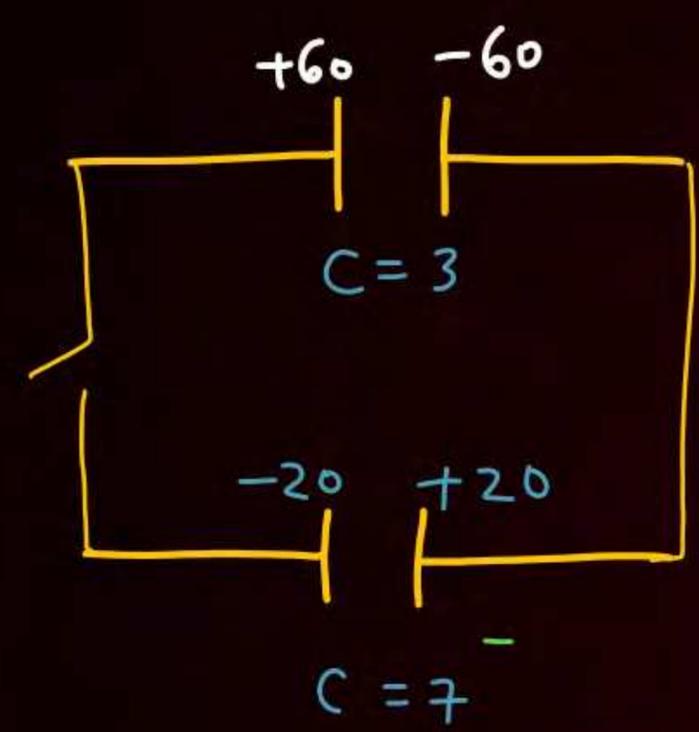

switch close




ATDB.uno

$$Q_{net} = C_{eq} \cdot V$$

$$40 = 10 V$$

$$V = 4$$

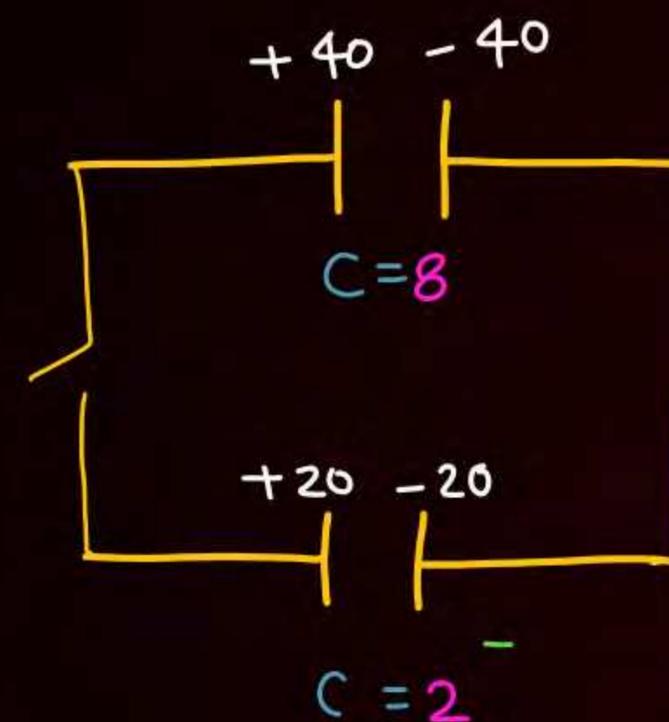

switch close \rightarrow



ATDB.uno

$$V_{\text{com}} = 6 \text{ volt}$$

$$U_f = \frac{1}{2} \times 8 \times 6^2 + \frac{1}{2} \times 2 \times 6^2$$

$$= 144 + 36 = 180$$

$$U_i = \frac{1}{2} \frac{(40)^2}{8} + \frac{1}{2} \frac{(20)^2}{2}$$

$$= 100 + 100 = 200$$




$$\text{heat loss} = 200 - 180$$



Q A capacitor $C_1 = 8F$ is fully charge from a battery of 5 volt. and an another capacitor of $C_2 = 2F$ is also fully charge with battery of emf 10 volt. Now both capacitor are disconnected from their battery & connect each other such that positive plate of one plate is connected to positive plate of another capacitor. final



- ① common potential
- ② heat loss

Solⁿ

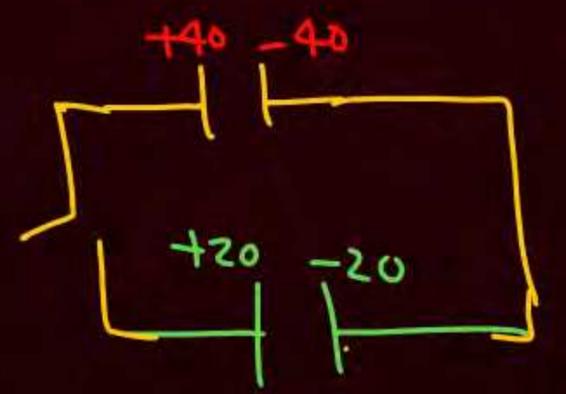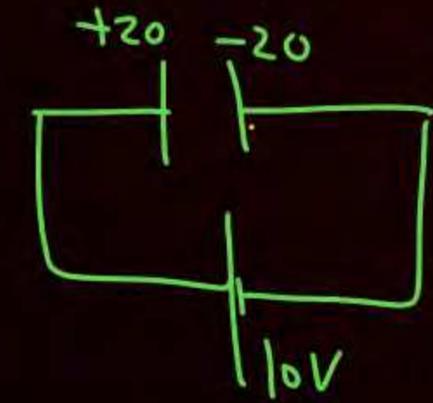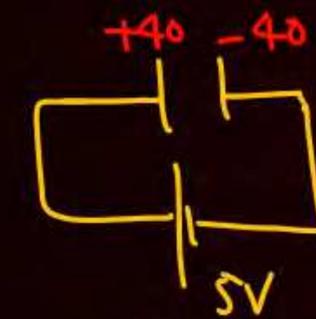




$$C_1V_1 + C_2V_2 = (C_1 + C_2)V_C$$

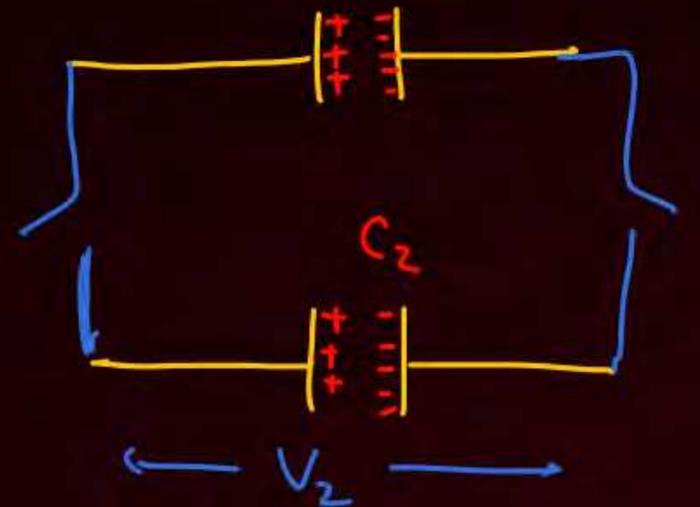
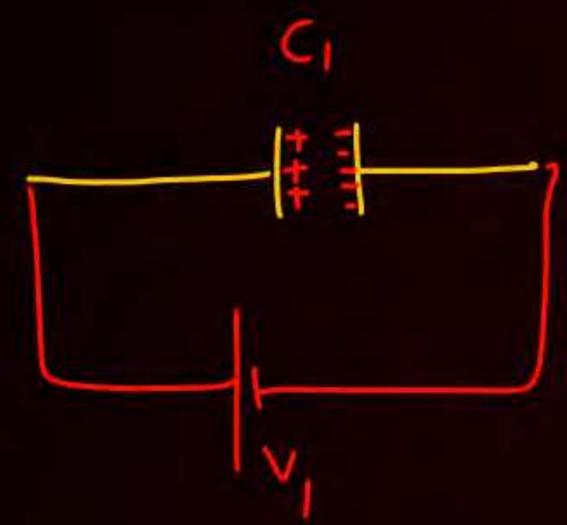


≡

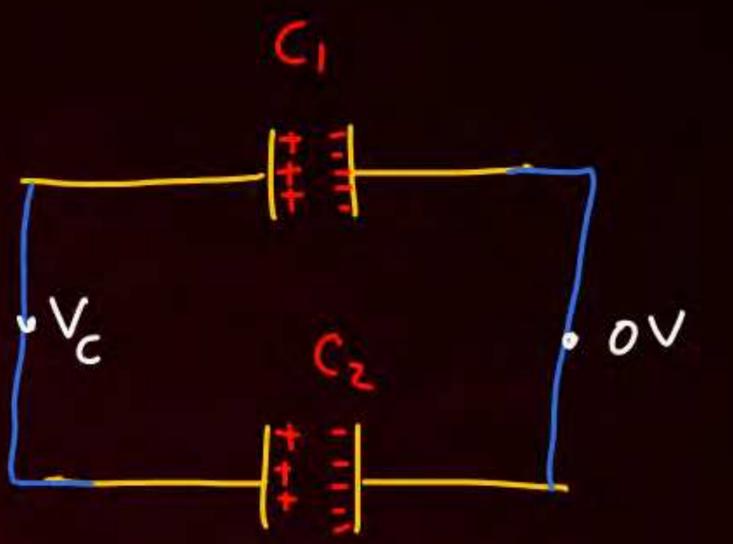

$$V_C = \frac{C_1V_1 + C_2V_2}{C_1 + C_2}$$


ATDB.uno

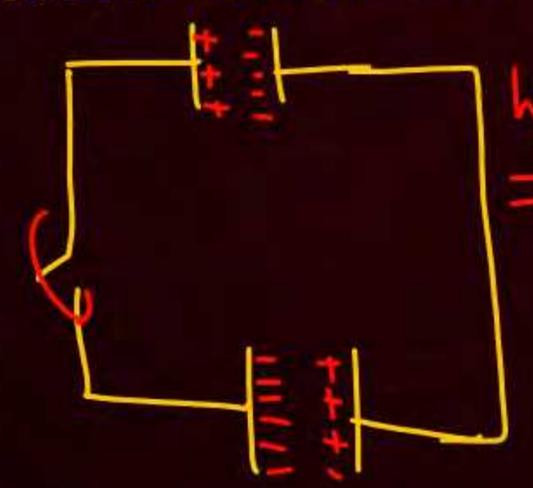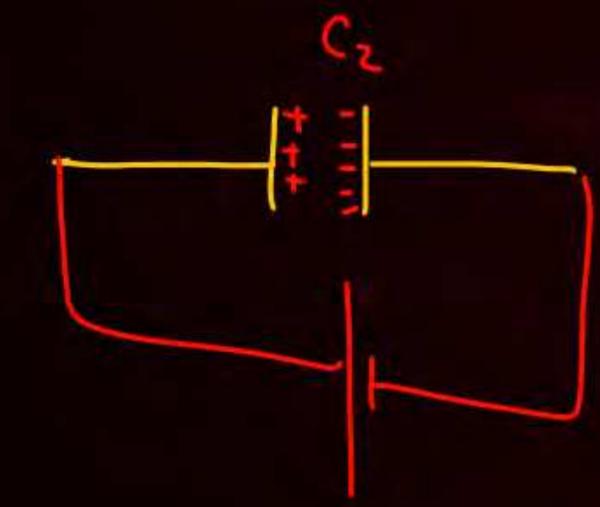

heat loss = $\frac{1}{2} \frac{C_1C_2}{C_1 + C_2} (V_1 - V_2)^2$

$$V_C = \frac{C_1V_1 - C_2V_2}{C_1 + C_2}$$

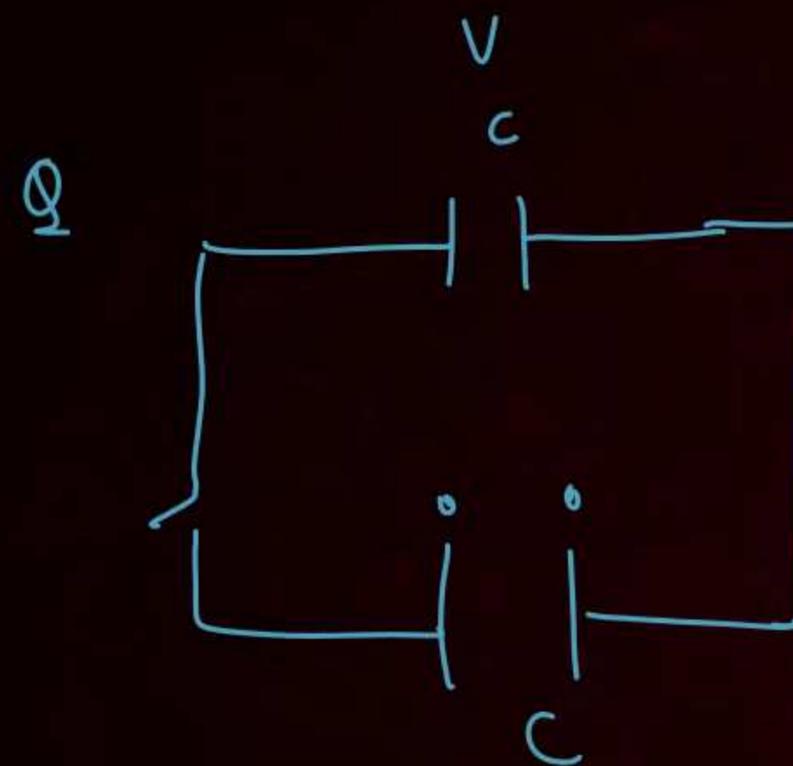heat loss = $\frac{1}{2} \left(\frac{C_1C_2}{C_1 + C_2} \right) (V_1 - V_2)^2$



$$\text{heat loss} = \frac{1}{2} \left(\frac{C \times C}{C + C} \right) (V - 0)^2$$

ATDB.uno



$$\begin{aligned}
 & \left(\frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \right) - \left(\frac{1}{2} C_1 (V_C)^2 + \frac{1}{2} C_2 (V_C)^2 \right) \\
 &= \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 - \frac{1}{2} (C_1 + C_2) \left(\frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \right)^2 \\
 &= \frac{1}{2} \left[\frac{C_1 C_2 (V_1 - V_2)^2}{C_1 + C_2} \right]
 \end{aligned}$$



THANK YOU

ATDB.uno

